 


microcomputer design



i

microcomputer design

by Donald P. Martin

Vice President, Product Development
MARTIN RESEARCH

edited and published by

Kerry S. Berland
Vice President, Marketing
MARTIN RESEARCH

SECOND EDITION
(Revised)
October, 1976

martin research

3336 Commercial Avenue
Northbrook, IL. 60062
(312) 498-5060



Martin Research has taken pains to ensure the accuracy of the information in this book. Nevertheless, Martin Research can not assume any responsibility for the circuits shown, nor do we represent that their use is free from patent infringement.

Copyright © 1976, Martin Research Ltd. All rights reserved. The contents of this book may not be reproduced by any method without written permission from Martin Research Ltd.

Library of Congress Card Catalog Number: 76-1530.

Printed in the United States of America

Martin Research, 3336 Commercial Ave., Northbrook, IL 60062 (312) 498-5060



microcomputer
design

This book covers both basic and advanced information on designing with microprocessors. It assumes that the reader is familiar with digital electronic circuit design, TTL (transistor-transistor logic) in particular.

We have avoided unnecessary duplication of the manufacturers' literature on the 8080 and 8008 microprocessors within the text of this book, preferring to reserve as much space as possible for original hardware design information. The 8080 and 8008 data sheets are reprinted at the end of the book for the reader's convenience. The reader should become familiar with them as he reads this book.

The novice might begin by reading through the 8008 and 8080 data sheets and the following chapters:

2. The 8008 CPU
3. The 8080 CPU
5. Main Timing Logic
23. Software Tricks
25. Minimal Microcomputers
26. Nineteen-Chip Microcomputer
471. Central Processing Unit, Model 471 (an 8080 CPU board)

The reader already familiar with the 8080/8008 might start with these chapters:

5. Main Timing Logic
7. Input/Output Instructions
11. Adding 8008 Instructions
13. Random Access Memory (especially the RAM-PAGE option, Sec. 13.4)
16. Interrupts
25. Minimal Microcomputers
26. Nineteen-Chip Microcomputer
471. Central Processing Unit, Model 471 (an 8080 CPU board)

No book can substitute for practical hands-on experience with microcomputers. The modular micros from Martin Research provide an excellent series of hardware for educational and prototyping purposes. As this book goes to press, both 8080 and 8008 versions are available, and microcomputers based on other CPUs are due for announcement shortly. For more information on the modular micros, contact Martin Research.

Martin Research will appreciate receiving your comments on this book, including criticisms both negative and positive. Ideas and corrections will, with your permission, be used in future editions.



microcomputer
design

TK
7888
.3
M3531
1976
ENGI

| | | | |
|----|-------------------------------|----|--|
| 1. | INTRODUCTION | .1 | MICROCOMPUTER DESIGN |
| | | .2 | Designing with Microprocessors |
| | | .3 | Microcomputers |
| | | .4 | Notes on the 8008, 8080, and MOS Memories |
| 2. | THE 8008 | .1 | Brief Introduction to Microcomputers |
| | | .2 | 8008 Architecture |
| | | .3 | 8008 Timing Signals |
| | | .4 | PCI Instruction Cycle |
| | | .5 | PCR Read Cycle |
| | | .6 | PCC Command Cycle |
| | | .7 | PCW Write Cycle |
| | | .8 | Instruction Cycle |
| | | .9 | A Simple Program |
| 3. | THE 8080 | .1 | The 8080 |
| | | .2 | 8080 Hardware |
| | | .3 | 8080 Software |
| | | .4 | Selected 8080 Technical Notes |
| 4. | MICROPROCESSOR COMPARISONS | .1 | Introduction |
| | | .2 | Systems Design |
| | | .3 | Processor Comparisons |
| | | .4 | The MIKE 5 Microcomputer |
| 5. | MAIN TIMING | .1 | 8008 Clock Circuits |
| | | .2 | Enable and Strobe Generation |
| | | .3 | Master Reset |
| | | .4 | Additional Circuitry Required for Basic Microcomputer |
| | | .5 | 8080 Clock Generation |
| 6. | BUS STRUCTURES | .1 | Introduction to Bus Structures |
| | | .2 | Latching Logic |
| | | .3 | Three-State Devices |
| | | .4 | Advanced Strobe Techniques |
| | | .5 | Types of Bus Structure |
| | | .6 | Bus Transceivers and Bi-Bus Drivers |
| | | .7 | The 8008 Data Bus |
| 7. | INPUT/OUTPUT INSTRUCTIONS | .1 | I/O Address Modes |
| | | .2 | 8008 Input/Output Instructions |
| | | .3 | Input and Output Symbols |
| | | .4 | Generating Input Enables and Output Strobes |
| | | .5 | Peripheral Strobe Decoding Techniques |
| | | .6 | 8080 I/O Instructions |
| 8. | INPUT DESIGN APPROACHES | .1 | Input Design |
| | | .2 | 8008/8080 Data Bus Input Voltages |
| | | .3 | Input Multiplexers |
| | | .4 | Input Enable and Select Signals |
| | | .5 | Expanding 8008 Input Ports with Conditional Inputs |
| | | .6 | Additional Input Ports Defined as Memory |



| | | | |
|-----|-----------------------------|-----|--|
| 9. | OUTPUT TECHNIQUES | .1 | 8008 Outputs |
| | | .2 | Pulse Outputs |
| | | .3 | Latching Outputs |
| | | .4 | 8080 Outputs |
| | | .5 | 16-Bit Output Ports for the 8080 |
| 10. | COMBINED INPUT/OUTPUTS | .1 | Combined Input/Output Techniques |
| | | .2 | Table Lookups |
| | | .3 | Byte-Swapping |
| | | .4 | Adding a UART |
| 11. | ADDING 8008 INSTRUCTIONS | .1 | Adding Instructions to the 8008 |
| | | .2 | Output Any Register |
| | | .3 | One-Byte PUSH-POP Instructions |
| | | .4 | Numbered Instructions |
| | | .5 | WAIT Instruction |
| 12. | EXPANDING 8008 CAPABILITIES | .1 | Expanding the Capabilities of the 8008 |
| | | .2 | One-Byte Push-Pop (LIFO) Register |
| | | .3 | Sixteen-Byte LIFO Register |
| | | .4 | A 32-Byte FIFO Register |
| | | .5 | Other 8008 Improvements |
| 13. | RANDOM ACCESS MEMORY | .1 | Need for Memory in Microcomputers |
| | | .2 | Memory Referencing |
| | | .3 | Memory Address Conventions |
| | | .4 | RAM-PAGE Option |
| | | .5 | Random Access Memories |
| | | .6 | The 256 x 4 RAM |
| | | .7 | The 1024 x 1 Static RAM |
| | | .8 | The 4096 x 1 Dynamic RAM |
| | | .9 | Transparent Dynamic RAM Refresh |
| 14. | READ-ONLY MEMORY | .1 | ROMs and Other Memories |
| | | .2 | Diode Programmable ROMs (DiROM) |
| | | .3 | Field-Programmable ROMs (F/ROMs) |
| | | .4 | Reprogrammable PROMs |
| | | .5 | Comparison of ROM Types |
| | | .6 | The ROMIN Option |
| 15. | DIRECT MEMORY ACCESS | .1 | Direct Memory Access |
| | | .2 | DMA with the 8080 |
| 16. | INTERRUPTS | .1 | Need for Interrupts |
| | | .2 | Initial Interrupt |
| | | .3 | How the Interrupt is Used |
| | | .4 | Synchronizing Interrupt Requests (8008) |
| | | .5 | Simple Interrupts |
| | | .6 | Introduction to Priority Interrupt Systems |
| | | .7 | Interrupt Request Register |
| | | .8 | Interrupt Request Synchronization Register |
| | | .9 | Priority Encoders |
| | | .10 | Priority Registers |

| | | | |
|-----|---------------------------------|-----|---|
| 16. | INTERRUPTS cont'd | .11 | Interrupts Being Serviced Register |
| | | .12 | Priority Comparator |
| | | .13 | Interrupt Jam Logic |
| | | .14 | Numbered Return Instructions |
| | | .15 | An Addressable Latch as an Interrupt Register |
| | | .16 | Three-Level Priority Interrupt System |
| | | .17 | Full Eight-Level Priority Interrupt System |
| | | .18 | Daisy-Chain Interrupt System |
| 17. | SAVING STATUS DURING INTERRUPTS | .1 | Saving Status |
| | | .2 | The Program Counter Stack |
| | | .3 | Index Registers |
| | | .4 | Flags (Condition Flip-Flops) |
| | | .5 | Status-Saving Techniques |
| | | .6 | Software Techniques |
| | | .7 | Saving Registers with Hardware |
| | | .8 | Saving Flags with Hardware |
| | | .9 | Latching Up the Flags |
| | | .10 | Saving All Four Flags with Hardware |
| | | .11 | Saving Four Flags, Bus Structured Hardware |
| | | .12 | Status-Saving System, Example I |
| | | .13 | Status-Saving System, Example II |
| | | .14 | Status-Saving System, Example III |
| | | .15 | Status-Saving System, Example IV |
| 18. | INTERVAL TIMERS | .1 | Interval Timers |
| | | .2 | Interrupt Interval Timer |
| | | .3 | Timers for Input Ports |
| | | .4 | Clocks for Interval Timers |
| | | .5 | Precounters |
| 19. | DIGITAL DISPLAYS | .1 | Digital Displays |
| | | .2 | Segment Decoders |
| | | .3 | Multiplexing |
| 20. | PERIPHERAL INTERFACE DESIGN | .1 | Systems |
| | | .2 | Cost-Effective Modularity |
| | | .3 | An Efficient Microcomputer Bus Structure |
| 21. | KEYBOARDS | .1 | Keyboards and Microcomputers |
| | | .2 | The Keyboard Encoder |
| | | .3 | The FIFO |
| | | .4 | Input to Microprocessor |
| | | .5 | The Repeat Function |
| | | .6 | Doing It with Interrupts |
| 22. | ANALOG INPUTS AND OUTPUTS | .1 | An Analog Interface System for Microcomputers |
| | | .2 | Analog Input Amplifiers |
| | | .3 | One-Channel Tracking A/D Converter |
| | | .4 | Sample/Hold and Track/Hold |
| | | .5 | Analog Multiplexer |



| | | | |
|------|--|------|---|
| 22. | ANALOG INPUTS AND OUTPUTS <i>cont'd</i> | .6 | <i>Successive Approximation A/D Converter</i> |
| | | .7 | <i>D/A Converter</i> |
| | | .8 | <i>Multiple Analog Outputs</i> |
| | | .9 | <i>Analog Range Switching</i> |
| 23. | SOFTWARE | .1 | <i>Software Tricks</i> |
| | | .2 | <i>Clear the A Register Instruction</i> |
| | | .3 | <i>Complement Instruction</i> |
| | | .4 | <i>Multiple Precision Add and Subtract</i> |
| | | .5 | <i>Incrementing H and L Registers</i> |
| | | .6 | <i>Clear RAM Memory</i> |
| | | .7 | <i>Indexed Jump Table</i> |
| | | .8 | <i>Indexed Loops</i> |
| | | .9 | <i>Hard HALT Instruction</i> |
| | | .10 | <i>Push ALL Registers</i> |
| | | .11 | <i>8080 PUSH/POP Instructions</i> |
| 24. | TESTING | .1 | <i>Testing Microprocessors</i> |
| | | .2 | <i>Designing for Easy Testing</i> |
| | | .3 | <i>Sixteen-Channel Oscilloscope Display</i> |
| | | .4 | <i>Octal Data Display</i> |
| | | .5 | <i>Keeping the Ready Line Open</i> |
| | | .6 | <i>Using the Self-Transfer Instructions for Testing</i> |
| 25. | MINIMAL MICROCOMPUTERS | .1 | <i>A Nine-Chip Microcomputer</i> |
| | | .2 | <i>Using the CC-DH Register as a Buffer</i> |
| | | .3 | <i>A Twenty-Dollar Microcomputer</i> |
| | | .4 | <i>A Seven-Chip Microcomputer</i> |
| 26. | NINETEEN-CHIP MICROCOMPUTER | .1 | <i>A Nineteen-Chip 8080-1 Microcomputer</i> |
| | | .2 | <i>The Microprocessor</i> |
| | | .3 | <i>Main Timing</i> |
| | | .4 | <i>State Decoding</i> |
| | | .5 | <i>DH and DL Registers</i> |
| | | .6 | <i>RAM and ROM Memory</i> |
| | | .7 | <i>I/O Strobe/Enable Decoding</i> |
| | | .8 | <i>Input Port</i> |
| | | .9 | <i>Keyboard Encoder</i> |
| | | .10 | <i>Interrupt Function</i> |
| 471. | 8080 CENTRAL PROCESSING UNIT | 1.1 | <i>Introduction</i> |
| | | 1.2 | <i>8080 CPU</i> |
| | | 1.3 | <i>Bus Drivers</i> |
| | | 1.4 | <i>Main Timing</i> |
| | | 1.5 | <i>System Control Logic</i> |
| | | 1.6 | <i>I/O Instruction Modes</i> |
| | | 1.7 | <i>Reset Circuitry</i> |
| | | 1.8 | <i>Interrupt Logic</i> |
| | | 1.9 | <i>Hold Circuitry</i> |
| | | 1.10 | <i>Wait Circuitry</i> |
| | | 1.11 | <i>Indicators</i> |
| | | 1.12 | <i>Power Required</i> |
| 8008 | DATA SHEET | | |
| 8080 | DATA SHEET | | |

SEC. 1.1 MICROCOMPUTER DESIGN

This book is about how to design a *microcomputer*. It focuses on microcomputers based on the first single-chip eight-bit microprocessor to reach high-volume production--the 8008--and on the improved second-generation device, the 8080.

The microprocessor itself is the miniaturized *central processing unit (CPU)* of a small computer. The significance of the microprocessor in electronic design is that the flexibility, adaptability, and logical processing power of the digital computer are now realizable in relatively small and inexpensive electronic products.

This book fills a gap in the literature presently available on microprocessors, since it concentrates on the hardware necessary to make the microprocessor a part of a practical and cost-effective electronic system.

SEC. 1.2 DESIGNING WITH MICROPROCESSORS

1.2.1 Simple Microcomputers The first 8008 circuits published and produced by the 8008 originator, Intel Corporation, were designed to exhibit the full potential of these CPUs. They used complex circuits to generate asymmetrical clocks, which optimized 8008 speed, but which--together with other such needless complicated designs--made using microprocessors look difficult. This was at a time when the technology was new, and the need was for design concepts to help engineers get started.

The first edition of this book presented the simplest possible microcomputer designs, using the fewest possible standard ICs to achieve the desired features. It is easier to add ICs to a simple design, to increase its potential, than it is to rework a needlessly complex design. Thus, for example, Chapter 5 greatly simplifies 8008 main timing circuitry, and Chapter 7 simplifies the creation of I/O interface signals.

The second generation 8080 is a step forward for the designer. Largely because it is housed in a 40-pin package (while the 8008 comes with 18), the 8080 makes more of its essential signals directly available to external control circuitry. Still, upon reading the manufacturers' 8080 literature, many designers are needlessly confused. The timing diagrams are complex and essential information is scattered among many data sheets.

In this second edition, our goal remains the same: to show how to use microprocessors--8080 and 8008--in practical microcomputers. The section on the 8080, Chapter 3, is expanded, and a data sheet for the Model 471 8080 computer is reprinted near the end of the book.



microcomputer
design



microcomputer
design

SEC. 1.2 DESIGNING WITH MICROPROCESSORS (cont'd)

1.2.2 *LSI Chip Design and Circuit Board Design* The integrated circuits now available which make use of LSI (large-scale integration) are impressively complex. One package may contain the equivalent of dozens of ordinary ICs and over a thousand transistors. The 8008 and 8080 microprocessors are good examples of this trend.

There is a distinct difference between an effective circuit design meant to be implemented *within* an LSI integrated circuit, and a good logic design using conventional ICs on a printed circuit board. The circuit designer needs to be aware of these differences, or his design may not be very efficient.

Take for example the 8008 microprocessor. Eight of the pins on its eighteen-pin package are used for its eight-bit bidirectional data bus. Nearly all communications between the 8008 and the outside world take place via this bus. Information on this bus may travel to and from the 8008's arithmetic logic unit; its seven eight-bit data registers; its eight fourteen-bit memory address registers; its memory control logic; and its instruction decoding logic. The data on the bus may represent input information, output data, an instruction code, or a memory address. All of these processes take place at distinct times in the CPU's internal processor operations. (For details, see Chapter 2.)

Within the microprocessor, the eight-bit bus is piped around to all the major sections of the CPU. One of the most important elements in the chip's architecture is the control circuitry that selects which of the various sections within the CPU drive the bus, and which receive from the bus, at each stage in internal processor operations. (See Chapter 6 on bus structures generally.)

Consider for a moment the implementation of a bus control circuit using ordinary TTL ICs on a printed circuit board. These timing signals must be decoded into their eight possible state combinations, and used to activate a variety of devices connected to the bus at different locations on the PC board. The board would need a 3-to-8-line decoder, and a likely choice would be a single TTL IC. This chip would contain eight 3-input NAND gates plus six inverters. The disadvantage of using a single-chip decoder is that, since eight decoder output lines are needed in many different places on the PC board, eight rather than three copper wires must be run all over the board. Still, no board designer we know is likely to choose separate gates over the one decoder.



microcomputer
design

SEC. 1.2 DESIGNING WITH MICROPROCESSORS (cont'd)

The more complex IC and extra PC wires are generally much cheaper than buying, stocking, testing, stuffing, and soldering extra ICs. After all, adding just two IC pins means two extra bonding pads on the chip, two bonds to the IC lead frame, two pins, two holes in the PC board, a copper foil pattern, and two solder joints.

Contrast the design decisions which face the *chip designer* when laying out the mask used in etching the silicon wafer from which a CPU is made. An on-chip 3-to-8 decoder may well be implemented with eight discrete 3-input NAND gates and up to twelve inverters, each gate and any needed inverters located right where the decoded signal is needed. Only the three lines to be decoded are bussed to the far corners of the chip, rather than the eight decoded outputs. Otherwise, the five extra bus lines would probably take up more chip area than any duplication in gates.

These considerations affect the way the microprocessor is organized. First, a relatively large number of special-purpose timing and control signals are developed on the chip, at multiple locations; they are derived from a *minimal* number of general-purpose timing signals. Second, only these few undifferentiated timing signals are brought out of the IC package to the outside world. This means that the hardware external to the 8008 must redevelop many special-purpose control signals in order to interface memory, input ports, and output ports with the CPU.

If one looks at the photomicrograph of the 8008, one sees that it was laid out by an excellent chip designer, who uses extra gates sooner than extra bus lines. But it is not effective for the hardware designer to mimic the chip designer in developing his microcomputer control and timing logic. He needs to develop circuitry which does its job with a minimum number of parts. Thus his timing and control logic may not look exactly the same as that used inside the CPU.

First, the designer must thoroughly grasp the internal processor operations of the CPU. Next, he must understand how the microprocessor's basic timing signals relate to the internal operations. (In the case of the 8008, there are six basic timing signals: $\phi 1$, $\phi 2$, S2, S1, S0, and SYNC). Only then should the design of his hardware begin. This approach is much more likely to be productive than copying, or trying to simplify, the 8008 designs published by the chip's manufacturers. And, using this method, the chip count for the basic 8008 microcomputer can be cut from 20 to 50%, depending on the application. (See Chapter 5 on main timing logic; Chapters 25 and 26 for design examples.)

The designer who thoroughly understands the operation of the microprocessor is also in a position to do things with the CPU that do not appear in the manufacturers' manuals. (For a simple example, note how extra input instructions can be added to the 8008, in Chapter 8.)



microcomputer
design

SEC. 1.3 MICROCOMPUTERS

1.3.1 Applications Ultimately the speed and versatility of coming generations of microprocessors will allow designers to build microcomputers which will rival today's best minicomputers. Much of the current excitement in the engineering community about microprocessors seems to be focused on this prospect.

However, many applications exist already for the microcomputers that can be built with today's microprocessors. The products in which microcomputers are used are not necessarily *computers* themselves; the word *computer* would not even occur to the average person using many of them. They include a wide variety of digital electronic devices, from automatic scales, to computer peripherals, to industrial controls, to communications devices--OEM equipment marketing for as little as \$500.00 or less.

Some examples: fancy programmable calculators, electronic games, autotuning digital-display radios. Automotive carburetion and emission control; anti-skid braking. Building security and temperature monitoring; elevator controls. Machine tool programmers, traffic light systems. Medical patient-monitoring consoles, biochemical analyzers. Low-frequency digital filters and Fourier analyzers. Complex electronic measurement instrumentation; circuit testers. Telephone exchanges, computer peripherals, typesetters, point-of-sale cash register/computer terminals.

Sometimes a microcomputer is employed because this technology has made the use of digital electronics commercially feasible for the first time. In many products, the microcomputer displaces a random logic design because it is more cost-effective--either in simple cost per unit, or because of the design flexibility afforded the manufacturer by the programmable microcomputer.

1.3.2 What a Microcomputer Does A microcomputer is a programmable logic unit based on a microprocessor. As the name implies, the basic principles of *computer* technology are used in the *microcomputer*. The electronic circuitry is configured to perform logical operations on discrete blocks of binary-encoded data (eight-bit *bytes*, in the 8008/8080). Each operation takes place sequentially at a set speed, and is under control of binary-encoded *instructions*. The versatility of the microcomputer depends in part on the microprocessor's *instruction set*, which generally provides basic logic operations (AND, EXCLUSIVE OR, etc.) and arithmetic operations (ADD, SUBTRACT, etc.). Also provided are instructions which receive (INPUT) data and transmit (OUTPUT) data to and from associated equipment.



microcomputer
design

SEC. 1.3 MICROCOMPUTERS (cont'd)

The programs needed by the microcomputer in carrying out its functions are usually stored in a permanent semiconductor memory (read-only memory, or ROM). The microprocessor *reads* each instruction from memory, *executes* it and then proceeds to the next instruction. The *conditional* instructions cause the microprocessor to jump nonsequentially to a designated step in the program *only* if the results of the previous operation meet a specified condition. These instructions are basic to computer programming, and are really what makes a microcomputer a *computer*, rather than just a moderately complex programmable logic unit.

Most microcomputers require more temporary data storage capacity than is available within the microprocessor itself, and therefore include an array of RAM (random access memory). The microprocessor can *write* data into RAM, *read* data from RAM, or read instructions from RAM. The CPU includes facilities for *addressing* any given *location* in memory, as specified by the programming.

1.3.3 Advantages of Microcomputers A certain degree of design flexibility is possible with conventional digital logic designs. For example, an accessory can plug into a main circuit board in order to add a desired feature. However, microprocessor technology implies a whole new level in design flexibility.

First of all, with conventional logic, a design change usually necessitates a redrafted printed circuit board. When microcomputers are used, frequently the only change necessary is a change in *software* (programming)--which involves reprogramming (ie remasking) a ROM, or reprogramming a PROM--more economical and rapid procedures in large-scale production.

Second, the microcomputer can serve as the basic digital logic element in a whole family of related equipment. For illustration, let us assume that the designer is working with a series of computer peripheral devices: a CRT display, a line printer, a send/receive terminal with keyboard, etc. The microcomputer itself fits on one printed circuit board, and is used in each of these devices. It consists of the microprocessor, main timing circuitry, ROM to store the programs, RAM, and some general-purpose input and output interface chips.

On separate boards go the components needed for the specialized functions of the machine: power drivers, keyboard encoders, deflection amplifiers, modems, etc. The ROM needed to store the appropriate instructions for these different machines plugs into a socket on each separate board. An efficient bus-structure design optimizes flexibility and modularity.



microcomputer
design

SEC. 1.4 NOTES ON THE 8008, 8080, AND MOS MEMORIES

The technology used in the manufacture of the 8008 microprocessor is a fourteen-volt P-channel process. That is, the device requires +5 and -9 volt power supplies, for a total potential of 14 volts. This process is also used to produce the 1101 (256 x 1 RAM) and the 1103 (1024 x 1 Dynamic RAM). A similar process is used in the production of the 1702A (256 x 8 PROM).

Microprocessors are produced in relatively low volumes, at least in comparison to the semiconductor memories which make up the bread-and-butter sales for these manufacturers. The 1103 1024 x 1 dynamic RAM was the first semiconductor memory to begin successful large-scale competition with core memories, for application in computer mainframes. But since the same 14-volt P-channel process is used to manufacture both these memory devices and the 8008, the extensive efforts to improve the process have resulted in improvements in the 8008. Many standard 8008s test to 8008-1 speed specifications (60% faster). Though you must buy an 8008-1 to be sure you get one, it is not surprising for an ordinary 8008 to beat the 8008-1's 2.5-microsecond cycle time.

Similar comments apply to the 8080 and its 17-volt N-channel process. For example: the Intel 2104 high-speed 4K RAM uses the same process as the 8080, requiring power supplies of +12, +5, and -5 volts. With competition to capture the 4K RAM market very tight, it is to be expected that the 8080 microprocessor will benefit from further improvements to the 17-volt N-channel process.

For every microprocessor made and sold, a number of memory chips change hands. Even in a small microcomputer, it is typical for there to be a greater dollar investment in memory than in the CPU chip. From the manufacturer's standpoint, moreover, the microprocessor is a relatively expensive device to develop. A large amount of his cost is tied up in initial R & D (especially if he originated the device), in documentation, and in software support (if it is offered). Often, for competitive reasons, there is a great deal of price pressure on the CPU. The result: microcomputer component "packaging." Production-volume quotations from microprocessor manufacturers often include not only the CPU, but various peripheral logic devices (clock generators, bus drivers, etc.), plus an array of solid state memory (PROM and RAM). The current price of a given microprocessor, in large quantities, is often a well-kept secret, varying from transaction to transaction, depending partly on the amount of adjunct circuitry purchased at the same time.

SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS

In the past, only the simplest logic design techniques could be used in small and inexpensive electronic systems. The technology whereby many transistors can be included in a single package has made it feasible to employ very sophisticated designs in low-cost products. The *micro-processor* provides the most advanced example of this trend. The paragraphs that follow trace the evolution in logic design that led to the microcomputer.

2.1.1 Binary Logic Engineers discovered long ago that complex machines may readily be designed through the use of *binary logic*. Perhaps the best early example is the telephone switching system, making use of electro-mechanical switches (relays). Each contact may be in one of two states, open or closed. These states are generally represented as *logic one (1)*, or *true*, and as *logic zero (0)*, or *false*.

Switches have long since been replaced with transistors, and voltage levels represent the logical states. Since only *positive logic* is used in this book, a logic one always represents a *higher* (more positive) voltage, and a logic zero represents a *lower* (more negative) voltage.

The reader is presumably familiar with these matters in general, and with transistor-transistor logic (TTL) in particular. *For the novice, a good place to start is with The TTL Applications Handbook (August, 1973, Fairchild Semiconductor, 464 Ellis St., Mountain View, CA 94042.)*

2.1.2 Combinational Circuits A circuit which contains only gates, and no latching elements, belongs to that class called *combinational circuits*. Figure 2.1.1 shows a block containing only combinational logic, with m inputs and n outputs. For any given set of inputs, there is a unique set of outputs, which does not depend on the previous history of the inputs. (This overlooks the propagation delay of the gates, which is usually a negligibly short portion of the history being considered.)

Logic equations, Boolean algebra, truth tables, and Karnaugh maps are useful tools in analyzing combinational logic.



SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS (cont'd)

 


Fig. 2.1.1--Combinational Logic

2.1.3 Sequential Circuits Combinational circuits are often combined with latching elements such as flip-flops, registers, latches, one-shots (monostable multivibrators), etc. A circuit designed with latching elements does not necessarily have a unique set of outputs for a given set of inputs. In general, the outputs depend not only on the current set of inputs, but also on the sequence of inputs received in the past. For this reason such designs are called *sequential machines*.

Simple sequential circuits often consist of a number of gates and flip-flops arranged in a manner which is specifically related to the structure of the inputs and outputs required. Such circuits are often referred to as *random logic*. Figure 2.1.2 shows the block diagram of a random logic sequential circuit with m inputs and n outputs.



Fig. 2.1.2--Random Logic Sequential Circuit

As mentioned above, the advent of *large scale integration* (LSI) has made more compact logic circuits feasible. For very high-volume applications, a random logic design of moderate complexity may be put onto a single integrated circuit. For small-volume applications, this approach is not cost effective. The advantages of LSI may still be obtained,

SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS (cont'd)

however, using *structured sequential circuits*. Figure 2.1.3 shows a structured circuit where the memory elements are separated from the combinational logic elements. This allows the integrated circuit manufacturers to design general purpose logic arrays on some *chips* (integrated circuits) and general purpose memory elements on other chips. This means that the same chips may be used by many different customers for totally different logic designs. In this way the low cost advantage of volume production may be realized.

In addition, structured sequential circuits are often more easily understood and modifications or corrections are more easily implemented. Figure 2.1.3 shows a structured sequential circuit where the combinational logic is implemented with a read-only memory (ROM) or programmable logic array (PLA), and the latching memory elements are implemented with chips containing multiple flip-flops with a common clock. Another set of flip-flops for the purpose of synchronizing the inputs, and a two-phase clock, complete the necessary elements of a simple structured sequential circuit.

Whereas this circuit is excellent for a medium-complexity application, there are more complex problems where the size of the combinational logic required becomes unwieldy. In addition the number of memory elements may not be adequate to perform larger tasks.

 


Fig. 2.1.3--Simple Structured Sequential Circuit

2.1.4 Computers More complex sequential circuits are often called *computers*. The structure shown in Figure 2.1.4 is a simplified representation of a computer. Note that, near the center of the diagram, the computer contains an array of combinational logic. More importantly, the overall structure is that of a sequential machine--since memory elements are inserted in a digital feedback path between the output and input of the combinational logic.

SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS (cont'd)

 


Fig. 2.1.4--Simplified Block Diagram of a Computer



microcomputer
design

SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS (cont'd)

In Figure 2.1.4, input data is brought into the system at the left. A *multiplexer (MUX)* switches between several sources of input data, including the memory array (ROM and RAM) which is part of the system. After being synchronized with the system's time frame, the input data passes to an *index (I) register*, and thence to an array of combinational logic which is used to decode the information and produce various *strobe, enable, and other control signals*. These signals, in turn, are used to route input data to other registers and to the *arithmetic logic unit (ALU)*.

The ALU can perform arithmetic operations like addition and subtraction; logical operations like AND, OR, and ROTATE; and, in complex units, other operations like MULTIPLY and DIVIDE.

The control signals may also be used to pass data to the outside world through an output register.

The key to the computer is its use of memory. The computer carries out one operation at a time, under control of a *program* which is stored in memory. After carrying out each operation, the computer *fetches* another *instruction* from memory, and then carries out the new operation which is designated by the new instruction. Thus, referring to Figure 2.1.4, the sequence might occur as follows:

Old operation is finished.

Get ready to fetch a new instruction.

Enable the *PC Register*, which *addresses* the location in memory where the next instruction is stored.

Get ready for the next instruction by incrementing the *PC register*.

Enable memory.

Read the new instruction by switching the input multiplexer to the memory bus.

Decode the instruction to see what it wants.

Execute the instruction, i.e., carry out the designated operation.

Example: an *Input 7* instruction. Switch the input multiplexer to *input port* number 7; create the required strobe signals, and pass this information along for temporary storage in the A register.

Fetch the next instruction from memory.

Etc.



microcomputer
design

SEC. 2.1 BRIEF INTRODUCTION TO MICROCOMPUTERS (cont'd)

As implied by the above example, the computer is a highly structured sequential machine which moves through its operations in a very regular manner. The *PC* register, or *program counter*, keeps track of the machine's operations.

The real power of the computer depends on instructions which do not necessarily follow the strict numerical sequence of instructions stored in memory. For example, a *JUMP* instruction might tell the computer to leave the current instruction number and fetch its next instruction from an entirely different address in memory. Even more powerful are *conditional branch* instructions, which send the computer to a new memory address *only* if the contents of an index register meet a specified condition. For example, a *JUMP TRUE ZERO 010 300* instruction would cause the computer to test an index register to see if the current contents are zero. If so, the program counter is loaded with memory address 010 300, and this is where the next instruction comes from. If the register contents were *not* zero, the computer simply proceeds with the next instruction, in ascending numerical order.

Though Figure 2.1.4 shows the use of memory for storing instructions, for simplicity's sake it does *not* show the other important function of memory--particularly random-access memory (RAM). That is, memory is used for temporary data storage by the computer in the course of complicated operations.

SEC. 2.2 8008 ARCHITECTURE

The 8008 was the first eight-bit microprocessor on a single chip. Essentially the miniature *central processing unit* of a small computer, the *microprocessor* performs the essential logical and control functions of a *microcomputer*. Figure 2.2.1 shows the block diagram for the 8008. Though more complex than the sequential machines shown earlier in this chapter, the basic principles are the same. And even while the 8008 is being superseded by the second-generation 8080 CPU (discussed in the next chapter), 8008 architecture provides a useful transition between these sequential machines, and more complex microprocessors.

2.2.1 Bus Structure The 8008 handles data in eight-bit *bytes*. Thus, most of the elements within the CPU are interconnected via an eight-bit data bus. The *data bus buffer*, a bidirectional bus driver, is used to drive external devices from the CPU, or (when the driving direction is reversed), to input data from external devices onto the CPU's internal data bus. (See Chapter 6 on bus structures.)

SEC. 2.2 8008 ARCHITECTURE (cont'd)

 


Fig. 2.2.1--8008 Block Diagram



microcomputer
design



microcomputer
design

SEC. 2.2 8008 ARCHITECTURE (cont'd)

2.2.2 Instruction Decoding The *instruction register* is an eight-bit temporary storage register which receives instructions from external memory devices. The *instruction decoder* deciphers what operations should be performed by the microprocessor.

2.2.3 Program Counter The *program counter* stores the address in memory from which the CPU is currently fetching instructions. The counter is made up of a *stack* of eight registers, in eight levels. This enables the program counter to keep track of subroutines in the program. For example, a CALL instruction makes the CPU leave off processing the microcomputer's *main line program* (on level no. 0), and jump to a subroutine whose instructions are stored at a new location in memory. The former memory address remains on level no. 0, and the new memory address is now at level no. 1 in the stack. Thus, the 8008 permits *nesting* of seven subroutines in the PC stack. At the end of the subroutine, a RETURN instruction causes the CPU to return to level no. 0 in the stack. The *stack pointer* keeps track of which level in the stack is currently being processed.

Often it is said that a CALL instruction *pushes down* one level in the stack, and that the RETURN instruction *pops* the stack. Actually the stack itself does not change; i.e., the contents of the various levels do not get transferred among each other; only the stack pointer is moved.

Note that each level in the PC stack has a fourteen-bit capacity. This allows the 8008 to address 2^{14} , or 16 K bytes of memory (see *Chapter 13*). The memory address is divided into eight *low-order* bits (PCL) and six *high-order* bits (PCH).

2.2.4 Index Registers During the processing of data, it is useful to have a *scratch-pad*: a small array of easily-accessible memory. The 8008 has seven general-purpose *index registers*, labeled A, B, C, D, E, H, and L. Transfers of data between these registers are easily accomplished in a direct manner through the 8008's instructions: i.e., LAB (load the A register from the B register).

The A register, also called the *accumulator*, is specially designated as the register used for communications between various elements in the microcomputer. Thus, *input* data to the 8008 from an input device outside the 8008 ends up in the A register at the end of an input instruction. *Output* data, intended for an external output port, must first be loaded into the A register before an output instruction is executed. And, the arithmetic logic unit both operates on data in the A register, and stores its results in the A register.

SEC. 2.2 8008 ARCHITECTURE (cont'd)

The *H and L registers* are specially designated for referencing memory external to the CPU, for the purpose of *reading* data from memory (random-access memory, or RAM, or read-only memory, ROM) and for writing data into memory (RAM only). (This function should be distinguished from the PCH and PCL registers, which reference memory for the purpose of *fetching instructions*.)

2.2.5 Arithmetic Logic Unit The 8008's *arithmetic logic unit* (ALU) is capable of addition, subtraction, and several logical operations: AND, OR, EXCLUSIVE OR, comparison, and rotation. (For details, see discussion of the instruction set below.)

2.2.6 Flag Flip-Flops Four *flag* flip-flops may be set by the operation of the ALU: the *carry* (C), *parity* (P), *sign* (S), and *zero* (Z) flags. (They are discussed further in the 8008 Manual and in Chapter 17.) In turn, each flag may be tested through the use of conditional branch instructions, with subsequent program flow dependent on the state of the tested flag. For example, a *Jump True Zero--J TZ--* instruction will cause the CPU to jump to another location only if the zero flag is true, i.e., logic one.

2.2.7 Temporary Registers Two *temporary registers* provide storage of intermediate data. They are used by the CPU for internal data transfers, and are not directly accessible through program instructions (as are the index registers). Labeled the *a and b registers*, these temporary registers should not be confused with the index registers, A and B.

2.2.8 Timing and Control The 8008 requires a two-phase clock, generated by external circuitry (Chapter 5). The $\phi 1$ and $\phi 2$ signals are used to synchronize the various stages in the 8008's internal processor operations, as described below.

SEC. 2.3 8008 TIMING SIGNALS

For complete details on 8008 processor operations, the reader is referred to the 8008 data sheet which is reprinted near the end of this book.



SEC. 2.3 8008 TIMING SIGNALS (cont'd)

| | | CYCLE | | |
|-----|-----|--------|--|--|
| cc2 | cc1 | SYMBOL | NAME & DESCRIPTION | |
| 0 | 0 | PCI | <i>Instruction Cycle.</i> The first byte of the instruction is read from memory. | |
| 1 | 0 | PCR | <i>Read Cycle.</i> Data, or additional instruction byte(s), read from memory. | |
| 0 | 1 | PCC | <i>Command Cycle.</i> Data to be inputted or outputted. | |
| 1 | 1 | PCW | <i>Write Cycle.</i> Data to be written into RAM. | |

Fig. 2.3.2--The Four 8008 Machine Cycles

The two control bits, *cc2* and *cc1*, are present on the data bus at T2 time. They appear as the two high-order bits, *D7* and *D6*, on the bus during the T2 state. In most 8008 microcomputers, these bits are latched up in the *CC-DH register*, external to the 8008, at T2 time, and are used to control external circuitry (see Chapter 5).

The 8008 does not pass through every state, or every machine cycle, during the execution of every instruction. Flow-charts in the 8008 Manual show the state transitions which occur. The sections below describe the functions of the four machine cycles.

Figure 2.3.3 is a chart of 8008 internal processor operations. Perhaps the most important single page in the manufacturers' manuals, this chart is a basic prerequisite for the 8008 designer.

SEC. 2.4 PCI INSTRUCTION CYCLE

PCI is used to fetch the first byte of an instruction from memory. The *PCI* cycle is always the first cycle in any instruction, and there is only one *PCI* cycle per instruction. (If there is more than one byte in the instruction code, *PCR* cycles are used to fetch the remaining bytes.) During *PCI*, the CPU decodes the instruction internally and (for most instructions) prepares to complete the instruction in subsequent *PCC*, *PCR*, or *PCW* cycles.

2.4.1 *PCI-T1* The T1 state is the normal first state of a *PCI* cycle. During *PCI-T1* time, the CPU outputs the low-order eight bits of the memory address where the first byte of the next instruction is located. That is, the 8008 outputs the internal *PCL* register. At the end of *PCI-T1*, the *PCL* register is incremented, in preparation for the following instruction. If as a result an overflow occurs in the *PCL* register, the overflow is saved and used at *PCI-T2* time.

SEC. 2.4 PCI INSTRUCTION CYCLE (cont'd)

2.4.2 *PCI-T1I* The T1I state replaces T1 during *PCI* cycles *only* if the 8008's INTERRUPT terminal has been brought to logic one. During *PCI-T1I*, the internal program counter (*PCL*) is *not* incremented, as it would be during a *PCI-T1* cycle; in every other respect, the *PCI-T1I* is identical to *PCI-T1*. The T1I state is decoded externally and used to jam in a special interrupt instruction (see Chapter 16); *PCL* is not incremented so that after the interrupt subroutine is over, the CPU will resume operations just where it left off.

2.4.3 *PCI-T2* *PCI-T2* is the second state of every *PCI* cycle. During *PCI-T2* the CPU outputs the six high-order memory address bits (ie, the *PCH* register) on the CPU bus, bits *D5* through *D0*. If the low-order address overflowed during *PCI-T1* time, then the high-order address (*PCH*) is incremented. The two high-order bits on the data bus, *D7* and *D6*, are the two cycle control bits, *CC2* and *CC1*--and will be *00*, indicating that this is an instruction cycle (*PCI*).

2.4.4 *WAIT STATE* The CPU enters the *WAIT* state when the *READY* input is brought low before the beginning of T2 time. During a *PCI-WAIT* state, the CPU is inputting data just as though it were in the *PCI-T3* state (below). Thus, the *WAIT* state is a form of extended anticipation of the T3 state. It lasts until the *READY* line is brought high again. The sequence *not ready* (or *busy*); *WAIT*; *T3* is used in systems employing slow memories and for other purposes. The *WAIT* state is skipped altogether when the *READY* line remains high.

2.4.5 *PCI-T3* The third state of a *PCI* cycle is always *PCI-T3*. During this state, the CPU's internal bidirectional bus driver drives inwards onto the chip, and the 8008 receives the first byte of the instruction code from memory.

2.4.6 *STOPPED STATE* The CPU enters the *STOPPED* state following T3 only if a *HALT* instruction is being executed. This ends the instruction. The CPU remains *STOPPED* until interrupted; thus the next state entered must always be *PCI-T1I*. During the *STOPPED* state, the CPU data bus is driving inwards onto the chip, and the CPU stays in the *PCI-T3* state internally. Externally the state signals indicate a *STOPPED* state.

2.4.7 *PCI-T4* The T4 state is skipped during the execution of many instructions. When it does occur, it is used to transfer information between internal CPU registers via the CPU's internal data bus.



SEC. 2.4 PCI INSTRUCTION CYCLE (cont'd)

2.4.8 *PCI-T5* Like T4, the T5 state is also skipped in many instructions, and, when it appears, it is used for internal data transfers. When T5 occurs, it always terminates the instruction.

SEC. 2.5 PCR READ CYCLE

When a *PCR (READ)* cycle occurs, it is the second or third cycle of an instruction. PCR cycles are used to read memory. They occur during instructions which carry out the following functions: reading data from memory into an index register; loading an index register with a value contained in the second byte of an instruction code (*Load immediate* instructions); *jumping* to or *calling* an address in memory; and performing an arithmetic operation on a value stored in memory, or a value contained in the instruction code.

2.5.1 *PCR-T1* The PCR cycle always begins with PCR-T1. If the PCR cycle is being used to read additional bytes of instruction, then the PCL register is outputted at PCR-T1 time. In that case the PCL register is then incremented, as with the *PCI-T1* state. If the PCR cycle is being used to read data from memory (for loading into an index register or for an arithmetic operation), then the L register is outputted at PCR-T1 time. (Recall that the PCL register addresses memory for the purpose of fetching instructions, and the L register addresses memory for the purpose of storing data.)

2.5.2 *PCR-T2* PCR-T2 always follows PCR-T1 as the second state in a memory read cycle. If the PCR cycle is reading additional bytes of an instruction, then PCH appears on the data bus at PCR-T2 time; if the PCL register overflowed after incrementing, at PCR-T1 time, the PCH register is incremented at the end of PCR-T2. When the PCR cycle is reading data from memory, the six low-order bits of the H register go out on the data bus at PCR-T2 time. The high-order bits are the control bits, ccl and cc2, and are 10, designating a PCR cycle.

2.5.3 *WAIT* The READY line may be used to make the CPU enter the WAIT state during a PCR cycle, when reading from slow memory.

2.5.4 *PCR-T3* PCR-T3 is always the third state of a PCR cycle (unless a WAIT state intercedes). If the PCR cycle is the *second* cycle in the instruction, then data is read into the internal *b* register. If the PCR is the *third* cycle, then data is read into the internal *a* register.

SEC. 2.5 PCR READ CYCLE (cont'd)

2.5.5 *PCR-T4* T4 takes place only in some PCR cycles. When there is a T4 state, and the PCR is the third cycle of an instruction, it is used to transfer the *a* register to the PCH register on the 8008 chip. If the instruction is a *call*, the PC stack pointer is *pushed* at the beginning of T4 time. During an arithmetic operation, PCR-T4 provides a pause to the ALU which allows it to perform its operation.

2.5.6 *PCR-T5* PCR-T5 always follows PCR-T4. During arithmetic operations, the flag flip-flops are set according to the results in the ALU, at the same time that the results are transferred to the A register (accumulator). Other internal data transfers take place during other PCR-T5 states.

SEC. 2.6 PCC COMMAND CYCLE

PCC cycles are used during input and output instructions. When it occurs, the PCC cycle is the second cycle of a two-cycle instruction. See Chapter 7 for an extended discussion of PCC cycles.

2.6.1 *PCC-T1* The contents of the accumulator (A register) appear on the data bus at PCC-T1 time. Note that the PCL register is *not* referenced and is not incremented.

2.6.2 *PCC-T2* The contents of the internal *b* register appear on the bus. This contains the binary code for the input/output instruction being executed. The two high-order bits, D7 and D6, are the two cycle control bits, cc2 and ccl, which read 01, indicating a PCC cycle is being executed. Note that all the binary codes for all the I/O instructions begin with this 01 combination.

2.6.3 *WAIT* If the READY line has been brought low, the CPU will enter the WAIT state; the bus floats until the WAIT state ends.

2.6.4 *PCC-T3* During *input* instructions, the CPU data bus receives information from an input port external to the CPU at PCC-T3 time. During *output* instructions, PCC-T3 is present as an idle state only; the CPU will check the READY line before completing the instruction. PCC-T3 time is used by circuitry external to the CPU to complete external data transfers into an output port.



SEC. 2.6 PCC COMMAND CYCLE (cont'd)

2.6.5 PCC-T4 There is no PCC-T4 or T5 during an output instruction. During an input instruction, the four flags appear on the data bus at PCC-T4 time. (See Chapter 17.)

2.6.6 PCC-T5 During PCC-T5 time of an input instruction, the input data is transferred within the CPU from the b to the A register.

SEC. 2.7 PCW WRITE CYCLE

PCW cycles are used for writing data into random-access memory (RAM). The PCW is the second cycle of an LMI instruction and the third cycle of an LMI instruction.

2.7.1 PCW-T1 The internal L register is outputted at PCW-T1 time; this represents the low-order address of memory to be written into.

2.7.2 PCW-T2 The six low-order bits of the internal H register come out at PCW-T2 time; this is the high-order memory write address. The two high-order bits on the bus are cc2 and ccl, the cycle control bits, which read 11, denoting a PCW cycle.

2.7.3 WAIT In anticipation of PCC-T3, the WAIT state may be used to begin outputting data onto the CPU bus. This provision, for writing into slow memory, is accomplished by bringing the READY line low before PCW-T2 time.

2.7.4 PCW-T3 The PCW-T3 state is the only case where the CPU bus is pointing outwards (driving external devices) during T3 time. The memory write data is outputted from the internal b register, where it was stored temporarily during a previous internal data transfer. The PCW-T3 state ends the memory write instruction.

SEC. 2.8 INSTRUCTION SET

The 8008 instruction set is explained in the manufacturers' manuals. For the convenience of the reader, the 256 eight-bit instruction codes are set forth in numerical order in Figure 2.8.1.

SEC. 2-8 INSTRUCTION SET (cont'd)

| OCTAL | BINARY | MNEMONIC | DESCRIPTION | OCTAL | BINARY | MNEMONIC | DESCRIPTION |
|-------|------------|----------|---------------------------------------|-------|------------|----------|----------------------------------|
| 000 | 00 000 000 | HLT | Halt until interrupted | 100 | 01 000 000 | JFC* | Jump false carry |
| 001 | 00 000 001 | HLT | Halt until interrupted | 101 | 01 000 001 | INP 0 | Input #0 to A; out A reg. |
| 002 | 00 000 010 | RLC | Rotate A register left | 102 | 01 000 010 | CFC* | Call false carry |
| 003 | 00 000 011 | RFC | Return false carry | 103 | 01 000 011 | INP 1 | Input #1 to A; out A reg. |
| 004 | 00 000 100 | ADI* | Add immediate to the A register | 104 | 01 000 100 | JMP* | Jump to indicated memory address |
| 005 | 00 000 101 | RST 000 | Restart at location 000000 | 105 | 01 000 101 | INP 2 | Input #2 to A; out A reg. |
| 006 | 00 000 110 | LAI* | Load A immediate | 106 | 01 000 110 | CAL* | Call the indicated subroutine |
| 007 | 00 000 111 | RET | Return one level down in stack | 107 | 01 000 111 | INP 3 | Input #3 to A; out A reg. |
| 010 | 00 001 000 | INB | Increment the B register | 110 | 01 001 000 | JFZ* | Jump false zero |
| 011 | 00 001 001 | DCB | Decrement the B register | 111 | 01 001 001 | INP 4 | Input #4 to A; out A reg. |
| 012 | 00 001 010 | RRC | Rotate A register right | 112 | 01 001 010 | CFZ* | Call false zero |
| 013 | 00 001 011 | RFZ | Return false zero | 113 | 01 001 011 | INP 5 | Input #5 to A; out A reg. |
| 014 | 00 001 100 | ACI* | Add immediate with carry to A reg. | 114 | 01 001 100 | JMP* | (Same as 104) |
| 015 | 00 001 101 | RST 010 | Restart at location 000010 | 115 | 01 001 101 | INP 6 | Input #6 to A; out A reg. |
| 016 | 00 001 110 | LBI* | Load B immediate | 116 | 01 001 110 | CAL* | (Same as 106) |
| 017 | 00 001 111 | RET | (Same as 007) | 117 | 01 001 111 | INP 7 | Input #7 to A; out A reg. |
| 020 | 00 010 000 | INC | Increment the C register | 120 | 01 010 000 | JFS* | Jump false sign |
| 021 | 00 010 001 | DCC | Decrement the C register | 121 | 01 010 001 | OUT 10 | Output A reg. to output #10 |
| 022 | 00 010 010 | RAL | Rotate A reg. left thru carry | 122 | 01 010 010 | CFS* | Call false sign |
| 023 | 00 010 011 | RFS | Return false sign | 123 | 01 010 011 | OUT 11 | Output A reg. to output #11 |
| 024 | 00 010 100 | SUI* | Subtract immediate from A register | 124 | 01 010 100 | JMP* | (Same as 104) |
| 025 | 00 010 101 | RST 020 | Restart at location 000020 | 125 | 01 010 101 | OUT 12 | Output A reg. to output #12 |
| 026 | 00 010 110 | LCI* | Load C immediate | 126 | 01 010 110 | CAL* | (Same as 106) |
| 027 | 00 010 111 | RET | (Same as 007) | 127 | 01 010 111 | OUT 13 | Output A reg. to output #13 |
| 030 | 00 011 000 | IND | Increment the D register | 130 | 01 011 000 | JFP* | Jump false parity |
| 031 | 00 011 001 | DCD | Decrement the D register | 131 | 01 011 001 | OUT 14 | Output A reg. to output #14 |
| 032 | 00 011 010 | RAR | Rotate A reg. right thru carry | 132 | 01 011 010 | CFP* | Call false parity |
| 033 | 00 011 011 | RFP | Return false parity | 133 | 01 011 011 | OUT 15 | Output A reg. to output #15 |
| 034 | 00 011 100 | SBI* | Subtract immediate with borrow from A | 134 | 01 011 100 | JMP* | (Same as 104) |
| 035 | 00 011 101 | RST 030 | Restart at location 000030 | 135 | 01 011 101 | OUT 16 | Output A reg. to output #16 |
| 036 | 00 011 110 | LDI* | Load D immediate | 136 | 01 011 110 | CAL* | (Same as 106) |
| 037 | 00 011 111 | RET | (Same as 007) | 137 | 01 011 111 | OUT 17 | Output A reg. to output #17 |
| 040 | 00 100 000 | INE | Increment the E register | 140 | 01 100 000 | JTC* | Jump true carry |
| 041 | 00 100 001 | DCE | Decrement the E register | 141 | 01 100 001 | OUT 20 | Output A reg. to output #20 |
| 042 | 00 100 010 | --- | (Undefined) | 142 | 01 100 010 | CTC* | Call true carry |
| 043 | 00 100 011 | RTC | Return true carry | 143 | 01 100 011 | OUT 21 | Output A reg. to output #21 |
| 044 | 00 100 100 | NDI* | AND immediate with A register | 144 | 01 100 100 | JMP* | (Same as 104) |
| 045 | 00 100 101 | RST 040 | Restart at location 000040 | 145 | 01 100 101 | OUT 22 | Output A reg. to output #22 |
| 046 | 00 100 110 | LEI* | Load E immediate | 146 | 01 100 110 | CAL* | (Same as 106) |
| 047 | 00 100 111 | RET | (Same as 007) | 147 | 01 100 111 | OUT 23 | Output A reg. to output #23 |
| 050 | 00 101 000 | DNH | Increment the H register | 150 | 01 101 000 | JTZ* | Jump true zero |
| 051 | 00 101 001 | DCH | Decrement the H register | 151 | 01 101 001 | OUT 24 | Output A reg. to output #24 |
| 052 | 00 101 010 | --- | (Undefined) | 152 | 01 101 010 | CTZ* | Call true zero |
| 053 | 00 101 011 | RTZ | Return true zero | 153 | 01 101 011 | OUT 25 | Output A reg. to output #25 |
| 054 | 00 101 100 | XRI* | EXCLUSIVE OR immediate with A reg. | 154 | 01 101 100 | JMP* | (Same as 104) |
| 055 | 00 101 101 | RST 050 | Restart at location 000050 | 155 | 01 101 101 | OUT 26 | Output A reg. to output #26 |
| 056 | 00 101 110 | LHI* | Load H immediate | 156 | 01 101 110 | CAL* | (Same as 106) |
| 057 | 00 101 111 | RET | (Same as 007) | 157 | 01 101 111 | OUT 27 | Output A reg. to output #27 |
| 060 | 00 110 000 | INL | Increment the L register | 160 | 01 110 000 | JTS* | Jump true sign |
| 061 | 00 110 001 | DCL | Decrement the L register | 161 | 01 110 001 | OUT 30 | Output A reg. to output #30 |
| 062 | 00 110 010 | --- | (Undefined) | 162 | 01 110 010 | CTS* | Call true sign |
| 063 | 00 110 011 | RIS | Return true sign | 163 | 01 110 011 | OUT 31 | Output A reg. to output #31 |
| 064 | 00 110 100 | ORI* | OR immediate with A reg. | 164 | 01 110 100 | JMP* | (Same as 104) |
| 065 | 00 110 101 | RST 060 | Restart at location 000060 | 165 | 01 110 101 | OUT 32 | Output A reg. to output #32 |
| 066 | 00 110 110 | LLI* | Load L immediate | 166 | 01 110 110 | CAL* | (Same as 106) |
| 067 | 00 110 111 | RET | (Same as 007) | 167 | 01 110 111 | OUT 33 | Output A reg. to output #33 |
| 070 | 00 111 000 | --- | (Undefined) | 170 | 01 111 000 | JTP* | Jump true parity |
| 071 | 00 111 001 | --- | (Undefined) | 171 | 01 111 001 | OUT 34 | Output A reg. to output #34 |
| 072 | 00 111 010 | --- | (Undefined) | 172 | 01 111 010 | CTP* | Call true parity |
| 073 | 00 111 011 | RTP | Return true parity | 173 | 01 111 011 | OUT 35 | Output A reg. to output #35 |
| 074 | 00 111 100 | CPI* | Compare immediate with A reg. | 174 | 01 111 100 | JMP* | (Same as 104) |
| 075 | 00 111 101 | RST 070 | Restart at location 000070 | 175 | 01 111 101 | OUT 36 | Output A reg. to output #36 |
| 076 | 00 111 110 | LMI* | Load memory immediate | 176 | 01 111 110 | CAL* | (Same as 106) |
| 077 | 00 111 111 | RET | (Same as 007) | 177 | 01 111 111 | OUT 37 | Output A reg. to output #37 |

* First byte of a multi-byte instruction.

Fig. 2.8.1--The 8008 Instructions in Numerical Order (Page 1)



SEC. 2.8 INSTRUCTION SET (cont'd)

| OCTAL | BINARY | MNEMONIC | DESCRIPTION | OCTAL | BINARY | MNEMONIC | DESCRIPTION |
|-------|------------|----------|------------------------------------|-------|------------|----------|---------------------------------|
| 200 | 10 000 000 | ADA | Add A register to A register | 300 | 11 000 000 | LAA | Load A register from A register |
| 201 | 10 000 001 | ADB | Add B register to A register | 301 | 11 000 001 | LAB | Load A register from B register |
| 202 | 10 000 010 | ADC | Add C register to A register | 302 | 11 000 010 | LAC | Load A register from C register |
| 203 | 10 000 011 | ADD | Add D register to A register | 303 | 11 000 011 | LAD | Load A register from D register |
| 204 | 10 000 100 | ADE | Add E register to A register | 304 | 11 000 100 | LAE | Load A register from E register |
| 205 | 10 000 101 | ADH | Add H register to A register | 305 | 11 000 101 | LAH | Load A register from H register |
| 206 | 10 000 110 | ADL | Add L register to A register | 306 | 11 000 110 | LAL | Load A register from L register |
| 207 | 10 000 111 | ADM | Add memory to A register | 307 | 11 000 111 | LAM | Load A register from memory |
| 210 | 10 001 000 | ACA | Add A reg. to A reg. with carry | 310 | 11 001 000 | LBA | Load B register from A register |
| 211 | 10 001 001 | ACB | Add B reg. to A reg. with carry | 311 | 11 001 001 | LBB | Load B register from B register |
| 212 | 10 001 010 | ACC | Add C reg. to A reg. with carry | 312 | 11 001 010 | LBC | Load B register from C register |
| 213 | 10 001 011 | ACD | Add D reg. to A reg. with carry | 313 | 11 001 011 | LBD | Load B register from D register |
| 214 | 10 001 100 | ACE | Add E reg. to A reg. with carry | 314 | 11 001 100 | LBE | Load B register from E register |
| 215 | 10 001 101 | ACH | Add H reg. to A reg. with carry | 315 | 11 001 101 | LBH | Load B register from H register |
| 216 | 10 001 110 | ACL | Add L reg. to A reg. with carry | 316 | 11 001 110 | LBL | Load B register from L register |
| 217 | 10 001 111 | ACM | Add memory to A reg. with carry | 317 | 11 001 111 | LBM | Load B register from memory |
| 220 | 10 010 000 | SUA | Subtract A reg. from A reg. | 320 | 11 010 000 | LCA | Load C register from A register |
| 221 | 10 010 001 | SUB | Subtract B reg. from A reg. | 321 | 11 010 001 | LCB | Load C register from B register |
| 222 | 10 010 010 | SUC | Subtract C reg. from A reg. | 322 | 11 010 010 | LCC | Load C register from C register |
| 223 | 10 010 011 | SUD | Subtract D reg. from A reg. | 323 | 11 010 011 | LCD | Load C register from D register |
| 224 | 10 010 100 | SUE | Subtract E reg. from A reg. | 324 | 11 010 100 | LCE | Load C register from E register |
| 225 | 10 010 101 | SUH | Subtract H reg. from A reg. | 325 | 11 010 101 | LCH | Load C register from H register |
| 226 | 10 010 110 | SUL | Subtract L reg. from A reg. | 326 | 11 010 110 | LCL | Load C register from L register |
| 227 | 10 010 111 | SUM | Subtract memory from A reg. | 327 | 11 010 111 | LCM | Load C register from memory |
| 230 | 10 011 000 | SBA | Subtract A reg. from A with borrow | 330 | 11 011 000 | LBA | Load D register from A register |
| 231 | 10 011 001 | SBB | Subtract B reg. from A with borrow | 331 | 11 011 001 | LDB | Load D register from B register |
| 232 | 10 011 010 | SBC | Subtract C reg. from A with borrow | 332 | 11 011 010 | LDC | Load D register from C register |
| 233 | 10 011 011 | SBD | Subtract D reg. from A with borrow | 333 | 11 011 011 | LDD | Load D register from D register |
| 234 | 10 011 100 | SBE | Subtract E reg. from A with borrow | 334 | 11 011 100 | LDE | Load D register from E register |
| 235 | 10 011 101 | SBH | Subtract H reg. from A with borrow | 335 | 11 011 101 | LDH | Load D register from H register |
| 236 | 10 011 110 | SBL | Subtract L reg. from A with borrow | 336 | 11 011 110 | LDL | Load D register from L register |
| 237 | 10 011 111 | SBM | Subtract memory from A with borrow | 337 | 11 011 111 | LDL | Load D register from memory |
| 240 | 10 100 000 | NDA | AND the A reg. with the A reg. | 340 | 11 100 000 | LEA | Load E register from A register |
| 241 | 10 100 001 | NDB | AND the B reg. with the A reg. | 341 | 11 100 001 | LEB | Load E register from B register |
| 242 | 10 100 010 | NDC | AND the C reg. with the A reg. | 342 | 11 100 010 | LEC | Load E register from C register |
| 243 | 10 100 011 | NDD | AND the D reg. with the A reg. | 343 | 11 100 011 | LED | Load E register from D register |
| 244 | 10 100 100 | NDE | AND the E reg. with the A reg. | 344 | 11 100 100 | LEE | Load E register from E register |
| 245 | 10 100 101 | NDH | AND the H reg. with the A reg. | 345 | 11 100 101 | LEH | Load E register from H register |
| 246 | 10 100 110 | NDL | AND the L reg. with the A reg. | 346 | 11 100 110 | LEL | Load E register from L register |
| 247 | 10 100 111 | NDM | AND memory with the A reg. | 347 | 11 100 111 | LEM | Load E register from memory |
| 250 | 10 101 000 | XRA | EXCL. OR the A reg. with A | 350 | 11 101 000 | LHA | Load H register from A register |
| 251 | 10 101 001 | XRB | EXCL. OR the B reg. with A | 351 | 11 101 001 | LHB | Load H register from B register |
| 252 | 10 101 010 | XRC | EXCL. OR the C reg. with A | 352 | 11 101 010 | LHC | Load H register from C register |
| 253 | 10 101 011 | XRD | EXCL. OR the D reg. with A | 353 | 11 101 011 | LHD | Load H register from D register |
| 254 | 10 101 100 | XRE | EXCL. OR the E reg. with A | 354 | 11 101 100 | LHE | Load H register from E register |
| 255 | 10 101 101 | XRH | EXCL. OR the H reg. with A | 355 | 11 101 101 | LHH | Load H register from H register |
| 256 | 10 101 110 | XRL | EXCL. OR the L reg. with A | 356 | 11 101 110 | LHL | Load H register from L register |
| 257 | 10 101 111 | XRM | EXCL. OR memory with A | 357 | 11 101 111 | LHM | Load H register from memory |
| 260 | 10 110 000 | ORA | OR the A reg. with the A reg. | 360 | 11 110 000 | LHA | Load L register from A register |
| 261 | 10 110 001 | ORB | OR the B reg. with the A reg. | 361 | 11 110 001 | LHB | Load L register from B register |
| 262 | 10 110 010 | ORC | OR the C reg. with the A reg. | 362 | 11 110 010 | LHC | Load L register from C register |
| 263 | 10 110 011 | ORD | OR the D reg. with the A reg. | 363 | 11 110 011 | LHD | Load L register from D register |
| 264 | 10 110 100 | ORE | OR the E reg. with the A reg. | 364 | 11 110 100 | LHE | Load L register from E register |
| 265 | 10 110 101 | ORH | OR the H reg. with the A reg. | 365 | 11 110 101 | LHH | Load L register from H register |
| 266 | 10 110 110 | ORL | OR the L reg. with the A reg. | 366 | 11 110 110 | LHL | Load L register from L register |
| 267 | 10 110 111 | ORM | OR memory with the A reg. | 367 | 11 110 111 | LHM | Load L register from memory |
| 270 | 10 111 000 | CFA | Compare A reg. with A reg. | 370 | 11 111 000 | LMA | Load memory from A register |
| 271 | 10 111 001 | CFB | Compare B reg. with A reg. | 371 | 11 111 001 | LMB | Load memory from B register |
| 272 | 10 111 010 | CFD | Compare C reg. with A reg. | 372 | 11 111 010 | LMC | Load memory from C register |
| 273 | 10 111 011 | CFD | Compare D reg. with A reg. | 373 | 11 111 011 | LMD | Load memory from D register |
| 274 | 10 111 100 | CPE | Compare E reg. with A reg. | 374 | 11 111 100 | LME | Load memory from E register |
| 275 | 10 111 101 | CFH | Compare H reg. with A reg. | 375 | 11 111 101 | LMH | Load memory from H register |
| 276 | 10 111 110 | CPL | Compare L reg. with A reg. | 376 | 11 111 110 | LML | Load memory from L register |
| 277 | 10 111 111 | CFM | Compare memory with A reg. | 377 | 11 111 111 | HIT | Halt until interrupted |

Fig. 2.8.1--The 8008 Instructions in Numerical Order (Page 2)

SEC. 2.8 INSTRUCTION SET (cont'd)

Note that in Figure 2.8.1, six instructions are labeled *undefined*, since the 8008 manufacturers do not specify what these instruction codes do. However, the 8008 user may consider these *NOP* (pronounced "no-op") or *no-operation* instructions. They can be used as time-fillers during a program. The instructions 042, 052, 062, 070, 071, and 072 operate as follows. Since the 8008 does not decode the instruction, it cannot perform any data manipulations or skip over any states. The CPU goes through all five states, T1 through T5, of a single PCI cycle. T5 terminates the instruction, as it always does. During T4 and T5 times, the CPU drives its data bus with the octal number 377. This implies that no internal register is either listening or talking at this time.

Note also that several instructions have multiple binary codes. Chapter 11 shows how these may be used to add extra instructions to the 8008 vocabulary. Chapter 16 puts some of these to practical use.

SEC. 2.9 A SIMPLE PROGRAM

In order to provide a feeling of how a microprocessor works, this section reviews how a short program gets executed.

```

PROGRAM TO SWAP B AND C REGISTERS
LAB LOAD A REGISTER FROM B REGISTER
LBC LOAD B REGISTER FROM C REGISTER
LCA LOAD C REGISTER FROM A REGISTER
    
```

Fig. 2.9.1 Swap B and C Using A Register

In this example, before execution of the program, the A register contained the number 123, the B register contained 234, and the C register contained 345. The execution of the program is illustrated in the chart in Figure 2.9.2.

| INSTRUCTION | REGISTER | | | DESCRIPTION |
|-------------|----------|-----|-----|----------------|
| | A | B | C | |
| | 123 | 234 | 345 | ORIGINAL STATE |
| LAB | 234 | " | 345 | LOAD A FROM B |
| LBC | 234 | 345 | " | LOAD B FROM C |
| LCA | " | " | 234 | LOAD C FROM A |
| | 234 | 345 | 234 | FINAL STATE |

Fig. 2.9.2--Chart Showing Transfers of Registers



SEC. 2.9 A SIMPLE PROGRAM

After the execution of these three instructions, the contents of the B and C registers are reversed from what they were originally. In the process of swapping, the contents of the A register were *destroyed*. Of course, it was not the object of the program to change (or save) the A register. The fact that a program destroys the contents of a particular register must be remembered by the programmer. Many programmers insert comments at the beginning of each program segment or subroutine telling which registers are needed as information by the program, which registers contain the results of the program's execution, and which registers are *used* or destroyed during the execution of the program.

Chapter 23 contains some Software Tricks which further illustrate how 8008 programs work.

SEC. 3.1 THE 8080

The 8080 was developed by Intel Corporation as an update of their first-generation microprocessor, the 8008. The 8080 has a great many advantages over the 8008; there are also a few minor disadvantages. This chapter discusses the main features of the 8080, with comparisons to the 8008.

SEC. 3.2 8080 HARDWARE

The 8080 is a much faster CPU than the 8008. The extra speed is attained partially by using the 17-volt N-channel MOS process. The 8080 requires three power supply voltages: +12, +5, and -5 volts. (The 8008 requires +5 and -9 volts). The +12 volt requirement is also for the external two-phase clock generator. Though the large voltage swing required cannot be supplied by ordinary TTL components--and generating the asymmetrical clock would take several TTL ICs--the problem is simplified by the availability of the type 8224 clock generator IC. Many computers need ± 12 V supplies already, for such accessories as EIA interfaces, analog circuitry, and the like. Further, -5 or -9 V supplies are needed for many memory devices (RAM and PROM) commonly used in microcomputers; these voltages may easily be dropped down from the -12 V supply.

The standard 8080 clock frequency is 2.0 MHz, as compared to the 500 KHz clock used with the standard 8008 (or the 800 KHz frequency of the 8008-1).

Another reason for the increased speed of the 8080 is that a full 16-bit memory address is available at separate address terminals on the 8080's 40-pin package. (The 18-pin 8008 requires its data bus to carry the low-order memory address, the high-order address, and a data word in successive cycles.) Thus, while an 8008 takes 20 μ s for a simple instruction (12.5 μ s, 8008-1), the 8080 takes 2.0 μ s for a simple instruction. (In either case, a complex instruction prolongs the cycle.)

Since 16 address bits are used for memory addressing, the 8080 can work directly with up to 64 K bytes of memory (65,536 8-bit data words). (The 8008 addresses 16 K.) Because of thermodynamic considerations, a 17-volt N-channel MOS processor inherently has the potential for higher speeds than a 14-volt P-channel processor (like the 8008) or a 5-volt N-channel CPU (such as the 6800). 8080s with instruction cycle times as fast as 1.0 μ s were available as this book went to press.

Improvements in the 17-volt MOS manufacturing process have resulted in benefits other than higher speed. For example, the size of the silicon die on which the 8080 is etched has been reduced significantly.



SEC. 3.2 8080 HARDWARE (cont'd)

Comparing die sizes among three 8080 manufacturers, one is 230 by 210 mils, or 48,300 square mils; the second is 170 by 197 mils, or 33,490 square mils; the third is 131 by 169 mils, or 22,139 square mils. Everything else being equal, these reductions in die size mean that more 8080s can be produced from each silicon wafer--which leads to a reduction in cost. Prices have fallen far since the \$360 single-quantity price tag for the 8080 was introduced. One advertisement has placed the price in lots of one million at \$6.00. Prices in more moderate quantities are not this low, but at any reasonable price the implication is clear: a powerful microcomputer can now be assembled at a cost that would have seemed incredibly low only a few years ago.

The 8080 is available from multiple suppliers, guaranteeing its acceptance as a standard part. These include Intel Corporation (3065 Bowers Ave., Santa Clara, CA 95051); Texas Instruments (P.O. Box 5012, Dallas, TX 75222); Advanced Micro Devices (901 Thompson Place, Sunnyvale, CA 94086); NEC Microcomputers (Five Militia Drive, Lexington, MA 02173); and National Semiconductor (2900 Semiconductor Dr., Santa Clara, CA 95051).

SEC. 3.3 8080 SOFTWARE

The 8080 does not include a program counter (PC) stack. Instead, the PC stack is located in external RAM memory. The stack pointer (SP), which points to the PC stack level from which instructions are currently being fetched, is a full 16 bits wide. Any area in the 8080's 64 K memory complement can be used for stack operations. A number of instructions have been added to the 8080 which permit direct manipulation of the stack.

The 8008 is much more limited with regard to stack operations. Addressed internally by a three-bit stack pointer, the 8008 PC stack is not externally addressable. This limits 8008 program subroutine nesting, a major disadvantage in long and complicated programs, and in interrupt handling.

Two obvious disadvantages accrue from the 8080's external stack. The first is that the minimal 8080 system must have at least some RAM in it--which adds to the cost of small industrial controllers. The second is that the stack pointer must be initialized to a valid RAM address as programming begins. (The 8008 does not require any special attention to its stack pointer when being initialized--which occurs through an initial interrupt sequence.) Once again, however, these disadvantages are outweighed by the unlimited subroutine nesting and by the availability of PUSH and POP instructions for storing and retrieving registers other than the PC.

SEC. 3.3 8080 SOFTWARE (cont'd)

A program written for the 8008 can be translated for the 8080 with little trouble. The internal microcoding of the 8080 dictated a rearrangement of opcodes, and the binary machine codes for most 8008 instructions have been changed. In most cases, a one-to-one substitution can be made. There are two notable exceptions. First, since the SP is entirely under program CPU control in the 8080, the stack pointer must be initialized to a valid address in RAM when the machine is started so that the PC may be pushed and popped when CALL and RETURN instructions are executed, as discussed above. Second, 8080 INP and OUT instructions take two bytes, rather than one as they did in the 8008. The corresponding advantage: an increase in the number of addressable I/O ports.

Figure 3.3.1 shows a list of 8080 instructions, condensed from a listing frequently seen in manufacturer's publications. Though the order in which the instructions appear may seem arbitrary, there is an organizing principle. Namely, the instructions which appear in the first two columns are all found in the 8008 microprocessor. The opcodes have been changed, as well as the mnemonics.

The 8080 IN and OUT instructions, marked with an asterisk, are similar to the 8008 equivalents, except (as noted above) they are two bytes in length.

The instructions in the third and fourth columns of Fig. 3.3.1, starting with LXI B, are those which have been added to the 8080 instruction set.

Note that with the 8080, the program is permitted to address certain *pairs* of registers--not only the usual address registers, the H and the L, but the B and C together, and the D and E together. Direct loading and storing of the HL register pair at any memory location is also allowed. Together with the double-precision add (DAD) and increment/decrement instructions, these almost make the HL register pair into a 16-bit accumulator (while the A register is certainly an 8-bit accumulator).

Also added are instructions to load immediate the register pairs; and the BC and DE register pairs may be used as addresses for loading and storing the A register.

The 8080 can increment or decrement either the A register, or memory (the data word in memory addressed by the HL register pair) -- both of which instruction types were not provided with the 8008.



SEC. 3.3 8080 SOFTWARE (cont'd)

| Mnemonic | Description | XRI | Exclusive Or immediate with A | IN | Input | XTHL | Exchange top of stack, H & L |
|-------------------------------------|---------------------------------------|------|-------------------------------|----------|------------------------------------|--------|------------------------------|
| MOV r ₁ , r ₂ | Move register to register | ORI | Or immediate with A | OUT | Output | SPHL | H & L to stack pointer |
| MOV M, r | Move register to memory | CPI | Compare immediate with A | LXI B | Load immediate register Pair B & C | PCHL | H & L to program counter |
| MOV r, M | Move memory to register | RLC | Rotate A left | LXI D | Load immediate register Pair D & E | DAD B | Add B & C to H & L |
| HLT | Halt | RRC | Rotate A right | LXI H | Load immediate register Pair H & L | DAD D | Add D & E to H & L |
| MVI r | Move immediate register | RAL | Rotate A left through carry | LXI SP | Load immediate stack pointer | DAD H | Add H & L to H & L |
| MVI M | Move immediate memory | RAR | Rotate A right through carry | PUSH B | Push register Pair B & C on stack | DAD SP | Add stack pointer to H & L |
| INR r | Increment register | JMP | Jump unconditional | PUSH D | Push register Pair D & E on stack | STAX B | Store A indirect |
| DCR r | Decrement register | JNC | Jump on no carry | PUSH H | Push register Pair H & L on stack | STAX D | Store A indirect |
| INR M | Increment memory | JZ | Jump on zero | PUSH PSW | Push A and Flags on stack | LDAX B | Load A indirect |
| DCR M | Decrement memory | JNZ | Jump on no zero | POP B | Pop register pair B & C off stack | LDAX D | Load A indirect |
| ADD r | Add register to A | JP | Jump on positive | POP D | Pop register pair D & E off stack | INX B | Increment B & C registers |
| ADC r | Add register to A with carry | JM | Jump on minus | POP H | Pop register pair H & L off stack | INX D | Increment D & E registers |
| SUB r | Subtract register from A | JPE | Jump on parity even | POP PSW | Pop A and Flags off stack | INX H | Increment H & L registers |
| SBB r | Subtract register from A with borrow | JPO | Jump on parity odd | STA | Store A direct | INX SP | Increment stack pointer |
| ANA r | And register with A | CALL | Call unconditional | CMA | Complement A | DCX B | Decrement B & C |
| XRA r | Exclusive Or register with A | CALL | Call on carry | CMC | Complement carry | DCX D | Decrement D & E |
| ORA r | Or register with A | CC | Call on no carry | DAA | Decimal adjust A | DCX H | Decrement H & L |
| CMP r | Compare register with A | CNC | Call on carry | SHLD | Store H & L direct | DCX SP | Decrement stack pointer |
| ADD M | Add memory to A | CZ | Call on zero | LDA | Load A direct | CMA | Complement A |
| ADC M | Add memory to A with carry | CP | Call on positive | LDI | Load A direct | STC | Set carry |
| SUB M | Subtract memory from A | CM | Call on minus | XCHG | Exchange D & E, H & L Registers | CMC | Complement carry |
| SBB M | Subtract memory from A with borrow | CPE | Call on parity even | NO | No operation | DAA | Decimal adjust A |
| ANA M | And memory with A | CPO | Call on parity odd | | | SHLD | Store H & L direct |
| XRA M | Exclusive Or memory with A | RET | Return | | | LHLD | Load H & L direct |
| ORA M | Or memory with A | RC | Return on carry | | | EI | Enable interrupts |
| CMP M | Compare memory with A | RNC | Return on no carry | | | DI | Disable interrupt |
| ADI | Add immediate to A | RZ | Return on zero | | | NO | No operation |
| ACI | Add immediate to A with carry | RNZ | Return on no zero | | | | |
| SUI | Subtract immediate from A | RP | Return on positive | | | | |
| SBI | Subtract immediate from A with borrow | RM | Return on minus | | | | |
| ANI | And immediate with A | RPE | Return on parity even | | | | |
| | | RPO | Return on parity odd | | | | |
| | | RST | Restart | | | | |

Fig. 3.3.1--8080 Instructions.

Fig. 3.3.2 shows the 8080 instruction set by alphabetical order. The format is designed to aid the 8080 user in learning the 8080 instruction codes. As stated in the note on this chart, the 8080 is microcoded in such a manner that its instruction set is more easily memorized when presented in octal (rather than hex) format. Nevertheless, hex is frequently used.

Fig. 3.3.3 presents the 8080 instruction set graphically. The organization of this chart illustrates how various memory-referencing instructions work, and should be useful to the 8080 user just becoming familiar with its instruction set.

A detailed description of each 8080 instruction is presented in the 8080 data sheet, reprinted near the end of this book.

SEC. 3.3 8080 SOFTWARE (cont'd)

8080 INSTRUCTION SET

Summary of Processor Instructions in Alphabetical Order

| Mnemonic | Description | Octal Code | Mnemonic | Description | Octal Code |
|--------------|-------------------------------|------------|----------|--------------------------------|------------|
| ACI data | Add immediate to A with carry | 3 1 6 | ORA r | OR register with A | 2 6 r |
| ADC r | Add register to A with carry | 2 1 r | ORI data | OR immediate with A | 3 6 6 |
| ADD r | Add register to A | 2 0 r | OUT port | Output | 3 2 3 |
| ADI data | Add immediate to A | 3 0 6 | PCHL | HL to program counter | 3 5 1 |
| ANA r | AND register with A | 2 4 r | POP rp | Pop register pair off stack | 3 rp 1 |
| ANI data | AND immediate with A | 3 4 6 | | (only B, D, H) | |
| CALL addr | Call unconditional | 3 1 5 | POP PSW | Pop A and flags off stack | 3 6 1 |
| Cc addr | Call on condition | 3 c 4 | PUSH rp | Push register pair onto stack | 3 rp 5 |
| CMA | Complement A | 0 5 7 | | (only B, D, H) | |
| CMC | Complement carry | 0 7 7 | PUSH PSW | Push A and flags onto stack | 3 6 5 |
| CMP r | Compare register with A | 2 7 r | RAL | Rotate A left through carry | 0 2 7 |
| CPI data | Compare immediate with A | 3 7 6 | RAR | Rotate A right through carry | 0 3 7 |
| DAA | Decimal adjust A | 0 4 7 | Rc | Return on condition | 3 c 0 |
| DAD rp | Add register pair to HL | 0 rp+1 1 | RET | Return | 3 1 1 |
| DCR r | Decrement register | 0 r 5 | RLC | Rotate A left | 0 0 7 |
| DCX rp | Decrement register pair | 0 rp+1 3 | RRC | Rotate A right | 0 1 7 |
| DI | Disable interrupts | 3 6 3 | RST n | Restart | 3 n 7 |
| EI | Enable interrupts | 3 7 3 | SBB r | Subtract reg. from A w/borrow | 2 3 r |
| HLT | Halt | 1 6 6 | SBI data | Subtract imm. from A w/borrow | 3 3 6 |
| IN port | Input | 3 3 3 | SHLD | Store HL direct | 0 4 2 |
| INR r | Increment register | 0 r 4 | SPHL | HL to stack pointer | 3 7 1 |
| INX rp | Increment register pair | 0 rp 3 | STA addr | Store A direct | 0 6 2 |
| JMP addr | Jump unconditional | 3 0 3 | STAX rp | Store A indirect (only B, D) | 0 rp 2 |
| Je addr | Jump on condition | 3 c 2 | STC | Set carry | 0 6 7 |
| LDA addr | Load A direct | 0 7 2 | SUB r | Subtract register from A | 2 2 r |
| LDAX rp | Load A indirect (only B, D) | 0 rp+1 2 | SUI data | Subtract immediate from A | 3 2 6 |
| LHLD addr | Load HL direct | 0 5 2 | XCHG | Exchange DE, HL register pairs | 3 5 3 |
| LXI rp, data | Load immediate register pair | 0 rp 1 | XRA r | Exclusive OR register with A | 2 5 r |
| MOV d, s | Move register to register | 1 d s | XRI data | Exclusive OR immediate with A | 3 5 6 |
| MVI r, data | Move immediate register | 0 r 6 | XTHL | Exchange top of stack with HL | 3 4 3 |
| NOP | No operation | 0 0 0 | | | |

3

ABBREVIATIONS

| Abbrev. | Description | Bits |
|---------|----------------|------|
| addr | Memory address | 16 |
| c | Condition | 3 |
| d | Destination | 3 |
| data | Data | 8/16 |
| port | I/O port | 8 |
| r | Register | 3 |
| rp | Register pair | 2 |
| s | Source | 3 |

INSTRUCTION CODE VALUES

| OCTAL CODE | REGISTER (d, r, s) | REGISTER PAIR (rp) (rp+1) | CONDITION (c) | Abbrev. | Description | Flag |
|------------|--------------------|---------------------------|---------------|---------|-------------|--------|
| 0 | B | BC | -- | NZ | Not zero | Z = 0 |
| 1 | C | -- | BC | Z | Zero | Z = 1 |
| 2 | D | DE | -- | NC | No carry | CY = 0 |
| 3 | E | -- | DE | C | Carry | CY = 1 |
| 4 | H | HL | -- | PO | Parity odd | P = 0 |
| 5 | L | -- | HL | PE | Parity even | P = 1 |
| 6 | M | SP | -- | P | Plus | S = 0 |
| 7 | A | -- | SP | M | Minus | S = 1 |

8080 INSTRUCTIONS IN OCTAL FORMAT

The 8080 is an 8-bit microprocessor, and its instruction code tends to break down into a 2/3/3-bit grouping. This is why it was convenient in this chart to list 8080 instructions in octal format, where digits follow this same pattern.

Hexadecimal notation (4/4-bit grouping) is often used instead of octal, but since hex does not correspond directly to the way in which the 8080 is microcoded, hex instruction codes are not readily listed in condensed graphic form, and are more difficult for the programmer to learn.

Copyright © 1976, Martin Research

Figure 3.3.2



SEC. 3.3 8080 SOFTWARE (cont'd)

| OCTAL | HEX | 8080 SYMBOL | 8080 SYMBOL | OCTAL | HEX | 8080 SYMBOL | 8080 SYMBOL |
|-------|-----|----------------|----------------|-------|-----|----------------|----------------|
| 200 | 80 | ADD B | ADB | 300 | 00 | RNZ | RFZ |
| 201 | 81 | ADD C | ADC | 301 | C1 | POP B | |
| 202 | 82 | ADD D | ADD | 302 | C2 | JNZ | JFZ |
| 203 | 83 | ADD E | ADE | 303 | C3 | JMP | JMP |
| 204 | 84 | ADD H | ADH | 304 | C4 | CVZ | CFZ |
| 205 | 85 | ADD L | ADL | 305 | C5 | PUSH B | |
| 206 | 86 | ADD M | ADM | 306 | C6 | ADI | ADI |
| 207 | 87 | ADD A | ADA | 307 | C7 | RST 0 | RST 000 |
| 210 | 88 | ADC B | ACB | 310 | C8 | RZ | RTZ |
| 211 | 89 | ADC C | ACC | 311 | C9 | RET | RET |
| 212 | 8A | ADC D | ACD | 312 | CA | JZ | JTZ |
| 213 | 8B | ADC E | ACE | 313 | CB | (Undefined) | |
| 214 | 8C | ADC H | ACH | 314 | CC | CZ | CFZ |
| 215 | 8D | ADC L | ACL | 315 | CD | CALL | CAL |
| 216 | 8E | ADC M | ACM | 316 | CE | ACI | ACI |
| 217 | 8F | ADC A | ACA | 317 | CF | RST 1 | RST 010 |
| 220 | 90 | SUB B | SUB | 320 | DO | RNC | RFC |
| 221 | 91 | SUB C | SUC | 321 | D1 | POP D | |
| 222 | 92 | SUB D | SUD | 322 | D2 | JNC | JFC |
| 223 | 93 | SUB E | SUE | 323 | D3 | OUT | OUT |
| 224 | 94 | SUB H | SUH | 324 | D4 | CNC | CFC |
| 225 | 95 | SUB L | SUL | 325 | D5 | PUSH D | |
| 226 | 96 | SUB M | SUM | 326 | D6 | SUI | SUI |
| 227 | 97 | SUB A | SUA | 327 | D7 | RST 2 | RST 020 |
| 230 | 98 | SBB B | SBB | 330 | D8 | RC | RTC |
| 231 | 99 | SBB C | SBC | 331 | D9 | (Undefined) | |
| 232 | 9A | SBB D | SBD | 332 | DA | JC | JTC |
| 233 | 9B | SBB E | SBE | 333 | DB | INP | INP |
| 234 | 9C | SBB H | SBH | 334 | DC | CC | CTC |
| 235 | 9D | SBB L | SBL | 335 | DD | (Undefined) | |
| 236 | 9E | SBB M | SBM | 336 | DE | SBI | SBI |
| 237 | 9F | SBB A | SBA | 337 | DF | RST 3 | RST 030 |
| 240 | A0 | ANA B | NDE | 340 | EO | RPO | RFP |
| 241 | A1 | ANA C | NDC | 341 | E1 | POP H | |
| 242 | A2 | ANA D | NDD | 342 | E2 | JPO | JFP |
| 243 | A3 | ANA E | NDE | 343 | E3 | XTHL | |
| 244 | A4 | ANA H | NDH | 344 | E4 | CPO | CFP |
| 245 | A5 | ANA L | NDL | 345 | E5 | PUSH H | |
| 246 | A6 | ANA M | NDM | 346 | E6 | ANI | NDI |
| 247 | A7 | ANA A | NDA | 347 | E7 | RST 4 | RST 040 |
| 250 | A8 | XRA B | XRB | 350 | E8 | RPE | RTP |
| 251 | A9 | XRA C | XRC | 351 | E9 | PCHL | |
| 252 | AA | XRA D | XRD | 352 | EA | JPE | JTP |
| 253 | AB | XRA E | XRE | 353 | EB | XCHG | |
| 254 | AC | XRA H | XRH | 354 | EC | CPE | CTP |
| 255 | AD | XRA L | XRL | 355 | ED | (Undefined) | |
| 256 | AE | XRA M | XRM | 356 | EE | XRI | XRI |
| 257 | AF | XRA A | XRA | 357 | EF | RST 5 | RST 050 |
| 260 | B0 | ORA B | ORB | 360 | FO | RP | RTP |
| 261 | B1 | ORA C | ORC | 361 | F1 | POP PSW | |
| 262 | B2 | ORA D | ORD | 362 | F2 | JP | JFS |
| 263 | B3 | ORA E | ORE | 363 | F3 | DI | |
| 264 | B4 | ORA H | ORH | 364 | F4 | CP | CFP |
| 265 | B5 | ORA L | ORL | 365 | F5 | PUSH PSW | |
| 266 | B6 | ORA M | ORM | 366 | F6 | ORI | ORI |
| 267 | B7 | ORA A | ORA | 367 | F7 | RST 6 | RST 060 |
| 270 | B8 | CMP B | CPB | 370 | F8 | RM | RFS |
| 271 | B9 | CMP C | CPC | 371 | F9 | SPHL | |
| 272 | BA | CMP D | CPD | 372 | FA | JM | JTS |
| 273 | BB | CMP E | CPE | 373 | FB | EI | |
| 274 | BC | CMP H | CPH | 374 | FC | CM | CTS |
| 275 | BD | CMP L | CPL | 375 | FD | (Undefined) | |
| 276 | BE | CMP M | CPM | 376 | FE | CFI | CFI |
| 277 | BF | CMP A | CPA | 377 | FF | RST 7 | RST 070 |

Figure 3.3.4
(Part 2)

microcomputer
design

SEC. 3.4 SELECTED 8080 TECHNICAL NOTES

In order to give the clearest possible explanation of a practical 8080 circuit, we have reprinted the data sheet for the Model 471 8080 CPU board near the end of this book. This data sheet includes a schematic diagram with a full description of operations, including such adjuncts as memory-mapped I/O addressing and interrupt reset and hold circuitry.

This section presents important technical matters concerning 8080 designs generally. Some are to clarify points not made clearly in existing 8080 applications literature; other reflect design experience. We recommend that the reader start with the chapter on the 471 CPU and familiarize himself with the 8080 data sheet before reading the following discussions.

3.4.1 Memory Access Time The designer unused to memory system design may have difficulty in divining from the 8080 and memory data sheets whether a given chip meets the 8080 requirements.

An 8080 microcomputer addresses memory with its sixteen-bit address bus; data transfers take place via the 8-bit data bus. The memory address must be valid before the data transfer takes place, so that circuitry external to the CPU can decode the address and provide suitable enabling signals to the memory device that has been selected. The memory chip cannot instantaneously make the selected data word available, moreover; there is always an appreciable delay between the time the chip is enabled and the time that it can reliably be read from or written into.

The chart below, Fig. 3.4.1, relates 8080 speed to memory speed requirements. The figures are based on an 8080 system making use of the 8224 clock generator.

| CPU | Clock Cycle | Read Access Time | Write Access Time | Write Pulse Time |
|----------|-------------|---------------------|----------------------|---------------------|
| 8080A | 500 ns | 610 ns | 720 ns | 500 ns |
| 8080A-2 | 375 ns | 405 ns | 465 ns | 375 ns |
| 8080A-1* | 325 ns | 340 ns | 400 ns | 325 ns |
| 8080A-4* | 250 ns | 225 ns | 285 ns | 250 ns |

*See text

Figure 3.4.1--8080 Speeds Related to Memory Speed Requirements



microcomputer
design

SEC. 3.4 SELECTED 8080 TECHNICAL NOTES

The values shown in Figure 3.4.1 are based on data sheets for the 8080 variations shown and on the 8224 clock driver. Note that the 8080 versions marked with an asterisk require an oscillator speed greater than 27 MHz, the speed limit of early Intel 8224 clock generators; a premium device is needed. The read and write access figures shown are based on ideal calculations, based on 8080 and 8224 characteristics alone--plus 40 ns to allow for system delays. The paragraphs that follow support these calculations.

The 8080 accommodates memory timing characteristics with the following timing sequences. Within a machine cycle which addresses memory, there are three states, T1-T3, each lasting one clock period. As ϕ_2 goes high during T1, a memory address is clocked onto the 8080 address bus. The time it takes for this address to settle on the bus is t_{da} (address output delay from ϕ_2). At T3 time--two clock cycles later--data transfers take place. The interval between T1 and T3 is provided principally so that memory access is assured before a data transfer takes place.

When the 8080 is *reading* from memory, input data must be available on the data bus before ϕ_2 of T3, when the 8080 latches up this data internally. It must be stable previous to ϕ_2 by the period t_{ds2} (data set-up time to ϕ_2 during DBIN). The preceding factors give the formula for memory access time during 8080 read cycles: $2 t_{cy} - t_{da} - t_{ds2}$, where t_{cy} is the clock cycle time. For an 8080A running at the standard 2.0 MHz clock frequency, this is 2 (500 ns) - 200 ns - 150 ns, or 650 ns. However, this figure is ideal; no delays have been allowed for bus drivers, memory decoders, interconnecting cables, or other factors. A safe practice is to specify memory with a *read* mode access time of 610 ns or better.

During the memory *write* mode, the minimum required memory access time is measured from the time that the address becomes stable, to the beginning of the memory write pulse. This signal, \overline{WR} , is initiated by the 8080 at the leading edge of ϕ_1 during T3 time. It lasts one full clock cycle, 500 ns at standard speed. Thus, the 8080 again provides memory with two clock cycles--here diminished by the address set-up time, and by the amount of time that ϕ_1 precedes ϕ_2 (t_{d3} , typically 120 ns with the 8080A). The formula provided by Intel is $t_{aw} = 2 t_{cy} - t_{d3} - t_{r\phi_2} - 140$ ns, where $t_{r\phi_2}$ is the clock rise time (20 ns with the 8224 clock generator)--working out to 760 ns. Again, this figure should be reduced to allow for system delays. Safe practice is to specify a *write* mode access time of 720 ns or better.

Factors to be considered in a practical memory design include how the memory chip is selected and its address decoded. These matters are discussed further in Chapter 13.



microcomputer
design

SEC. 3.4 SELECTED 8080 TECHNICAL NOTES

3.4.2 Memory Wait Cycles A slow memory device, which does not meet 8080 speed requirements, can be synchronized with the CPU by pulling down the 8080's READY terminal shortly after it has been selected. Detected by the CPU during T2 time, this condition causes the 8080 to enter one or more TW states, essentially extra T3 clock cycles. Effectively, the DBIN enable signal (or \overline{WR} output strobe) is lengthened by the period t_{cy} for each wait cycle incurred.

Summary: To produce n wait states in an 8080 system, pull down the RDYIN input to the 8224 clock generator for a period of approximately $(n - 1/6) t_{cy}$, starting at the beginning of the STB system strobe.

The following paragraphs explain this formula, and the circuit for the 471 CPU board shows a practical wait circuit. (See the 471 data sheet, near the end of this book, Sec. 1.10.) Assume that one wait state is required in an 8080 computer operating with a 2.0 MHz clock, in order to add 500 ns to the 8080 memory access cycle.

The 8080 samples the READY line at the falling edge of ϕ_2 , during T2 time. To provide proper data set-up time, the RDYIN input of the 8224 clock generator is generally used to synchronize wait requests with the *rising* edge of ϕ_2 . This means that to cause a wait state, the request must be received by the 8224 before the rising edge of ϕ_2 during T2 time. The selected memory device must enter its request sometime during the period starting when it was selected by an address on the address line--at about T1- ϕ_2 , plus delays--and ending at T2- ϕ_2 , when the 8224 samples for requests. The request must be *removed* before the rising edge of ϕ_2 of the last required wait cycle, to avoid causing another wait.

The one-shot requesting a wait is triggered by the leading edge of the system strobe, STSTB (STB for short), which falls at ϕ_1A time, just at the end of T1. This is about $1/9 t_{cy}$ before T2- ϕ_1 , and $1/3 t_{cy}$ before T2- ϕ_2 . The 8224 clocks this request at the beginning of T2- ϕ_2 ; the 8080 sees it at the end of T2- ϕ_2 , entering a wait state. The one-shot withdraws the request sometime after ϕ_2 begins; by the next ϕ_2 , the 8224 sees no request; the 8080 realizes that the wait should end; and so it does.

In order to avoid precision timing components, the one-shot period is chosen to end midway between ϕ_2 pulses (rising edges). For one wait state, a delay (after the first ϕ_2) of $1/2 t_{cy}$ is chosen; for two wait states, the delay is $1\frac{1}{2} t_{cy}$; etc. This generalizes to $(n - \frac{1}{2}) t_{cy}$ for n wait states. But, since STB fires the one-shot $1/3 t_{cy}$ before T2- ϕ_2 , this period must be added: $(n - \frac{1}{2}) t_{cy} + 1/3 t_{cy} = (n - 1/6) t_{cy}$.



microcomputer
design

SEC. 3.4 SELECTED 8080 TECHNICAL NOTES

3.4.3 8080 Variations The 8080 devices available from the different manufacturers may vary in electrical characteristics. For example, the 9080A from Advanced Micro Devices offers improved output drive current capability. Other distinctions are discussed in the 471 data sheet, Sec. 1.2. The reader should secure current specifications from the manufacturers to supplement this information, since new developments are frequent.

Worthy of further note is the 8080 version available from NEC Microcomputers, which operates from a 5-volt symmetrical clock (using circuitry very similar to that discussed in Chapter 5 for the 8008).

3.4.4 Preventing 8080 Hang-up States An active concern in micro-computer systems used as controllers is that if some unforeseen failure should cause the CPU to leave its normal program path, most likely the system will "walk out" of the bad state and continue its controlling job as well as possible.

Two design goals are important in preventing hang-up states. The first is to minimize the probability that a noise spike can derail the microprocessor. This is both a software and a hardware problem; the hardware aspect requires the engineer to design the power supply, packaging, wiring, and shielding to minimize interference from noise sources. In terms of software, the 8080 is superior to the 8008 in the respect that the 8080 has only one code for the HALT instruction--166--whereas, the 8008 has three--000, 377, and 001--the first two of which might easily result from access to a non-existent memory location.

The other objective is to provide a method whereby the micro-processor will recover its normal program mode. In interrupt systems, the 8080 presents the problem that interrupts may be disabled by software, and if the computer enters the HALT state while interrupts are disabled, then there is no way for the CPU to continue unless it is reset. A solution appears in the data sheet for the 471 CPU board (Sec. 1.7).



microcomputer
design

SEC. 4.1 INTRODUCTION

In electronics, the word *microprocessor* has become the buzz-word of the mid-seventies. But there is a great deal of confusion surrounding the term. When for example does a *microcomputer* become a *mini-computer*? Advertising claims tend to obscure the differences, and much energy, time, and money are wasted by designers who mismatch a computer with an application.

As a first approximation in clarifying the issue, let us use price as a criterion. A computer costing less than \$25.00 is a *microcomputer*; a computer costing between \$25 and \$250 is a *milli-computer*; one with a cost between \$250 and \$2500 is a *minicomputer*; and a computer costing over \$2500 is a *main frame computer*. These are prices in volume to an original equipment manufacturer (OEM), and include the approximate cost of the central processing unit with all control logic and associated memory.

Microprocessors which could be used to build *microcomputers* by this definition would include the 9002 from Electronic Arrays; the F8 chip set from Fairchild; and the TMS 1000 series from Texas Instruments. The Intel 4004 and 4040 are also in this category.

Millicomputers would be based on such processors as the Motorola 6800 (also available from American Microsystems); the Intel 8080 (also available from Texas Instruments, Advanced Micro Devices, and NEC Micro-computers); the MOS Technology 6500 series; and the Sigmetics 2650. Computer Automation makes a computer called the *Naked Milli* which fits roughly at the top end of the millicomputer price range.

Minicomputers, of course, are a class of small computers which have been available since the early sixties. Finding wide use in industrial, educational, and business applications, they are offered by a number of manufacturers. Until the advent of integrated circuits using large-scale integration (LSI)--based chiefly on metal-oxide semiconductors (MOS)--minicomputers were the smallest computers available.

Another way of distinguishing computing devices is by their intended application. If the device in its final form looks like a computer--with a console, and the ability to start and stop operations in order to enter new programs under operator control--then it is properly called a *computer*. But if the processor is especially dedicated to the control of a particular machine--and there are no operating controls relating directly to the functioning of the computer as such--then the processor operates as a *controller*.

There are at least two special characteristics of controllers. First, an important feature is its ability to walk out of bad states. In other words, there should ideally be no condition into which the machine can get--through noise or hardware/software bugs-- from which



microcomputer
design

SEC. 4.1 INTRODUCTION (cont'd)

it cannot successfully exit, resuming the task of machine control. A hangup state might cause the machine to malfunction disastrously--or sit inoperative until a skilled technician can reset it. This would not be so important with a computer (used as such), which encounters little noise--and which, in case of failure, can simply be reset by the operator, restarting the program.

A second way of distinguishing a controller from a computer is the kind of programming it is called upon to execute. The processing power, memory-addressing capability, and (sometimes) the speed of a general-purpose computer may be wasted on many small controllers--whose main function is often to control data I/O functions and to time various machine functions. When the machine is to be produced in high volumes, a simpler processor will optimize the cost of the machine without sacrificing any machine potential.

If the application requires a great deal of complex data handling, the cost of including a computer in the final product depends not just on the hardware, but on the software. Large computer users were forced to realize in the fifties and sixties that the cost of programming is often greater than the cost of the computers themselves. Many micro-computer and millicomputer users are discovering this in the seventies. Fortunately high-level languages are becoming available for use in developing software for these computers. Even so, there remain many applications needing complex software where the availability of tested programs makes minicomputers competitive. This is especially true when the production volume is expected to be relatively low; it makes no sense to develop thousands of dollars of software, to save hundreds of dollars in hardware.

SEC. 4.2 SYSTEMS DESIGN

When planning a computer application, the designer should be thinking at the systems level--not just about the CPU. The microprocessor revolution has focused so much attention on the processor that this point is often lost. As a result, one often hears someone planning to interface 32 K bytes of memory, a floppy disc controller, and a \$2000 video terminal--to a millicomputer or even a microcomputer. The CPU itself accounts for a very tiny part of the system cost--too small a proportion, in fact. This is analogous to purchasing a high-fidelity music system with a \$300 record changer, a \$600 tape deck, and a \$500 stereo receiver--and connecting it to two \$5 four-inch speakers. The computer system would be limited by the abilities of the processor--which cannot access 32 K of memory in a reasonable time, or input a megabyte of data rapidly.



microcomputer
design

SEC. 4.2 SYSTEMS DESIGN (cont'd)

Along the same lines, it makes little sense for a retail store owner to purchase a millicomputer or microcomputer for doing inventory for his store, plus compiling bookkeeping records at the end of the month--at least, unless he is an expert programmer, or can purchase a specially designed program tailor-made for his application. Here, software availability limits the computer, as much as the hardware; but the limitation is just as significant.

However, a large manufacturer might be able to produce 2,000 such business machines profitably. The costs of developing the software could be spread out over a number of products, justifying the effort.

Microcomputers and millicomputers very definitely have their place. Many are ideally suited as controllers, buried inside a piece of business or industrial equipment that the user might not suspect has a computer in it at all. Here is where the *minicomputer* makes little sense. Its memory-addressing power, its powerful instruction set, and its speed are just overkill for an automobile emission control system, or inside a printer, or for hundreds of other such applications.

In addition, microcomputers are ideal for educational purposes, in teaching computer science principles at all school levels. Microcomputers offer students the first practical opportunity to own their own computers. In a classroom setting, multi-processor arrays can be assembled, allowing many students to perform problems, and to access a central computer for complex subroutines and high-speed peripherals on a time-shared basis.

SEC. 4.3 PROCESSOR COMPARISONS

This section consists of brief sketches of selected current micro-processors (including some that might more properly be termed *milli-processors*). By no means exhaustive, this compilation is intended only to summarize some important features, and to sketch limitations and advantages.

4.3.1 *8008 and 8080* Discussed in detail in this book, the 8080 is generally used in new applications. 8008 machines are being upgraded to the 8080, where the added features are advantageous. A comparison between these processors appears in Chapter 3 above.

The disadvantages of the 8080 include the necessity for three power supplies: +12, +5, and -5 V. However, the current required at -5 V is very low, and a negative voltage is necessary anyway for many



microcomputer
design

SEC. 4.3 PROCESSOR COMPARISONS (cont'd)

PROMs, some RAMs, and much analog circuitry (including EIA circuitry for interfacing with terminals). A concomitant advantage: with 17 V of on-chip potential, the 8080 is available in high-speed versions which are significantly faster than 5-volt processors.

A programming disadvantage: the lack of branch relative instructions in the 8080 (or 8008). These instructions, well-known to mini-computer programmers, allow one to create jumps to locations near the current instruction location, without having to specify an absolute memory address. This facilitates the writing of program loops, and greatly simplifies the task of relocating programs during software development. Instead of loading the second and third bytes of a branch instruction into the program counter (as is done with the 8080), the value of the second instruction byte is added to the program counter using two's complement arithmetic. The machine jumps to the specified new location, ranging forward 127 bytes or backward 128 bytes, depending on the value of the second instruction byte.

On the other hand, the 8080 (and 8008) include a relatively large number of internal index registers--six eight-bit registers, addressable (in the 8080) as three 16-bit registers for many purposes. This both facilitates memory addressing, and at the same time, allows many data storage needs to be satisfied without recourse to external memory at all.

The 8080 is multiply-sourced, and has clearly become a standard eight-bit milliprocessor (though not the only one). Software is available, and is likely to continue being generated for some time to come.

4.3.2 6800 The 6800 was the second processor of second-generation capabilities to reach production. If only because the 8008/8080 came first, the 6800 took longer to become widely used by large manufacturers. But the designer who is just now making a choice may find it difficult to choose between the 6800 and the 8080. The 6800 often has the edge, except where maximum speed is important.

One of the outstanding advantages of the 6800 is its single power supply, +5 V, which cuts the cost of those systems which do not otherwise need ± 12 V supplies.

Equally important, the 6800 instruction set looks like classic computer software. A minicomputer programmer is more likely to feel comfortable with the 6800, at least at first glance, than with the 8080. Included are relative addressing instructions, outlined briefly above.



microcomputer
design

SEC. 4.3 PROCESSOR COMPARISONS (cont'd)

The 6800 requires a two-phase clock generator with high-capacitance drive capability and fast rise and fall times. Special hybrid clock generators are available, since these requirements are not easily met with standard TTL circuitry; however, they are inherently more costly than monolithic clock drivers such as the 8224 (for the 8080). Just as with the 8080, the requirement for an external clock generator is a disadvantage--especially in small computers where low price is critical.

The 6800 uses an external general purpose stack, in RAM (similar to the 8080), providing for subroutine nesting and facilitating interrupt handling.

The 6800 is second-sourced, and is likely to remain another standard eight-bit milliprocessor. Its die size is relatively large (when compared to some 8080 versions), which may put the 6800 at a cost disadvantage in high volumes, compared to the 8080.

4.3.3 6500 Series Patterned after the 6800, the 650X processors are especially attractive for microcomputer applications. Like the 6800, these processors address an external general purpose stack--but the stack pointer is only eight bits long, limiting the stack to 256 bytes. This is not however a practical limitation. In fact, because the stack pointer is *circular*--ie, instead of underflowing into the next page in RAM, starts again at hex FF--the system cannot so easily go wild when an excessive number of stack levels are used. That is, in a microcomputer allowing unlimited subroutine nesting, the stack pointer is free to run into areas of RAM dedicated to other data storage, destroying information; or it may overflow and point to non-existent memory locations.

The 6501 is pin-compatible with the 6800, differing only slightly in hardware interfacing. Its instruction set, while similar to the 6800, is not directly compatible.

The 6502, also in a 40-pin package, features an on-chip clock oscillator. Requiring only an external capacitor (or crystal) and a resistor for main timing, this CPU effectively requires less PC board area, and saves on component cost. Similar in features to both the 6501 and 6800, it is attractive as a 6800 replacement in new designs.

A number of 650X versions are available, including CPUs in 28-pin packages where some 6501/6502 features are sacrificed. Aggressively priced, the 650X series is available both from MOS Technology and from a second-source, Synertek. A microcomputer chip with many millicomputer features, the 650X should prove very competitive.



microcomputer
design

SEC. 4.3 PROCESSOR COMPARISONS (cont'd)

For the purposes of illustration, a sketch of a 650X-based micro-computer--the *MIKE 5*--appears in Sec. 4.4 below.

4.3.4 *2650* The 2650 would rank as an excellent milliprocessor--at least, considering its instruction set, which is probably the best of the currently available eight-bit processor chips. However, its weakest link is an on-chip, non-addressable PC stack with only eight levels. This limits subroutine nesting and interrupt handling (just as the same fault impedes the 8008), and relegates the 2650 to the micro-computer category.

Available from Signetics, other 2650 advantages include a TTL clock; a single power supply; and completely microcoded indexed addressing.

4.3.5 *F8* Available from Fairchild and Mostek, the F8 is a well-designed microprocessor chip set. It requires +5 and +12 V power supplies, and a simple RC combination suffices to complete its on-chip clock oscillator. The F8 lacks a general-purpose stack; instead, each chip in the series (RAM, PROM, etc.) includes an on-chip program counter and one-level program stack. The F8's instruction set is quite versatile. Its disadvantage: does not interface readily with standard general-purpose memory parts. Though memory interface chips do exist, their use in production designs would remove the advantages of the F8 over other processors, such as the 650X series. The main F8 application: large-volume microcomputers, especially controller applications.

4.3.6 *SC/MP* The SC/MP is an eight-bit microprocessor from National Semiconductor (second source, Rockwell). Designed to fill the gap between four-bit CPUs (4004, 4040) and eight-bit milliprocessors, the SC/MP features a 12-bit address bus, interfacing directly to 4 K bytes of standard memory; provision for simple interrupts and DMA; on-chip serial data input port and output port; versatile memory addressing, including relative addressing instructions; and an on-chip clock oscillator, requiring only an external capacitor. Perhaps most important is its single power-supply requirement, +10 to +14 volts, permitting use of an unregulated power supply, and providing CMOS compatibility.

Disadvantages: TTL-compatible version (metal mask option) requires two supplies, +5 and -9 V. Most important, the SC/MP is manufactured with the older P-channel MOS technology, and is much slower than N-channel CPUs. The simplest instruction takes five microcycles, each 2 us long--making the SC/MP about as fast as the 8008. Nevertheless, SC/MP should be attractive in industrial controllers in which speed is not critical.

SEC. 4.3 PROCESSOR COMPARISONS (cont'd)

4.3.7 *Z-80* The Z-80 is a third-generation member of the eight-bit microprocessor family which includes the 8008 and 8080. Produced by a new corporation, Zilog, the Z-80 is compatible with the 8080 in terms of software, right down to the instruction code level. In addition, the Z-80 employs some of the 8080's unused opcodes to add a number of very useful instructions, including relative addressing and block transfers. The Z-80 incorporates such useful features as on-chip prioritized interrupt handling, and memory refresh circuitry for dynamic RAM. Finally, the Z-80, like the 6800, requires only a single +5 volt supply. Beginning in the last quarter of 1976, the Z-80 is available from Mostek as well as from Zilog.

The advent of the Z-80 is effectively a great advantage to the 8080 family, insofar as the Z-80 combines all the advantages of the 8080 processor with those of the 6800. As this book went to press, Martin Research was introducing a Z-80 based microcomputer to its product line--the *MIKE 8*.

SEC. 4.4 THE MIKE 5 MICROCOMPUTER

For the sake of illustration, this section includes a sketch of a small microcomputer based on the 6502 CPU (Fig. 4.4.1). Including only six ICs in addition to the CPU, the *MIKE 5* has one page of RAM (256 bytes), a page of PROM, an input port, and an output port. The power supply required is simply +5 volts--unless the PROM employed requires an additional supply.

Full eight-bit I/O ports could be provided by replacing the six-bit latch and driver ICs with eight-bit devices. The 74LS174 can be replaced with a 74LS273, and the 74367 with a 74LS241--both available from Advanced Micro Devices.

The *MIKE 5* is an example of a small microcomputer suitable for incorporation into industrial controllers. For developing software, however, a computer with full expansion capabilities and a Monitor program is preferable. For typical examples, see the information on the *modular micro* series at the end of this book.



SEC. 4.4 THE MIKE 5 MICROCOMPUTER (cont'd)

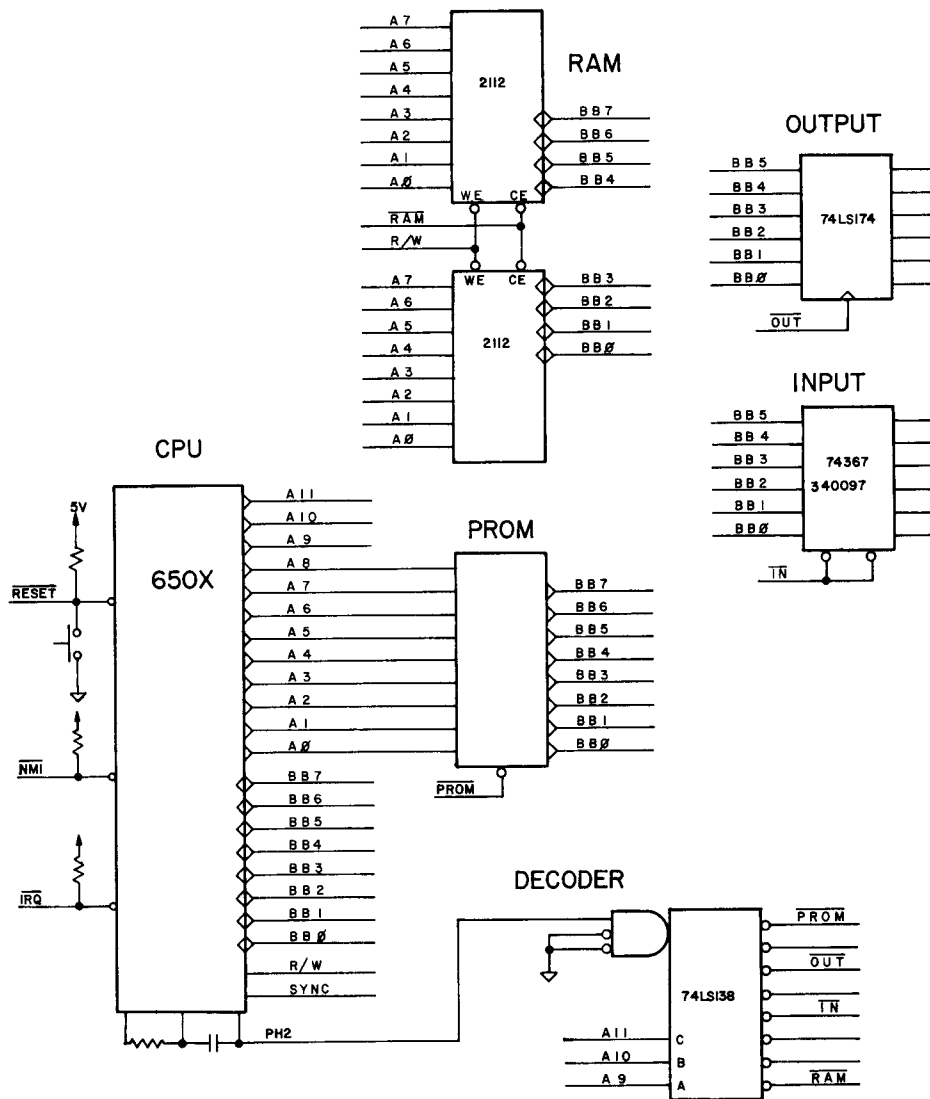


Figure 4.4.1--Sketch of the MIKE 5, a 650X-Based Microcomputer



microcomputer design

Both the 8080 and 8008 microprocessors require two-phase clock signals, which must be generated by circuitry outside the microprocessor. The 8008 requires clock voltages at standard TTL voltage levels, while the 8080 requires PH1 and PH2 signals referenced to +12 V.

The first part of this chapter is devoted not only to the generation of clock signals for the 8008, but to other main timing requirements as well. Since the 8008 does not include internal DH and DL address registers, these must be added (Sec. 5.4). 8080 clock circuitry is discussed in Sec. 5.5.

SEC. 5.1 8008 CLOCK CIRCUITS

Symmetrical clocks are the best place for the 8008 designer to start. CPU circuits may be converted to skewed clocks, for slight improvement in system speed during the late stages of circuit design if it is found advantageous.

Most symmetrical clock designs are made up of three sections:

- (1) the oscillator;
- (2) the counter;
- (3) the decoder.

The oscillator section provides the basic signal source at a constant frequency. The counter section then divides the frequency by two to provide two related frequencies, f_0 and $1/2 f_0$. The decoder section then selects the 01 and 11 states from the counter, providing the $\phi 1$ and $\phi 2$ signals required.

Figure 5.1.1 shows the timing diagram for a two-phase clock generator which uses a positive-logic decoder.

 


Figure 5.1.1--Two Phase Clock Generator Timing Diagram



microcomputer design

SEC. 5.1 8008 CLOCK CIRCUITS (cont'd)

5.1.2 *Oscillators* Two basic oscillator circuits are described here. Other oscillators which provide approximate square waves may also be used.

The first oscillator shown, in Figure 5.1.2, is very inexpensive and uses readily available components. The disadvantage to this oscillator is that it is inaccurate. Adjustment components may be added to this circuit, as shown in the figure, but the temperature drift may be significant, depending on the application.

 


Figure 5.1.2--Inexpensive CPU Oscillator: Three Inverters and Capacitor

The second type of oscillator is also quite simple, but uses a crystal, which makes it more expensive. The main advantage to this circuit is its stability. (A microcomputer built into instrumentation needing an accurate frequency or time standard will need such an oscillator anyhow.) Figure 5.1.3 shows the crystal oscillator schematic. The value of R must be

 


Figure 5.1.3--CPU Oscillator: Two Inverters, Crystal for Stability

SEC. 5.1 8008 CLOCK CIRCUITS (cont'd)

decreased for crystals with high internal resistance. Resistor values may range between 270 and 1000 ohms. If the characteristics of the crystal are unknown, a 270-ohm resistance is generally recommended.

Sometimes a precounter may be used with a crystal oscillator, as shown in Figure 5.1.5 below. The precounter implies the use of a higher-frequency crystal, which is smaller and less expensive. For prototypes, the precounter may be eliminated. For the production version, the cost-effective approach should be used.

5.1.3 *Counter Section* The simplest counter is a single flip-flop.

Whether the desired flip-flop should be positive- or negative-edge-triggered depends on the type of decoder used. In order to avoid race conditions, a negative-edge-triggered flip-flop is used with a positive decoder, and a positive-edge triggered flip-flop is used with a negative decoder. (See following section on race conditions.)

5.1.4 *Decoders* The two phases, $\phi 1$ and $\phi 2$, can be decoded from the counter section with only two gates. Since positive pulses are required for the 8008, either AND or NOR gates are used because their exceptional output states are logic one. (The exceptional output state is that state occurring with only one combination of inputs.) Figure 5.1.5 shows the use of AND gates for a positive decoder (exceptional input state of logic one). Figure 5.1.6 shows a negative decoder, which uses a pair of NOR gates (exceptional input state of logic zero). Notice the use of negative-edge-triggered flip-flops with positive decoders, and vice versa, as mentioned previously.

When using TTL decoders, it is advisable to add 1 K ohm pullup resistors (to +5 volts) to ensure an adequate voltage swing to drive the CPU's MOS inputs. If a CMOS decoder is used, these resistors may be eliminated.

The following should help explain the cautions on avoiding race conditions in this section. A binary counter made up of flip-flops (including multi-count ripple counters like the 7490 series) exhibits certain inherent race conditions during count transitions. Take for example the single flip-flop counter shown in Fig. 5.1.5, which goes through four states (see Figure 5.1.4):

| STATE NUMBER | BINARY COUNTER STATES | | COUNT DIRECTION | POSITIVE DECODERS STATE NAME | COUNT DIRECTION | NEGATIVE DECODERS STATE NAME |
|--------------|-----------------------|---------|-----------------|------------------------------|-----------------|------------------------------|
| | \bar{f}_0 | $f_0/2$ | | | | |
| 0 | 0 | 0 | ↓ | RACE-PRONE STATE | ↑ | $\phi 1$ |
| 1 | 0 | 1 | | $\phi 1$, PHASE ONE | | RACE |
| 2 | 1 | 0 | | RACE-PRONE STATE | | $\phi 2$ |
| 3 | 1 | 1 | | $\phi 2$, PHASE TWO | | RACE |

Figure 5.1.4--Two-Phase Clock Generator Timing Diagram

SEC. 5.1 8008 CLOCK CIRCUITS (cont'd)

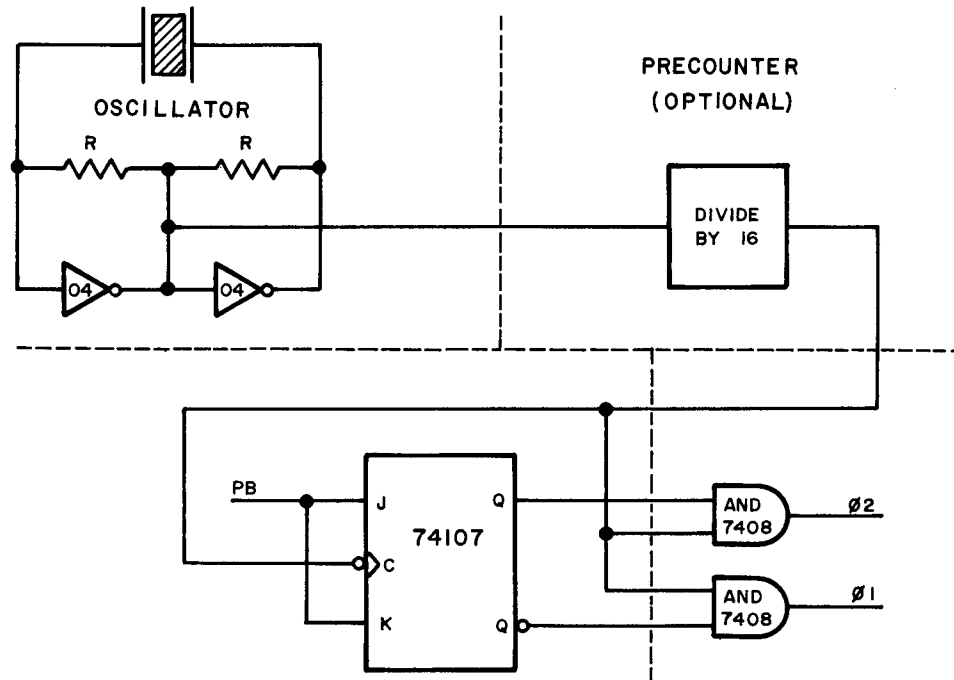


Figure 5.1.5--A Single Flip-Flop Functions as Counter. Negative-Edge-Triggered Flip-Flop Used with Positive Decoders.

 


Figure 5.1.6--Counter Using a Positive-Edge-Triggered Flip-Flop and Negative Decoders.



SEC. 5.1 8008 CLOCK CIRCUITS (cont'd)

During the transition between state number 1 (binary output code 01) and state number 2 (binary output code 10), both bits must change state. This transition is not immediate, and in this kind of counter, the low-order bit must change before the high-order bit can change. This means the count is really 01, (00), 10 (where the 00 count is very short, just a glitch). If the decoder were looking for the 00 state, a glitch would appear at this point. Similarly, in the transition between state 3 (11) and state 0 (00), the counter passes through the 10 count. Glitches are avoided by making sure not to decode the 00 or 10 counts.

A similar situation occurs when positive-edge-triggered flip-flops are used, except that the safe states are now the even counts, and the counting direction is reversed (Figure 5.1.4, to the right). Schematic: Figure 5.1.6.

5.1.5 *Monolithic Clocks* Instead of the TTL-based two-phase clock circuits shown above, the designer may choose to specify a monolithic clock generator. One such is the National Semiconductor MH8803 two-phase oscillator/clock driver. A circuit diagram is shown in Figure 5.1.7. With the frequency control pins left open, as shown, the oscillator runs at 300 KHz, with a 750-nanosecond pulse width.

 


Figure 5.1.7--Monolithic Two-Phase Clock Generator

SEC. 5.2 ENABLE AND STROBE GENERATION

One of the functions of the main timing logic in the 8008-based microcomputer is to develop the signals necessary to activate associated input selectors, memory, and output ports at the proper times.

Chapter 2 has already covered the basic timing characteristics of the 8008. Here the hardware is developed to accommodate the 8008's requirements.



SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

5.2.1 Eight-State Decoder Most of the 8008 designs previously published have used decoders to transform the S2, S1 and S0 state outputs from the microprocessor and develop eight separate state signals. The schematic for this circuit is shown in Figure 5.2.1. Usually the WAITING and STOPPED signals are then used to control lamp driver circuits which inform the user when the CPU is waiting for memory or has hit a HLT instruction. Then a large number of inverters, gates, and flip-flops are added to generate strobe and enable signals to perform the appropriate data transfers to and from the CPU at the proper times. The presence of this large and often confusing mass of TTL has probably discouraged more designers from using the 8008 microprocessor than any other single factor.

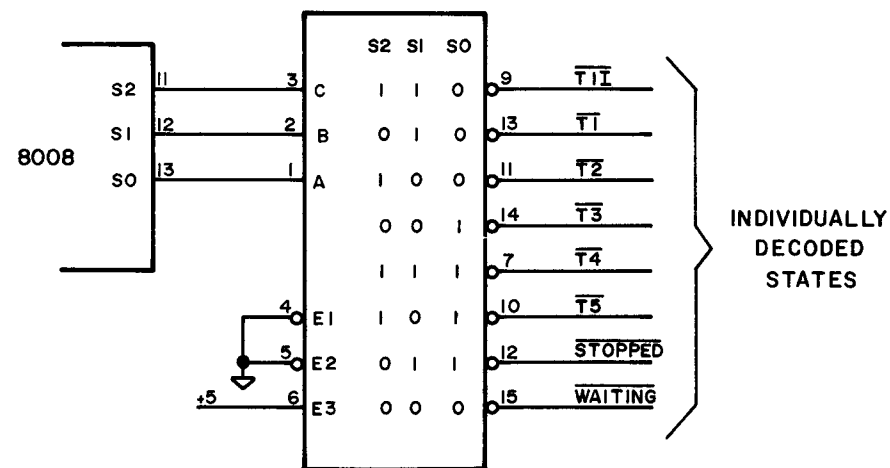


Figure 5.2.1--Octal Decoder Generates State Signals

SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

5.2.2 A Practical Strobe Generator A very significant savings in gates can be accomplished by using the strobe inputs of the decoder to eliminate the need for these additional gates, as shown in Figure 5.2.2.

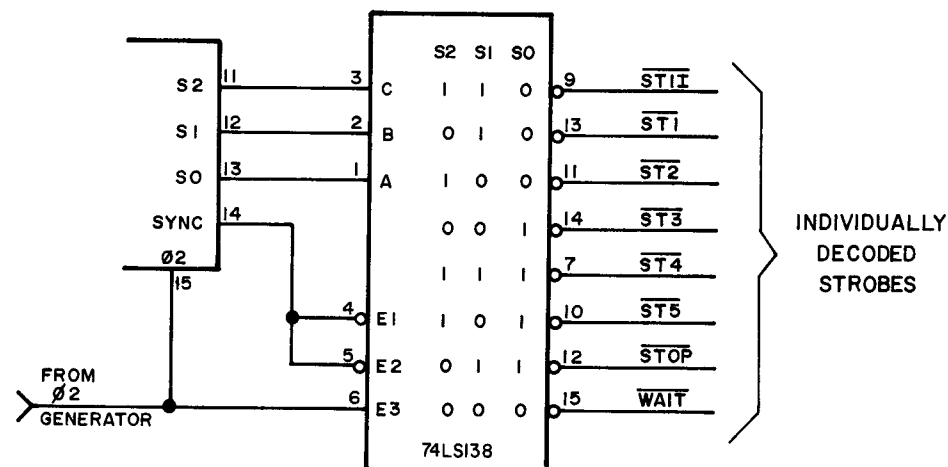


Figure 5.2.2--Strobed State Decoder Simplifies CPU Logic Design

The only potential objection to this technique is that the STOP and WAIT lines become a string of pulses rather than a steady level. If someone is using an oscilloscope to look for STOP or WAIT states, he will actually find it advantageous, since a string of pulses is more quickly recognized than a level, and pulses will trigger his scope sweep more readily than a level. If STOP or WAIT indicator lamps are required, the pulse signals again will work better than level signals in driving LED readouts. The designer merely calls for a smaller current-limiting resistor in series with the LED display, since it is being driven in the pulse mode.

SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

Figure 5.2.3 shows a circuit to perform these functions.

 


Figure 5.2.3--Pulse-Driven WAIT and STOPPED Lamps

5.2.3 Generating the T3A Enable/Strobe When the CPU is inputting data during T3 time, it needs an enable pulse which comes between the ST2 strobe and ST3 strobe. This signal anticipates the T3 state in order to give time for the information coming into the CPU to settle on the bus. This signal is called T3A. See Chapter 2 for a further description of T3A.

There is more than one way to generate the T3A enable pulse, but perhaps the most convenient one is shown in Figure 5.2.4.

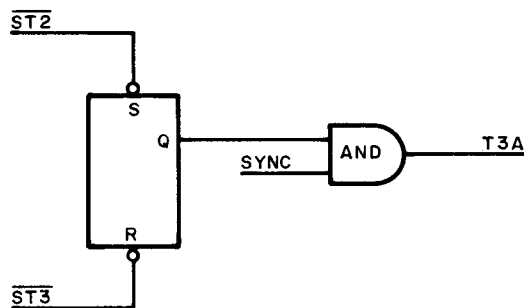


Figure 5.2.4--A T3A Enable Generator to Enable CPU Input Sources

SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

The flip-flop is set by $\overline{ST2}$ and reset by $\overline{ST3}$. During the interval between these signals, while the output of the flip-flop remains high, the SYNC signal is passed through the AND gate to the output. The pulse width of T3A is approximately equal to the PHASE TWO clock period.

It may be desirable to suppress the T3A enable signal during a PCW (memory write) cycle, when the CPU is outputting onto its bus rather than inputting. In order to accomplish this, the reset of the flip-flop is connected to PCW rather than to $\overline{ST3}$. $\overline{ST3}$ still resets the flip-flop, now a D-type device, through its clock. Figure 5.2.5 shows this revision.


 


Figure 5.2.5--Blanking of T3A During PCW Memory Cycles

 SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)



NOTE: The instruction being executed is LMA.

Figure 5.2.6--Shows How the T3A Enable Pulse is Eliminated During PCW Cycles



SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

Section 5.2.4 describes the generation of RAM write pulses. Since this usually requires the generation of the PCW signal anyway, the T3A generation circuit of Figure 5.2.5 is still minimal.

It is necessary when using the circuit of 5.2.5 to load the CC2 and CC1 bits on the beginning of the ST2 pulse. With rising-edge-triggered flip-flops, this is usually accomplished with the STAG signal. Figure 5.2.6 shows the timing diagram associated with the circuit of 5.2.5. The instructions being executed are an LMA, followed by the fetch portion of the next instruction (which might be any instruction). Notice how the PCW cycle suppresses T3A. The use of this circuit is more fully explained in Chapter 26.

5.2.4 Generating the "STEW" Strobe The other signal which is often (but not always) needed in an 8008 microprocessor system is ST3W. This strobe is generated when the CPU is outputting information (during T3 cycle) to be stored in RAM. This output condition occurs only when a PCW cycle is being executed. Since the PCW cycle is denoted by CC2 and CC1 being high, strobe generation may be as simple as a NAND gate and an inverter. Figure 5.2.7 shows two possible circuits which both fit equivalent logic equations.

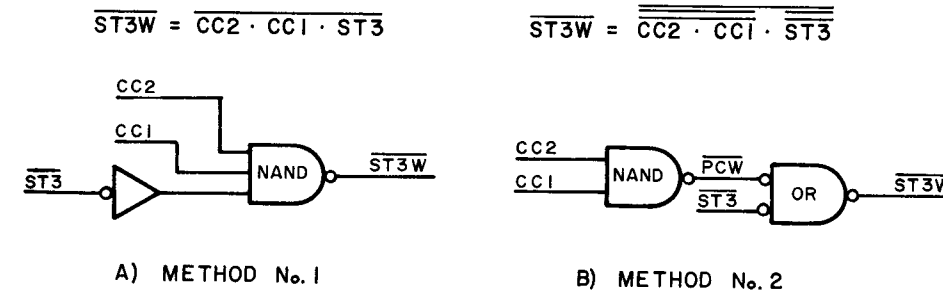


Figure 5.2.7--Methods for Generating "STEW"

The limitation of this circuit is that the $\overline{ST3W}$ pulsewidth is only as long as ST3 (the width of a PHASE IWO pulse). For an 8008-speed clock this pulse would be 500 nanoseconds wide. This pulse is quite sufficient for many RAMS. The ST3W signal is called "STEW" probably because it is more easily pronounced.



SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

5.2.5 Generating the "STEWED" Strobe For those RAMS requiring wider write pulses the circuit in Figure 5.2.8 may be used. The normal ST3W pulse is generated, as in Figure 5.2.7, and a set-reset flip-flop is added to broaden the write pulse.

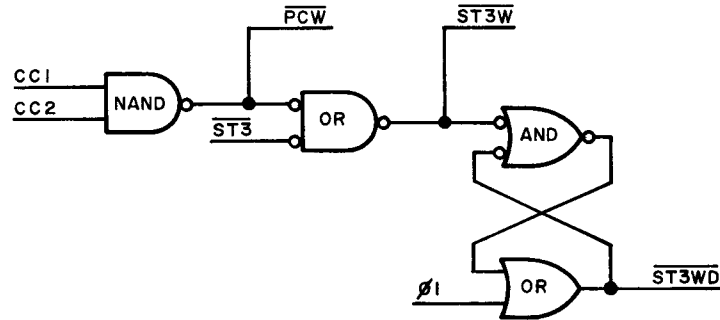


Figure 5.2.8--Generating "STEWED," a Wider Write Pulse

The flip-flop shown is an AND-OR design. (For a description, see the article "Another Way to Build a Two-Gate Flip-Flop" by the present author in Electronics, June 13, 1974, page 124.) It is reset to a low level by the negative-going ST3W strobe, starting the ST3WD pulse. The positive-going edge of the next PHASE 1 clock pulse sets the flip-flop to a high level and terminates the strobe. For systems using a symmetrical clock, this flip-flop doubles the write pulse width. Therefore, with a clock designed for normal 8008 speed, the write pulse will be a full microsecond in width. In any case, the STEWED signal always staggers around a little longer for systems with slower memory.

SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

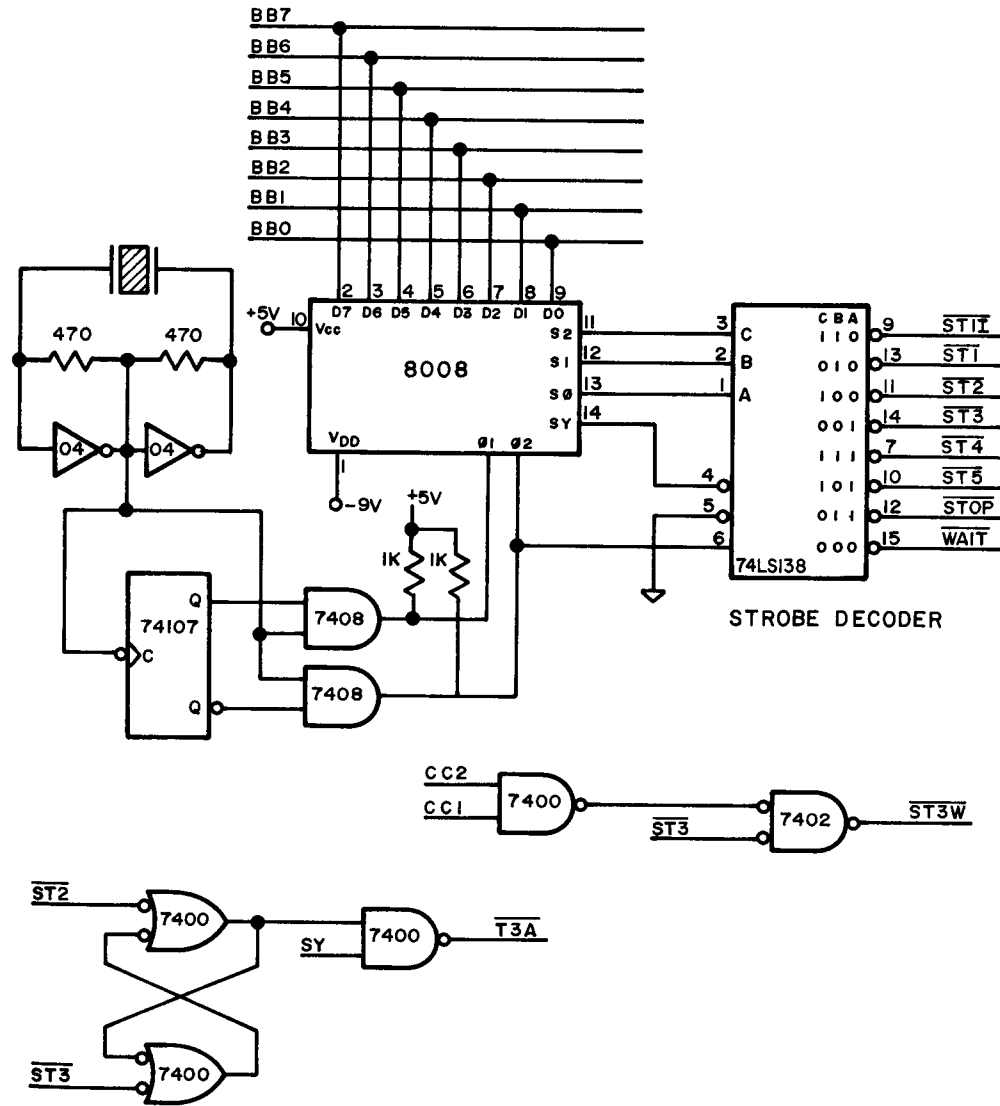


Figure 5.2.9--Basic 8008 Timing with Little Peripheral Logic

 


Fig. 5.2.10--Basic Main Timing Signals for an 8008 Microcomputer



microcomputer
design

SEC. 5.2 ENABLE AND STROBE GENERATION (cont'd)

5.2.6 Summary The above main timing circuits are combined in Figure 5.2.9, which shows:

- (1) the clock which produces $\phi 1$ and $\phi 2$;
- (2) the CPU itself;
- (3) the strobed decoder;
- (4) the ST3A generator; and
- (5) the ST3W generator.

Figure 5.2.10 shows the main timing logic signals used by an 8008. The relative simplicity of firing up an 8008 CPU is becoming more clear.

SEC. 5.3 MASTER RESET

Nearly every complex logical system requires some method for initialization when power is first applied. Otherwise flip-flops, latches, counters, and other devices with bistable logical states will take on arbitrary and possibly undesirable values. The system might even enter an illegal state, where the machine hangs up and refuses to respond to inputs at all--a most frustrating habit, as every designer who has encountered it knows well. The solution is generally a *master reset* circuit which develops a reset signal for a fraction of a second when power is first applied.

5.3.1 Simple Master Reset Circuits A simple master reset circuit which uses only one or two TTL gates is shown in Figure 5.3.1. The capacitor is initially discharged, so that the 7404 output is initially high. After the capacitor charges to the 7404 logic one threshold value, the output goes low, and remains low as long as the power is on. The output signal is commonly called MR, and is used for devices (such as a 7490 decade counter) with positive-logic resets. When a negative-logic signal is needed (as to reset a 7474 flip-flop), the MR signal can be inverted using another 7404 stage, producing $\overline{\text{MR}}$.

 


Figure 5.3.1--(A) Simple Master Reset Circuit Using TTL; (B) CMOS Version



microcomputer
design

SEC. 5.3 MASTER RESET (cont'd.)

With a standard TTL gate, as shown, R should normally be not less than 1 K ohms (to protect the gate against power supply transients), nor more than 25 K ohms (to provide sufficient input current). The diode shown is optional, and forces the capacitor C to follow the power supply voltage down rapidly when power is turned off.

Note that the circuit is power-supply rise-time dependent. If the +5-volt supply tends to come up more rapidly than other supplies in the machine, consideration should be given to increasing the capacitor's value.

The circuit of Figure 5.3.1-B, using CMOS, allows the use of smaller capacitors and larger resistors. Of course, drive capabilities are also reduced (2 TTL loads with the chip shown). The circuit of Figure 5.3.2 can be used to minimize power supply rise-time dependency.

 


Figure 5.3.2--Master Reset with Reduced Power Supply Dependency

5.3.2 8008 Initialization The 8008, which contains a number of internal registers and other bistable elements, has its own initialization provisions. As the power supply and system clock come on, the CPU executes a HALT instruction automatically. During the ensuing STOPPED condition, the CPU automatically clears its internal memories in sixteen clock periods. The CPU may be started by causing its INTERRUPT terminal to go to logic one.


For more information on initial interrupts with the 8008, see Chapter 16. See also the practical example in Chapter 25.

SEC. 5.4 ADDITIONAL CIRCUITRY REQUIRED FOR BASIC MICROCOMPUTER

5.4.1 Address/Data Registers During T1 time, the CPU outputs information on its data bus which is intended for temporary storage in an external register, called the *DL Register*. In most instances, the DL register contains the *low-order* portion (eight bits) of the address in memory which is being read or written into by the CPU. When an output instruction is being executed, the data transferred to the DL register--during memory cycle two--is intended for an output port. (For clarification, the reader may study the chart on internal processor operation in the 8008 manual.)

The strobe used to load the DL register from the data bus at the proper time is $\overline{ST1}$. It occurs far enough into T1 time to ensure that the data which the CPU is outputting has had time to settle on the bus.

Figure 5.4.1 shows how simply the DL register may be added to the CPU. The eight-bit latch used should be a low-power device, whose input current requirements will not overload the CPU output bus drive capabilities.

 

(A) DL Register

(B) DH Register

Figure 5.4.1--The DL and DH Registers Connected to the CPU Bus

SEC. 5.4 ADDITIONAL CIRCUITRY REQUIRED FOR BASIC MICROCOMPUTER (cont'd)

During T2 time, the CPU outputs the address or instruction intended for the DH register. The two high order bits (DH7 and DH6) are, in all cases, used to determine the type of instruction cycle being performed. Since they are control bits, rather than memory-addressing bits, DH7 and DH6 are usually referred to as CC2 and CC1 (respectively) in this book.

The remaining six low-order bits of the DH register usually contain the high-order memory address information. In the case of input or output instructions, the CPU loads the DH register with the I/O instruction itself, in its eight-bit binary code.

The strobe used to clock the data bus information into the DH register is called ST2.

Figure 5.4.1(B) shows an eight-bit latch being used as the DH register. Cautions similar to those mentioned for the DL register must be observed with regard to loading down the CPU data bus.

5.4.2 Basic 8008 Microcomputer A working 8008 microcomputer requires the addition of read-only memory (ROM) for program storage, and an input/output/memory select decoder. These matters are outside the scope of a chapter on main timing logic, and are discussed elsewhere in the book. However, we are now very close to a design for a minimally configured microcomputer. See Chapter 25 for a design example.

SEC. 5.5 8080 CLOCK GENERATION

The 8080 CPU requires a two-phase clock referenced to +12 V. System timing requirements dictate an asymmetrical clock, where PH1 has a duty cycle of 2/9, followed immediately by PH2 with a duty cycle of 5/9, followed with a gap of 2/9. The standard 8080 clock cycle is 500 ns (2.0 MHz frequency), derived from a crystal oscillator running at nine times that frequency, or 18.0 MHz. PH1 and PH2 are produced by decoding the outputs of a divide-by-nine counter.

SEC. 5.5 8080 CLOCK GENERATION (cont'd)

A collection of TTL circuits--crystal oscillator, divide-by-nine counter (74LS193), and decoders--plus two high-level buffers would produce the required circuitry. Hybrid 8080 clock generators are also available. However, it is more efficient simply to use the type 8224 clock chip from the 8080 manufacturers. The 8224 saves PC board space, especially since it incorporates special gating for producing the 8080 system strobe and two flip-flops for synchronizing external wait and reset signals. The hybrid circuits lack these extra features, include a relatively high labor content, and will probably always be more expensive than the 8224 in production volumes.

For a practical application of the 8224, with functional description, see the 471 data sheet near the end of this book (Sec. 1.4).



SEC. 6.1 INTRODUCTION TO BUS STRUCTURES

6.1.1 *What is a Bus?* A bus consists of a number of actual wires which may be driven by more than one source. The following sections will concentrate on the types of busses most commonly applicable to microprocessors.

The wired-AND function (sometimes called the wired OR) used in DTL is a primitive example of a one-bit bus. Figure 6.1.1 shows two RTL inverters with their outputs wired together. RTL is used in this example for simplicity: the gates have passive (resistor) pullups rather than active (transistor) pullups as in TTL devices with totem-pole outputs.

 


Figure 6.1.1--A "One-Bit Bus" Example

Referring to the figure: if either point A or point B is raised to logic one, the associated transistor will turn on and the "one-bit bus" will be actively pulled down to logic zero. The portion of the figure enclosed in the dashed rectangle is considered the bus. This orientation is important in clearly defining the difference between a bus input and a bus output.

Thus, when the RTL inverter outputs are connected to the bus, they become bus inputs. The RTL inverters themselves function here as bus drivers. Naturally the bus is not very useful until a *bus receiver* is connected to it. A bus receiver uses the *output* of the bus to drive its *input*. Many bus receivers may be attached to a bus.

SEC. 6.1 INTRODUCTION TO BUS STRUCTURES (cont'd)

The real value of a bus structure becomes apparent when one uses the same bus to transmit different information at different, well-defined times. Information can then be *time multiplexed* onto the bus. Only one bus driver can be active at one time, and bus receivers should pay attention to the information on the bus only when it pertains to them.

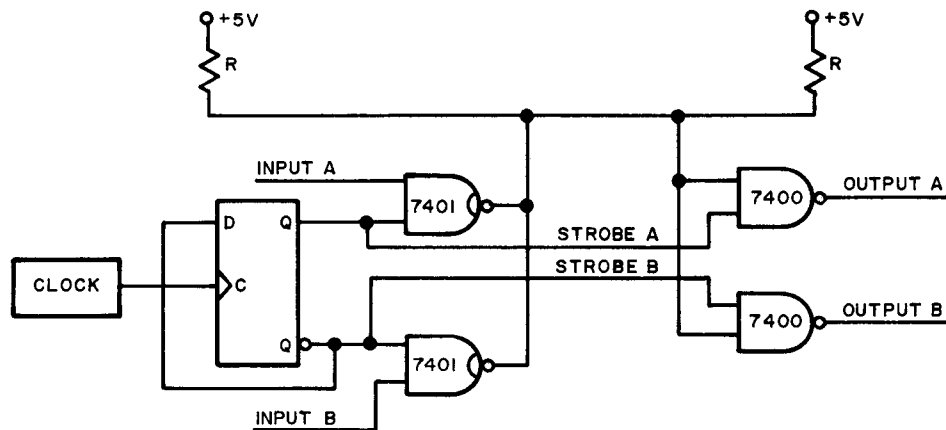


Figure 6.1.2--Two Drivers and Two Receivers on One-Bit Bus

Figure 6.1.2 shows a bus circuit with two bus drivers and two bus receivers. The timing circuit consists of a clock driving a single flip-flop. The flip-flop alternately enables the two 7401 gates. When STROBE A is high, the information on INPUT A is impressed onto the bus, and the top-most 7400 gate is enabled. OUTPUT A then follows INPUT A logically. When the next clock pulse occurs, the flip-flop complements, which disables STROBE A and enables STROBE B. Now the information on INPUT B goes onto the bus and is recognized by OUTPUT B.

SEC. 6.1 INTRODUCTION TO BUS STRUCTURES (cont'd)

6.1.2 Why Bother? All this effort is hardly justified with a one-bit bus; three wires are used (a bus and two strobe lines) to transport information that could have been communicated over two wires with no extra logic. However, consider an eight-bit bus: similarly configured, it would need ten wires (the eight bus lines and two strobe lines), as opposed to sixteen wires. As the system becomes more complex, the savings become more apparent. And when the designer is using large-scale-integration (LSI) chips, the cost of the real estate of the silicon chip is less expensive than the extra printed circuit board copper, PC board connectors, and backplane wiring. And LSI chips intended for time-multiplexed bus use are themselves less expensive, ultimately, because fewer pins and bonds are required.

SEC. 6.2 LATCHING LOGIC

The next step is to improve the circuit of Figure 6.1.2 by adding a latch to the bus receiver. Naturally it is necessary to latch up the information at OUTPUT B only when it is valid. This may be difficult to do with the circuit in Figure 6.1.2. The problem which arises is that the information on OUTPUT A should not be latched up until ENABLE A has been on long enough for the data to propagate down the bus and settle on the output of the 7400.

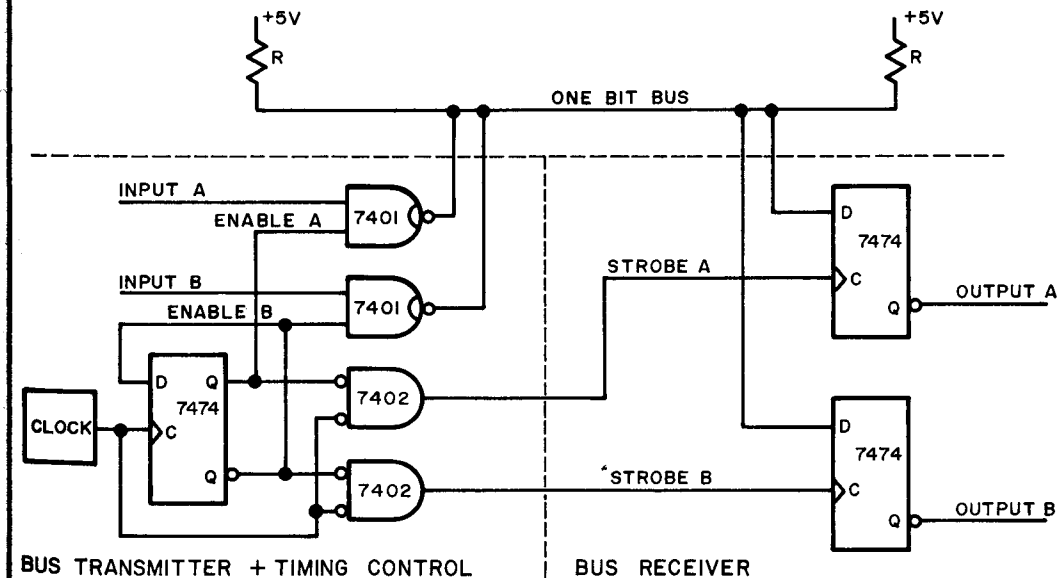


Figure 6.2.1--One-Bit Bus with Enables and Latches

SEC. 6.2 LATCHING LOGIC (cont'd)

In order to do this a timing signal is needed for each driver and each receiver. Figure 6.2.1 shows a circuit which not only transfers the information, but latches it in flip-flops so that it is continuously available at OUTPUT A and OUTPUT B.

The timing diagram in Figure 6.2.2 shows the sequence of events as information is transferred from each of the bus driver inputs to the appropriate bus receiver output latch without any problem. The clock must be slow enough to let the enabled data settle on the bus before the receiver strobe causes the data to be latched.

 


Figure 6.2.2--Timing Diagram for Figure 6.2.1

The arrows in Figure 6.2.2 indicate the points at which the output flip-flops are loaded. Note that loading occurs a significant time--one-half clock cycle--after the associated bus driver has been enabled onto the bus.

The bus-structured designs discussed up to this point have used open-collector bus drivers. Integrated circuits with open-collector outputs have only two output states: that is, the gate can either pull the bus down to logic zero, using an *active* circuit element (the gate's internal output transistor); or it can allow the bus to be pulled back up to logic one by a *passive* circuit element (an external pull-up resistor). To disable the bus driver, a signal is applied to an extra input terminal which

SEC. 6.2 LATCHING LOGIC (cont'd)

causes the gate's internal output transistor to turn off. The disabled bus driver then allows the pull-up resistor to pull the bus up to the logic one state--or allows some other bus driver on the same bus, which is enabled, to pull the line down to logic zero.

SEC. 6.3 THREE-STATE DEVICES

A relatively new class of logic devices is available which offers better performance in bus-structured designs than the open-collector devices described in the previous sections of this chapter. The integrated circuit with *three-state* outputs has both active pull-up transistors, and active pull-down transistors, in its output stage--like ordinary TTL with totem-pole outputs. To disable the outputs, an extra terminal is used, commonly termed OUTPUT ENABLE. When the outputs are *disabled*, the output *floats*; that is, the output stages neither sink nor source a significant amount of current, but allow the output voltage to be determined by another circuit element connected to the output bus. This third state is often called the *high-Z* or high-impedance state.

The term *TRI-STATE* is often used; this is the registered trademark of National Semiconductor Corporation for three-state devices.

Figure 6.3.1 shows some common symbols for three-state buffers. Circuit (c) is similar in circuit function to the 7401 open-collector gate described above.

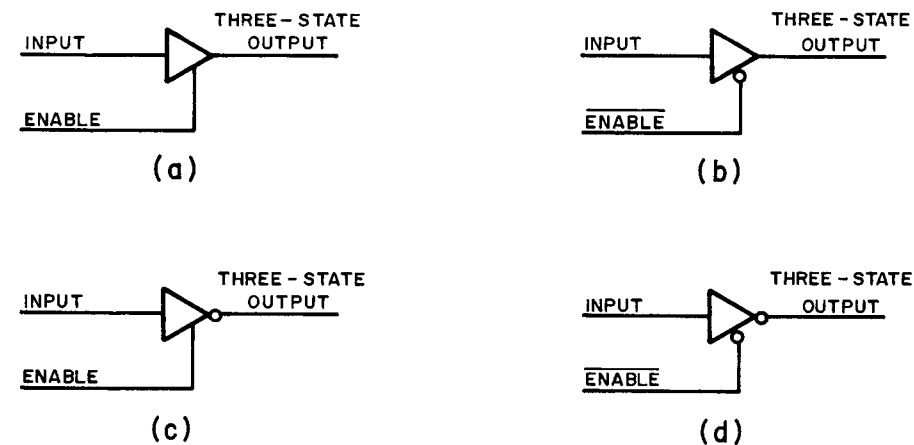


Figure 6.3.1--Common Symbols for Three-State Buffers

SEC. 6.3 THREE-STATE DEVICES (cont'd)

A very valuable property of almost all three-state buffers is that, when disabled, not only the outputs but the inputs are in a high-Z state. If a number of three state devices are connected to an ordinary TTL output, the load factor is defined by the maximum number of three-state devices which may be enabled at one time, not by the total number. This property is very handy in the design of large bus-structured systems.

To minimize the possible conflict between two three-state devices trying to drive the same bus line at the same time, most manufacturers have designed their devices such that the output enable time is longer than the output disable delay time. The designer should design his system timing and strobe signals to make use of these properties and avoid any output overlaps between two bus drivers. Otherwise current spikes may appear. While not likely to destroy the buffers--whose outputs are generally current-limited--these spikes can easily disrupt normal system functions.

SEC. 6.4 ADVANCED STROBE TECHNIQUES

The bus circuits discussed earlier are extended further here through the use of three-state buffers. The circuit in Figure 6.4.1 is similar

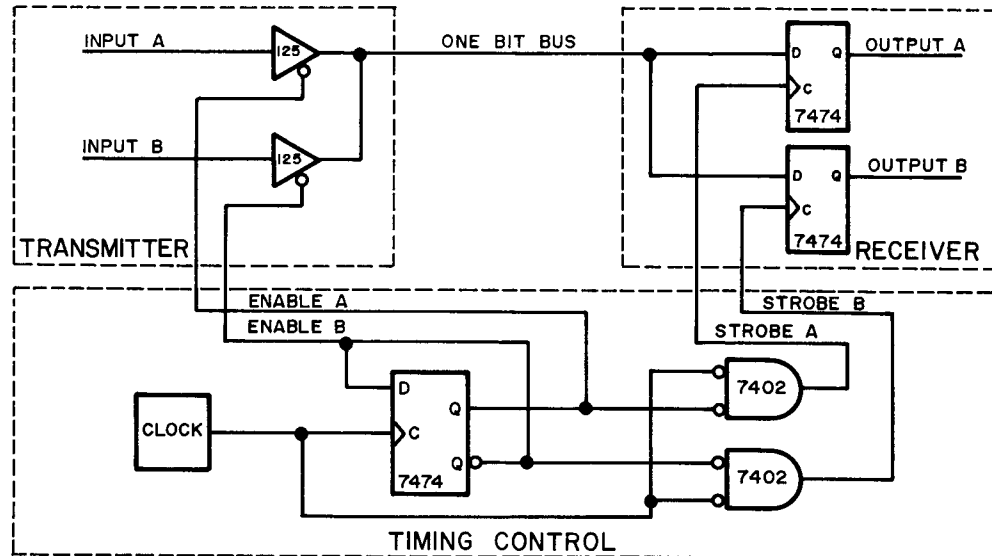


Figure 6.4.1--Three-State Buffers Replace Open-Collector Devices--Timing Control Shown Separately

SEC. 6.4 ADVANCED STROBE TECHNIQUES (cont'd)

to that in Figure 6.2.1, except that three-state buffers are used in place of open-collector gates. The timing logic is separated into a third section of the schematic. The timing circuitry could have been included either with the bus drivers, or the bus receivers.

The 7474 flip-flop in the timing control section of Figure 6.4.1 may be considered a one-bit counter, and the pair of 7402 gates may be considered a two-bit decoder. Note the similarity between the above schematic and the 8008 main timing circuitry in Chapter 5.

The capabilities of the timing section shown above can be expanded by using multiple-bit counters and decoders, as shown in Figure 6.4.2.

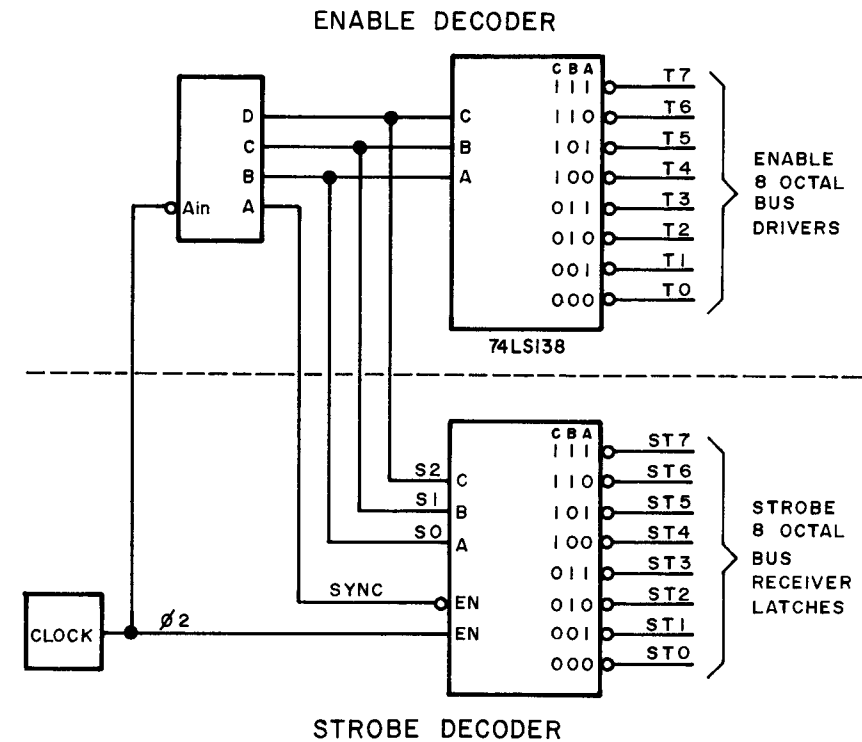


Figure 6.4.2--Expanding Number of Bus Drivers and Receivers with Only a Few Chips

SEC. 6.5 TYPES OF BUS STRUCTURE

6.5.1 Input Bus An input bus is a bus which drives only one set of receivers, but has more than one driver. An example: the three-state data outputs of many RAMs and ROMs are connected together to the inputs of a single set of buffers. Figure 6.5.1 shows a CPU input bus which accepts information from a ROM or one of two RAMS, all of which have three-state outputs. The decoder must provide enable signals to ensure that no more than one memory IC is driving the input bus at one time.

6.5.2 Output Bus An output bus is a bus which contains only a single set of drivers, but several sets of receivers. In the example in Figure 6.5.1, the CPU is connected to eight buffers, whose outputs constitute the CPU output bus. The RAM chips receive data to be stored from this CPU output bus. The WRITE STROBE line both enables the RAM, and strobes the data to be written onto the chip at a time when the data on the CPU output bus is stable.

6.5.3 Bi-Directional Bus A bi-directional bus employs more than one set of drivers and more than one set of receivers. Non-overlapping enable signals should be provided to the drivers, and correctly-timed strobes should be provided to each of the receivers at a time when the bus is stable.

Note that, in Figure 6.5.1, the symbol *NB* is used to represent an input bus; the symbol *TB* denotes an output bus; and *BB* is a bi-directional bus.

6.5.4 Tri-Bus A bus structure whose hardware is designed using three-state devices is called a *tri-bus* in this book. Unlike the above bus designations, this term refers primarily to hardware (electrical) considerations. A tri-bus normally has several bus drivers connected to one or several bus receivers, and is otherwise unterminated—ie, no pull-up resistors are used to +5, nor pull-down resistors to ground. This distinguishes the tri-bus not only from open-collector bus structures (discussed above) but from other bus configurations with 120-ohm impedance characteristics.

For a good introduction to tri-bus circuitry, the reader is referred to the data sheets for the National 8830 series (and to *Application Note 83, Data Bus and Differential Line Drivers and Receivers*).

Figure 6.5.2 gives a brief summary of the types of busses defined above.

SEC. 6.5 TYPES OF BUS STRUCTURE (cont'd)

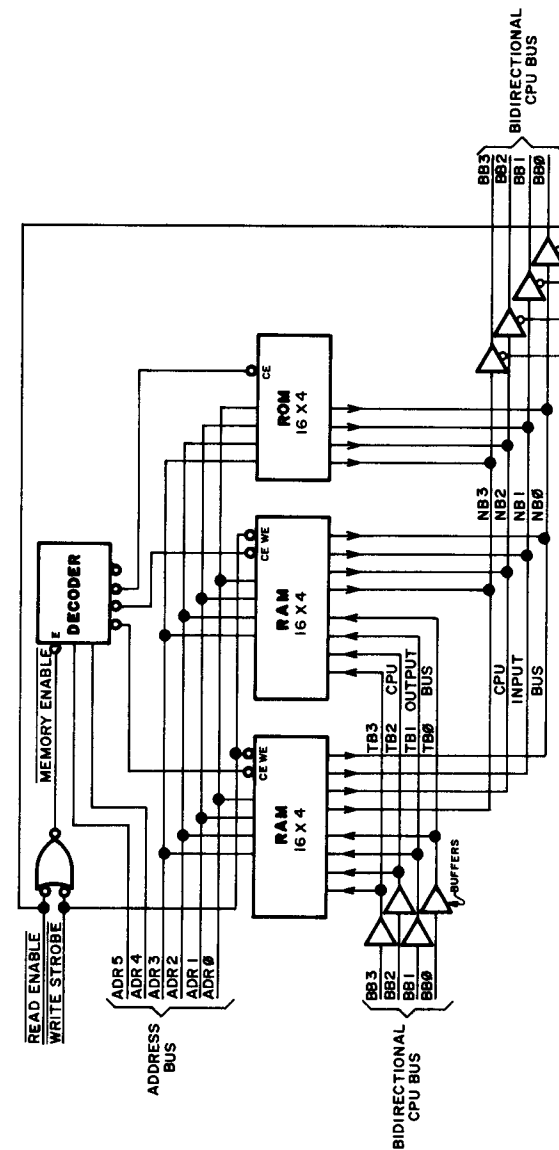


Fig. 6.5.1--Examples of Different Kinds of Bus Configuration, in a Hypothetical Four-Bit Data System

SEC. 6.5 TYPES OF BUS STRUCTURE (cont'd)

| # OF RECEIVERS ON BUS | # OF TRANSMITTERS ON BUS | NAME OF BUS | TYPE OF BUS | CONTROL SIGNALS NEEDED | EXAMPLES |
|-----------------------|--------------------------|--------------------|-------------|------------------------|--|
| Only One | More Than One | Input Bus | Tri-Bus | Enables, Strobe | "NB" Bus; Data from memories |
| More Than One | Only One | Output Bus | Direct Bus | Strobes | "TB" Bus; outputs of DL register; data to RAM memories |
| More Than One | More Than One | Bi-Directional Bus | Tri-Bus | Enables, Strobes | "BB" Bus (CPU Bus, D7-D0) |

Figure 6.5.2--Names and Types of Bus Structures

SEC. 6.6 BUS TRANSCEIVERS AND BI-BUS DRIVERS

6.6.1 Bus Transceivers Various interconnections of the terminals of bus receivers and bus drivers, on the same integrated circuit, produce devices which are useful in bus-structured communications. For example, a *bus transceiver* is formed when the output of a bus driver is connected to the input of an associated bus receiver. Figure 6.6.1 shows a bus transceiver, often used to add peripheral devices to provide three-state buffering and interface to long bus lines. The dotted line is often drawn solid in device schematics, to indicate that the drive section does not load the driver input when the driver is disabled.

SEC. 6.6 BUS TRANSCEIVERS AND BI-BUS DRIVERS (cont'd)

 


Figure 6.6.1--Bus Transceiver Circuit

A number of varying circuit configurations are available--ie, clamped or unclamped inputs, inverting or noninverting buffers, and various disabling schemes.

6.6.2 Bi-Bus Drivers A very useful device in bus-structured designs is the *bi-bus driver*. We use this term to refer to the circuit of Figure 6.6.2(a), where two three-state bus drivers are connected in parallel, with complementary driving direction. The two enable terminals are shown separately in Figure 6.6.2, and part (b) shows a convenient symbol to designate the bi-bus driver. When ENABLE #1 is activated,

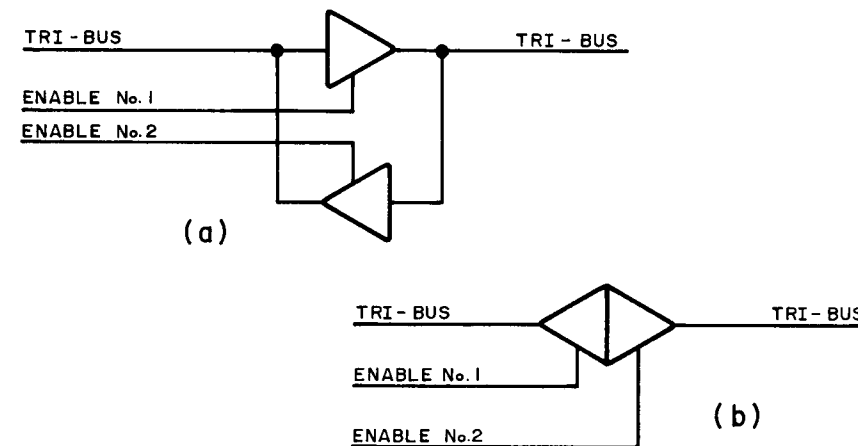


Figure 6.6.2--(a) Dual-Enable Bi-Bus Drivers; (b) Convenient Symbol

SEC. 6.6 BUS TRANSCEIVERS AND BI-BUS DRIVERS (cont'd)

the tri-bus to the left drives the tri-bus to the right, and when ENABLE #2 is activated, the direction is reversed. When neither is enabled, no data transfer occurs between the two busses. The control signals are designed such that at no time are both ENABLE terminals activated.

Figure 6.6.3 shows a bi-bus driver where the two ENABLE signals are connected to the same terminal, and where one driver is enabled by an active low input. Thus the enable terminal is labeled DIRECTION CONTROL, and one or the other of the drivers is normally on at any given time. (As with other three state devices, internal circuitry assures that each driver can be *disabled* more quickly than it can be *enabled*, so as to avoid driver overlap.)

 


Figure 6.6.3--Single-Enable Bi-Bus Drivers

The bi-bus driver finds application in large bus systems where a long bus is broken into two or more sections, each of which has lower capacitance (and thus higher speed) than a whole bus would have.

Bi-bus drivers also are used in the input/output structures of LSI integrated circuits. Take for example an LSI chip which has an internal bus structure, and provisions for bus-structured communications (both inputs and outputs) to the outside world. If each of the various internal bus drivers were constructed so as to be able to drive bus receivers on the outside of the chip, each would have to have relatively high power capabilities. This is indicated graphically in Figure 6.6.4(a), in "Integrated Circuit No. 1," where large bus drivers are shown. Compare this with part (b), "Integrated Circuit No. 2." Here a bi-bus driver is used to interface the chip's low-power internal drivers and receivers with the outside world. The bus drivers within the integrated circuit can be made much smaller (as shown graphically), that is, take up less chip area and consume less current, since they need only drive the chip's internal bus receivers and the input to the bi-bus driver.

SEC. 6.6 BUS TRANSCEIVERS AND BI-BUS DRIVERS (cont'd)

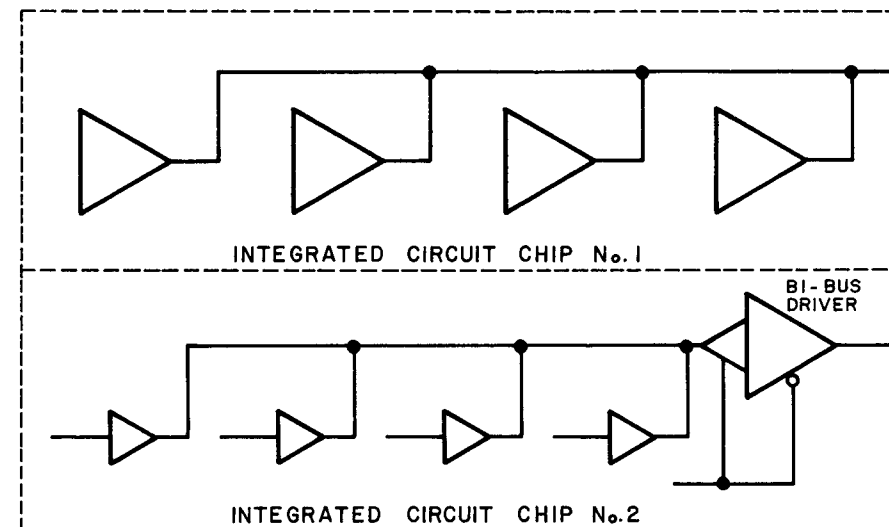


Figure 6.6.4--Bi-Bus Drivers Save Chip Area by Handling Interface with External Bus

SEC. 6.7 THE 8008 DATA BUS

6.7.1 *Bi-Bus Drivers in the 8008* The 8008 microprocessor employs what amount to single-enable bi-bus drivers at its eight data bus pins. These bi-bus drivers connect the bi-directional bus internal to the CPU chip, D7 through D0, with the bi-directional data bus external to the CPU, called in this book BB7 through BB0. The single-enable signal which controls the driving direction of the bi-bus drivers is developed within the CPU.

The CPU bi-bus driver drives *outwards* during most of its states. That is, the internal eight-bit data bus is transmitted outward to the external BB bus.

The CPU bi-bus driver drives *inwards* during the T3 state, except during PCW cycles. That is, the data on the external BB bus drives the CPU's internal data bus. The directionality is inwards also during the WAIT and the STOPPED state, when the external BB bus is *not* being driven.

SEC. 6.7 THE 8008 DATA BUS (cont'd)

6.7.2 *T4 and T5 Times* The T4 and T5 states occur in the 8008 during idle states, and during internal processor operations which require data transfers internal to the chip. That is, during T4 and T5 times, bus drivers within the 8008 are transmitting to bus receivers on the internal data bus. During these states, the 8008's bi-bus drivers clearly must be enabled in such a manner that information on the external BB bus is *not* driven inwards, or else the internal data bus would be disrupted. Thus, the bi-bus drivers drive *outwards* during T4 and T5 times, and the state of the internal data bus is available on the external BB bus.

The chip manufacturers state, in a footnote to the chart called *INTERNAL PROCESSOR OPERATIONS* (reprinted in Chapter 2), that the "Content of the internal data bus at T4 and T5 is available at the data bus. This is designed for testing purposes only." The above discussion should demonstrate that this fact is a logical consequence of the bus structure used within the 8008. An unnecessarily complex bi-bus driver circuit would be required to design this feature out (one with dual enables and extra gating). Thus one need not fear that the availability of this information is likely to change on future 8008 devices.

The availability of internal bus data during T4 and T5 times is used in Chapter 11 of this book for adding extra instructions to the 8008.

6.7.3 *8008 Data Bus Buffering* As discussed in Chapter 2 above, the 8008's internal bi-bus drivers are just capable of sinking 1.4 MA under normal voltage and temperature conditions. Many 8008 designs therefore add low-power TTL buffers (or CMOS buffers followed by regular TTL buffers) to the 8008's eight data outputs, producing an output bus which, in this book, would be labeled TB7 through TB0. The direct connections to the 8008 data terminals now form the *input* bus, labeled NB7 through NB0.

Another approach, used in the designs in this book, is to use low-power Schottky integrated circuits for interfacing with the 8008 data bus. Up to three such devices may be driven directly by the 8008. The additional cost of these devices must be considered, but so must the cost of the buffers (including stocking, testing, and insertion) and the PC board space saved.

When buffers are not used, the same bi-directional bus (BB) serves both for inputs and outputs to the CPU. This leads to added simplicity in the bus structure on the microcomputer PC board.

Input bus considerations are discussed further in Chapter 8 below.

SEC. 7.1 I/O ADDRESS MODES

Communications between a microprocessor and data-handling circuitry external to the central processing unit are commonly implemented by executing *input* and *output* (I/O) instructions. Special circuitry generates timing signals necessary for synchronizing the I/O device with the CPU--a *strobe* signal which causes an *output port* to latch up information on a bus at the appropriate time, or an *enable* signal which activates the bus-driving circuitry associated with an *input port*, causing the input data to be transmitted to the CPU.

Just as when the CPU is reading from or writing into memory, a means must be provided for *addressing* the desired I/O port. This I/O port address must be available outside the CPU board at the same time that the I/O data transfer takes place--in practice, for proper synchronization, a little earlier.

Examples of I/O ports are printers; keyboards; television typewriters and graphic displays; analog to digital converters and digital to analog converters; digital displays; cassette recorders; and so on.

There are at least three common modes for addressing I/O ports, each being used by a different standard eight-bit microprocessor.

8008 Mode--In the 8008, the simplest of these processors, the I/O port address appears on five bits of the high-order address bus, namely DH5 through DH1. *Output* data appears on the low-order address register, DL7-DL0. *Input* data is transmitted to the CPU via the CPU data bus, DB7-DB0.

8080 Mode--In the 8080, the I/O port address appears in duplicate on both address busses, DH7-DH0 and DL7-DL0. Both *input* and *output* data transfers take place via the CPU data bus, DB7-DB0. The 8080 microprocessor provides signals which are used to create I/O strobes for activating these data transfers at the appropriate time. Data transfer is unidirectional--i.e., *input* only or *output* only.

6800 Mode--In the 6800, there are no I/O instructions as such; I/O ports are simply addressed as memory. Typically, one section of memory is set aside for I/O use. Just as with memory, I/O data transfers take place via the data bus, DB7-DB0.

The first part of this chapter concentrates on 8008-type instructions. A method of decoding the strobe and enable signals for these instructions is described next. Finally, information is presented on 8080-type I/O instructions. A method of generating a universal I/O strobe enable signal, *COMPATIBLE WITH ALL THREE I/O ADDRESSING MODES*, ends the chapter.



SEC. 7.2 8008 INPUT/OUTPUT INSTRUCTIONS

7.2.1 *Instruction Codes* The 8008 has a complement of eight *input* instructions and 24 *output* instructions, as shown in Figure 7.2.1.

| INSTRUCTION BINARY | | INSTRUCTION OCTAL | | INSTRUCTION MNEMONIC | | INSTRUCTION BINARY | | INSTRUCTION OCTAL | | INSTRUCTION MNEMONIC | |
|-----------------------|-----|----------------------|----|-------------------------|-----|-----------------------|----|----------------------|--|-------------------------|--|
| 01RRMMM1 | | | | | | 01RRMMM1 | | | | | |
| 01111111 | 177 | OUT | 37 | 01011111 | 137 | OUT | 17 | | | | |
| 01111101 | 175 | OUT | 36 | 01011101 | 135 | OUT | 16 | | | | |
| 01111011 | 173 | OUT | 35 | 01011011 | 133 | OUT | 15 | | | | |
| 01111001 | 171 | OUT | 34 | 01011001 | 131 | OUT | 14 | | | | |
| 01110111 | 167 | OUT | 33 | 01010111 | 127 | OUT | 13 | | | | |
| 01110101 | 165 | OUT | 32 | 01010101 | 125 | OUT | 12 | | | | |
| 01110011 | 163 | OUT | 31 | 01010011 | 123 | OUT | 11 | | | | |
| 01110001 | 161 | OUT | 30 | 01010001 | 121 | OUT | 10 | | | | |
| 01101111 | 157 | OUT | 27 | 01001111 | 117 | INP | 07 | | | | |
| 01101101 | 155 | OUT | 26 | 01001101 | 115 | INP | 06 | | | | |
| 01101011 | 153 | OUT | 25 | 01001011 | 113 | INP | 05 | | | | |
| 01101001 | 151 | OUT | 24 | 01001001 | 111 | INP | 04 | | | | |
| 01100111 | 147 | OUT | 23 | 01000111 | 107 | INP | 03 | | | | |
| 01100101 | 145 | OUT | 22 | 01000101 | 105 | INP | 02 | | | | |
| 01100011 | 143 | OUT | 21 | 01000011 | 103 | INP | 01 | | | | |
| 01100001 | 141 | OUT | 20 | 01000001 | 101 | INP | 00 | | | | |

Fig. 7.2.1--The 32 8008 I/O Instructions

These instructions are one byte long, as shown in the chart above. The binary instruction code takes the form *01RRMMM1*. If *RR* = 00, the instruction is an input instruction--*Input 7* through *Input 0*--where the input number is defined by the eight combinations of *MMM*. If *RR* = 01, 10, or 11, the instruction is one of the 24 possible output instructions, *Output 37* through *Output 10*.

The 8008 user may find the following rule convenient in remembering I/O instruction codes. Take the number of the input or output port; double it (using base 8 arithmetic); add 101. The result is the octal instruction code.

SEC. 7.2 8008 INPUT/OUTPUT INSTRUCTIONS (cont'd)

Actually all 32 I/O instructions can be used to *output* data from the 8008. Only eight can be used for *inputting* data. This point is discussed and developed further in Chapter 9.

During an input instruction, the information at the selected input port is transferred into the 8008's internal A register. Subsequent instructions may be used to process the inputted data.

Before an output instruction is executed, the data to be transferred out is first loaded into the 8008's A register. During the execution of the instruction, this data is transferred to the selected output port.

7.2.2 *The PCC Memory Cycle* I/O instructions in an 8008 microcomputer system require two memory cycles to execute. The first memory cycle, a PCI (instruction) cycle, is used to fetch the I/O instruction from memory, and is just like the first part of any other 8008 instruction. It consists of the T₁, T₂, and T₃ states only--T₄ and T₅ are skipped. See Figure 7.2.2.

| INSTR. | PCI MEMORY CYCLE | | | PCC MEMORY CYCLE | | | | |
|--------|------------------|------------|--|------------------|------------------|----------------------|--------------|------------------------|
| | T1 | T2 | T3 | T1 | T2 | T3 | T4 | T5 |
| OUTPUT | PCL OUT | PCH OUT | FETCH INST. TO IR & REG. b | REG. A TO OUT | REG. b TO OUT | IDLE | [none] | [none] |
| INPUT | " | " | " | " | " | DATA TO b REG. | FLAGS OUT | REG. b TO REG. A |

Fig. 7.2.2--8008 I/O Instructions: Internal Operations



SEC. 7.2 8008 INPUT/OUTPUT INSTRUCTIONS (cont'd)

During the second memory cycle, a PCC (command) cycle, an I/O instruction departs significantly from the other 8008 instructions.

During *PCC-T1 time*, the data in the A register goes out on the 8008 data bus. (This information was loaded into the A register by a previous instruction.) As always, the DL register external to the 8008 latches up whatever is on the data bus at $\overline{ST1}$ time. Usually the information on the bus during T1 time is part of a memory address, so this use of the DL register is somewhat unexpected.

During *PCC-T2 time*, the instruction itself goes out on the 8008 data bus. It is latched up in the external DH register at $\overline{ST2}$ time. Now the DH register serves (temporarily) as a source from which the control logic can derive the binary code for the I/O instruction. The relevant bits are DH5 through DH1.

7.2.2 Output Instruction Sequence Consider the case where data is being outputted. The output information has been loaded into the A register by a previous instruction. During T1 time of the PCC cycle, this data leaves the CPU. But the external hardware does not yet have any indication where this information is going! So, the information is stored temporarily in the DL register. Then, at T2 time of the PCC cycle, the instruction is latched into the DH register. Now the destination can be decoded. At T3A time, which during output instructions is an idle state for the CPU, the appropriate output port is strobed. The information then passes from the DL register to the output port. See the top half of Figure 7.2.2 below.

Thus, output information from the 8008 normally travels via the DL register, rather than directly from the CPU data bus to the output ports. This is necessary to accommodate the 8008's internal processor operations. This feature is actually convenient to the hardware designer because the eight-bit latch which makes up the DL register serves as a buffer which keeps the output ports from overloading the CPU data bus.

After T3 time of the PCC cycle the output instruction has done its job, and the T4 and T5 states are skipped.

7.2.3 Input Instruction Sequence During T2 time, PCC memory cycle, of an *input* instruction, the instruction code is used to select the input port designated by the

SEC. 7.2 8008 INPUT/OUTPUT INSTRUCTIONS (cont'd)

INPUT INSTRUCTIONS

| TIME | CPU | | | | EXTERNAL HARDWARE | | | |
|-------------|--------------|-------------|-------|----------|-------------------|--------------|---------|-------------|
| | A REG. | b REG. | FLAGS | DATA BUS | INPUT DEVICE | DL REG. | DH REG. | OUTPUT PORT |
| PCC-T1 | OUTPUT DATA* | | | (X) | | (X) | | |
| PCC-T2 | | INSTR. CODE | | (X) | | | (X) | |
| PCC-T3 | | (X) | | (X) | INPUT DATA | OUTPUT DATA* | | (X) |
| PCC-T4 | | | FLAGS | (X) | | | | |
| PCC-T5 | (X) | INPUT DATA | | | | | | |
| NEXT INSTR. | PROCESS | | | | | | | |

OUTPUT INSTRUCTIONS

| TIME | CPU | | | | EXTERNAL HARDWARE | | | |
|--------------|-------------|-------------|-------|----------|-------------------|-------------|---------|-------------|
| | A REG. | b REG. | FLAGS | DATA BUS | INPUT DEVICE | DL REG. | DH REG. | OUTPUT PORT |
| PREV. INSTR. | LOADED | | | | | | | |
| PCC-T1 | OUTPUT DATA | | | (X) | | (X) | | |
| PCC-T2 | | INSTR. CODE | | (X) | | | (X) | |
| PCC-T3 | IDLE | | | | | OUTPUT DATA | | (X) |

*An input instruction may also be used to output data, as shown by the steps marked with an asterisk. See Chapter 9.

Figure 7.2.3--Data Transfers During PCC Cycle of 8008 I/O Instructions

SEC. 7.2 8008 INPUT/OUTPUT INSTRUCTIONS (cont'd)

instruction. Then, at T3A time, the CPU bus inputs data to its internal b register. At T5 time, the input data is transferred to the A register, and the input instruction has achieved its purpose.

(At T4 time of a PCC cycle, the four flags appear on the data bus. This is an auxiliary function unrelated to I/O data transfers. It is useful in equipment where the flag conditions are displayed on a front panel, or in flag-saving hardware: see Chapter 17).

Figure 7.2.3 illustrates the data transfers which take place during I/O instructions.

SEC. 7.3 INPUT AND OUTPUT SYMBOLS

An eight-bit digital input device from which the CPU derives data is called an *input port*. Generally it is a multiplexer with open-collector output circuitry, or an integrated circuit with three-state output circuitry (as discussed in Chapter 8). The eight-bit digital output devices to which the CPU sends data are called *output ports*. Digital ports are represented by the symbol *D*, and analog ports by *A*. Inputs are referred to by the symbol *N* and outputs by the symbol *T*. Thus *DN* refers to a digital input, and *AT* to an analog output.

DT17 refers to digital output 17, and when used without a suffix, is used to denote the strobe signal used for loading output port 17. Similarly, an enable signal for digital input 5 would be represented as *DN5*. Since such enable and strobe signals are usually provided by the outputs of active-low decoders, the signals are often shown in their complemented state--*DT17*, *DN5*, etc.

Figure 7.4.1 in the next section shows all possible digital input and output strobes.

In order to refer to an input or output strobe in a general way, the characters *X*, *Y*, or *Z* replace numerical designations. Thus, \overline{ANX} is a reference to an active-low strobe for an undefined analog input port.

A particular digital input or output *bit* is referenced by adding a dashed suffix to the associated enable or strobe symbol. Hence, bit 7 of digital input 3 would be called *DN3-7*. When these symbols are used with *analog* inputs, they refer to one of several analog signals in a multi-channel (multiplexed) analog system. *AN4-7* would refer to the eight-bit digital value at digital input port #4 which derives from analog input channel number 7. (See Chapter 22.)

SEC. 7.4 GENERATING 8008 INPUT ENABLES AND OUTPUT STROBES

During input instructions the 8008 CPU receives data on its bidirectional bus during T3 time, PCC cycle. In practice, the input devices are enabled slightly in advance of the beginning of T3 time, that is, during T3A time. Output ports are also loaded, from the DL register, at T3A time of an output instruction, PCC cycle. A general-purpose strobe/enable signal which occurs only at T3A time of I/O instructions may be formed by gating the T3A state (developed by the main timing circuitry discussed in Chapter 5) with $\overline{CC2}$ and $\overline{CC1}$ (the latter two signals defining a PCC cycle). In this book, this signal is called \overline{DIN} --or \overline{DIN} when it is an active-low signal.

Figure 7.4.2 shows \overline{DIN} generated by a three-input NAND gate, and being used to enable I/O strobe/enable decoders. The encoded number of the input or output port is obtained from the DH register, where the I/O instruction was stored during T2 time, PCC cycle. Note how simply the signals for all 32 input/output instructions are generated. In a practical microcomputer design, not all 32 ports would necessarily be used. For example, the lower decoder in Figure 7.4.2 would be omitted in a system needing all eight inputs but only eight output ports.

Figure 7.4.1 shows a 74LS138 3-to-8 decoder being used to generate four output strobes and four input enables--all with only one chip. Note that in this example, the \overline{DIN} signal is not accessible: it is generated within the 74LS138 chip.

 


Fig. 7.4.1--I/O Decoder for Four Inputs, Four Outputs

SEC. 7.4 GENERATING 8008 INPUT ENABLES AND OUTPUT STROBES (cont'd)

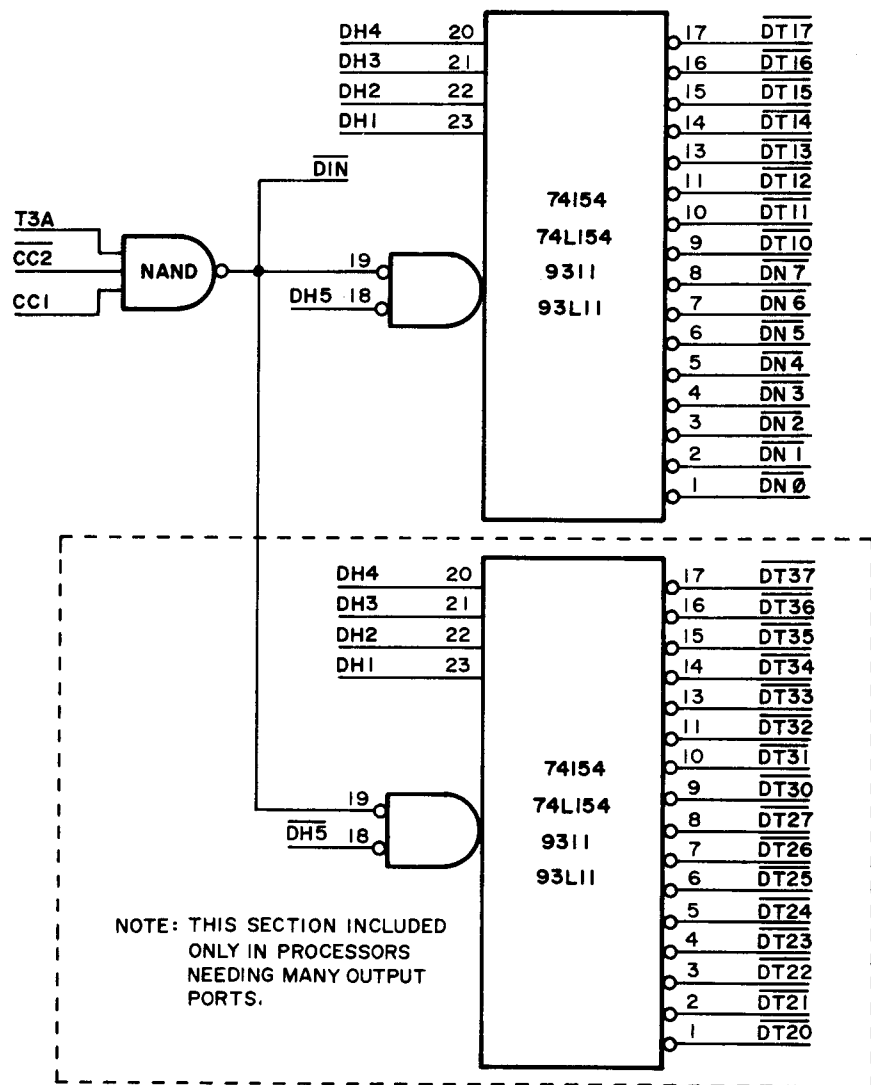


Fig. 7.4.2--Generating All 32 8008 I/O Strokes and Enables



microcomputer
design

SEC. 7.4 GENERATING 8008 INPUT ENABLES AND OUTPUT STROBES (cont'd)

Note that the circuit of Figure 7.4.1 ignores DH5 and DH3. This means that the decoder does not distinguish between I/O instructions which are identical with regard to DH4, DH2, and DH1, but may differ so far as DH5 and DH3 are concerned. This decoder is restricted as to the number of inputs and outputs available; and different I/O instructions will produce the same strobe. For example, a \overline{DNO} pulse will be generated by INP 000, INP 004, OUT 010, or OUT 030. Any one of these instructions can be used as an *output* instruction: the data left in the A register by a previous instruction can be strobed into an output port at PCC-T3A (\overline{DIN}) time. But, as discussed in the previous sections of this chapter, only in the case of the two input instructions--INP 000 or INP 004--will input information present on the data bus at PCC-T3A time end up in the A register when the instruction is finished. With this distinction in mind, the programmer might find places where he would use an OUT 010 and others where the INP 000 instruction would be needed.

SEC. 7.5 PERIPHERAL STROBE DECODING TECHNIQUES

7.5.1 Using \overline{DIN} and the DH Register When peripheral devices are being connected to the main logic board in a microcomputer, it may be very cumbersome to decode all the needed strobe signals on the CPU board and provide all those extra pins on the connector. A more efficient approach is to provide the DH register and the \overline{DIN} signal. Then the needed strobes are decoded by the peripheral itself.

This approach also leads in the direction of a universal and flexible peripheral bus structure. See Chapter 20 for a more complete description of how peripheral busses should be designed.

7.5.2 Developing a Peripheral Strobe Approach Every input or output instruction in an 8008 microcomputer contains five address bits. If all combinations of inputs and outputs are to be utilized, then any strobe generated should depend on *all five* bits of this instruction address. (The example in Figure 7.4.1 does not *uniquely* decode inputs and outputs.) The strobe should depend not only on the five bit addresses; it should be enabled only when the \overline{DIN} signal is active (logic zero). Therefore there are six signals which must be gated together to provide any one uniquely-defined I/O strobe. These six signals are DH5, DH4, DH3, DH2,



microcomputer
design

SEC. 7.5 PERIPHERAL STROBE DECODING TECHNIQUES (cont'd)

DH1, and \overline{DIN} . Figure 7.5.1 shows a six-input NAND gate and three inverters being used to decode an INPUT 007 strobe ($\overline{DN7}$). By inserting and deleting inverters in all the various combinations at the DH5 through DH1 inputs, all 32 of the 8008 I/O strobe/enable signals could be generated.

 


Fig. 7.5.1--A NAND Gate Decodes the Six Signals Necessary to Produce a Strobe or Enable

This NAND gate is obviously quite awkward. What is needed is a single integrated circuit which combines the six required input bits and provides a number of input/output strobe/enable signals. This one IC could be located in the peripheral device and decode the few I/O control signals which it might need.

The 74LS138 TTL integrated circuit is a 3-to-8 decoder with three strobe inputs. Two of the strobes are active-low, and one is active-high. This turns out to be very convenient for many decoding applications, and therefore members of the '138 family appear frequently in this book. They include the 74S138 (Schottky) as well as the commonly-used 74LS138 or 3205 (8205) (low-power Schottky).



SEC. 7.5 PERIPHERAL STROBE DECODING TECHNIQUES (cont'd)

Figure 7.5.2 illustrates the 74138 decoder with the strobe functions shown to the left as an AND gate. All three inputs must be in their active positions in order for any output to be enabled (ie, to go low). The inputs labeled 0 must be at logic zero, and the input marked 1 must be at logic one. One and only one of the eight outputs can be active at a time; which is selected depends on the C, B, and A input lines. Each output line is labeled with an octal number which corresponds to the three-bit binary combination at the C, B, and A inputs which selects that output line.

 


Fig. 7.5.2--74LS138 3-to-8 Decoder Schematic

This integrated circuit satisfies the requirements outlined above for a peripheral strobe decoder, since it has exactly the six inputs desired, and provides eight active low outputs.

In application, the active-low \overline{DIN} strobe must be gated with all outputs, and thus must be connected to one of the 74138's two active-low enable inputs. Then the DH register bits--DH5 through DH1--are connected to the remaining input terminals in any order.



SEC. 7.5 PERIPHERAL STROBE DECODING TECHNIQUES (cont'd)

7.5.3 Selecting the Desired Combination of Strobes There are twenty unique ways in which the five DH register bits may be connected to the 74138 peripheral strobe decoder. They are shown in Figure 7.5.3. Eight of these combinations provide *output* strobes, while the remaining twelve combinations provide some inputs and some outputs.

Note that with this scheme, INP 000 is never decoded. This strobe can be generated only when all five DH register bits are logic zero, but the 74138 requires that there be at least one active high input bit (at pin 6). For a similar reason, the DT37 strobe cannot be generated. Therefore INP 000 and OUT 037 are usually designated as I/O ports located right on the main CPU logic board.

In evaluating the usefulness of the various combinations of signals provided, note that an "output instruction" in the 8008 is really an *output-only* instruction: it cannot be used to input data to the CPU. On the other hand, an "input instruction" is really an *input/output* instruction, and may be used for either inputting or outputting (or both). This point is elaborated further in Chapter 9.

For the further convenience of the designer, the twenty rows in Figure 7.5.3 are realigned in Figure 7.5.4 as *columns*. This diagram is a graphic representation of how the decoder inputs may be wired, and what control signals result.

The decoders on the various peripheral circuit boards of a system need not completely avoid overlap in input/output signals. All that is necessary is to develop a sufficient number of *unique* input/output control signals to fulfill the needs of each peripheral device.

As design examples of this peripheral strobe technique, Figures 7.5.5 and 7.5.6 show the circuit diagrams which correspond to columns 15 and 18 respectively of the table in Figure 7.5.4. If these two decoders were used in two different peripherals, each would have eight I/O ports which do not conflict with the other peripheral.

Chapter 20 more fully describes the bus structure to which these peripherals might be attached, and gives a block diagram of an efficient peripheral bus system.

With slight modifications, the same bus structure is used in the modular micro series of microcomputers, available from Martin Research. The Model 471 CPU board, based on the 8080, is described near the end of this book. The 471 supports not only 8080 I/O instructions of the standard variety, but also 8008-compatible I/Os, as well as memory-mapped I/O instructions using the DIN strobe. Therefore the strobe decoding techniques described in this chapter are very useful in an 8080 system.



microcomputer
design

SEC. 7.5 PERIPHERAL STROBE DECODING TECHNIQUES (cont'd)

| LINE NO. | DH BITS | OUTPUTS ONLY | | | | | | | | | | INPUT/OUTPUTS | | | | | | | | | | | | | | | | | | | | | | | |
|----------|---------|--------------|----|----|----|----|----|----|----|----|----|---------------|----|----|----|----|----|----|----|----|----|----|----|----|----|---|---|---|---|---|---|---|---|--|--|
| | | 37 | 36 | 35 | 34 | 33 | 32 | 31 | 30 | 27 | 26 | 25 | 24 | 23 | 22 | 21 | 20 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | | |
| 1. | 10CBA | | | | | | | | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | | | | | | | | | | | | | | | | | | | |
| 2. | 1C0BA | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 3. | 1CB0A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 4. | 1CBA0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 5. | C10BA | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 6. | C1B0A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 7. | C1BA0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 8. | CB10A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 9. | CB1A0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 10. | CBA10 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 11. | 01CBA | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 12. | 0C1BA | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 13. | 0CB1A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 14. | 0CBA1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 15. | C01BA | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 16. | C0B1A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 17. | COBA1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 18. | CB01A | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 19. | CB0A1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 20. | CBA01 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

Fig. 7.5.3--The 20 Combinations of Outputs Produced by the Peripheral Strobe Decoder

SEC. 7.6 8080 I/O INSTRUCTIONS

The 8080 instruction set includes the two instructions IN (input) and OUT (output). Each is a two-byte instruction, the second byte of which is an eight-bit I/O port address. Thus, the 8080 is able to address 256 input ports and 256 output ports. The 8080 develops a distinct output strobe signal (output write, \overline{IOW}), and a separate input enable signal (input read, \overline{IOR}). These are related to IN and OUT instructions in the same way that memory read and write signals (\overline{MEMR} and \overline{MEMW}) relate to memory-referencing instructions. These distinct strobe signals mean that the I/O ports are addressed independently from memory.

This 8080 I/O mode is similar to the 8008 in its separation from memory-referencing instructions. However, in the 8080, output data appears on the data bus, rather than on the low-order address bus.

Also, with the 8080, there are eight I/O address bits (rather than five) which appear redundantly on both the high-order and low-order address lines (DH7-DH0 and DL7-DL0). To produce output strobe signals, a decoder combines the output strobe, \overline{IOW} , with various combinations of the eight address lines. Similarly, to create input enable signals, a decoder combines \overline{IOR} with the address lines.

Unless an unusually large number of I/O ports is required in an 8080 system, it is unnecessary to use all eight address lines in the I/O decoding circuitry. Five lines are often more than adequate--producing 32 input ports and 32 output ports. This allows the 74LS138/3205 IC to be used in an 8080 system, just as described earlier in this chapter (Sec. 7.5).

One method is simply to ignore three of the address lines in the I/O decoding circuitry. Then referring to the decoding circuitry in Sec. 7.5, \overline{IOR} or \overline{IOW} replaces the 8008 signal \overline{DIN} .

Another technique is to create an 8080 version of the signal \overline{DIN} , and to use it for *memory-mapped* I/O instructions. That is, a given area in memory is assigned to I/O ports, and memory read/write instructions are used instead of IN and OUT. The signal \overline{DIN} is produced by combining 8080 memory read/write signals with three selected address bits, thus uniquely defining a portion of the memory map for I/O ports. The remaining five address bits are combined with \overline{DIN} by the 74LS138 peripheral strobe decoder to produce any eight of the 32 possible I/O strobe/enable signals.

These techniques are discussed in further detail, with examples, in the 471 data sheet, Sec. 1.6, near the end of this book.

A method of creating a 16-bit output port for the 8080 is discussed at the end of Chapter 9.



microcomputer
design

SEC. 7.6 8080 I/O INSTRUCTIONS (cont'd)

The appendix on the 471 CPU board (near the end of this book) presents a method for generating strobe/enable signals which may be used for all three I/O addressing methods: 8080 I/O instructions; 8008-type I/O instructions; and memory-mapped (6800 style) I/O instructions. This circuitry confers the advantages of all three I/O modes, including combined I/O instructions. The 471 data sheet briefly presents the software necessary for implementing these I/O address modes with the 8080 CPU.



microcomputer
design

SEC. 8.1 INPUT DESIGN

This chapter describes several methods for inputting digital information to a microcomputer. It is assumed that the information is available at TTL logic levels.

Both the 8008 and the 8080 microprocessors receive input data through an eight-bit bidirectional data bus. The data bus is used not only for receiving data, but also for outputting data from the CPU and for addressing memory, all at different stages in the internal processor operations. This imposes the first input design requirement: the input devices on the bidirectional data bus must be disabled when the CPU is not supposed to be accepting data.

Since more than one eight-bit data source is usually required, the second requirement is some method of selecting the desired input source.

After a preliminary discussion of 8008/8080 data bus input voltages, this chapter discusses two basic input approaches: using multiplexers, and using three-state bus structures.

SEC. 8.2 8080/8008 DATA BUS INPUT VOLTAGES

The 8008 and 8080 microprocessors have been designed for compatibility with TTL circuitry. However, their internal MOS circuitry needs a little help in recognizing logic high voltages. TTL devices typically output logic high voltages of about +3.4 volts, but are not guaranteed to deliver more than +2.4. The 8008 requires a logic high input of $V_{CC} - 1.5$ V, or +3.5 V with a +5 volt supply. The 8080 requires +3.3 V. (The AM9080A from Advanced Micro Devices requires only +3.0 V, but to allow interchangeability, the designer should provide for +3.3.)

In early 8008 designs, an array of pullup resistors was usually connected from each data bus line to +5 V. In one published circuit, the resistors were connected through diodes to a transistor switch, which was activated during input selection cycles. The 8080 internalizes this feature with active pullup resistors which are switched on during DBIN cycles. Still, these resistors are not guaranteed to turn on until the minimum V_{IH} is reached. (The NEC uPD8080A omits them.)

When the CPU data bus terminals are connected to bus drivers, to increase the CPU's ability to address an expanded system, a bidirectional bus driver IC may be chosen which is rated to provide voltage levels of over 3 volts when driving inwards. Examples: Signetics 8T26 and 8T28; Intel 8216 and 8228. (The 8228 is a special driver/controller for the 8080.) In small systems, MOS memory connected directly to the data bus (2102 RAM, 2708 PROM, for example) provides the required voltage levels; MOS memory ICs are manufactured with the same (or very similar) process as the 8080 or 8008 itself. The 340097 CMOS driver (Fairchild) also interfaces to MOS microprocessors.

SEC. 8.2 8008/8080 DATA BUS INPUT VOLTAGES (cont'd)

There are two basic methods of driving these MOS microprocessors with TTL ICs. The first is to use pullup resistors, as do the manufacturers in their prototype designs. Resistors in the range of 10 to 22 K ohms are suitable for data busses using three-state input devices.

The other approach is to make sure that the devices driving the CPU data input bus are specified for a logic high output voltage of +3.5 volts or better. Many off-the-production-line TTL devices meet this specification already.

As manufacturers are called upon to deliver integrated circuits in quantity which can drive MOS LSI devices without pullup resistors, they will probably comply by supplying respecified parts (perhaps at premium prices). Intel Corporation has announced the availability of ICs guaranteed to deliver a +3.65-volt logic high level, which provides a safety margin for protection against noise. An example of this is the 8212, an octal latch with three-state outputs, available in a 24-pin package.

SEC. 8.3 INPUT MULTIPLEXERS

8.3.1 Three-State Multiplexers The multiplexer is essentially a digital electronic switch, which selects the input designated by its data select code. TTL designers will be familiar with such devices as the 74153, a dual 4-to-1 multiplexer with TTL totem-pole outputs. A multiplexer which is to interface with the bidirectional CPU bus must be capable of being disabled. Figure 8.3.1 outlines a design in which multiplexers with three-state outputs connect to the CPU bus.

The block diagram in Figure 8.3.1 shows a three-state multiplexer array with six eight-bit input ports. Input ports #2 and #4 are connected directly to the multiplexer. The circuitry used here is totem-pole TTL.

Multiplexer input ports #0 and #1 are connected to a three-state input bus. (See Chapter 6 for definitions of bus types. In the diagram, the symbol $\bar{3}/s$ indicates a three-state device.) A second input bus funnels information from inputs #6 and #7 into the multiplexer.

SEC. 8.3 INPUT MULTIPLEXERS (cont'd)

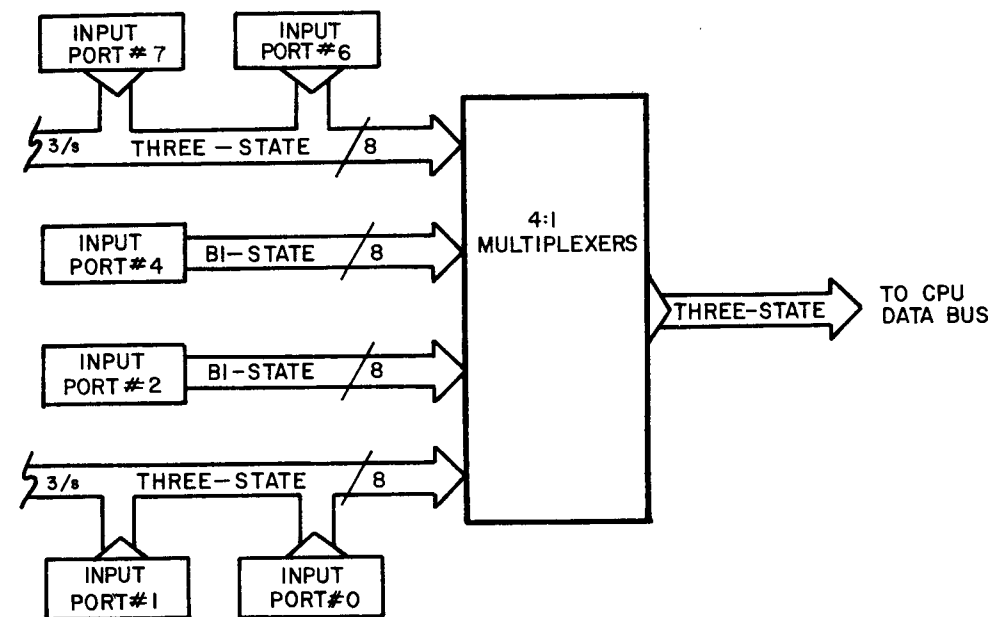


Figure 8.3.1--Input Design Uses Both Multiplexers and Three-State Input Bus

Figure 8.3.2 shows the essential details of the multiplexer portion of the preceding figure. This circuit uses 74253 three-state multiplexers in a 32-to-8-line array. A few sample input connections are shown. The symbol $DN1/0-7$ refers to the high-order bit (bit 7) of either input #1 or input #0. The line labeled BBO refers to the low-order bit of the CPU's bidirectional data bus. Other lines are labeled in similar notation.

8.3.2 Open-Collector Multiplexers As implied in the general discussion of bus structures in Chapter 6, open-collector multiplexers may be used to interface with the CPU bidirectional data bus. For example two 8267 open-collector multiplexers could be connected to the CPU data bus. The designer may choose to emulate this approach; but consider that it may necessitate pullup resistors on the data bus.

SEC. 8.3 INPUT MULTIPLEXERS (cont'd)

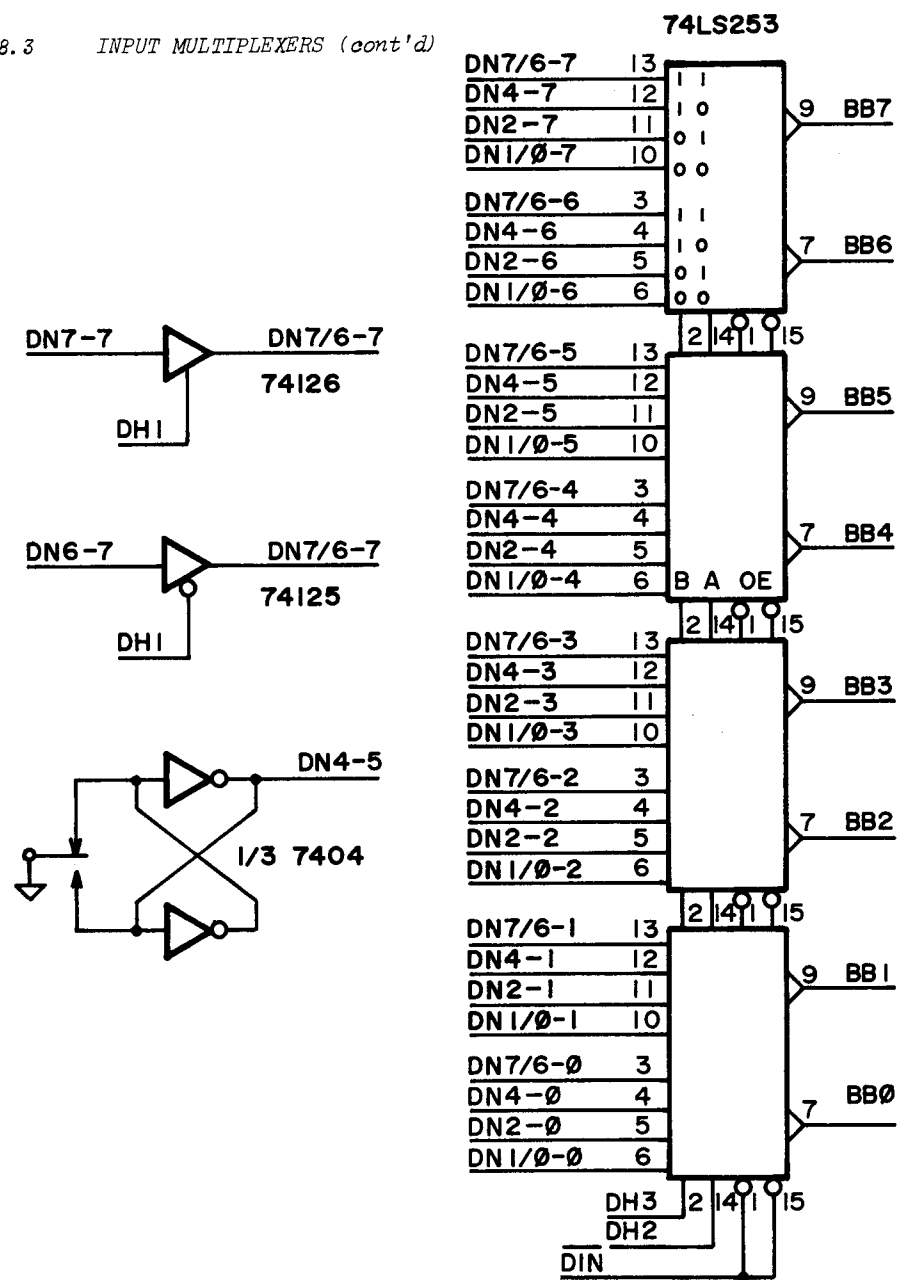


Fig. 8.3.2--Essential Circuitry for Figure 8.3.1



microcomputer
design

SEC. 8.4 INPUT ENABLE AND SELECT SIGNALS

8.4.1 Decoding the Input Enable Signal--8008 CPU The 8008 reads input data during T3A time of an input instruction. Therefore, in Figure 8.3.2, the 74LS253's three-state output enable pins (1 and 15) could be connected to a 3-input NAND gate, one of whose inputs is connected to T3A. Only during memory cycle two of an input (or output) instruction (PCC cycle) will the high-order control bit, CC2 (sometimes referred to as DH7) be logic zero, AND CC1 be logic one. Therefore the other two inputs to the 3-input NAND are $\overline{CC2}$ and $\overline{CC1}$ --and now the multiplexers will be enabled during T3A time of either an input or an output instruction. If, at this time, DH5 and DH4 are low, then the instruction being executed is an input instruction. DH5 and DH4 could have been added as additional inputs to the NAND gate (which would then have to be a 5-input NAND)--but this logic is unnecessary. It does not matter if the multiplexer tries to input data during an output instruction. The T3 state of the PCC cycle during an output instruction is an idle state. The 8008's bidirectional data bus driver reads data inward onto the internal data bus, but nobody is listening inside. The designer can thus reduce a 5-input NAND to a 3-input NAND. In a complex 8008 system, this concept can save a number of ICs.

8080 CPU--The I/O strobe signal to be used depends on which I/O addressing mode is used with the 8080, as discussed in Chapter 7. \overline{IOR} is the normal 8080 input enable signal, but \overline{DIN} or \overline{MEMR} may also be used. (See the 471 data sheet, Sec. 1.6.)

8.4.2 Selecting Input Ports--8008 CPU As discussed in Chapter 7, the eight-bit binary code for the input instruction itself appears on the data bus at T2 time of memory cycle two (PCC cycle). It is latched up in the DH register, and the DH3, DH2, and DH1 bits contain the three-bit binary code for one of the eight possible 8008 input ports. In the circuit of Figure 8.3.2, DH3 and DH2 are used as the multiplexer data select lines, thereby selecting one of four combinations of two input ports (7 and 6; 5 and 4; 3 and 2; 1 and 0). To select one input port from any of these pairs, the low-order input select bit, DH1, must be used. The 74126 three-state buffer at the top left of Figure 8.3.2 uses DH1 to select one bit of input port 6. These techniques may easily be extended to provide an array of up to eight 8-bit input ports, the normal 8008 input capacity.

8080 CPU--The 8080 outputs the I/O port number on both the DH and DL address registers, redundantly, at T1 time during an I/O instruction. A full eight-bit decoder may be used, or, a predecoded strobe signal (\overline{DIN}) may be used for 8008-compatible I/O instructions or for straight memory-mapped I/O using \overline{MEMR} and \overline{MEMW} . See the 471 data sheet, Sec. 1.6.



microcomputer
design

SEC. 8.5 BUS-ONLY INPUT DESIGN

8.5.1 Direct Bus Approach In small microcomputers, all of the input devices may simply be connected directly to the CPU bidirectional data bus, using three-state devices. Only the selected input device is enabled during an input instruction (and, permissibly, during output instructions: see paragraph 8.4.1 above). At other times, all of the input devices are disabled, and draw only a small leakage current from the bidirectional data bus. For an example of this approach, see the microcomputer design in Chapter 26.

The practical limitations to the direct three-state bus approach are bus line capacitance and the leakage currents demanded by disabled three-state devices.

8.5.2 Bus Capacitance The data bus terminals of both the 8080 and 8088 are specified at rated speed for up to 100 picofarads of load capacitance. It is difficult to predict the capacitance of a given bus circuit with accuracy, because of the influence of printed circuit geometry. As a rule of thumb, the designer can estimate 7 picofarads of capacitance for each IC pin added to the bus. Large arrays, or long bus lines, are likely to cause trouble.

Capacitance loads greater than 100 pf will of course cause longer delays in data transfer. The 8008 specifications indicate that an increase from 100 to 200 pf causes the output delay to move from about 0.85 us to 1.01 us. In the 8080, adding 50 pf will add only 20 ns of output delay. These delays may be tolerable in slow-speed systems, but if the CPU is operating close to its maximum speed, the clock may have to be slowed down accordingly to compensate. When many three-state devices are to be connected to the BB bus, it is best to create a CPU input bus system using a three-state bus driver, as described in paragraph 8.5.4. This is the practice in all but very small microcomputers.

8.5.3 Three-State Leakage A second limitation to the direct bus approach results from the leakage currents demanded by disabled three-state devices. Each output terminal of a typical three-state IC may demand up to 40 microamps of leakage current when disabled. A large array of input devices on the CPU data bus may cause total leakage currents that imperil the CPU's ability to drive external devices.

The Intel 8080A is capable of sinking 1.9 ma to 0.45 V, while the AMD Am9080A will sink 3.2 ma to 0.40 V. The designer should check current data sheets to note any updates to these figures. The specs differ between manufacturers, and between the 8080A and older 8080.

SEC. 8.5 BUS-ONLY INPUT DESIGN (cont'd)

The 8008 microprocessor is capable of sinking approximately 1.5 milliamps to a logic low level of 0.4 volts (+5 volt, -9 volt power supplies, 0-70°C). It is capable of sourcing approximately 3.2 milliamps from a logic high level of 3.0 volts. Any problems with leakage current are likely to derive from the logic low specification. Take for example a circuit where the 8008 is required to drive three low-power Schottky devices with 360-microamp logic low input currents. This leaves a margin of some 420 microamps--enough to supply leakage currents to about ten disabled three-state input devices.

Another possibility is that leakage currents will endanger the ability of *external* ICs to drive the CPU. This problem is most likely to occur with MOS memory chips connected directly to the CPU data bus.

The bus structure designer must calculate these factors carefully when designing small microcomputers with multiple three-state input devices directly on the CPU data bus.

8.5.4 Adding an Input Bus When many three-state devices are to be used as inputs to the microprocessor, it is best to create a CPU input bus system. An eight-bit three-state buffer array is connected between the individual three-state input devices and the CPU data bus. The three-state buffers drive the CPU data bus when enabled by a T3A enable signal, as shown in Figure 8.5.1. The inputs to the buffer array make up the input bus (NB), relabeled because it is no longer bidirectional. The same NB bus is often connected not only to input ports, but to three-state memory devices, as shown in Figure 8.5.1.

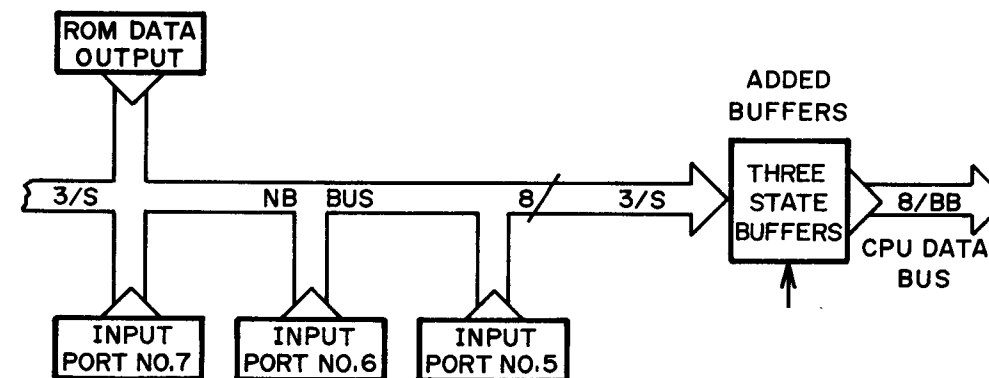


Figure 8.5.1--Block Diagram of Input System Using NB Bus

SEC. 8.5 BUS-ONLY INPUT DESIGN (cont'd)

So far as the loading of the CPU bus is a factor, the three-state buffer circuitry of Figure 8.5.1 is similar to the three-state multiplexer circuitry in Figure 8.3.1 above. Each places only one three-state device on the BB bus. The choice of circuitry depends on the number and type of input port devices to be used in the microcomputer being designed.

SEC. 8.6 EXPANDING 8008 INPUT PORTS WITH CONDITIONAL INPUTS

Some microcomputers require more than the eight input ports which can easily be provided in an 8008 system. The problem is not the input multiplexer chain which can easily be extended. An input bus structure can be expanded even more readily simply by adding more three-state devices to the bus. The problem comes in performing an input instruction with the 8008 which will create more than eight distinct input enable signals.

During memory cycle two of an input instruction--a PCC cycle--the instruction itself appears at T2 time. Only three bits of that instruction--DH3, DH2, and DH1--are available for selection of input ports, as discussed in Chapter 7 and earlier in this chapter.

A simple and convenient method of expanding inputs is to decode the DL register during the execution of input instructions. As an example, the following design decodes the seven conventional input instructions, INP 006 through INP 000. The eighth input instruction, INP 007, is broken down into eight different instructions, numbered CDN 077 through CDN 070.

Immediately before executing a conventional INP 007 instruction, the programmer must set up the three low-order bits of the A register. During execution of the input instruction, the content of the A register appears during memory cycle two (PCC cycle) at T1 time. This information is latched up in the DL register, which is always strobed at ST1 time.

In the circuit shown in Figure 8.6.1, the decoder to the left produces the conventional eight input strobes. The input #7 strobe is fed to an additional 3-to-8 decoder chip, which decodes the three low-order DL register bits--DL2, DL1, and DL0--to produce the eight conditional input strobes labeled CDN77 through CDN70.

8080 CPU--Although this conditional input technique could be used in an 8080 system, it is generally unnecessary. The normal 8080 I/O addressing mode supports up to 256 input ports and 256 output ports. If 8008-compatible I/O ports are used in an 8080 system--using DIN--all 32 I/O addresses can be used for inputs, as well as outputs. See the 471 data sheet near the end of this book, Sec. 1.6.3.

SEC. 8.6 EXPANDING 8008 INPUT PORTS WITH CONDITIONAL INPUTS (cont'd)

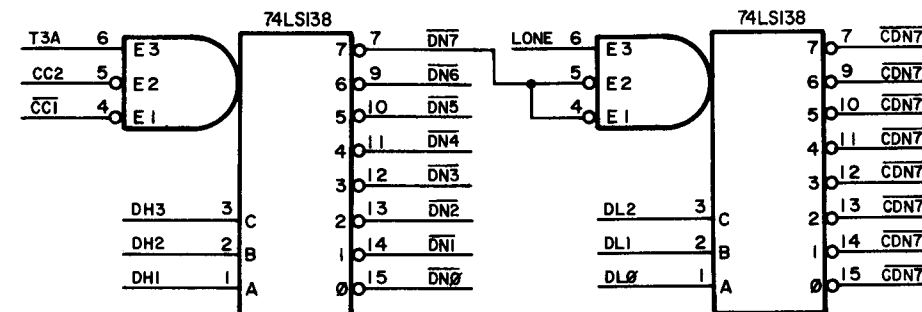


Figure 8.6.1--Input Strobe Decoder Provides Fifteen Input Ports

The circuit shown expands the number of 8008 input ports from eight to fifteen. Obviously the number can be expanded still further with this approach, with a hardware cost of one 3205 decoder for each seven new input instructions afforded. Bits other than the three low-order DL register bits may also be used.

Figure 8.6.2 shows 8008 software examples. The instruction pairs shown are used to create conditional input strobes.

```
LAI 007      GENERATE A . . .
INP 007      . . . . .CDN77 STROBE.

XRA         GENERATE A . . .
INP 007      . . . . .CDN70 STROBE.
```

Figure 8.6.2--Instruction Pairs Used in Expanding Input Ports

This approach is an interesting example of how the designer can make full use of the 8008 microprocessor by thoroughly understanding its internal processor operations. Consider what happens during memory cycle two (PCC cycle) of an input instruction. At PCC-T1 time, the content of the 8008's internal A register is outputted on the CPU bus and latched up in the external DL register. This data transfer

SEC. 8.6 EXPANDING 8008 INPUT PORTS WITH CONDITIONAL INPUTS (cont'd)

is not ordinarily of any importance in an *input* instruction, whose purpose is usually to select data from a designated input port, and transfer that information to the CPU's internal A register at PCC-T5 time. Luckily for the conditional input approach, the A register can be loaded with a conditional input address during the previous instruction.

It might be asked why the 8008 bothers to output the content of the A register during PCC-T1 time of an input instruction in the first place. Certainly this information is not normally needed outside the 8008 at this time. The principal reason is that it was easiest to design the microprocessor so that input and output instructions are as similar as possible. The transfer of the A to the DL register is an essential part of an *output* instruction (Chapters 7 and 9).

SEC. 8.7 ADDITIONAL INPUT PORTS DEFINED AS MEMORY

Input ports may be added to a microcomputer simply by defining certain memory locations as inputs. This is an important technique in systems using the 8008 microprocessor, which has only eight regular input instructions.

An input port can be added using the technique shown in Figure 8.7.1. At left is a circuit showing a 1702A 256 x 8 PROM with its eight address bit terminals connected to the microcomputer's DL register. The active low chip enable terminal is connected to a memory select signal--PAG77--which enables the chip when it is addressed during memory read cycles. The outputs of the memory chip are connected to the microprocessor input bus.

At right a four-bit three-state buffer replaces the memory chip. It can be expanded to a full eight-bit input port by adding another 74125. The new 74S241, an eight-bit buffer, may also be specified (Schottky clamping; Schmitt-trigger inputs; 20-pin, 0.3" *Skinny-DIP* package).

This kind of input port is not addressed with an input instruction like a normal input, but with a memory-reading instruction. In an 8008-based microcomputer, this would mean an LrM instruction. The input port designation would not be included in the binary-encoded instruction, as with input instructions. Instead, the appropriate memory location must be set up in the H register before executing the memory-reading instruction.



SEC. 8.7 ADDITIONAL INPUT PORTS DEFINED AS MEMORY (cont'd)

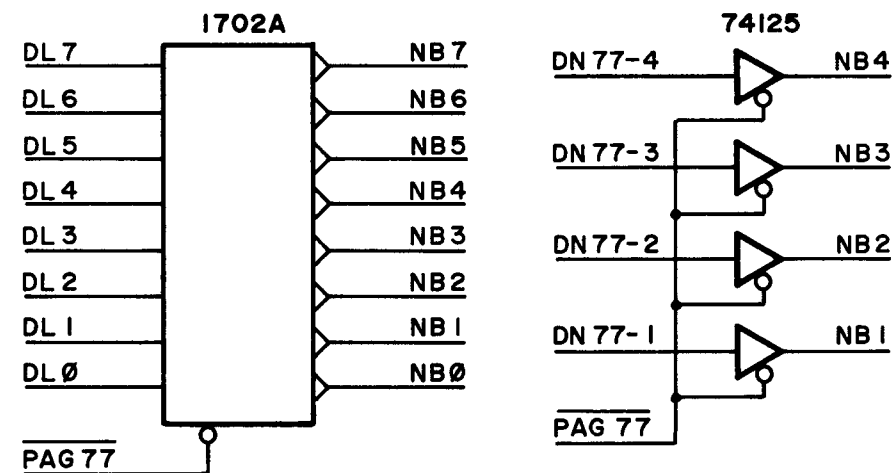


Figure 8.7.1--The Memory at Left Replaced by Three-State Buffer "Input Port" at Right

In the example shown, the H register is loaded with 077 (PAGE 77), an LrM instruction is executed, and the four bits (DN77-4 through DN77-1) are read into register *r*. The disadvantage of this input port technique is that it requires the use of a high-order memory address. An advantage is that the input information may be read into any internal register--not only the A register, as with input instructions, but the B, C, D, E, H, or L registers.

The memory-mapped I/O technique is applicable to nearly all microprocessors, with variations as to connections and software. Schematics, circuit descriptions, and typical software for the 8080 are presented in the 471 data sheet, near the end of this book (Sec. 1.6).



This chapter begins with a section devoted to 8008 output signals. Starting with Sec. 9.2, a number of output techniques are discussed which are applicable in any microcomputer. Sec. 9.4 discusses variations applicable to microcomputers based on the 8080.

SEC. 9.1 8008 OUTPUTS

Chapter 7 outlines the similarity in internal processor operations between the 8008's eight input instructions and 24 output instructions. From the point of view of this section, on 8008 outputs, it may be said that the 8008 has 32 output instructions, eight of which also perform the input function.

During memory cycle two of an output instruction, the $\overline{ST2}$ strobe will load CC2 with zero, and CC1 with a logic one. This bit combination defines an I/O operation. This chapter refers to all 32 I/O instructions as *outputs*: the first eight as *input/outputs*, and the last 24 as *output-only* instructions (see Figure 9.1.1). Therefore, when CC2 = 0 and CC1 = 1 (defining a PCC cycle), it *always* indicates that an *output* instruction is being performed.

Recalling from Chapter 7: input/output and output-only instructions are identical in their first five states. At T1 time of memory cycle *two* (PCC cycle), the contents of the A register are latched up in the external DL register. At T2 time the instruction itself is latched up in the DH register. In *input/output* instructions, T3, T4, and T5 times are used to input the data from the input port to the CPU's internal A register.

During memory cycle two of an *output-only* instruction, T4 and T5 times are omitted. T3 time is *not* used to input information into the CPU, as with input/output and many other instructions. T3 time is an idle state within the CPU, which effectively waits for hardware/external to the CPU to take the output data which has been stored in the DL register, back at T1 time, and load it into an output port.

A typical microcomputer output port would be an eight-bit latch, the data inputs of which are connected to the appropriate bits of the DL register. The eight output bits of the DL register are connected to the data inputs of all the microcomputer's output ports, and as such constitute an *output bus* (as defined in Chapter 6). Each output port latches up the information on the output bus only when it is strobed at T3 time, memory cycle two, of the appropriate output instruction.

For the sake of convenience, the T3A signal is generally used to produce output strobes. The T3A signal is developed in 8008 microcomputer primarily to produce *input enable* signals. T3A begins late in T2 time, before T3 proper begins. This is because, during *input/output* instructions, one desires to put the input data onto the CPU data bus for a short period before the CPU begins to input data at T3 time, to be sure that the input data has time to settle on the data bus.

SEC. 9.1 8008 OUTPUTS (cont'd)

| INSTRUCTION BINARY | INSTRUCTION OCTAL | INSTRUCTION MNEMONIC | INPUT ENABLE | OUTPUT STROBE | DESCRIPTION | ALTERNATE DESCRIPTION |
|-----------------------|----------------------|-------------------------|-----------------|------------------|--------------|--------------------------|
| 01111111 | 177 | OUT 037 | (NA) | <u>DT37</u> | OUTPUT-ONLY | OUTPUT |
| 01111101 | 175 | OUT 036 | (NA) | <u>DT36</u> | OUTPUT-ONLY | OUTPUT |
| 01111011 | 173 | OUT 035 | (NA) | <u>DT35</u> | OUTPUT-ONLY | OUTPUT |
| 01111001 | 171 | OUT 034 | (NA) | <u>DT34</u> | OUTPUT-ONLY | OUTPUT |
| 01110111 | 167 | OUT 033 | (NA) | <u>DT33</u> | OUTPUT-ONLY | OUTPUT |
| 01110101 | 165 | OUT 032 | (NA) | <u>DT32</u> | OUTPUT-ONLY | OUTPUT |
| 01110011 | 163 | OUT 031 | (NA) | <u>DT31</u> | OUTPUT-ONLY | OUTPUT |
| 01110001 | 161 | OUT 030 | (NA) | <u>DT30</u> | OUTPUT-ONLY | OUTPUT |
| 01101111 | 157 | OUT 027 | (NA) | <u>DT27</u> | OUTPUT-ONLY | OUTPUT |
| 01101101 | 155 | OUT 026 | (NA) | <u>DT26</u> | OUTPUT-ONLY | OUTPUT |
| 01101011 | 153 | OUT 025 | (NA) | <u>DT25</u> | OUTPUT-ONLY | OUTPUT |
| 01101001 | 151 | OUT 024 | (NA) | <u>DT24</u> | OUTPUT-ONLY | OUTPUT |
| 01100111 | 147 | OUT 023 | (NA) | <u>DT23</u> | OUTPUT-ONLY | OUTPUT |
| 01100101 | 145 | OUT 022 | (NA) | <u>DT22</u> | OUTPUT-ONLY | OUTPUT |
| 01100011 | 143 | OUT 021 | (NA) | <u>DT21</u> | OUTPUT-ONLY | OUTPUT |
| 01100001 | 141 | OUT 020 | (NA) | <u>DT20</u> | OUTPUT-ONLY | OUTPUT |
| 01011111 | 137 | OUT 017 | (NA) | <u>DT17</u> | OUTPUT-ONLY | OUTPUT |
| 01011101 | 135 | OUT 016 | (NA) | <u>DT16</u> | OUTPUT-ONLY | OUTPUT |
| 01011011 | 133 | OUT 015 | (NA) | <u>DT15</u> | OUTPUT-ONLY | OUTPUT |
| 01011001 | 131 | OUT 014 | (NA) | <u>DT14</u> | OUTPUT-ONLY | OUTPUT |
| 01010111 | 127 | OUT 013 | (NA) | <u>DT13</u> | OUTPUT-ONLY | OUTPUT |
| 01010101 | 125 | OUT 012 | (NA) | <u>DT12</u> | OUTPUT-ONLY | OUTPUT |
| 01010011 | 123 | OUT 011 | (NA) | <u>DT11</u> | OUTPUT-ONLY | OUTPUT |
| 01010001 | 121 | OUT 010 | (NA) | <u>DT10</u> | OUTPUT-ONLY | OUTPUT |
| 01001111 | 117 | INP 007 | <u>DN7</u> | <u>DN7</u> | INPUT/OUTPUT | OUTPUT |
| 01001101 | 115 | INP 006 | <u>DN6</u> | <u>DN6</u> | INPUT/OUTPUT | OUTPUT |
| 01001011 | 113 | INP 005 | <u>DN5</u> | <u>DN5</u> | INPUT/OUTPUT | OUTPUT |
| 01001001 | 111 | INP 004 | <u>DN4</u> | <u>DN4</u> | INPUT/OUTPUT | OUTPUT |
| 01000111 | 107 | INP 003 | <u>DN3</u> | <u>DN3</u> | INPUT/OUTPUT | OUTPUT |
| 01000101 | 105 | INP 002 | <u>DN2</u> | <u>DN2</u> | INPUT/OUTPUT | OUTPUT |
| 01000011 | 103 | INP 001 | <u>DN1</u> | <u>DN1</u> | INPUT/OUTPUT | OUTPUT |
| 01000001 | 101 | INP 000 | <u>DN0</u> | <u>DN0</u> | INPUT/OUTPUT | OUTPUT |

NOTE: See the 471 data sheet, Sec. 1.6, for the equivalent 8080 instructions.

Fig. 9.1.1--8008 I/O Instructions, with Associated Strokes and Enable Signals, and Descriptions

SEC. 9.1 8008 OUTPUTS (cont'd)

Chapter 7 describes how \overline{DNX} and \overline{DTY} signals are produced at T3A time, for use as strobe/enable signals. When used to load information from the output bus into an output port, these signals are functioning as *strokes*, following the nomenclature of this book.

This method of generating strokes makes it possible to realize a number of kinds of output hardware with ease. The following sections show a number of techniques for generating both levels and pulses. They all are based on the principle that output data is derived from the output bus (DL register), and is valid when the \overline{DN} or \overline{DT} strobe goes low, signifying execution of the appropriate output instruction.

 


Fig. 9.1.2 Showing the DL (Output) Bus.

SEC. 9.2 PULSE OUTPUTS

9.2.1 *Using the Strobes* Figure 9.2.1 shows the simplest possible pulse output. It consists simply of one of the output strobes. Up to 32 such outputs may be provided in an 8008 microcomputer, and they are so simple that they are often forgotten.



Fig. 9.2.1--Very Simple Pulse Output

The pulse width of this output is 2.0 μ s for an 8008 running at its normal speed (500 KHz symmetrical clock); 1.25 μ s for an 8008-1 (800 KHz); and 500 ns for an 8080 (2.0 MHz clock cycle). This output technique is inexpensive in hardware, but costs a whole output instruction for only one pulse. It is useful in an 8080 system, where there are usually plenty of I/O ports, and in an 8008 system where there are sufficient I/O ports.

The four examples in Figure 9.2.2 show pulses which are controlled by one of the output bits. The pulses in Parts (a) and (b), for example, occur during an *Output 15* instruction, only when the high-order data bit being outputted is *low*. Up to eight independent pulse outputs may be driven with one particular output strobe.

9.2.2 *Conditional Output Pulses* A conditional output is one where the particular output, either pulse or latch, depends on *more than one* of the DL register bits. An *addressable output* is one which uses a decoder to provide more than one conditional output. The circuit of Figure 9.2.3 is conditional because the enable inputs of the 3205 are connected to DL4 and DL3. It is also addressable because the decoder address inputs are connected to DL2, DL1, and DL0.

SEC. 9.2 PULSE OUTPUTS (cont'd)

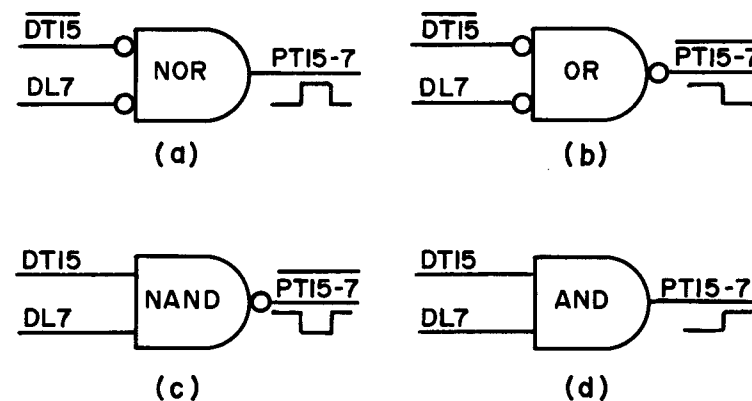


Fig. 9.2.2--Pulse Outputs Using Gates

 


Fig. 9.2.3--Conditional Pulse Outputs

SEC. 9.2 PULSE OUTPUTS (cont'd)

Eight distinct pulse outputs are provided by one IC in Figure 9.2.3. A pulse may be generated by an *Output 15* instruction, but only when the output word contains a particular two-bit combination: $DT15-4 = 0$, $DT15-3 = 1$. Only one of the eight pulses occurs, as selected by the three low order bits of the output word. Thus, in an 8008 microcomputer, the instruction sequence *LAI 013*, *OUT 15* would cause a $\overline{PCT15-3}$ pulse.

9.2.3 Modified Pulse Widths Pulses longer or shorter than the available output strobe signal may be obtained by using one-shot multivibrators such as the 74123 (or 26123 for more accuracy). Notice, in Figure 9.2.4, how conveniently the inverting A input may be connected to the output strobe, and the non-inverting B input to a particular bit on the output bus (DL register). In the example shown, an output pulse will occur only if the sign bit of the A register is set when an *OUT 013* instruction is executed. (In other words, $DT13-7 = 1$.) The RESET input may be connected to MR, from the microcomputer master reset circuitry, or it might be connected to a negative-going pulse output. If a 74221 dual one-shot is used, it cannot be retrigged once fired by a previous output pulse, unless reset.

 


Fig. 9.2.4--Other Pulse Widths Generated With a One-Shot



microcomputer
design

SEC. 9.3 LATCHING OUTPUTS (cont'd)

9.3.1 Latching Registers It is often desirable to have an output port *latch up* the data it receives when strobed, and to store the output data until it receives another output command. Figure 9.3.1 shows D-type latches, such as the 7475, being used for this kind of output-with-memory. Since the 7475 has two strobe connections, it can function (as shown) as a dual two-bit output port. The uppermost two latches are controlled by the *Output 15* strobe, bits 7 and 6. Both true and inverting outputs are presented. The two lower latches are strobed during an INP 2 instruction. Here an *input/output* instruction is being used as an output instruction--that is, an *OUT 002* instruction.

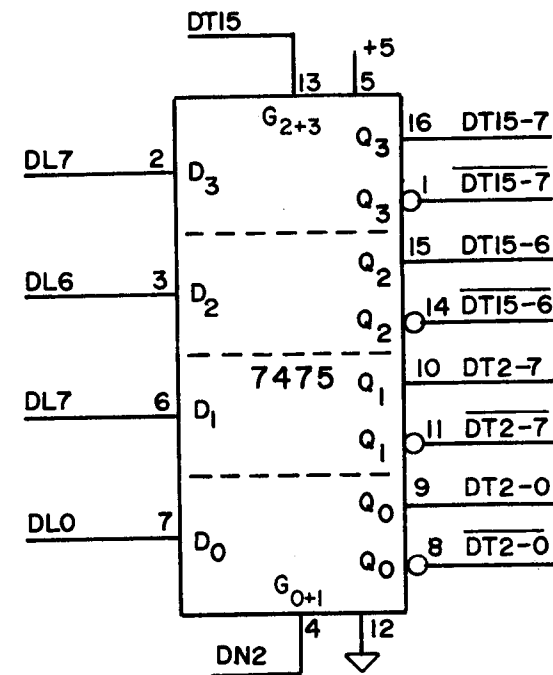


Fig. 9.3.1--Four Latched Output Bits

Of course, the DL and DH registers themselves are examples of this kind of latching circuitry. These registers, however, receive their input data directly from the CPU data bus, at T1 and T2 times respectively, while output latches receive data from the DL register at T3A time.



microcomputer
design

SEC. 9.3 LATCHING OUTPUTS (cont'd)

9.3.2. *Conditional Latches* The conditional output approach can be applied to output latches, as shown in Figure 9.3.2. Here, the value stored in one of the four latches can be changed by an OUT 035 instruction, only when the two high-order bits of the A register are zero. This may be considered a simple output multiplexing circuit. Note that the output bits are labeled as conditional outputs, CT035-5, etc. The four latches are cleared to zero by an OUT 010 instruction. In this circuit, the three-state capabilities of the 74173 are not used.

 


Fig. 9.3.2--Four Conditional Output Latches

9.3.3 *Addressable Latches* A form of conditional latch, the 9334 addressable latch in Figure 9.3.3 drives eight current-limited light-emitting diodes (LEDs). The states of the three low-order bits of the A register, before executing an OUT 021 instruction, define which lamp is to be addressed. The next higher-order bit defines whether the lamp is to be turned on or off (0 = on, 1 = off). Thus the instruction sequence LAI 013, OUT 021 would cause output CT21-3 to go high, turning on the associated lamp. LAI 001, OUT 021 would turn lamp CT21-1 on.

SEC. 9.3 LATCHING OUTPUTS (cont'd)

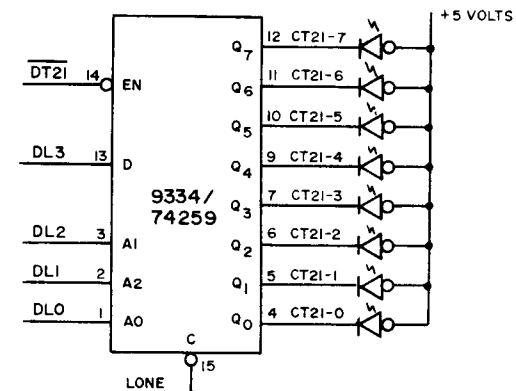


Fig. 9.3.3--Addressable Latch Controlling Current-Limited LEDs

The addressable latch concept is useful for driving outputs other than LEDs, of course.

9.3.4 *Lamp-Driver Latches* The circuit of Figure 9.3.4 uses an integrated circuit designed specifically for driving LEDs. The DM8559 has a pin for adjusting the current to the LEDs.

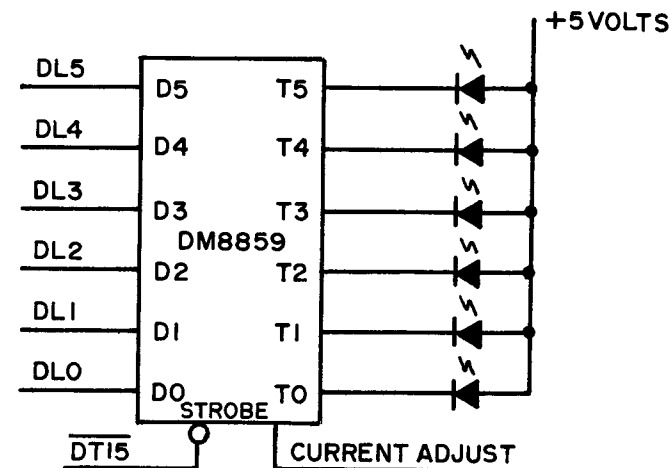


Fig. 9.3.4--LED Driver-Latch IC as an Output Port



SEC. 9.3 LATCHING OUTPUTS (cont'd)

Chapter 19 contains an extended discussion of digital displays.

9.3.5 *Flip-Flop Latches* An ordinary D-type flip-flop provides the simplest one-bit latch. As shown in Figure 9.3.5, one half of a 7474 connects to an output strobe and to a DL bit to provide a single output bit and its complement.

 


Fig. 9.3.5--A D-Type Flip-Flop Provides One-Bit Latch

Hex or octal D-type flip-flops may be connected to provide many output bits with one IC. The circuit shown in Figure 9.3.6 shows a 74174 hex D flip-flop, which provides six output bits. The reset line on the flip-flop may be connected to MASTER RESET NOT (MR) so that all outputs will reset to zero during power-on initialization. A 74273 octal D flip-flop would provide eight output bits.

 


Fig. 9.3.6--Hex Flip-Flop Provides Six Output Bits

9.3.6 *Alternate-Action Flip-Flops* Various special output functions may be provided by using simple flip-flops and gates. One example is shown in Figure 9.3.7. This flip-flop

SEC. 9.3 LATCHING OUTPUTS (cont'd)

changes state every time the sign (high-order) bit is set to one during an OUT 015 instruction. If the sign bit is zero, the flip-flop will not toggle.

 


Fig. 9.3.7--Alternate-Action Flip-Flop

SEC. 9.4 8080 OUTPUTS

The output examples earlier in this chapter have been based on the 8008 microprocessor. However, the techniques presented--pulse outputs, conditional pulses, latched registers, and so forth--are equally applicable to the 8080 (or to any other microprocessor).

As explained in Chapter 7, the 8008 is unusual in that output data is presented on the low-order address bus, DL7-DL0, rather than on the data bus. Thus, if the standard 8080 instruction mode is used--INPUT and OUTPUT instructions, creating the IOR and IOW strobe/enable signals--output data appears on the data bus. The connections shown in the diagrams in this chapter must then be modified. DB7 (data bus, bit 7) should replace DL7 (low-order address bus, bit 7); DB6 replaces DL6; and so forth.

The 8008-compatible I/O mode may nevertheless be useful in an 8080 system. This is true not only when compatibility with earlier 8008-based machines is necessary, but also to take advantage of combined I/O techniques (Ch. 10).



MICROPROCESSOR LIBRARY

SEC. 9.5 16-BIT OUTPUT PORTS FOR THE 8080

Though an eight-bit output word usually suffices, some micro-computer applications require a larger word length. For example, precision digital-to-analog converters often require a resolution better than eight bits (one part in 256: see Ch. 22 for representative eight-bit circuitry). Ten or 12 bits are typically required. Since DAC circuitry usually requires parallel input data, with all input data available simultaneously during conversion, two output instructions would be required if only eight-bit output data were available, with the complete data word becoming available only after a second output instruction.

Though the 8080 is an eight-bit microprocessor, it is capable of outputting 16-bit data. See Figure 9.5.1.

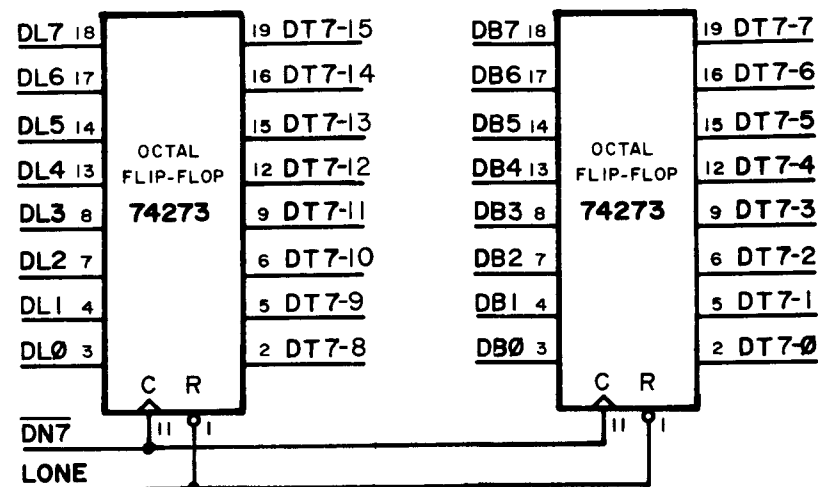


Fig. 9.5.1--16-Bit Output Port for 8080

SEC. 9.5 16-BIT OUTPUT PORTS FOR THE 8080 (cont'd)

The normal 8080 output instruction might be said to waste eight bits of output data. The output data itself appears on the data bus, and the output port number appears redundantly on both the DH and DL address lines. In Fig. 9.5.1, the low-order address bus (DL7-DL0) is used for eight bits of output data, and the data bus (DB7-DB0) is used for another eight bits.

A memory write instruction is used to output to the 16-bit output port. Assume the instruction to be MOV M,B (move to memory the contents of the B register). The L register--normally a low-order memory address--contains the eight high-order output bits. The B register contains the eight low-order output bits. The H register--a memory page address--is decoded by external circuitry to produce a suitable output strobe signal--here, DN7. 16 bits of output data appear in Output Port 7.

A convenient way of producing DN7 is to use DIN--essentially a predecoded strobe signal, addressing up to 32 I/O ports with memory-mapped instructions. (See the data sheet for the 471 CPU board, Sec. 1.6.4, near the end of this book.)

Alternately, the port address and high-order output data can be set up in the BC register pair, with the low-order output data in the A register. Then a STAX B instruction would produce the 16-bit output.

Notice that all 16 output bits become valid at the same time. This could prove important in a DAC (digital-to-analog converter) application. If the data were outputted to the DAC in two stages--eight bits at a time--the DAC would create an extraneous intermediate output voltage after the first byte had arrived. Of course, extra hardware could be added to delay data transfers to the DAC until the second output byte arrived--but this is unnecessary when the circuit in Fig. 9.5.1 is used.

Another way of creating a 16-bit output port is through straight memory-mapped I/O. Two memory locations, 012345 and 012346, serve as memory-mapped output ports. The 8080 instruction SHLD 012345 would output the data stored in the H and L registers to these two locations. The L register value would move to the I/O port at location 012345 during one memory cycle, and the H register value to location 012346 during a subsequent memory cycle. This technique--essentially a 6800-mode output instruction--works with the 8080, but differs from the technique described above (Fig. 9.5.1) in that the 16 bits do not appear simultaneously.



microcomputer
design



microcomputer
design

SEC. 10.1 COMBINED INPUT/OUTPUT TECHNIQUES

With the 8008 microprocessor, every input instruction is also an output instruction--as discussed in Chapters 7 and 9 above. Advantage may be taken of this fact by adding certain features to the microcomputer. The basic principle, with the 8008, is that during the PCC cycle of an input instruction, data flows both into and out of the CPU.

8008-compatible combined input/output instructions may be added to an 8080 CPU board. (See the 471 data sheet near the end of this book, 1.6.)

SEC. 10.2 TABLE LOOKUPS

One combined I/O technique involves *table lookups*. The microcomputer outputs a digital value, then inputs a new digital word which corresponds to some desired function of the original word. In a sense, the microcomputer is looking up the answer in a numerical table. The first of the following two subsections describes how a table lookup program would normally be written for an 8008 microprocessor. The second describes how the same function could be performed more efficiently using a combined I/O technique.

10.2.1 Table Lookup with 8008 Program A table containing the squares of the integers 0 through 5 is shown in Figure 10.2.1. The *LOCATION* column corresponds to an address in the microcomputer's read-only memory (ROM). The *CONTENTS* column shows the digital value stored at that location (in octal). If the 8008's H and L registers are loaded with a number between 000000 and 000006, and an LAM instruction is executed (Load A from Memory), the A register will then contain the square of the number.

| LOCATION Split Octal | CONTENTS in Octal | CONTENTS Decimal |
|-------------------------|----------------------|---------------------|
| 000000 | 000 | 0 |
| 000001 | 001 | 1 |
| 000002 | 004 | 4 |
| 000003 | 011 | 9 |
| 000004 | 020 | 16 |
| 000005 | 031 | 25 |
| 000006 | 044 | 36 |

Fig. 10.2.1--Table of Integer Squares Stored in Memory

SEC. 10.2 TABLE LOOKUPS (cont'd)

If the number to be squared was originally in the A register, then the program shown in Fig. 10.2.2 will convert this number to its square. (8008 mnemonics are shown.)

```

---      NUMBER IS IN A REGISTER.
LHI 000  POINT TOWARDS TABLE START.
LLA     POINT TOWARDS TABLE ENTRY.
LAM     LOAD SQUARE OF NUMBER.

```

Fig. 10.2.2--Program for Squaring a Number with a Lookup Table

The procedure used here to perform squaring can also be used to find the sine, cosine, or any trigonometric, algebraic, or arbitrary function of an eight-bit variable. A 256-byte lookup table is convenient for many desired functions because the variable to be looked up may be placed in the CPU's L register, and the page number of the lookup table in the H register. Thus any convenient page in memory may be used, with the table values stored in PROM or ROM. Usually the H register is not used in referring to the variable itself, but addresses the lookup table in the same manner that other pages of memory are addressed. Of course, the lookup table is usually located at some other page number than 000--so the table of numbers shown in Figure 10.2.1 would more likely start at location 020000, and the LHI 000 instruction in Figure 10.2.2 would be replaced with LHI 020.

10.2.2 Table Lookup Using a Combined I/O Technique The 256-byte table lookup program discussed above could instead be implemented using a combined I/O technique. Figure 10.2.3 shows a 256-byte PROM--the same memory element that could have been used in the above subsection--as an input/output port. This configuration, called the *Table Lookup option*, requires little or no additional hardware in PROM-configured systems.

In an 8080 system, it makes more sense to address the lookup table as a page in memory. This is because several instructions must be used to address an 8008-compatible combined I/O port with an 8080, and the advantages of this technique are lost. (For the programming required, see the 471 data sheet, Sec. 1.6.) Though 8008-compatible combined I/O instructions make sense for the 8080 in some applications, they are impractical for table lookups.

SEC. 10.2 TABLE LOOKUPS (cont'd)

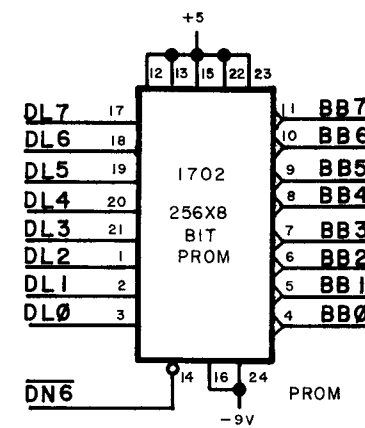


Fig. 10.2.3--Table Lookup Option: PROM Functions as I/O Port

With the 8008 CPU, addressing a table lookup with a combined I/O instruction produces a savings in programming. Only one instruction is required to transform the contents of the A register, instead of the three required when addressing the table lookup as memory (Figure 10.2.2). For the circuit shown in Figure 10.2.3, that one instruction is INP 006. During PCC-T1 time, the contents of the A register go out on the CPU bus and are latched up in the DL register. The DL register addresses the 1702 PROM. Then, during PCC-T3A time, the DN6 input enable pulse reads the contents at the selected table address back into the A register. Thus, when the input instruction is complete, the A register contains a new data word which corresponds to the desired function of the old A register.

Not only are two instructions saved, but there has been no need to disturb the H and L registers. Since these are the only two 8008 registers addressing memory, this enhances programming flexibility.

10.2.3 Four Table Lookups with an 8 K ROM The *Table Lookup option* may be applied to large ROMs as well. For example, in Figure 10.2.4, a 1024 x 8 ROM is used to perform four table lookups. The four pages (each 256 x 8) within the PROM cannot be enabled separately through the 8308's two chip enable terminals (CE1 and CE2), so a different addressing scheme is devised.

SEC. 10.2 TABLE LOOKUPS (cont'd)

This section applies to the addition of an 8308 to an 8008 system. To begin with, DH0 is always high during input instructions, and so cannot be used to distinguish table lookup pages from one another. Second, since OUTPUT instructions ignore any data that is on the 8008 data bus during PCC-T3A time (that is, DIN time), it is unnecessary to distinguish between input and output instruction modes in this circuit. Since the only purpose of using DH5 or DH4 in addressing the PROM would be to make this distinction, they too are unused. If it should happen that an output instruction is executed whose instruction code looks just like one of the four table lookup input instructions--except for DH5 and DH4--one of the 8308's stored data words will be addressed; the 8308 will be enabled with $\overline{\text{DIN}}$; and the table lookup value will be impressed onto the BB bus. But the CPU is simply not listening.

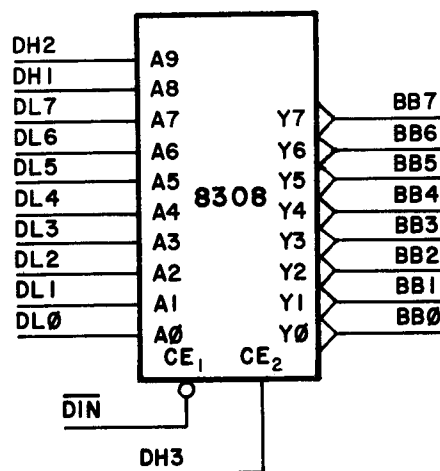


Fig. 10.2.4--A Single 8 K ROM Chip Serves as Four-Page Table Lookup

The DH3 bit connects to the noninverting chip enable terminal of the 8 K ROM. This prevents the chip from being activated during input instructions 3 through 0. Therefore, the circuit of Figure 10.2.4 provides four table lookups, activated by INP 007, INP 006, INP 005, and INP 004. The circuit is quite simple and requires only one integrated circuit.



SEC. 10.2 TABLE LOOKUPS (cont'd)

10.2.4 *Trigonometric Tables* In the following example, a lookup table allows a microcomputer to find the sine of an angle, by addressing a 256-location PROM.

Only the sines of angles between 0° and 90° are stored in the table. Values in the other three trigonometric quadrants (90° - 360°) may be readily calculated from the first quadrant values. And since $\sin(90^\circ - \theta) = \cos \theta$, the cosine function is also easily derived with a few added instructions.

Both the number representing the angle, and the value of the sine function, are limited to eight bits in this example. The address bits of the PROM must be weighted such that the octal numbers 000 to 377 correspond to angles between 0° and 90° . Figure 10.2.5 shows a typical scheme.

| Address bit | A7 | A6 | A5 | A4 | A3 | A2 | A1 | A0 |
|------------------|----------------------|----------------------|----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|
| Weighting factor | $\frac{90^\circ}{2}$ | $\frac{90^\circ}{4}$ | $\frac{90^\circ}{8}$ | $\frac{90^\circ}{16}$ | $\frac{90^\circ}{32}$ | $\frac{90^\circ}{64}$ | $\frac{90^\circ}{128}$ | $\frac{90^\circ}{256}$ |

Fig. 10.2.5--Weighting Factors for Address Bits of Sine Function Lookup Table

The range of the values of the sine function is from zero to one. The usual scheme allows all eight bits in the table to represent a binary fraction, with the *binary point* to the left of the high-order bit. This provides possible sine values between 0 and $255/256$ (*decimal*). Figure 10.2.6 shows the weighting of each data bit which provides for this range of values.

| Data bit | D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 |
|------------------|---------------|---------------|---------------|----------------|----------------|----------------|-----------------|-----------------|
| Weighting factor | $\frac{1}{2}$ | $\frac{1}{4}$ | $\frac{1}{8}$ | $\frac{1}{16}$ | $\frac{1}{32}$ | $\frac{1}{64}$ | $\frac{1}{128}$ | $\frac{1}{256}$ |

Fig. 10.2.6--Weighting of Data Bits in Sine PROM

The PROM is then programmed to give the best match between angles and their sines. For example, say the PROM address is 01010101 , or 125 *octal*. This corresponds to an angle of $125/400$ *octal* of 90° , or 85/256 *decimal* of 90° , or about $29^\circ 53'$. The sine of this angle is 0.49849 *decimal* (from a trig table). This value is converted into a binary



SEC. 10.2 TABLE LOOKUPS (cont'd)

| A | sin | A | sin | A | sin | A | sin | A | sin | A | sin |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|------|
| 000 | 000 | 053 | 103 | 126 | 201 | 201 | 266 | 254 | 337 | 327 | 370 |
| 001 | 002 | 054 | 104 | 127 | 202 | 202 | 267 | 255 | 340 | 330 | 370 |
| 002 | 003 | 055 | 106 | 130 | 204 | 203 | 270 | 256 | 340 | 331 | 371 |
| 003 | 005 | 056 | 107 | 131 | 205 | 204 | 271 | 257 | 341 | 332 | 371 |
| 004 | 006 | 057 | 111 | 132 | 206 | 205 | 272 | 260 | 342 | 333 | 371 |
| 005 | 010 | 060 | 112 | 133 | 210 | 206 | 274 | 261 | 343 | 334 | 372 |
| 006 | 012 | 061 | 114 | 134 | 211 | 207 | 275 | 262 | 343 | 335 | 372 |
| 007 | 013 | 062 | 115 | 135 | 212 | 210 | 276 | 263 | 344 | 336 | 372 |
| 010 | 015 | 063 | 117 | 136 | 214 | 211 | 277 | 264 | 345 | 337 | 373 |
| 011 | 016 | 064 | 120 | 137 | 215 | 212 | 300 | 265 | 345 | 340 | 373 |
| 012 | 020 | 065 | 122 | 140 | 216 | 213 | 301 | 266 | 346 | 341 | 373 |
| 013 | 021 | 066 | 123 | 141 | 220 | 214 | 302 | 267 | 347 | 342 | 374 |
| 014 | 023 | 067 | 125 | 142 | 221 | 215 | 303 | 270 | 347 | 343 | 374 |
| 015 | 024 | 070 | 126 | 143 | 222 | 216 | 304 | 271 | 350 | 344 | 374 |
| 016 | 026 | 071 | 130 | 144 | 223 | 217 | 305 | 272 | 351 | 345 | 374 |
| 017 | 030 | 072 | 131 | 145 | 225 | 220 | 306 | 273 | 351 | 346 | 375 |
| 020 | 031 | 073 | 133 | 146 | 226 | 221 | 307 | 274 | 352 | 347 | 375 |
| 021 | 033 | 074 | 134 | 147 | 227 | 222 | 310 | 275 | 353 | 350 | 375 |
| 022 | 034 | 075 | 136 | 150 | 230 | 223 | 311 | 276 | 353 | 351 | 375 |
| 023 | 036 | 076 | 137 | 151 | 232 | 224 | 312 | 277 | 354 | 352 | 376 |
| 024 | 037 | 077 | 141 | 152 | 233 | 225 | 313 | 300 | 355 | 353 | 376 |
| 025 | 041 | 100 | 142 | 153 | 234 | 226 | 314 | 301 | 355 | 354 | 376 |
| 026 | 042 | 101 | 143 | 154 | 235 | 227 | 315 | 302 | 356 | 355 | 376 |
| 027 | 044 | 102 | 145 | 155 | 237 | 230 | 316 | 303 | 356 | 356 | 376 |
| 030 | 046 | 103 | 146 | 156 | 240 | 231 | 317 | 304 | 357 | 357 | 377 |
| 031 | 047 | 104 | 150 | 157 | 241 | 232 | 317 | 305 | 357 | 360 | 377 |
| 032 | 051 | 105 | 151 | 160 | 242 | 233 | 320 | 306 | 360 | 361 | 377 |
| 033 | 052 | 106 | 153 | 161 | 244 | 234 | 321 | 307 | 361 | 362 | 377 |
| 034 | 054 | 107 | 154 | 162 | 245 | 235 | 322 | 310 | 361 | 363 | 377 |
| 035 | 055 | 110 | 155 | 163 | 246 | 236 | 323 | 311 | 362 | 364 | 377 |
| 036 | 057 | 111 | 157 | 164 | 247 | 237 | 324 | 312 | 362 | 365 | 377 |
| 037 | 060 | 112 | 160 | 165 | 250 | 240 | 325 | 313 | 363 | 366 | 1000 |
| 040 | 062 | 113 | 162 | 166 | 252 | 241 | 326 | 314 | 363 | 367 | 1000 |
| 041 | 063 | 114 | 163 | 167 | 253 | 242 | 327 | 315 | 364 | 370 | 1000 |
| 042 | 065 | 115 | 165 | 170 | 254 | 243 | 327 | 316 | 364 | 371 | 1000 |
| 043 | 067 | 116 | 166 | 171 | 255 | 244 | 330 | 317 | 365 | 372 | 1000 |
| 044 | 070 | 117 | 167 | 172 | 256 | 245 | 331 | 320 | 365 | 373 | 1000 |
| 045 | 072 | 120 | 171 | 173 | 257 | 246 | 332 | 321 | 365 | 374 | 1000 |
| 046 | 073 | 121 | 172 | 174 | 261 | 247 | 333 | 322 | 366 | 375 | 1000 |
| 047 | 075 | 122 | 173 | 175 | 262 | 250 | 334 | 323 | 366 | 376 | 1000 |
| 050 | 076 | 123 | 175 | 176 | 263 | 251 | 334 | 324 | 367 | 377 | 1000 |
| 051 | 100 | 124 | 176 | 177 | 264 | 252 | 335 | 325 | 367 | 400 | 1000 |
| 052 | 101 | 125 | 200 | 200 | 265 | 253 | 336 | 326 | 370 | | |

Fig. 10.2.7--Sine Table



SEC. 10.2 TABLE LOOKUPS (cont'd)

fraction with a resolution of 1/256 decimal: $0.49849 \times 256 = 127.61+$. The approximation used is 128/256 decimal, or 0.400 octal. This sine value corresponds to a decimal value of 0.500, which is what would be expected for an angle of 30°. The error is minimal.

The accuracy of the sine value stored in the PROM, assuming that the desired angle is represented exactly by the eight address bits, is plus or minus one part in 512, or better than 0.2%. Assuming as the worst case that the error in representing any given angle with eight bits is additive with the maximum error in the sine table, the lookup table still gives an accuracy better than 0.4%. This is more than adequate for many applications encountered using eight-bit microcomputers.

SEC. 10.3 BYTE-SWAPPING

A Swap register is often a very convenient addition to an 8008 microcomputer. The Swap register permits the programmer to exchange, or swap, the contents of the A and S (Swap) registers with one instruction at any desired place in the program.

A Swap register is connected to input/output port number 5 in Figure 10.3.1. The content of this register is read during PCC-T3A time of an INP 005 instruction. Meanwhile the previous value of the A register has been saved in the DL register at PCC-T1 time. At the end of the PCC-T3A enable pulse, this old value of the A register is loaded into the S register.

 


Fig. 10.3.1--The Swap Register Connected as I/O Port #5



U.C. BERKELEY LIBRARY

SEC. 10.3 BYTE-SWAPPING (cont'd)

| CYCLE TYPE | DATA TRANSFER TIMING SIGNALS | | | | 8008 CPU REGISTERS | | | | | EXTERNAL REGISTERS | | | | |
|------------|------------------------------|-------------|------------|------------------|----------------------|----------------------|--------|--------|-------|---------------------|---------|-------------|--------|------------|
| | EXT. ENABLE | EXT. STROBE | CPU STROBE | CPU ENABLE | PC _L REG. | PC _H REG. | A REG. | b REG. | FLAGS | DATA BUS | DL REG. | DH+CC REGS. | S REG. | ROM OUTPUT |
| PCI | INITIAL CONDITIONS | | | | PC _L | | AX | | | | | | AY | |
| | | STI | | T1 | PC _L | | | | | PC _L | | | | |
| | | | | T2 | PC _L +1 | | | | | PC _H CCI | | | | |
| | | | | T3 | | PC _H CCI | | | | INP5 | | | | |
| | | | | T1 | | | AX | | | AX | | | | |
| | | | | T2 | | | | | | INP5 | | | | |
| | | | | T3 | | | | | | AY | | | | |
| | | | | T4 | | | | | | AX | | | | |
| | | | | T5 | | | | | | AY | | | | |
| | | | | FINAL CONDITIONS | | | | AY | | | | | | |

Fig. 10.3.2--The Byte-Swapping Instruction (INP 005) Being Executed

SEC. 10.3 BYTE-SWAPPING (cont'd)

The chart in Figure 10.3.2 shows in detail how the original contents of the A register (called AX) and the original contents of the S register (called AY) are exchanged with the INP 005 instructions.

The state transition diagram in Figure 10.3.3 shows in a more simplified form the data transfers which take place during an INP 005 instruction, using the Swap register. The order in which the data transfers take place is shown by the numbers in parentheses.

 


Fig. 10.3.3--State Transition Diagram for Swap Register

SEC. 10.4 ADDING A UART

In many communications applications, data is transmitted asynchronously. For example, a teletypewriter sends and receives characters with pauses of variable length between. On the other hand, the microprocessor is a highly synchronous device, employing a relatively complex clocking scheme and requiring interfacing devices to be synchronized with the CPU. And, in communications applications, it is often convenient to use only one data line--one pair of wires. Data is transmitted *serially*, with each data word marked off with START and STOP codes. The 8008/8080 microprocessors, again, are eight-bit *parallel* devices, processing data made up of eight-bit words.

The *Universal Asynchronous Receiver/Transmitter (UART)* is an extremely useful adjunct to a microcomputer because it interfaces the microprocessor to the serial data world. Since the UART is both an input device and an output device, it provides a specialized example of a combined I/O technique.



SEC. 10.4 ADDING A UART

The UART converts eight-bit microprocessor output words into data by loading the parallel data into a shift register, adding START and STOP codes at the beginning and end of each word. Then all the bits are shifted onto the transmit line at regularly-spaced intervals. Each word is totally self-contained, since it is marked off by its own START and STOP bits, and therefore it is possible to insert a pause of any desired length between words being transmitted. The UART on the other end of the line watches for another START bit, which synchronizes its own receiver clock for proper reception. The relation between two START bits in a stream of data need not be synchronous, because of the variable-length pause which can occur between words.

An example of the most common type of UART is shown in Figure 10.4.1. There are actually two related devices, with the same pinouts, designed for slightly different serial data characteristics: the 2502 and 2017. The device shown is able to transmit 1.5 stop bits with 5-bit data codes.

This UART is very easily interfaced with microprocessors because of its bus-structured design. Nearly all the output terminals are three-state, and may be connected to the CPU input bus (NB bus) directly or to a bi-directional data bus. (*Definitions: Chapter 6.*) The *TR OUT* terminal (serial data output) does not, however, employ three-state circuitry; it is the output to the transmission line, and may be connected directly to the TTL-compatible serial data input of a peripheral machine, such as a teletypewriter. The *TR EMPTY* (transmit register empty) flag also does not employ three-state outputs, so that it can be used to generate an interrupt in the microcomputer, or strobe more data from a FIFO register, without first enabling the control section's output circuitry at the *SF ENAB* (status flag) terminal.

In the schematic of Figure 10.4.1, the three-state outputs from the UART receiver (RD8 through RD1) are connected directly to the CPU BB bus. So also are the three-state outputs from the control section of the UART. These status flags are tested by the microprocessor to control the flow of serial data.

When an INP 003 instruction is executed by the microprocessor, the DN3 signal goes low during T3A time, and the status flags from the UART's control section are enabled onto the CPU data bus. The CPU places this information into its (internal) A register, as it does during any input instruction. The microcomputer tests this information and proceeds through its functions accordingly.

The INP 004 instruction reads the received data from the UART into the microprocessor data bus. It also resets the DATA Ready flag within the UART. To do this, the DN4 strobe line is connected to both the READ ENABLE and DATA READY RESET pins on the UART. This allows the microcomputer to receive an eight-bit byte of information and to acknowledge

SEC. 10.4 ADDING A UART (cont'd)

Note: when using the UART in an 8080 microcomputer, the input bits shown connected to the low-order address bus, DL7-DL0, may be connected to the data bus, DB7-DB0--depending on the I/O instruction mode being used. See Chapter 7.

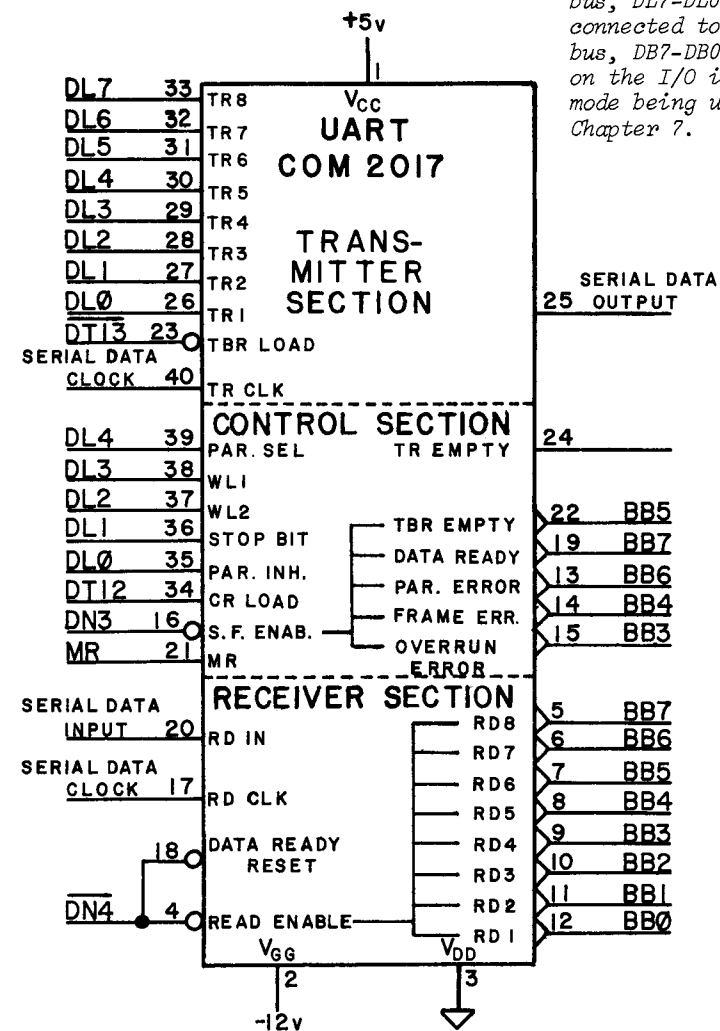


Fig. 10.4.1--UART Connects to Microcomputer

SEC. 10.4 ADDING A UART (cont'd)

reception to the UART--readying the UART for the next byte--with one simple input instruction. This design is an example of how a three-state bus-structured input device may be combined with the pulse output design discussed in Chapter 9.

The control word is loaded into the UART with an OUT 012 instruction. This control word defines the word length, parity, and length of stop bit. When the CPU has determined that the transmit buffer is empty (using an INP 003 instruction and testing bit 5), it may output another word to the transmit buffer using an OUT 013 instruction.

In this design, one LSI integrated circuit, two input instructions, and no further hardware are sufficient to provide an 8008-based microcomputer with asynchronous data communications capabilities. Note that this simple interface depends not only on the internal complexity of the LSI chips involved--the COM2017 and the microprocessor--but on the bus-structured input approach and the use of devices with three-state outputs.

The circuit shown in Figure 10.4.1 could be used with an 8080 microprocessor as well as with an 8008. However, the microprocessor lines which drive the UART would be changed: substitute B0 for DL0, B1 for DL1, etc.

The major intent of this section is to show how easily the UART may be connected to a microcomputer. For this reason we are not duplicating information which is readily available in the manufacturer's data sheet (SMS Microsystems Corp., 35 Marcus Blvd., Hauppauge, NY 11787). See also the data sheets for the 1602 and 1402 (Western Digital Corp., 19242 Red Hill Ave., Newport Beach, CA 92663); the TMS 6011 (Texas Instruments, PO Box 5012, Dallas, TX 75222); AY-S-1013 (General Instrument Corp., 600 W. John St., Hicksville, NY 11802).

SEC. 11.1 ADDING INSTRUCTIONS TO THE 8008

A number of 8008 instructions are not used in normal programming. With some external hardware, they may be used to perform new instructions. These include the undefined instructions and the self-transfer instructions, as shown in Figure 11.1.1.

| <u>OCTAL CODE</u> | <u>MNEMONIC</u> | <u>COMMENT</u> |
|-------------------|-------------------|----------------|
| 042 | <i>Undefined.</i> | NO OPERATION. |
| 052 | " | " |
| 062 | " | " |
| 070 | " | " |
| 071 | " | " |
| 072 | " | " |
| 300 | LAA | NO OPERATION. |
| 311 | LBB | " |
| 322 | LCC | " |
| 333 | LDD | " |
| 344 | LEE | " |
| 355 | LHH | " |
| 366 | LLL | " |

Fig. 11.1.1--Various 8008 NOP Instructions

These 8008 instructions have in common the fact that their execution leaves all flags and registers unchanged--except for the program counters (PCH and PCL registers), which increment one location as usual.

In addition, the 8008 has many instructions for which there are more than one *opcode* (instruction code). Usually only one of these opcodes is ever used for the designated function. Figure 11.1.2 shows these codes.

It should be added parenthetically that the 8080 chip designers have already used the extra codes which were left over on the 8008, and are shown in Figure 11.1.2. There are no redundant opcodes for the JMP, CAL, or RET instructions in the 8080 instruction set. By reducing redundancy, and by making input/output instructions into two-byte codes, room has been made for a number of extra 8080 instructions. (See Chapter 3.)



SEC. 11.1 ADDING INSTRUCTIONS TO THE 8008 (cont'd)

| OCTAL CODE | MNEMONIC | COMMENT |
|------------|----------|--------------------|
| 104 | JMP | USUAL CODE. |
| 114 | JMP | NOT NORMALLY USED. |
| 124 | JMP | " " " |
| 134 | JMP | " " " |
| 144 | JMP | " " " |
| 154 | JMP | " " " |
| 164 | JMP | " " " |
| 174 | JMP | " " " |
| 106 | CAL | USUAL CODE. |
| 116 | CAL | NOT NORMALLY USED. |
| 126 | CAL | " " " |
| 136 | CAL | " " " |
| 146 | CAL | " " " |
| 156 | CAL | " " " |
| 166 | CAL | " " " |
| 176 | CAL | " " " |
| 007 | RET | USUAL CODE. |
| 017 | RET | NOT NORMALLY USED. |
| 027 | RET | " " " |
| 037 | RET | " " " |
| 047 | RET | " " " |
| 057 | RET | " " " |
| 067 | RET | " " " |
| 077 | RET | " " " |
| 000 | HLT | OFTEN USED. |
| 001 | HLT | NOT NORMALLY USED. |
| 377 | HLT | OFTEN USED. |

Figure 11.1.2--Additional Unused Instructions

The basic technique for adding instructions to an 8008 microcomputer is to decode the execution of these normally unused instructions, and to use additional hardware to implement the desired operation.



SEC. 11.2 OUTPUT ANY REGISTER

An interesting way to put the 8008's normally unused instructions to work is to use them to output any index register with one instruction. When a self-transfer instruction is executed--LAA, LBB, etc.--the contents of that index register will appear at a specially designated output port.

The key to the *Output-Any-Register Option* is to use a four- or five-bit comparator IC to decode the instruction. Figure 11.2.1 shows a 93L24 five-bit comparator connected to the output bus of an 8008 microprocessor. Its output at pin 14 goes high only during an instruction fetch cycle (when PCI is low) and only when the following equations are valid: $D7 = D6 = 1$. $D5 = D2$; $D4 = D1$; $D3 = D0$. The first equation implies that the instruction's octal code begins with a 3. The following series of three equations means that the second and third digits of the instruction's octal code are the same. This will be seen to define the seven self-transfer instructions, LAA through LLL (see Figure 11.1.1 above).

At PCI-T3 time of a self-transfer instruction, when the instruction code appears on the data bus, the comparator output goes high. At the end of T3A time the 74107 flip-flop is set, causing its complementary output terminal to go low. At ST4 time the flip-flop is reset, and the SDT strobe goes high. This signal clocks a 74273 eight-bit latch, which latches up the data word on the output bus at PCC-T4 time. This word happens to be the contents of the index register referred to by the self-transfer instruction. The reader is referred to the first line of the 8008 *INTERNAL PROCESSOR OPERATION* chart (in the 8008 manual, and reprinted in Chapter 2).

Note that the comparator outputs may go high when the proper bit combinations appear on the output bus at PCI-T1 time, when the low-order memory address happens to match up with the code for a self-transfer instruction. But the 74107 is clocked only at the end of T3A time--by which time this memory address will have gone away, the comparator output will be low, and the output port will not be clocked.

Important: when the circuit shown in Figure 11.2.1 is being used, the microcomputer should NOT use the 377 HALT instruction. Consider what happens when a 377 instruction is executed. By extrapolation from the binary codes for the seven self-transfer instructions, 377 might be expected to stand for an LMM instruction: LOAD MEMORY FROM MEMORY. There is no such 8008 instruction, however; this is one of the three opcodes for the HALT instruction (Figure 11.1.2). Nevertheless the 93L24 will decode 377 as a self-transfer instruction at PCI-T3 time, and the 74107 will be set at the end of PCI-T3A time. The HALT instruction will stop the microprocessor at the end of PCI-T3 time, and the 8008 will wait for an interrupt before proceeding. No T4 time occurs during the HALT instruction, so the 74107 remains set. At T4 time of the very next instruction executed, the flip-flop is reset and an extraneous value



SEC. 11.2 OUTPUT ANY REGISTER (cont'd)

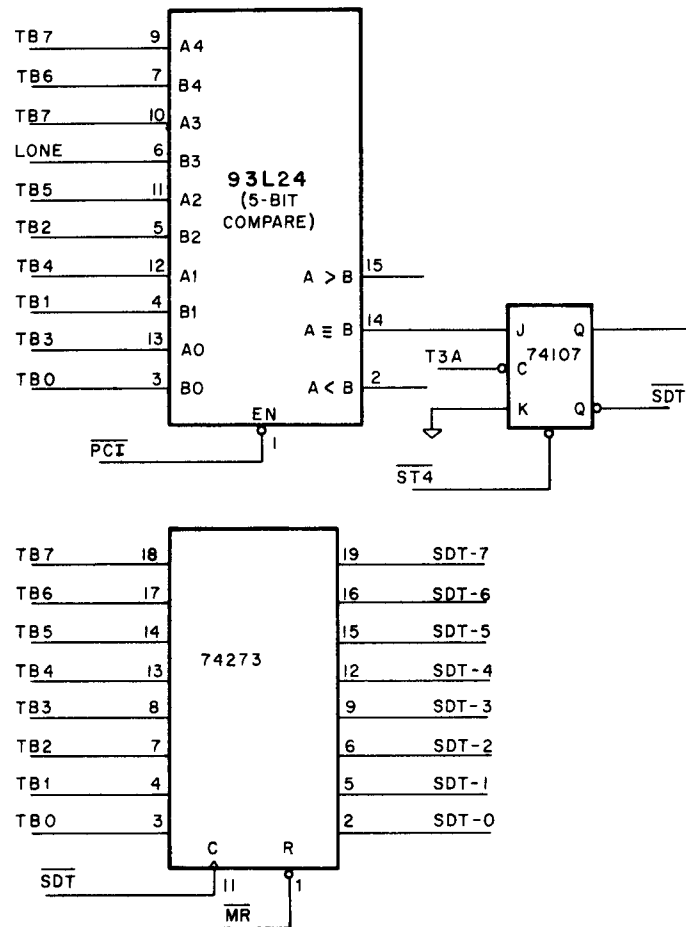


Fig. 11.2.1--One Instruction Outputs Any Index Register to Special Output Port



SEC. 11.2 OUTPUT ANY REGISTER (cont'd)

is strobed into the 74273 output port. Thus, either the 000 or 001 codes should be used for HALT instructions.

Only one output port is provided with the *Output Any Register* option, unlike normal 8008 output instructions, where the output word can be steered to any one of up to 32 output ports with a single-byte instruction.

Note that though the 8080 has self-transfer instructions--opcodes 111, 122, 133, 144, 155, and 177--this technique is difficult to apply. The 8080 has only one opcode for HALT, namely, 166, which would have to be trapped out and distinguished from the others to avoid the problem mentioned above.

SEC. 11.3 ONE-BYTE PUSH-POP INSTRUCTIONS

When a *Last-In, First-Out (LIFO)* register is connected in place of the 74273 latch, the *Output-Any-Register Option* allows the programmer to *push* any index register with one single-byte instruction, and to *pop* registers with another single-byte instruction.

A schematic for this circuit appears in Figure 11.3.1. (For a discussion of push-pop registers in general, and the LIFO portion of this circuit in particular, see Chapter 12.) A one-byte self-transfer instruction pushes the contents of the appropriate index register into the LIFO, and a single-byte INP 000 instruction pops the last-loaded register and reads it back into the microprocessor.

This circuit is particularly useful in systems making extensive use of the 8008's interrupt-handling capabilities. (See Chapter 17 for a discussion of saving and unsaving index registers and flags using push-pop software and hardware.)

Figure 11.3.2 shows the opcodes for the new PUSH and POP instructions provided by the hardware in Figure 11.3.1.

| OCTAL CODE | NEW MNEMONIC | COMMENT | OLD MNEMONIC |
|------------|--------------|--------------------------|--------------|
| 300 | PUSH A | PUSH A REGISTER | LAA |
| 311 | PUSH B | PUSH B REGISTER | LBB |
| 322 | PUSH C | PUSH C REGISTER | LCC |
| 333 | PUSH D | PUSH D REGISTER | LDD |
| 344 | PUSH E | PUSH E REGISTER | LEE |
| 355 | PUSH H | PUSH H REGISTER | LHH |
| 366 | PUSH L | PUSH L REGISTER | LLL |
| 101 | POP | POP LAST-LOADED REGISTER | INP 000 |

Fig. 11.3.2--One-Byte PUSH-POP Instructions



U.C. BERKELEY LIBRARY

SEC. 11.3 ONE-BYTE PUSH-POP INSTRUCTIONS (cont'd)

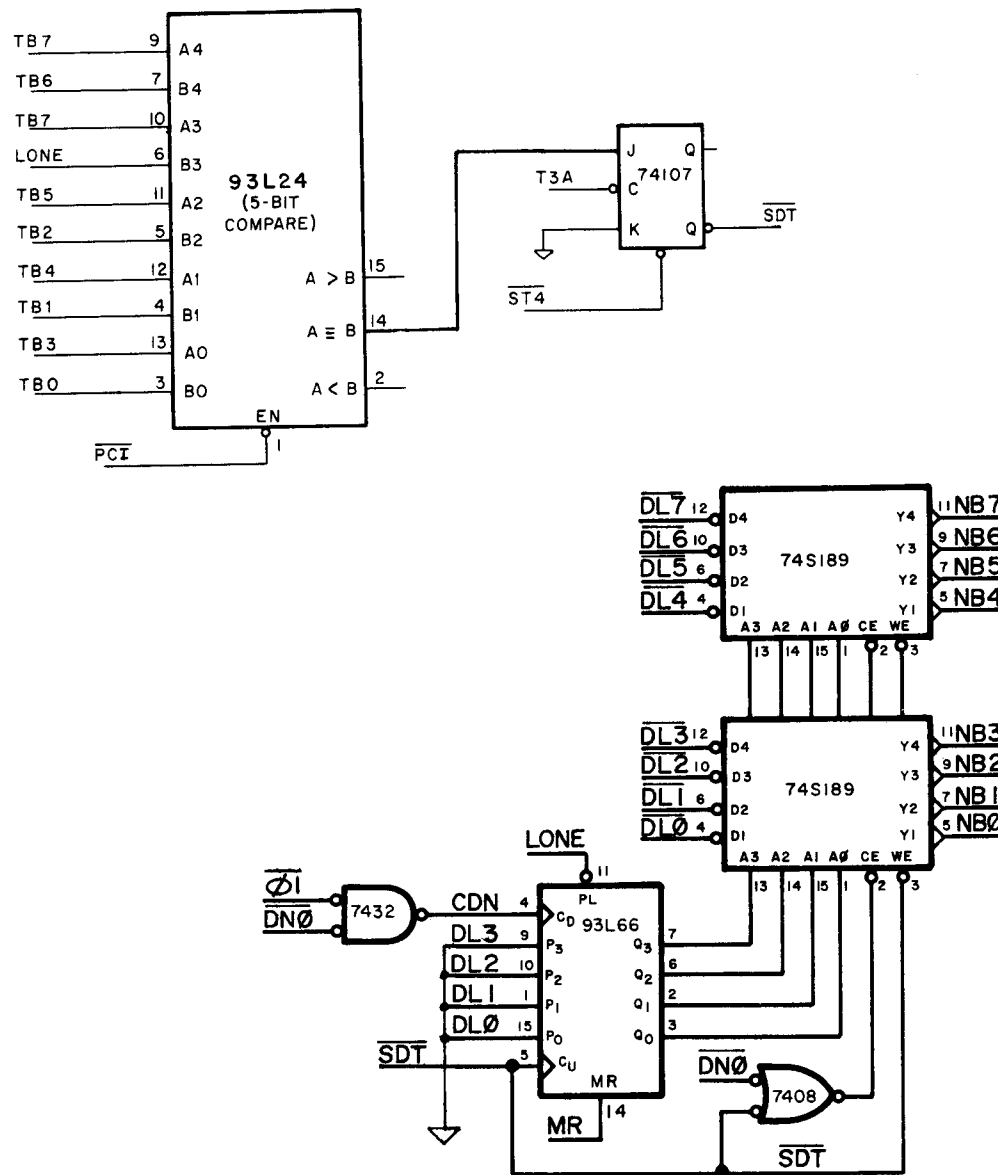


Fig. 11.3.1--Hardware Provides 8008 with One-Byte PUSH and POP Instructions



SEC. 11.4 NUMBERED INSTRUCTIONS

The RET, CAL, and JMP instructions for the 8008 microprocessor have in common the fact that the three middle bits--5, 4, and 3--may be varied without changing the normal functioning of the instruction. Thus there are eight codes for each of these instructions. A useful technique is to decode these separate instructions as they are executed and use the numbered instructions for special purposes.

| NEW MNEMONIC | CODE | NEW MNEMONIC | CODE | NEW MNEMONIC | CODE |
|--------------|------|--------------|------|--------------|------|
| RET | 007 | JMP | 104 | CAL | 106 |
| RET1 | 017 | JMP1 | 114 | CAL1 | 116 |
| RET2 | 027 | JMP2 | 124 | CAL2 | 126 |
| RET3 | 037 | JMP3 | 134 | CAL3 | 136 |
| RET4 | 047 | JMP4 | 144 | CAL4 | 146 |
| RET5 | 057 | JMP5 | 154 | CAL5 | 156 |
| RET6 | 067 | JMP6 | 164 | CAL6 | 166 |
| RET7 | 077 | JMP7 | 174 | CAL7 | 176 |

Fig. 11.4.1--Mnemonics, Codes for Additional Numbered Instructions

The numbered return instructions may be used for resetting an interrupt level, as described in Chapter 16. The numbered jump and call instructions may be used for pushing, popping, or outputting, or as tools in debugging programs and hardware (Chapter 24).

Figures 11.4.2 and 11.4.3 show circuits for decoding the execution of the numbered JMP and CAL instructions.



U.C. BERKELEY LIBRARY

SEC. 11.4 NUMBERED INSTRUCTIONS (cont'd)

D7 = 0
 D6 = 1
 D5 = C
 D4 = B
 D3 = A
 D2 = 1
 D1 = 0
 D0 = 0

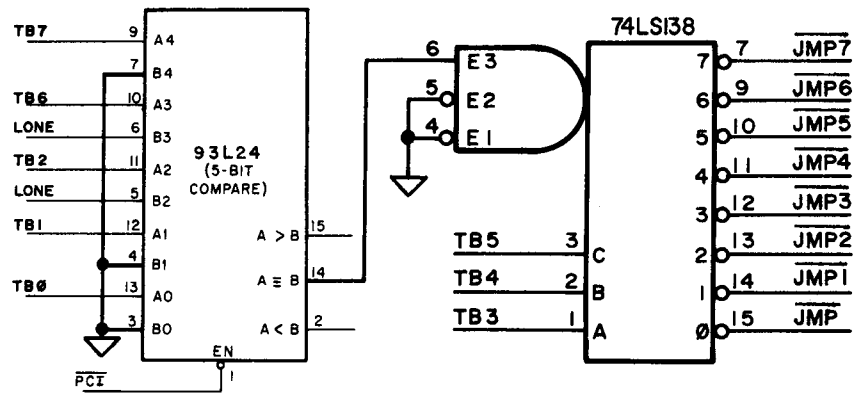


Fig. 11.4.2--Decoding the 8008 Numbered Jump Instructions

D7 = 0
 D6 = 1
 D5 = C
 D4 = B
 D3 = A
 D2 = 1
 D1 = 1
 D0 = 0

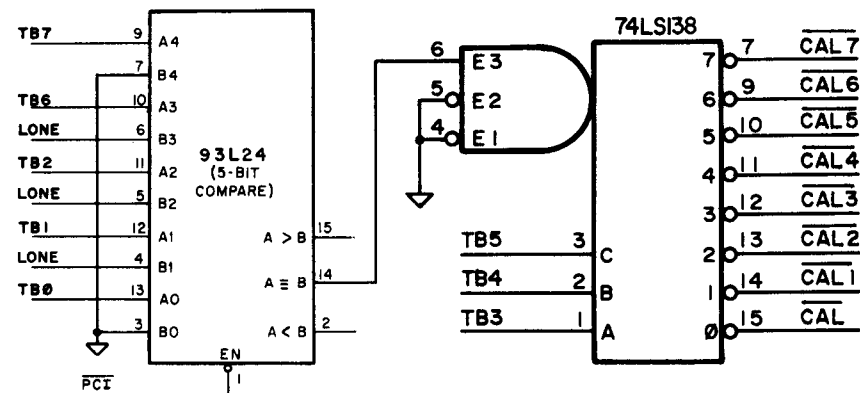


Fig. 11.4.3--Decoding the 8008 Numbered Call Instructions



microcomputer design

SEC. 11.5 WAIT INSTRUCTION

Both the 8080 and the 8008 have a READY terminal which, when brought low, causes the CPU to cease executing instructions. This function is intended primarily to allow the CPU to operate with slow memory or I/O devices. When READY goes low before T2 time, the CPU cycles in the T3 state and does not proceed further until the READY line goes high once more.

With simple hardware additions, the microprocessor can execute a simple WAIT instruction, causing it to enter the WAIT state. In an 8008 computer, the instruction is only one byte long; with an 8080, using the normal I/O mode, it is two bytes long. Figure 11.5.1 (A) shows a one-shot triggered by an 8008-mode INPUT 7 instruction; the CPU enters a wait state for a period determined by R and C. (For how to calculate the required one-shot period for an 8080, see Chapter 3.) In the circuit shown, the wait state is entered only when the low-order output bit is high, as set up by a previous instruction.

Figure 11.5.1 (B) shows a similar circuit. Here, however, the CPU cannot leave the wait state until a peripheral is ready. This may be useful in interfacing to a floppy disk.

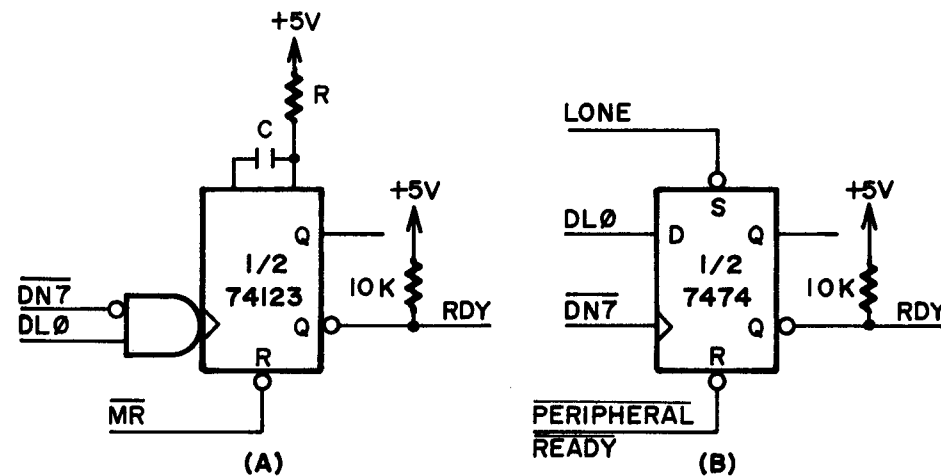


Fig. 11.5.1--Circuits for Implementing One-Byte WAIT Instruction



microcomputer design

SEC. 12.1 EXPANDING THE CAPABILITIES OF THE 8008

The first eight-bit microprocessor to hit volume production, the 8008 lacks some of the features introduced later with the 8080 CPU. This chapter contains several ideas for expanding the capabilities of the 8008, and may be useful not only for educational purposes, but to the designer considering design updates to an existing 8008 system.

SEC. 12.2 ONE-BYTE PUSH-POP (LIFO) REGISTER

12.2.1 LIFO and FIFO Registers A LIFO register is a temporary data storage device, usually having a capacity of at least several data words. It is organized as a number of single-word registers, often referred to as a *stack*. As each word is loaded into the LIFO, it *pushes down* the stack. When a word is read out of the LIFO, the last word loaded in is *popped* out. Thus the names *Last-In, First-Out (LIFO)* and *push-pop*. In operation, the LIFO can be analogized to a spring-loaded cafeteria tray stand, where the last tray laid down is the first picked up. Or the LIFO may be likened to an office elevator at quitting time. When the elevator reaches the main floor, the people who got on last are usually the first to get off. (The analogy breaks down in the morning, because as everyone knows, it is usually the first person who got on, standing at the back of the elevator, who wants to get off on the second floor. The crushed toes which result are the penalty for using the LIFO in a random-access application.)

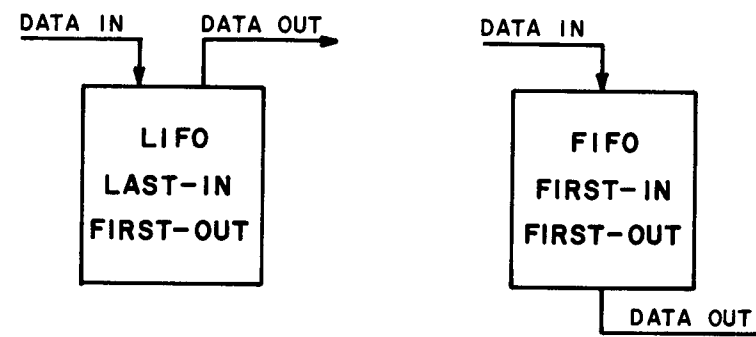


Fig. 12.2.1--Comparison of LIFO and FIFO Registers

SEC. 12.2 ONE-BYTE PUSH-POP (LIFO) REGISTER (cont'd)

As a contrast, the *FIFO* (*First-In, First-Out*) register is also shown in the drawing. The *FIFO* may be analogized to a queue of people waiting at a counter: first come, first served. The name *SILO* register is also used, by analogy to a silo on a farm, where the crop first stored is first removed from the bottom.

Both kinds of registers are often handy in a computer. For example, when returning from a subroutine in a program, the *Return* instruction refers automatically to the program location which *called* that subroutine in the first place. The memory location of the last *call* instruction needs to be stored--stored last and unloaded first. In practice, there is usually a stack with a capacity of many words of data, so that subroutines may be *nested* many levels deep. Subroutine A calls subroutine B, which calls subroutine C, etc.; then they return to the main line program in inverse order. In a related application, the contents of several data registers may need to be stored at the beginning of a subroutine, then restored at the end. (*For example, during interrupts: see Chapter 17.*) These examples call for a *LIFO* register, where the data most recently stored is the first retrieved.

On the other hand, data coming from a peripheral device is frequently handled on a first-come, first served basis and then a *FIFO* register is desirable.

12.2.2 One-Byte LIFO Register A one-byte register may be considered either a *LIFO* or *FIFO* register, of course. In an 8008-based microcomputer, a single-byte register is useful for temporary storage of the A register--for example, during interrupts. Since this function seems more closely analogous to the usual functions of the *LIFO*, the one-byte design in Figure 12.2.2 is labeled as such. This design is for handling eight-bit bytes, as are the other *LIFO* and *FIFO* designs in this chapter.

SEC. 12.2 ONE-BYTE PUSH-POP (LIFO) REGISTER (cont'd)

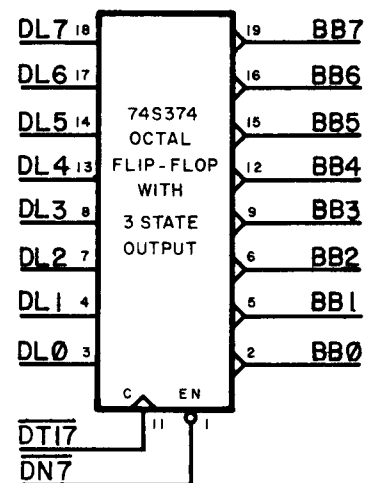


Fig. 12.2.2--One-Chip, One-Byte LIFO Register

This single-chip storage register is loaded when an output instruction OUT 017, is executed. The information is retrieved using an input instruction, INP 007. Unlike most multi-word *LIFO* and *FIFO* registers, the data stored may be retrieved (read out) as many times as desired without changing the information; only a new OUT 017 instruction changes the data. (If this one-byte register is both a *LIFO* and a *FIFO*, it is also a one-byte RAM, which is addressed using I/O instructions rather than memory read/write instructions.)

The circuit shown in Figure 12.2.3 is functionally identical, but shows the separate storage and retrieval functions more clearly. The one-byte register consists merely of an eight-bit latch and an eight-bit buffer with three-state outputs. The latch constitutes an output port, connected directly to the buffers, an input port. If a second byte of storage is needed, another 74S374 chip could be connected in a manner similar to the circuit in Figure 12.2.2, but using different input and output instructions.

SEC. 12.2 ONE-BYTE PUSH-POP (LIFO) REGISTER (cont'd)

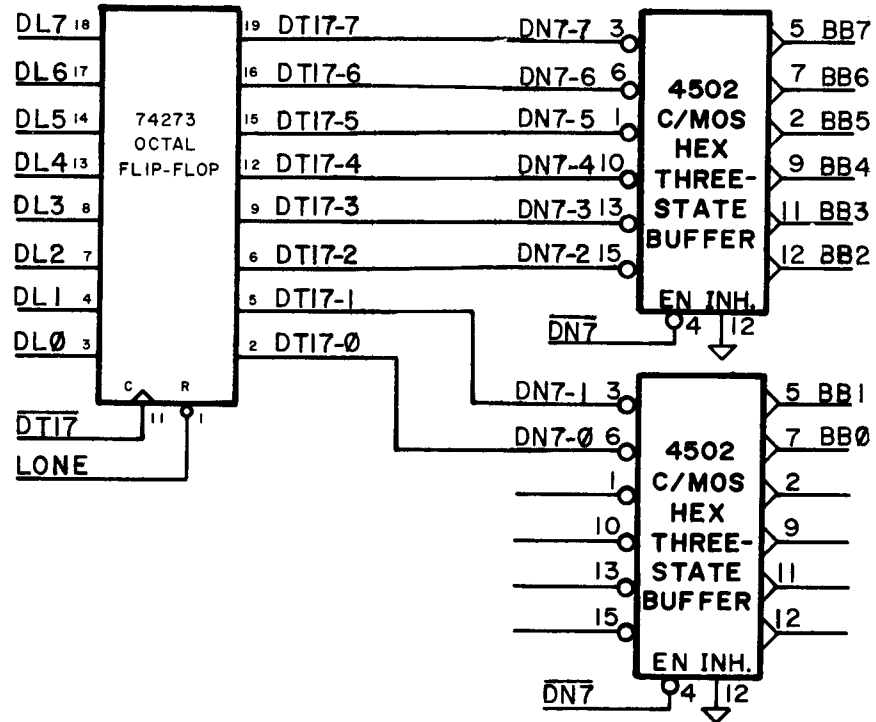


Fig. 12.2.3--A One-Byte LIFO Using Separate Latches and Buffers

SEC. 12.3 SIXTEEN-BYTE LIFO REGISTER

If more than two locations of LIFO storage are needed, then a sixteen-byte LIFO register may be constructed using three chips and a pair of gates (Figure 12.3.1). Two 16 x 4 RAM memory chips are used for data storage, and a four-bit up/down counter (plus two logic gates) are used to provide the last-in, first-out characteristic.

SEC. 12.3 SIXTEEN-BYTE LIFO REGISTER (cont'd)

 


Fig. 12.3.1--A Sixteen-Byte LIFO Register

When information is pushed (loaded) into the LIFO, or popped out (retrieved), the data does not actually move within the RAM. Instead, the pointer to the memory is stored in the 93L66 up/down counter, and moves with each operation. When an OUT 017 instruction is executed, the eight-bit data word is stored in the RAM, and then the RAM address is incremented. Since the DT17 strobe pulse is inverted, the incrementing of the 93L66 does not occur until the end of the strobe. And since the 74S189 is faster than the 93L66, the incrementing of the counter does not affect the RAM address until *after* the \overline{WE} (write enable) signals has disabled the 74S189 RAM chips. In this way a potential race condition is avoided.

SEC. 12.3 SIXTEEN-BYTE LIFO REGISTER (cont'd)

When a byte of data is being *popped* from the LIFO, the address must be decremented *before* the data is read. This is accomplished by strobing the 93L66 count-down command ($\overline{DN7}$) with a microcomputer main timing signal—here, $\overline{\phi 1}$ of the 8008 clock. This occurs early enough in the T3A phase to precede the actual reading of data by the CPU. If this technique unduly restricts the CPU speed, a flip-flop may be used to move the decrementing operation back to the beginning of $\phi 1$ time (Figure 12.3.2(a)). Even more speed may be obtained by using a one-shot for this function (Figure 12.3.2(b)).

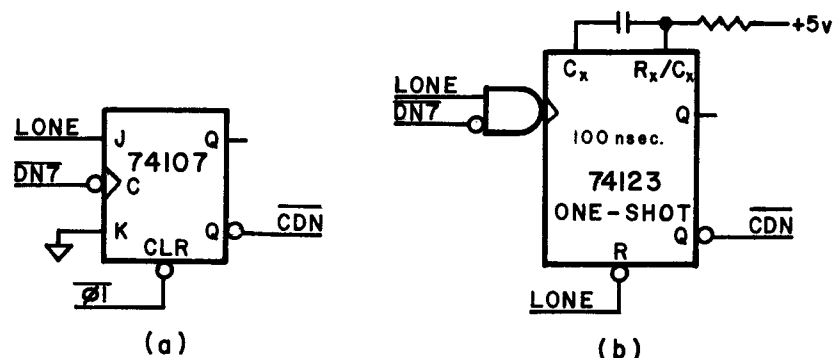


Fig. 12.3.2--Timing Modifications to Sixteen-Byte LIFO for Greater Speed

Note that the MR (master reset) pin of the up/down counter in Figure 12.3.1 is connected to the microcomputer master reset signal. This resets the counter to 0000 when power is first applied. Of course the circuit would still function if the initial counter output level were any random value. The microcomputer doesn't see the counter output address; the important thing is that the counter moves up and down through the stack as it receives the appropriate instructions. However, making the counter output addresses consistent from power-on to power-on, and machine to machine, facilitates debugging of defective chips.

An added feature of this circuit is that the LIFO address can be preset to a given level in the sixteen-level stack by using an OUT 027 instruction, whose four low-order bits load the up/down counter. If this function is unneeded, the counter's PL (parallel load) and parallel data (P3 through P0) can be connected to LONE (logic one: +5 volts through a 1 K ohm resistor). On the other hand, if the parallel load feature is included, it may be used to replace the MR signal by including a few instructions in the microcomputer's initialization

SEC. 12.3 SIXTEEN-BYTE LIFO REGISTER (cont'd)

sequence, which load the counters to 0000 (or any other value).

In Chapter 11 above, this sixteen-byte LIFO register is modified to permit the programmer to PUSH and POP the 8008's seven index registers with one-byte instructions.

SEC. 12.4 A 32-BYTE FIFO REGISTER

FIFO registers are frequently used to buffer data coming into the microcomputer from peripheral devices. An example is given in Chapter 21.

The FIFO is also useful in internal CPU operations, for instance, to store intermediate results of variable-length lists. The circuit in Figure 12.4.1 shows an AMD 2812 32 x 8 FIFO with its inputs connected as a microcomputer output port (OUT 016) and its three-state outputs connected to the microprocessor input bus. An OUT 016 instruction stores data, and an INP 006 instruction reads data from the FIFO.

This FIFO in this circuit may be cleared with a $\overline{DT37}$ strobe. The FIFO can thus be initialized to the empty state with an OUT 037 instruction, at any point in the program. The OR (output ready) signal goes low when the FIFO is cleared, either through execution of an OUT 037 instruction, or when all the data stored in the FIFO has been read into the microcomputer. If the register is full, the \overline{IR} (input ready) signal goes to a logic one. These conditions are read by the microcomputer using an INP 005 instruction. When an 8008 microprocessor is used, the INP 005 instruction can be followed by an instruction like JTS (jump true sign), which tests the high-order input bit, the FIFO *input ready* signal, and may branch to a sequence which reads the FIFO data into the microcomputer.

Note also that the 2812 has a half-full flag bit which outputs on pin 19 (not shown above). This terminal goes high when the FIFO contains more than 15 words. It could also be connected through a three-state buffer and used as one bit of the INP 005 input port.

Care must be taken, when designing with fast microprocessors, that data loaded into the FIFO has had time to ripple through the 32 internal registers to the output, before the FIFO is read. More information on the operation of the 2812 FIFO is included in Chapter 21 below.

SEC. 12.4 A 32-BYTE FIFO REGISTER (cont'd)

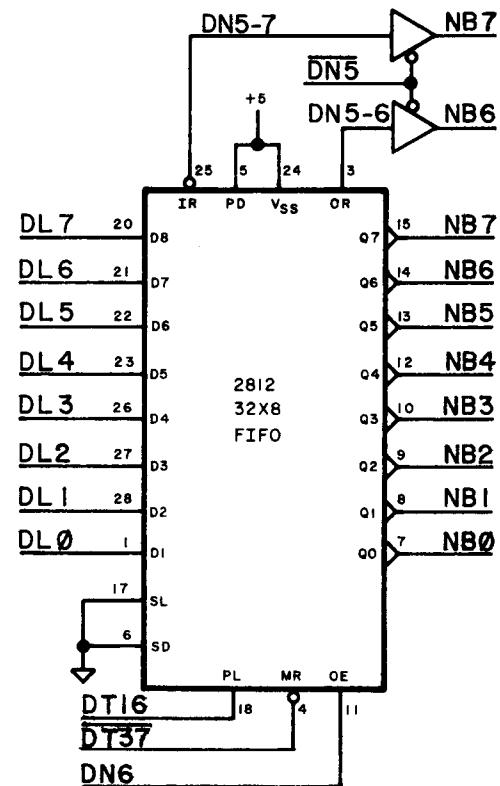


Fig. 12.4.1--A 32-Byte FIFO Register for Internal CPU Operations



microcomputer
design

SEC. 12.5 OTHER 8008 IMPROVEMENTS

This book contains a number of other methods for expanding 8008 capabilities, which are organized topically in other chapters of this book. They may be used singly, and in many cases in combination, to make the most of the 8008's capabilities. Most of the ideas presented involve the addition of only one or several integrated circuits to the basic 8008 microcomputer, plus, in many cases, some added instructions in the microcomputer's software. The purpose is twofold: first, to show how these extra functions can be added to a practical 8008 microcomputer; and second, for educational reasons, to demonstrate how basic microcomputer elements work.

Some expansion ideas are the following: expanding the number of input ports (Chapter 8); expanding output ports (Chapter 9); added instructions (Chapter 11); and interrupt handling (Chapters 16 and 17). Other sections of the book are devoted to *simplifying* the basic 8008 microcomputer--which is another way of getting the most out of a CPU.



microcomputer
design

SEC. 13.1 NEED FOR MEMORY IN MICROCOMPUTERS

Naturally the microprocessor is the heart of any microprocessor system. But memory is equally essential, and, in many microcomputers, represents more of the system cost than the microprocessor itself. A microcomputer needs digital storage elements external to the microprocessor for two reasons:

- (1) *Programming*--Because the microprocessor is a general-purpose computing device, it must be programmed to perform the particular functions needed in the system in which the microcomputer is used. The CPU derives its instructions from memory, and includes an internal program counter which keeps track of (*references*) the memory location from which instructions are being read.
- (2) *Temporary data storage*--Because the microprocessor itself has relatively little internal data storage capacity, most microcomputers need additional temporary data storage, usually provided by RAM. The CPU includes internal registers which reference the memory location for *writing* data into memory (in the case of RAM) and *reading* data from memory (ROM or RAM).

The following section details the way in which microprocessors use memory, both RAM and ROM. Later sections concentrate on RAM, and Chapter 14 focuses on ROM.

SEC. 13.2 MEMORY REFERENCING

The Program Counter (PC) register within the CPU contains the address of the next instruction to be fetched and executed. The address of memory into which data can be written (or from which data can be read) is typically stored in the H and L registers in an 8080--though the BC and DE register pairs may also be used. (Only the H and L registers are used for this purpose in an 8008.) During any instruction which references memory as a source to read from or write into, the appropriate memory address appears on the microcomputer's address lines, so that the selected location can be activated for the upcoming data transfer. The 8080 has 16 address terminals on its 40-pin package for this purpose, while the 8008 requires external DH and DL registers (Ch. 5) to address 14 lines. The ways in which memory is referenced are summarized below.

- 1) PROGRAM COUNTER (16 bits, 8080; 14 bits, 8008)
Address for READING instructions from memory.
- 2) H AND L REGISTERS (or B and C, D and E in 8080)
 - a) Address for READING data from memory.
 - b) Address for WRITING data into memory.

Fig. 13.2.1--Memory Addressing



SEC. 13.2 MEMORY REFERENCING (cont'd)

An 8008 instruction such as ADM (add memory) first reads a byte from memory, at the location specified by the H and L registers; then the CPU adds this value to the contents of the A register. The 8080 instruction ADD M is identical in substance.

| | | |
|----|-----|--|
| 1 | LMr | Load Memory from register r. |
| 2 | LMI | Load Memory Immediate. |
| 3 | LrM | Load register r from Memory. |
| 4 | ADM | Add Memory to the A register. |
| 5 | ACM | Add (with Carry) Memory to the A register. |
| 6 | SUM | Subtract Memory from the A register. |
| 7 | SBM | Subtract (with Borrow) Memory from the A register. |
| 8 | NDM | AND Memory with A register. |
| 9 | XRM | EXCLUSIVE OR Memory with A register. |
| 10 | ORM | INCLUSIVE OR Memory with A register. |
| 11 | CPM | Compare Memory with A register. |

Figure 13.2.2--The 11 8008 Instructions Which Reference Memory Using the H and L Registers as an Address

The 8080 includes all of the above instructions--however, note that the mnemonics usually used differ from the 8008 mnemonics. In addition, the 8080 includes a number of instructions which refer to memory in other ways. For a graphic presentation of these 8080 instructions--including double-precision transfer instructions; indirect transfers; and direct load and store instructions--see the chart in Chapter 3 (Fig. 3.3.3) above.

SEC. 13.3 MEMORY ADDRESS CONVENTIONS

Within the 8008, memory is referenced by the fourteen bits of the internal program counter (with regard to fetching instructions) or the fourteen bits of the internal H and L registers (with regard to reading and writing data). These fourteen bits address up to 2^{14} , or 16 x 1024, or 16 K bytes of memory.

In the 8080, the 16 address lines reference 2^{16} , or 64 K bytes. These address lines may flexibly be loaded from various CPU registers as well as the H and L. (Again, see Chapter 3.)

SEC. 13.3 MEMORY ADDRESS CONVENTIONS (cont'd)

The six high-order memory bits (DH5 through DH0) address 64 (*decimal*) pages of memory, where a *page* is a group of 256 bytes addressed by the eight low-order memory (DL) bits. The addresses are often written in octal notation to correspond to the eight-bit architecture of the micro-computer; thus, each page begins with location 000_8 and runs to 377_8 (for 256 *decimal* bytes).

The full memory address is, in this book, transcribed in *split octal* notation, where there are six octal digits. The right-hand triplet corresponds to the DL register and the left-hand triplet corresponds to the DH register. Thus a kilobyte RAM array (Figure 13.5.5) whose first location is 000000 runs through location 003377 in split octal notation. This notation clearly indicates that a 1 kilobyte RAM consists of four pages (000, 001, 002, 003).

Figure 13.3.1 shows the correspondence between the states of the fourteen binary address bits, and the split octal notation for that memory address. The asterisks appear above a sixth high order octal digit which is often seen in 8008 literature, and is used to address PROM programming stations if included in the system. The 8080 uses all 16 bits.

| DH7 | DH6 | DH5 | DH4 | DH3 | DH2 | DH1 | DH0 | DL7 | DL6 | DL5 | DL4 | DL3 | DL2 | DL1 | DL0 |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | | 3 | | | | 3 | | | 7 | | 7 | | | |

Figure 13.3.1--Split Octal Notation

SEC. 13.4 RAM-PAGE OPTION

13.4.1 How It Works The preceding sections set the stage for the introduction of a valuable design technique called the RAM-PAGE OPTION. This technique involves both hardware and software changes, and both eliminates hardware, and cuts down on program size and execution time for an 8008 microcomputer. RAM-PAGE also frees up the use of one of the index registers internal to the CPU (usually the D register), which is useful in handling interrupts. The limitation of the design is that it can be used only in systems with a single page (256 bytes) of RAM, or less.



SEC. 13.4 RAM-PAGE OPTION (cont'd)

As discussed previously, instructions which *read* from memory may refer either to ROM or to RAM. *Write* instructions, however, are normally used only with RAM, since by its very nature ROM (read-only memory) cannot be written into by the microcomputer. Since, with the *RAM-PAGE* option, there is only one page of RAM, the microcomputer may be designed to reference that one page automatically whenever a memory write instruction is executed. In other words, *the page number is ignored during memory write cycles.*

The 8008 instructions which cause a memory write cycle are LMA, LMB, LMC, LMD, LME, LML, and LMH. When these instructions are used in a microcomputer equipped with the *RAM-PAGE* option, the programmer need not set up the H register to point to the RAM address.

Figure 13.4.3 shows two sample 8008 programs written for systems with and without this option. The program written without uses two more bytes of program storage and takes 50% more time to execute.

The amount of savings attainable with *RAM-PAGE* varies greatly with the application and the style of program used. There is no doubt that many low cost, high production-volume microcomputers are being designed with only one page of RAM. As long as there is no intention of expanding the amount of RAM in the future, one should always opt for the *RAM-PAGE* approach. This is especially true since this option requires no additional hardware.

(However, note that other special purpose options described in Chapter 11 may conflict with the *RAM-PAGE* option.)

13.4.2 Another Ram-Page Advantage The *RAM-PAGE* option is most attractive in systems which have a need for interrupts. When an interrupt occurs, one has only to save the L register before being able to store the remaining registers in RAM. Without *RAM-PAGE* it is necessary to save both H and L registers before the remaining registers can be stored in RAM. In many current designs the interrupt routine moves the H register to the D register and the L register to the E register, then sets the H and L to point toward RAM, and stores the other registers in RAM. With the *RAM-PAGE* option only the L register need be moved to the E register before the saving of other registers in RAM can begin. This frees up the use of the D register for some other purpose. This extra register makes the programmer's job much easier and can cut the instruction count significantly. See Chapter 17 for more information on how the *RAM-PAGE* Option is used with interrupt programs.

In 8080 systems, a page or more in RAM is usually reserved for the program stack. The 8080 PUSH and POP instructions facilitate interrupts.



microcomputer
design

SEC. 13.4 RAM PAGE OPTION (cont'd)

| OBJECT OF PROGRAM: MOVE THE FIRST 100 ₈ BYTES FROM ROM [PAGE 40 ₈] TO RAM [PAGE 77 ₈] | | | |
|--|----------------------|-------|-------------------------|
| PROGRAM WITHOUT RAM-PAGE OPTION | NO. OF INSTR. CYCLES | | INSTRUCTION |
| | SINGLE | TOTAL | |
| 2 | 8 | 8 | LLI 100B |
| 2 | 8 | 512 | LHI 040B |
| 1 | 8 | 512 | LAM LOOP |
| 2 | 8 | 512 | LHI 077B |
| 1 | 7 | 448 | LMA |
| 1 | 5 | 320 | DCL |
| 3 | 11/9 | 702 | JFZ LOOP |
| 12 | | 3014 | |
| PROGRAM WITH RAM-PAGE OPTION | | | |
| NO. OF BYTES | NO. OF INSTR. CYCLES | | INSTRUCTION |
| | SINGLE | TOTAL | |
| 2 | 8 | 8 | LLI 100B |
| 2 | 8 | 8 | LHI 040B |
| 1 | 8 | 512 | LAM LOOP |
| 1 | 7 | 448 | LMA |
| 1 | 5 | 320 | DCL |
| 3 | 11/9 | 702 | JFZ LOOP |
| 10 | | 1998 | |
| COMMENTS | | | |
| | | | POINT TO END |
| | | | POINT TO PAGE IN ROM |
| | | | LOAD DATA FROM ROM |
| | | | POINT TO RAM PAGE |
| | | | STORE DATA IN RAM |
| | | | POINT TO NEXT DATA BYTE |
| | | | LOOP IF NOT DONE |
| | | | ---COMPARISON--- |

The *RAM-PAGE* option program is two bytes shorter, and requires only about two-thirds the execution time. With the *RAM-PAGE* option, the LAM and LMA instructions refer to two different pages in memory without changing the H register.

Figure 13.4.3--RAM-PAGE Option Cuts Program Time



microcomputer
design

SEC. 13.4 RAM-PAGE OPTION (cont'd)

13.4.3 RAM-PAGE Hardware Design Usually single 256 x 8 (or dual 256 x 4) bit RAM chips are used for designs needing only one page (256 bytes) of RAM. The more modern designs usually use a pair of 256 x 4 bi-directional bus-type RAMS connected directly to the CPU bus. For example, see Figure 13.4.1.

 


Figure 13.4.1--One Page of RAM Added Directly to CPU Bus

The RAMSEL (RAM select) signal in Figure 13.4.1 should go to logic one only when the DH register is selecting RAM, and CCl is logic zero.

The microcomputer design example in Chapter 26 shows how the RAM-PAGE option is implemented in hardware. See also paragraph 13.6.4.

SEC. 13.5 RANDOM ACCESS MEMORIES

13.5.1 General There are many RAM ICs available today. Of these, there are two basic types: (1) static and (2) dynamic.

SEC. 13.5 RANDOM ACCESS MEMORIES (cont'd)

The static RAM holds the data which has been stored in it as long as power is being applied. Normally, the data in a static RAM is stored in memory cells similar to flip-flops. Some of these RAMs will hold data when only a fraction of the normal voltage is being applied (e.g., Advanced Micro Devices 9102).

In the dynamic RAM, information is usually held by stored charge on the capacitance of each memory cell. The charge on this capacitor leaks off after awhile so that it is necessary to refresh the information stored periodically.

13.5.2 RAM For Small Microcomputers Many small microprocessor systems require only a few locations of RAM. Some are so small as to require none. (See the MM1 in Chapter 25.)

One of the smallest 8-bit RAM arrays consists of two 16 x 4 bipolar RAM chips and associated read-write logic. Figure 13.5.1 shows a simple

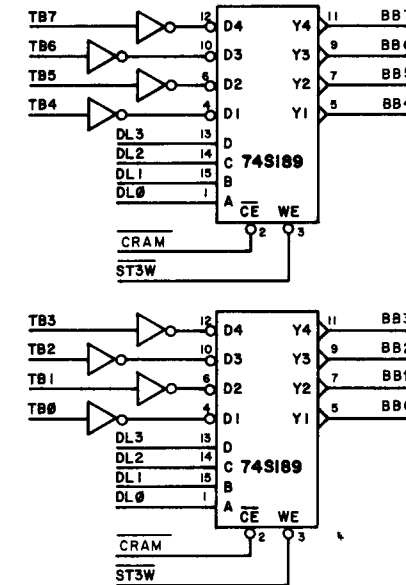


Figure 13.5.1--Sixteen Bytes of RAM with Two 16 x 4 RAM Chips

U.C. BERKELEY LIBRARY

SEC. 13.5 RANDOM ACCESS MEMORIES (cont'd)

circuit which uses these chips. 16 x 4 bipolar RAM chips are easily obtained from a number of manufacturers, but have the drawback of inverting stored data. Inverters may be added to the inputs or the program can compensate by inverting data. With the 8008, an *XRI 377B* instruction will complement (reinvert) the contents of the A register.

The 74S189 is a three-state device; the 31L01 and 7489 are open-collector types, which require pull-up resistors on the output bus (not shown).

SEC. 13.6 THE 256 x 4 RAM

A number of 256 x 4 RAMs are available. Most of these chips use the 5-volt N-channel technology. These memories are not only fast enough for the 8008, but are available in high-speed versions compatible with the 8080.

The fact that RAM may be added to the microcomputer with only two RAM chips and a few gates often makes these memory ICs very attractive for small 8-bit microprocessor systems.

There are three basic types of 256 x 4 RAM available. They may be generally categorized by the number of pins in their IC packages.

13.6.1 22 Pins The 22-pin versions have separate input and output pins for data. Figure 13.6.1 shows the schematic of the basic 256 x 4 RAM.

The 2101 chip manufactured by Intel has one chip enable (\overline{CE}), and although there is no separate output enable, the chip enable pin will float (three-state) the outputs when the chip is not selected. The chip schematic is the same as shown in Figure 13.6.1 except for the lack of $\overline{CE2}$, and \overline{OE} . The 2101 is usually less attractive for microprocessor designs with a small amount of RAM than are the 16-pin or 18-pin versions. However, a pin-compatible CMOS version, the Intel 5101, is now available, and is very attractive for battery-backed memory systems.



microcomputer
design

SEC. 13.6 THE 256 x 4 RAM (cont'd)

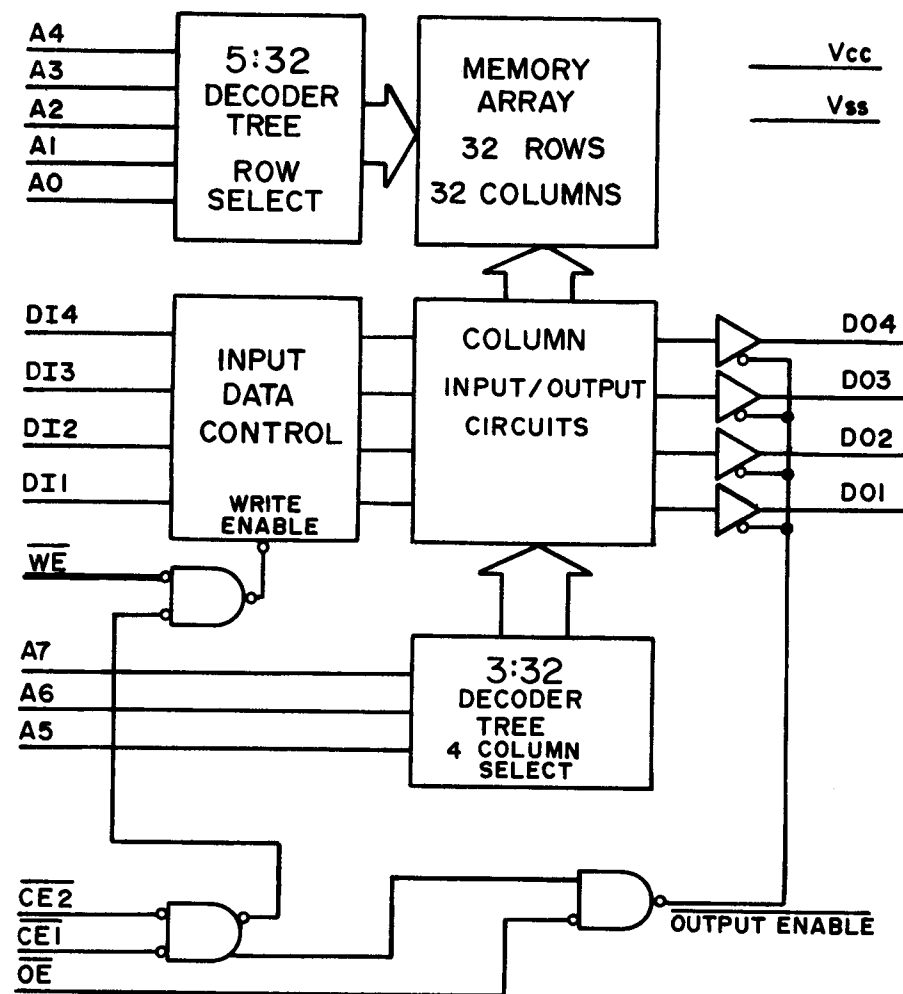


Figure 13.6.1--Schematic of 256 x 4 Random Access Memory Chip.
The Chip May be Packaged in 22, 18, and 16-pin Configurations.



microcomputer
design

SEC. 13.6 THE 256 x 4 RAM (cont'd)

For systems with a larger amount of RAM, the 2102 (1024 x 1) chip is more attractive, because of its smaller package (16 pins) and lower price.

13.6.2 18 Pins The 18-pin versions of the 256 x 4 RAM are now available from many suppliers. They are pin-for-pin compatible, following the design shown in Figure 13.6.1. The 18-pin version is just like the 22-pin version, except that DI₄ and DO₄ are connected internally in the IC package, as are the other pairs (DI₃, DO₃; DI₂, DO₂; DI₁, DO₁). This creates a 4-bit bidirectional bus structure, as compared to the 22-pin version, which may be connected to two separate busses.

13.6.3 16 Pins The 16-pin versions of the 256 x 4 RAM are probably the most attractive designs for 8008 and 8080 designs requiring only a small amount of RAM. Some designers prefer the 18-pin version for 8080 designs, but consideration should be given to the 16-pin configuration before making a decision. There are currently two types in the 16-pin version (Signetics and Intel). The Signetics 2606 chip was the first 256 x 4 RAM. The Intel version is not pin compatible with it. The major advantage to the Signetics 2606 and the Intel 2112-1 is their faster speed. The circuit of Figure 13.6.2 may be used with the 2606 and 2112-1 and 8008 microprocessor, even though the chip enable pulse on writing is only 500 nanoseconds.

The slower 2112 specification requires a 750-nanosecond pulse, which means that more complicated circuitry is needed to drive these RAM chips. Figure 13.6.3 shows a design for driving the 2112 RAM.

The Intel 18-pin version, the 2111, requires that READ ENABLE be connected to the OE pin (see Figure 13.6.4).

SEC. 13.6 THE 256 x 4 RAM (cont'd)

13.6.4 Circuits Suitable for RAM-PAGE Option The circuits shown in Figures 13.6.2 through 13.6.4 illustrate the differences in timing and connection for the different 256 x 4 RAM varieties. It should be noted that all three circuits are configured for the RAM-PAGE option discussed earlier in this chapter.

RAM memory is addressed in the READ mode, in these circuits, only if the high-order memory address bit (DH₅) is logic one. This means that any memory reference to the upper 8K of memory will be decoded as referring to this one page of RAM. The location within the page is selected, as usual, by the eight low-order address bits, defined by the DL register.

When any instruction writes into memory, the two 256 by 4 RAM chips will *always* be addressed, regardless of the states of the DH register bits. Thus these designs are suitable for microcomputers using only one page of RAM. The control signals shown in this section are for the 8008.

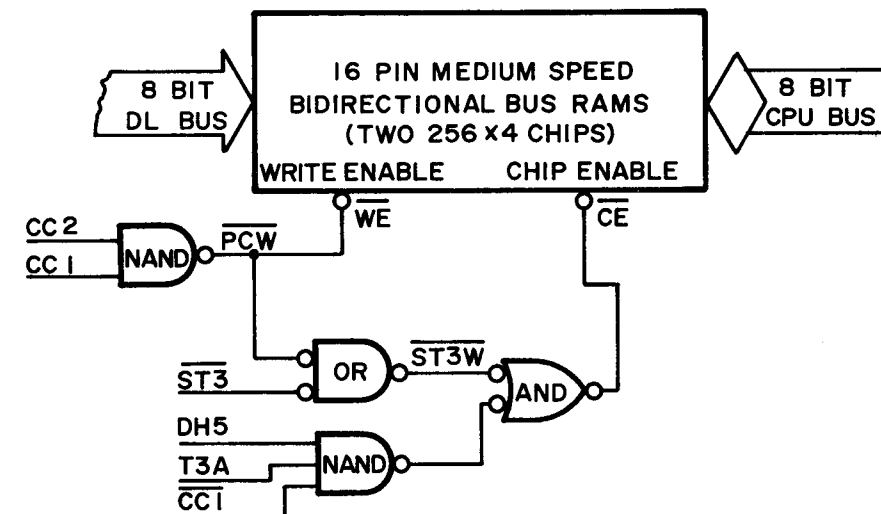


Figure 13.6.2--Two 256 x 4 Medium-Speed RAMs for an 8008 Microcomputer with the RAM-PAGE Option

SEC. 13.6 THE 256 x 4 RAM (cont'd)

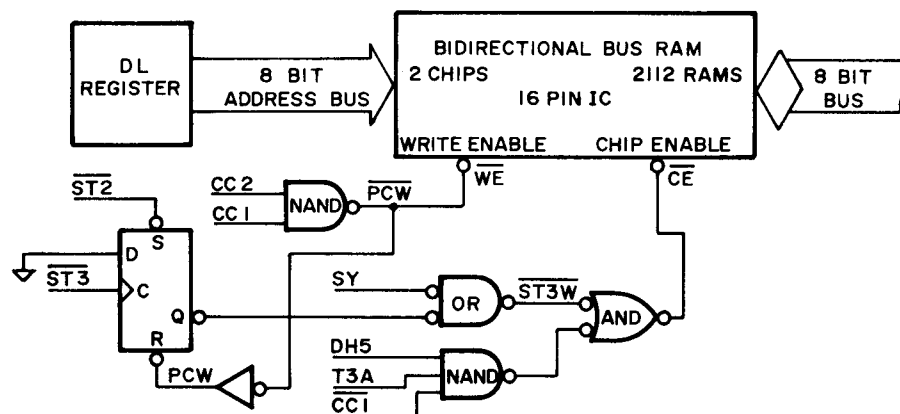


Figure 13.6.3--A Longer Chip-Enable Pulse Developed for Writing into Slower 256 x 4 RAMS

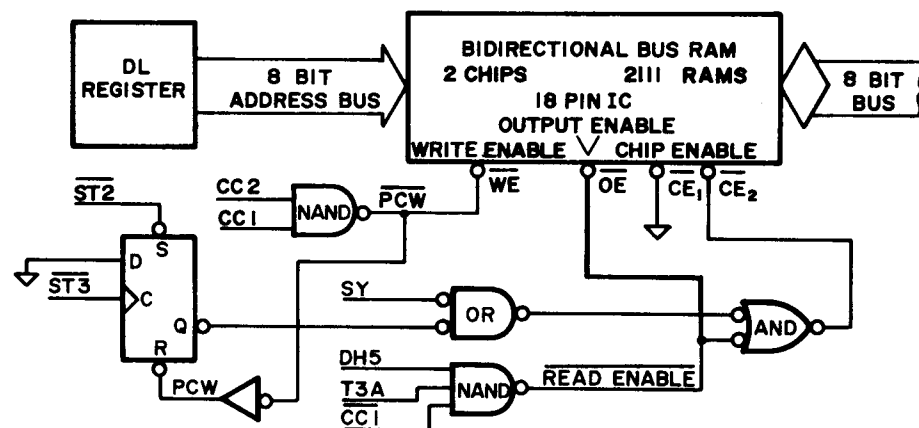


Figure 13.6.4--The Intel 18-Pin RAM Needs Output Enable Connection

SEC. 13.6 THE 256 x 4 RAM (cont'd)

Of the circuits shown in Figures 13.6.2, 13.6.3, and 13.6.4, the first is the simplest and would seem to be the most attractive. Whether it is really suitable depends in part on the 256 x 4 RAM's clock specifications. Figure 13.6.6 shows the timing diagram for the circuit of Figure 13.6.2.

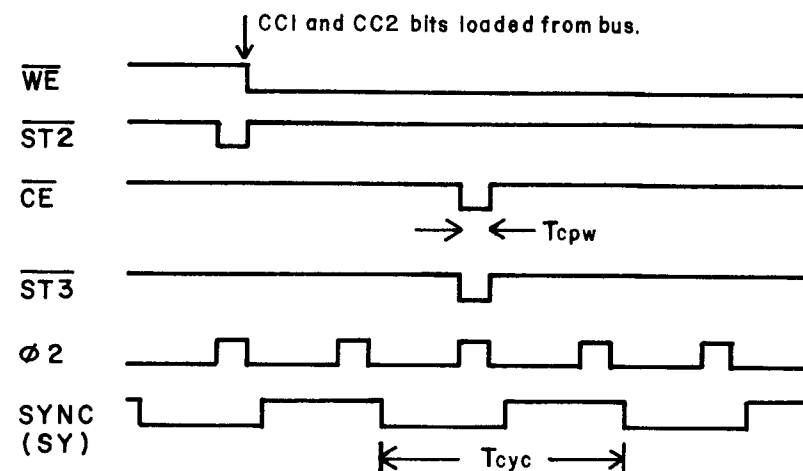


Figure 13.6.5--Timing Diagram Relating RAM Write Delay to CPU Cycle Time for Circuit in Figure 13.6.2

The symbol T_{cpw} is used here to designate the minimum time for which the RAM must be enabled to write properly. The CPU clock circuit is assumed to be of the symmetrical variety (as discussed in Chapter 5). It may be seen that the T_{cpw} pulse is one-eighth of the chip's cycle time, T_{cyc} . For a standard 8008 microcomputer, where T_{cyc} is 4.0 microseconds, T_{cpw} would come to 500 nanoseconds.

SEC. 13.6 THE 256 x 4 RAM (cont'd)

13.6.5 256 x 4 Circuit Without RAM-PAGE Option When it is desired to add a page of RAM to a microcomputer which does not use the RAM-PAGE option, the circuit in Figure 13.6.6 can be used. The signal labeled RAM ENABLE may derive from one of the eight outputs of a decoder, such as the 3205/74LS138. The inputs to the decoder would come from the DH register. The T3A enable signal is combined, in this circuit, with the other RAM select logic. The control signals are for an 8008 microcomputer system.

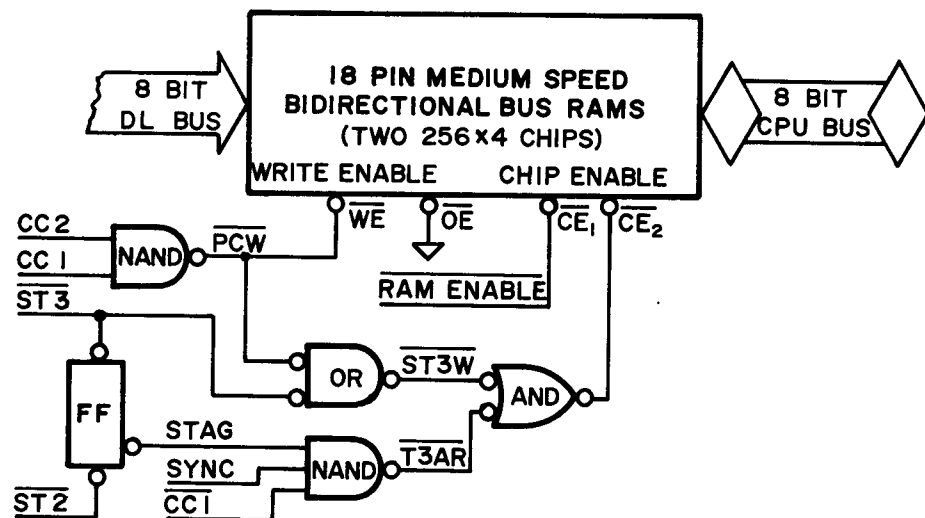


Figure 13.6.6--RAM Select Logic for Systems Requiring More than One Page of RAM

13.6.6 Warning Since the bidirectional bus RAMs are right on the CPU bus (BB), care must be taken in the circuit design that memory is disabled by more than just the lack of the correct address in the DH and DL registers. For example, the second cycle of an I/O instruction loads the DH and DL registers with information which may look like a RAM address. The RAM may be disabled in these cases by using the cycle control bits (CC2, CC1). This has been done in the examples given in the last section. The other major problem which may arise is that the RAM might be unintentionally enabled during an interrupt cycle. If memory is used as the source of interrupt instructions (as in most examples in this book) no problems will occur.



SEC. 13.7 THE 1024 x 1 STATIC RAM

13.7.1 The 2102 1K RAM The 2102 static RAM has gained much popularity among designers of microprocessor systems and of other machines requiring large configurations of medium-speed memory. The 2102 is available from many suppliers. Power supplies for the 2102 are convenient: +5 volts and ground. The 5-volt N-channel technology used in the fabrication of this chip has improved considerably; while still slower than the 17-volt N-channel process used for higher-speed RAMs, the 2102 is not only adequate for 8008-based microcomputers, but in the 2102 A version, compatible with the 8080.

A one-kilobyte (1024 x 8) RAM array using 2102 chips is shown in Figure 13.7.1. The outputs are three-state and may therefore be connected to the memory data input bus (MT bus) or directly to the CPU bus (BB bus).

13.7.2 Access Time and Address Bit Connections In working with the 2102 and other RAM chips with more than 256 locations, the designer should be aware of the considerations which affect access time.

For example, if the address bits have been stable for several microseconds or more, and the chip enable (\overline{CE}) pin is brought low, the access time is effectively T_{oe} , which is usually much faster than the chip's rated cycle time.

In an 8008-based microcomputer--to review what has been presented earlier in this chapter and in Chapters 2 and 5--the eight-bit low-order memory address comes out on the CPU bus at T1 time. The high-order bits are present on the bus at T2 time. The main timing circuitry develops strobe signals called ST1 and ST2, which occur slightly before the end of T1 and T2 times (respectively). These strobes are used to activate external eight-bit latches, called the DL and DH registers, which latch up the memory addresses. The delay in developing the strobes ensures that the information has had time to settle on the CPU data bus before it is latched up in the registers.

Thus the eight low-order address bits are available at ST1 time, and the high-order bits are available at ST2 time. Memory accessing itself usually takes place during state 3--during T3A time for memory read cycles, and ST3W for write cycles. This means that the low-order address bits have had plenty of time to travel from the DL register and settle down reliably into the low-order memory address ports. Therefore memory access time is effectively determined by the chip select time and by the settling time of the high-order bits.

In an 8080 microcomputer, all 16 address bits become valid at the same time. For 8080 memory speed requirements, see Chapter 3.



SEC. 13.7 THE 1024 x 1 STATIC RAM (cont'd)

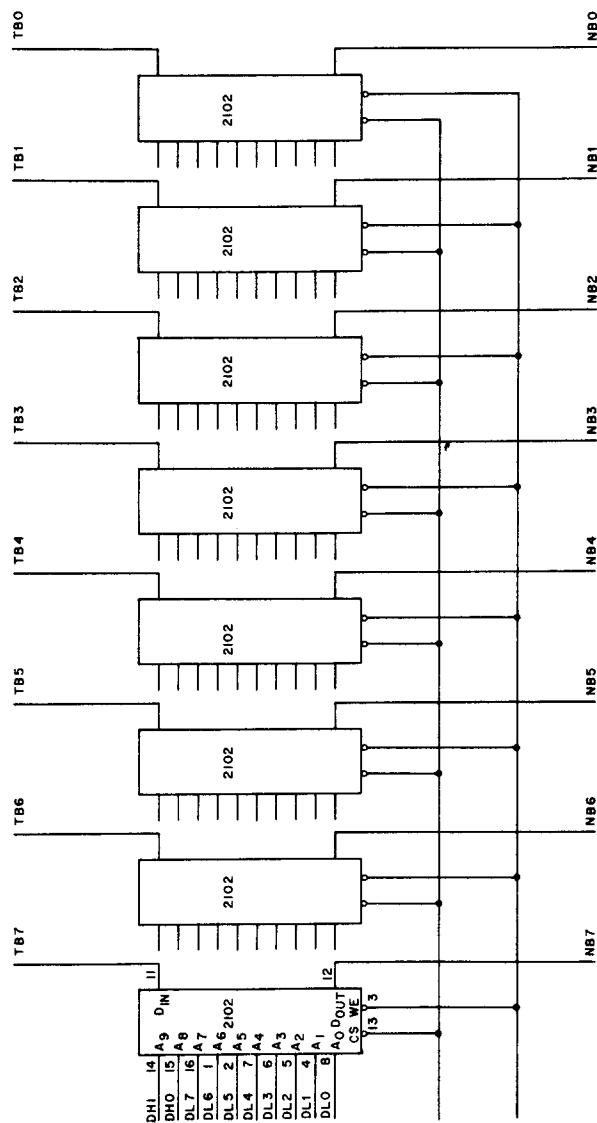


Figure 13.7.1--A One-Kilobyte RAM Using Eight 2102 RAM Chips



SEC. 13.7 THE 1024 x 1 STATIC RAM (cont'd)

 


Figure 13.7.2--8008 Memory Access Times

In the diagram shown in Figure 13.7.2, the DH register is loaded on the falling edge ST2 (normally defined as SY times $\phi 2$). It is obvious that the high-order access time Hacc, is the most critical.

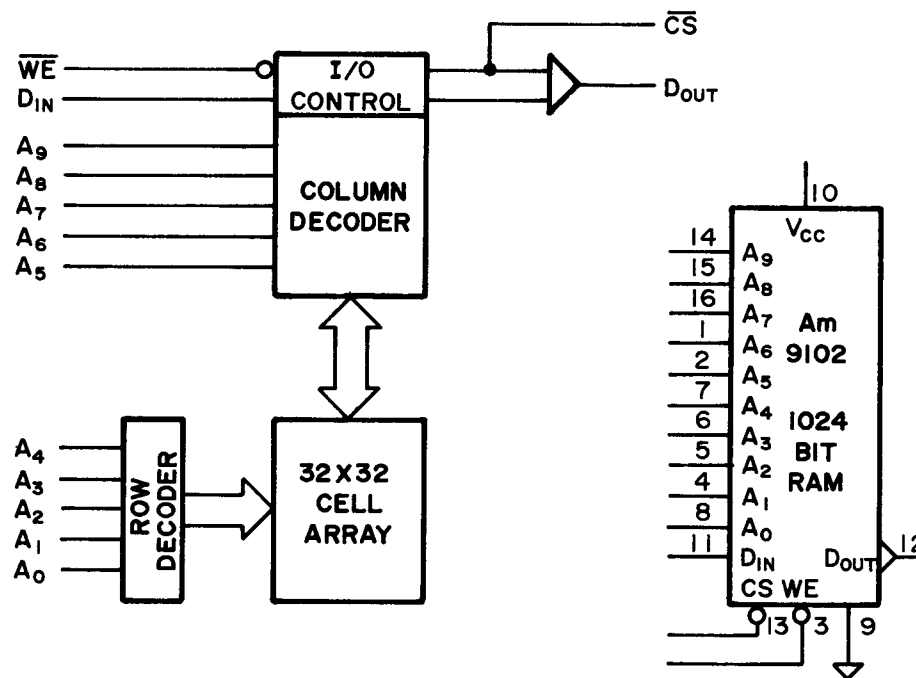


Figure 13.7.3--Block Diagram and Logic Symbol for 2102 1K RAM



U.C. BERKELEY LAB

SEC. 13.7 THE 1024 x 1 STATIC RAM (cont'd)

For most memories and most 8008 systems, the *Hacc* time is long enough for reliable operation. However, by using $\phi 1$ rather than $\phi 2$ to develop the $ST2$ strobe, the designer increases *Hacc* almost 100%. Or, $ST2A$ may be used: see Figures 13.7.5 and 13.7.6.

Most RAM chips have some addresses which are more quickly accessed than other addresses. For example, see the block diagram of a 2102 RAM in Figure 13.7.3. The access time for the *column decoder* section is shorter than that for the *row decoder*. This means that the high-order (DH) address bits should always be connected to the column decoder terminals, leaving the remaining column decoder terminals (the slower ones if this is known) and the row decoder terminals for the low-order address bits.

Figure 13.7.4 shows the results of access time experiments on a typical 2102 RAM chip.

| ADDRESS BIT | ADDRESS TO OUTPUT DELAY (nanoseconds) | ADDRESS DECODER AFFECTED |
|-------------|---------------------------------------|--------------------------|
| A9 | 400 | COLUMN |
| A8 | 415 | COLUMN |
| A7 | 415 | COLUMN |
| A6 | 425 | COLUMN |
| A5 | 415 | COLUMN |
| A4 | 535 | ROW |
| A3 | 535 | ROW |
| A2 | 505 | ROW |
| A1 | 515 | ROW |
| A0 | 525 | ROW |

Figure 13.7.4--Access Times for Different Address Bits of a Typical 2102 RAM Chip

If the chip were connected in an 8008 system with bits A9 and A8 connected to DH1 and DH0 (as shown in Figure 13.7.1), the address-to-output delay would be 415 nanoseconds (worst case between A8 and A9). This delay would, if reliably repeated in production quantities, allow use of the 2102 in an 8008 system operating at standard 8008 speed. The designer could do without having to specify the premium 2102-1, guaranteed for a maximum address-to-output delay of 500 nanoseconds.

SEC. 13.7 THE 1024 x 1 STATIC RAM (cont'd)

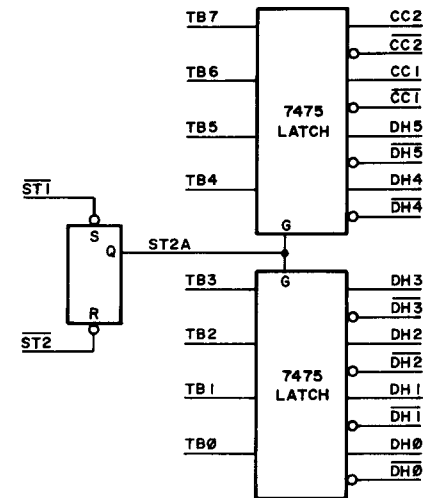


Fig. 13.7.5--Generating the $ST2A$ Strobe for Slow Memory Chips

 


Fig. 13.7.6--How the $ST2A$ Strobe Fits into the 8008's Main Timing

U.C. BERKELEY LABORATORY

SEC. 13.7 THE 1024 \times 1 STATIC RAM (cont'd)

Though manufacturers of 2102 RAMs may not be anxious to select devices based on their A9 and A8 access times, it is useful to the microcomputer designer to know about the practical margin of up to 100 ns between the chip's specified speed, and the speed needed in an 8008 system.

The above timing considerations relate to the way memory is addressed in 8008 systems. The 8008 outputs a low-order address first, then the high-order address a full clock cycle later. In an 8080 system, all 16 address bits become valid simultaneously, usually about the time $\phi 2$ is ending within T1 time. During T2 time, the CPU checks to see whether the memory requests a wait cycle; and at T3, the memory data transfers occur. Factors influencing memory access time in an 8080 system are discussed in Chapter 3 above.

SEC. 13.8 THE 4096 \times 1 DYNAMIC RAM

A number of 4K RAMs have been designed to date. It is not yet clear which designs are destined to become industry standards. The only thing that seems certain is that the single-transistor cell has been accepted as the most efficient design approach.

The key to the mass production of large memories using one-transistor cells is the use of on-chip differential amplifiers. The information read is compared with a voltage half-way between logic one and zero. In some designs, the actual value of the reference voltage is subject to the same process variables as the cell voltage levels. This means that process variations tend to cancel out. Another interesting design concept is to make the reference voltage depend on V_{cc} . The threshold voltage of the chip may be varied by changing the power supply voltage, thus testing the safety margins of the cells' voltage levels. The manufacturer can then test chips to pass given internal noise margin specifications.

The first single-transistor-cell 4K RAM designs to appear on the market were the Texas Instruments 4030 and the Mostek 4096. Both have already established a place in the 4K RAM market.

The major difference between the 4030 and 4096 is the number of pins on the package. Figure 13.8.1 shows the approximate relative size of the 22-pin and 16-pin packages. The 22-pin package terminals are on 400-mil dual-in-line centers, while on the 16-pin package the pin rows are 300 mils apart. The 22-pin package is about 1.1 inches long, while the 16-pin version is about 800 mils long. (Approximate dimensions are given because of variations in packaging style.)



microcomputer
design


SEC. 13.8 THE 4096 \times 1 DYNAMIC RAM (cont'd)

Fig. 13.8.1--Relative Size of 22- and 16-Pin Packages (Approx. 2 to 1)

4 K dynamic RAM designs usually use a six-bit multiplexer to switch the column address bits from the computer address bus to a memory refresh bus. (The refresh bus is usually connected to the outputs of a six-bit binary counter.) The Mostek designers decided that, since a 6 \times 2-bit multiplexer is required for the refresh circuit anyway, why not use a 6 \times 3-bit device and multiplex the twelve bit addresses onto the same six-bit bus. This design philosophy reduces the connections to the outside world, and also cuts in half the number of address drivers required.

The Mostek design also provides for TTL-compatible logic levels on all of the input and output terminals of the 4096. The 22-pin designs require a 12-volt swing on the chip enable pin. Still another advantage of the 16-pin design is that data is stored and read back in true logic form, while the data read from the 22-pin version is inverted from the data written. This last is particularly bothersome in small memory systems, which might otherwise be designed without any input or output buffering at all.

 

microcomputer
design

U.C. BERKELEY LIBRARY

SEC. 13.8 THE 4096 x 1 DYNAMIC RAM (cont'd)

| | MOSTEK 4096 | TI 4030 |
|--|------------------------------------|-----------------------------------|
| Pins on package | 16 | 22 |
| Chip enable voltage | TTL | 0, +12 |
| Address line drivers | 6 | 12 |
| Input to output data | true | inverting |
| Data inverters needed | none | 8 |
| Board area | less | about 50% more |
| Refresh circuitry needed | . . . about the same . . . | |
| Other manufacturers, second sources | Fairchild, Electronic Arrays | Intel, MIL, and many others |

Fig. 13.8.2--Comparison Between 16- and 22-Pin 4 K RAMs

Texas Instruments produces the 4050, an 18-pin 4K RAM, and a 4060--which is like the 4030, except with V_{bb} specs of -5 volts. Mostek has gone with $V_{bb} = -5$ V, and Intel second-sources this 16-pin 4K RAM version.

It is possible to read convincing claims that both the 16-pin 4K RAM, and the 22-pin 4K RAM, are *the* industry standard, each in exclusion of the other. The market in question includes large computer mainframes, the expectation being that the 4K RAM will finish off core memory. However, acceptance of 4K RAMs has been slower than initially expected--partly because of the lack of agreement on an industry standard device. Already the focus has shifted to the 16K RAM, being delivered in prototype quantities as this book went to press.

Note that TI offers an 18-pin 4K RAM package. But because the 16K RAMs now being delivered are in 16-pin packages, the 18-pin design seems unlikely to gain wide acceptance.



microcomputer
design

SEC. 13.9 TRANSPARENT DYNAMIC RAM REFRESH

Dynamic RAM arrays may be refreshed in a microcomputer without causing the CPU to halt, wait, or otherwise pause. A *transparent* refresh circuit works by inserting memory-refreshing cycles into gaps in CPU timing without disturbing the flow of processor instructions.

With an 8008, the key is to use the CPU's bidirectional data bus during T3B time. This is that portion of the T3 state immediately following T3A time; or, in other words, the second half of T3 time.

Since the $\overline{ST3}$ strobe occurs during T3B time, and this strobe (or a derivation of this strobe) is used when writing into memory during PCW cycles, memory cannot be refreshed at PCW-T3B time. Thus a new signal is defined, $E3B$, which is equal to $T3B \cdot \overline{PCW}$.

A practical RAM refresh circuit is implemented by scanning the low-order address bits while the chip is disabled, but in the WRITE mode. This scanning may be accomplished by driving a three-state binary counter onto the BB bus, and latching the DL register during E3B time. Between each E3B refresh cycle, the three-state counter is incremented.

Since the CPU has already completed its use of the DL register by E3B time, there will be no conflict between program execution and RAM refresh.

Figure 13.9.1 shows the memory refresh address counter. Other circuitry necessary includes a strobe and some gating to load the DL register at E3B time; gating to continue the refresh during the STOPPED state, if necessary; and specialized refresh driving circuitry suited to the design of the dynamic RAM chips being employed.

In an 8080 computer, transparency may not be complete, depending on the speed of the processor and the refresh time required by the memory. A convenient gap in processor timing occurs during the T4 state of an M1 (instruction fetch) machine cycle. The refresh circuit should request a hold from the 8080 during the M1 cycle; the 8080 acknowledges this request, floating its address and control busses, allowing the refresh controller to address memory and perform the desired refresh cycling. Since only internal data transfers take place during T4 and T5 time, the CPU will continue through these cycles. If refresh is accomplished quickly, then the processor can be allowed to return to normal operation without skipping a beat. Otherwise a machine cycle will be taken up by the refresh circuitry.

The designer should study the hold timing chart in the 8080 data sheet. See also the 471 data sheet, Sec. 1.9.



microcomputer
design

SEC. 13.9

TRANSPARENT DYNAMIC RAM REFRESH (cont'd)

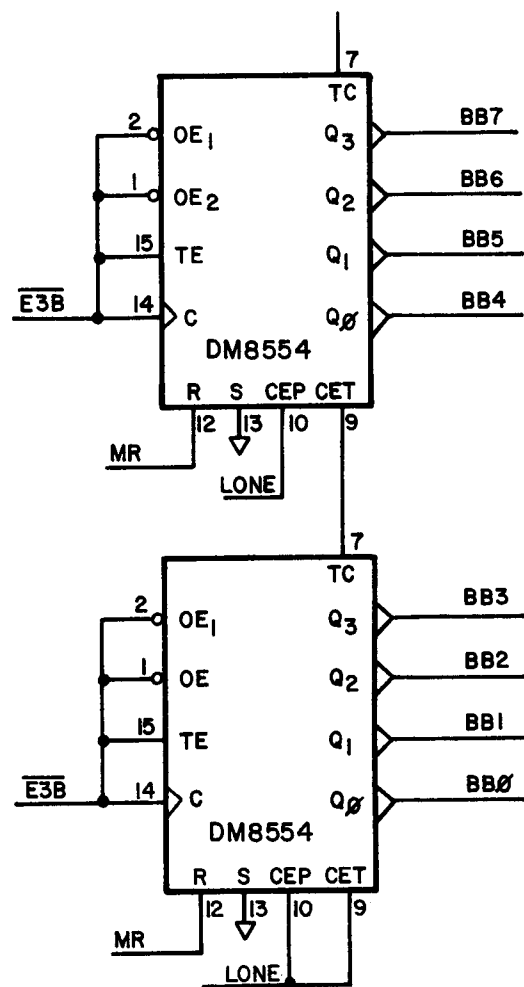


Fig. 13.9.1--Memory Refresh Address Counter



microcomputer
design

SEC. 14.1 ROMS AND OTHER MEMORIES

While core memories are being replaced by solid state memories in more and more data storage applications, it is easy to forget a prime advantage of these magnetic devices. That is, core can both be read from and written into quickly at speeds compatible with data processing needs, and can also retain information in the stored magnetism of the individual core elements when the system power supply is turned off.

With semiconductor memories, as indicated in the previous chapter, the designer chooses between RAM and ROM. Random access memory (RAM) has only one of the capabilities of core memory--fast reading and writing--but not the other, non-powered storage. The read-only memory (ROM) retains its information even when power is not applied, but is not easily changed (written into) during normal computer operations. There is little doubt that RAM memories--random access nonvolatile devices--will eventually become available. However, practical microcomputer designs at present depend on ROM and RAM.

A typical microcomputer system contains a block of ROM where instructions and data are stored permanently, and another block of memory, made up of RAM, which is used for temporary storage. Because these two types of memory are separate, rather than intermingled, the instructions found in microprocessors are somewhat different from those used in computers based on core memory. A very specific example would be an instruction like *Store Forward 77*, which might be found in a core-based minicomputer. This instruction causes a digital word to be addressed at a location which is 77 (octal) locations forward with reference to the current program counter location. In a microcomputer, since there are two different types of memory--one of which cannot be written into--this kind of relative memory addressing is not practical. In the 8008, for example, memory is always referenced through address pointers (H and L) and instructions like *LMA* are found in the instruction set.

Though a small microcomputer can conceivably do without any RAM at all, it must have at least a small amount of ROM--at least when general-purpose microprocessors like the 8008 and 8080 are used. Without ROM, the microprocessor could not be programmed at all. This chapter presents some practical ROM designs, starting with the very small.



microcomputer
design

SEC. 14.1 ROMS AND OTHER MEMORIES (cont'd)

| TYPE OF MEMORY | DESCRIPTION |
|----------------|---|
| CORE | Magnetic core memory. Non-volatile: retains data without power. Each bit or word alterable. |
| RAM | Semiconductor random access memory. Volatile: needs power to retain data. Each bit or word alterable. |
| ROM | Mask-programmed read-only memory. Non-volatile: retains data permanently. Programmed at IC factory. Not alterable. |
| F/ROM | Field-programmable read-only memory. Non-volatile. May be programmed after packaging. Once any given bit is altered from its original state, cannot be re-altered. |
| RePROM | Reprogrammable ROM (light-erasable). Non-volatile. May be programmed after packaging. Once any given bit is altered from its original state, cannot be re-altered by the PROM programmer. All of the bits may be erased simultaneously to the original logic zero state by exposing the chip to UV light. |
| E/PROM | Electrically erasable version of RePROM. |
| EAROM | Electrically alterable ROM. Non-volatile. Bits individually alterable. |
| RAN | Random access non-volatile memory. Core replacement. |

Fig. 14.1.1--Types of Memory



SEC. 14.2 DIODE PROGRAMMABLE ROMS (DiROM)

A simple ROM array can be constructed using TTL decoder circuits and diodes. The program can be changed easily merely by removing and adding diodes. The circuit shown in Figure 14.2.1 provides sixteen bytes of DiROM.

One sixteen-pin DIP socket is dedicated to each memory location. The eight pins on one side of the socket are all connected to one of the output lines of the 74154 decoder. The eight pins on the other side of the socket are connected to the eight separate data bus (BB) lines of the microcomputer. When using an 8008 or 8080, the BB lines should be provided with pullup resistors in the range of 10K to 22 K ohms which define the logic high state on the BB bus. The zero state is defined by the presence of a diode at the selected output address of the decoder, opposite the BB bit in question. If location 16₈ were read from the circuit shown in Fig. 14.2.1, the result would be a binary 01111111 on the BB bus.

Though handy in breadboarding and prototyping, this design is hardly cost-effective in production, of course. Another limitation has to do with the logic LOW input voltage requirements of the microprocessor. For example, the 8008 is specified to recognize a voltage of $V_{cc} - 4.2$ volts, or 0.8 volts, as the logic low voltage. Germanium diodes would have to be used for assurance that the 0.8-volt limit was not being exceeded. In practice silicon diodes are adequate for breadboards to be tested at room temperature. However, *this design is recommended only for prototyping, in low-noise environments.*

SEC. 14.3 FIELD-PROGRAMMABLE ROMS (F/ROMS)

14.3.1 F/ROMS The field-programmable ROM can be programmed electrically after the IC is packaged. Most F/ROMs incorporate a matrix of tiny fuses which may be blown out selectively to produce the desired bit pattern of ones and zeros. Most F/ROMs initially contain all zeros, and programming permanently stores ones in the locations where fuses have been blown. The voltages required to program the F/ROM differ from type to type.

For eight-bit microprocessors, F/ROMs with an eight-bit output structure are most convenient. 32 x 8 F/ROMs are often used for program storage, and especially for system characterization. That is, a line of similar machines may contain identical circuitry, with *system definition* provided by a large ROM or PROM. Those relatively few key variables which allow the implementation of special options--*system characterization*--are stored in the F/ROM, where they can easily be changed in the plant or in the field.



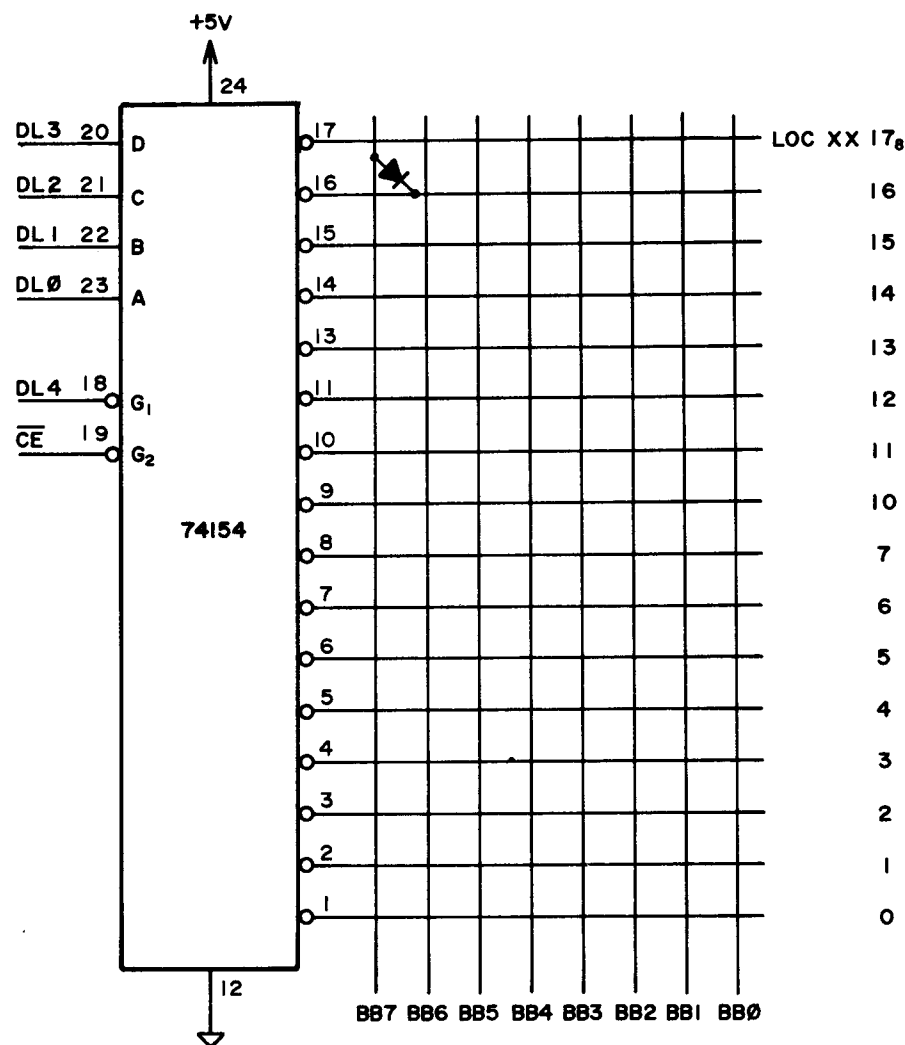
SEC. 14.2 DIODE PROGRAMMABLE ROMS (D \bar{L} ROM)

Fig. 14.2.1--16 Byte Diode-Programmable ROM

SEC. 14.3 FIELD-PROGRAMMABLE ROMS (F/ROMS) (cont'd)

14.3.1 F/ROM Programmers A F/ROM programmer circuit is very useful when a microcomputer must be reprogrammed in the field. A complete design should both program the desired bit locations, and then verify the F/ROM contents. The design discussed here is a microcomputer peripheral. That is, it may be placed in the cabinet housing the microcomputer. The F/ROM to be programmed is inserted into a socket on the programmer. The programmer uses the microcomputer to select the F/ROM locations to be programmed and verified, and is thus much more convenient to use than a bit-by-bit or byte-by-byte stand-alone programmer.

The programmer is more easily designed if programming may be accomplished mainly with voltages which are within TTL levels. The programmer circuitry may be composed mostly of TTL devices; the chance of circuit failure is decreased, and the verifying circuitry is simplified. F/ROMs which come from the factory as all logic zeros usually require a voltage larger than V_{cc} to be applied to output terminals during programming. But easier to design with are those F/ROMs which start out as all zeros, and require the programmed output to be held near *ground* during programming.

Figure 14.3.1 shows the circuit diagram for a F/ROM programmer designed for use with the TI 74S288 32 x 8 F/ROM. In the steps below, a sample programming sequence is given which describes the operation of the circuit. The notation used is for an 8008 microprocessor.

- (1) The F/ROM location to be programmed is read to determine its present state. The proper location must be addressed, the chip's three-state outputs must be enabled, and chip V_{cc} must be set to its normal TTL level of about +5 volts. First, the A register is loaded: the five low-order bits (A4 through A0) contain the F/ROM location. A5 is low to enable the F/ROM. A6 is low. A7 is low to set the V_{cc} to +5 volts. An *Output 35* instruction is executed, which strobes the 74273 eight-bit latch. The 7416 inverting open-collector buffers at Q7 pull current through the 5.6-V zener and a series diode, setting the voltage at the base of the NPN power darlington stage at about 6.3 volts. This value is dropped through two diode drops and powers the F/ROM.
- (2) The microcomputer executes an *Input 5* instruction, which activates an array of 74126 three-state buffers and places the F/ROM word for the address previously selected on the microprocessor input bus. The contents of the F/ROM may be compared with the desired contents and if equal the programming of this word may be skipped.

SEC. 14.3 FIELD-PROGRAMMABLE ROMS (F/ROMS) (cont'd)

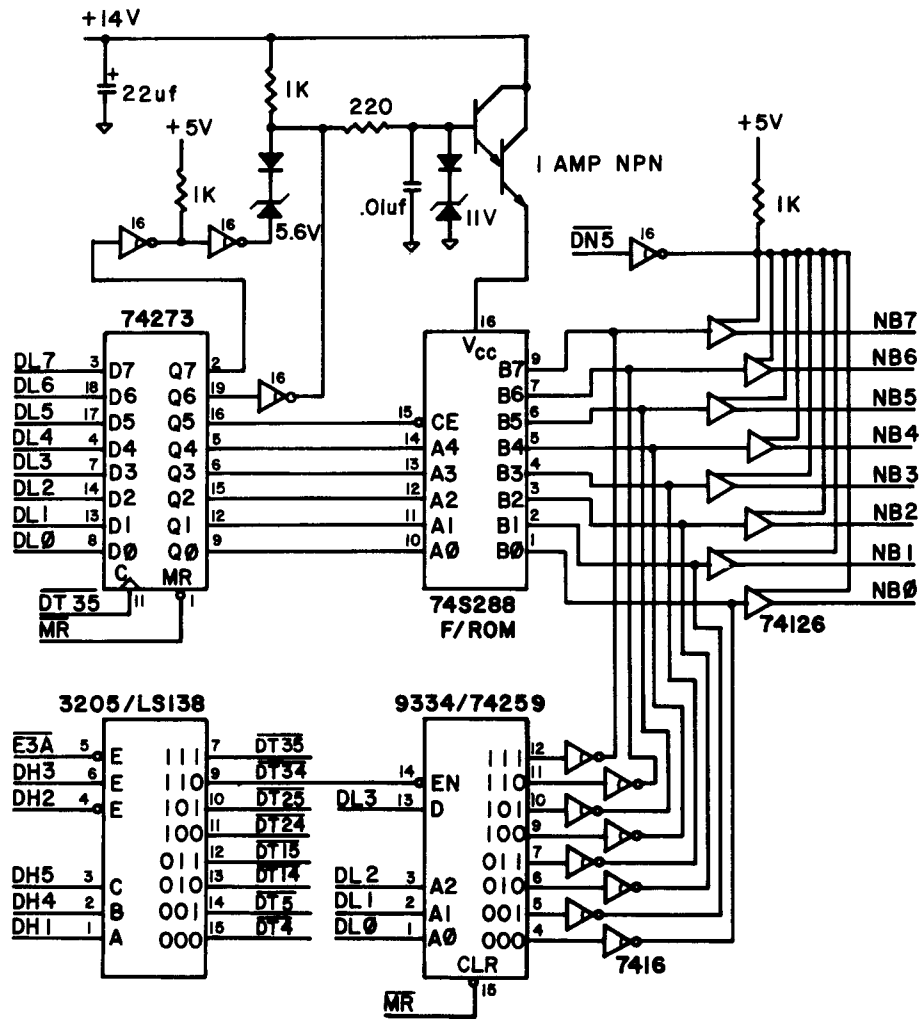


Fig. 14.3.1--F/ROM Programmer for the 74S288



SEC. 14.3 FIELD-PROGRAMMABLE ROMS (F/ROMS) (cont'd)

| | | | |
|---------|---|------------------------|---------------------------|
| | | DT 35-7 | |
| | | 0 | 1 |
| DT 35-6 | 0 | V _{cc} = +5 V | V _{cc} = +12.5 V |
| | 1 | V _{cc} OFF | V _{cc} OFF |

| | | |
|---------|---|---------------|
| DT 35-5 | 0 | ENABLE F/ROM |
| | 1 | DISABLE F/ROM |

| DESCRIPTION | |
|-------------|--------------------------|
| DT 35-4 | HIGH-ORDER F/ROM ADDRESS |
| DT 35-3 | F/ROM ADDRESS BIT |
| DT 35-2 | F/ROM ADDRESS BIT |
| DT 35-1 | F/ROM ADDRESS BIT |
| DT 35-0 | LOW-ORDER F/ROM ADDRESS |

Fig. 14.3.2--F/ROM Programmer OUTPUT 35 Bit Assignments



SEC. 14.3 FIELD-PROGRAMMABLE ROMS (F/ROMS) (cont'd)

- (3) The F/ROM may now be programmed, one bit at a time. The bit to be programmed is addressed by setting up its address in the three low-order bits of the A register then performing an *Output 34* instruction. A3 is set to LOW to program the addressed bit to zero. The selected output of the 9334/74259 addressable latch remains high until another *Output 34* instruction is performed. The selected output bit is pulled down near ground by the 7416 inverting open-collector buffer. More than one latch output can be high at any one time, but care must be taken not to overload the power supply or overheat the F/ROM.
- (4) The F/ROM V_{cc} is now increased to +12.5V so as to swamp an internal protective zener diode and provide enough current to blow the fuse for the bit to be programmed. Up to 750 MA is required. This is done by setting the five low-order bits of the accumulator to the correct F/ROM location (as in step 1), and executing an *Output 35* instruction. This time, however, the chip should be disabled: A5 should be high. A6 should be low. A7 should be high, which allows the 1 K ohm resistor to pull up to +14 v, charging the 0.01 microfarad capacitor. The NPN darlington stage ramps V_{cc} up to about 12.5 volts.
- (5) Within 10 microseconds to 1 millisecond after V_{cc} has reached 12.5 volts, the F/ROM should be enabled. Another *Output 35* instruction is executed, the settings remaining the same except that A5 should be low.
- (6) One millisecond later, A5 is toggled once again; another *Output 35* instruction is performed; and the F/ROM is disabled. The microcomputer may develop this time delay by using an interval timer (Chapter 18) or by executing a software loop calculated to take the required time.
- (7) Within 10 microseconds to 1 millisecond later after the F/ROM is disabled, V_{cc} should be returned to +5 volts by running another *Output 35* instruction, with the high order bit set low.
- (8) Within 10 microseconds to 1 millisecond after V_{cc} returns to +5 volts, the F/ROM is once again enabled by toggling bit 5 of the accumulator and running an *Output 35* instruction. Then an *Input 5* instruction is executed in order to test the programmed bit.

SEC. 14.3 FIELD PROGRAMMABLE ROMS (F/ROMS) (cont'd)

- (9) Before programming another bit, the program should wait a certain period of time to keep the F/ROM from burning up. V_{cc} should not remain at +12.5 volts for more than 10% of the total programming cycle. In order to further cool the chip, V_{cc} should be removed altogether between bit-programming times. This is done by performing an *Output 35* instruction with bit 6 high, which clamps V_{cc} near zero.
- (10) If step 8 above reveals that the bit did not program, steps 4 through 8 may be repeated for that bit, allowing the proper delay described in step 9 to avoid over-heating. If it once again fails to program, steps 4 to 8 may be repeated once again, this time applying +12.5 volts for 50 to 75 milliseconds. The +12.5-volt 10% duty cycle still must not be exceeded--that is, the corresponding wait time between programming bits must also be increased.
- (11) Once programming is accomplished for the bit originally selected, another bit may be programmed, using steps 1 through 10. Changing the bit to be programmed (step 3) requires two *Output 34* instructions. The first such instruction addresses the old bit number, but the accumulator is first set so that A3 (the 9334 D input) is low. This turns off the latch for the old bit. Then the accumulator points to the new bit address, setting the latch data input high, and performs another *Output 34*. Now the new bit address is ready, and the programming procedure may be resumed, starting with step 4.

Note that, when the microcomputer is first turned on, a master reset pulse will cause the addressable latch to output all zeros. The eight-bit latch points to location zero, the F/ROM is enabled, and V_{cc} is +5 volts.

A chart showing output bit assignments for the F/ROM programmer appears in Figure 14.3.2.

SEC. 14.4 REPROGRAMMABLE PROMS

The reprogrammable PROM has achieved wide popularity. A typical example is the 1702A, a 2 K RePROM in a 256 x 8 configuration. This ROM is very useful in the breadboarding stages of eight-bit microcomputer development. In the low-volume applications, the 1702A is popular even though F/ROMs like the 74S471 may be less expensive and take up less PC board area. One advantage of the 1702A is the availability of the 1302 ROM, a



SEC. 14.4 REPROGRAMMABLE PROMS

mask-programmable chip which is a direct plug-in replacement for the 1702A, and may be substituted when a design is finalized and high-volume production begins.

The 1702A is electrically programmable using a programmer of medium complexity, requiring a relatively high-voltage power supply. For this reason, programming of these chips is usually accomplished in the lab, or at centralized facilities. Suitable RePROM programmers are available from several sources, and may be purchased as accessories to microcomputer prototyping equipment sold by the microprocessor manufacturers.

The 1702A is erased to an all-zero state with an ultraviolet light source.

SEC. 14.5 COMPARISON OF ROM TYPES

The intended application will determine which type of ROM is most suitable. Figure 14.5.1 illustrates some of the many factors that influence the decision. Naturally the choice is most difficult in low-volume microcomputer production, when the cost of a mask-programmed ROM is not clearly justified.

| Symbol | DiROM | F/ROM | RePROM | ROM |
|--|-------------------------------------|---------------------------------------|----------------------------------|----------------------------------|
| Name | Diode-Programmable Read-Only Memory | Field-Programmable Read-Only Memory | Re-Programmable Read-Only Memory | Mask-Programmed Read-Only Memory |
| Number of locations for which ROM is practical | Small | Small-medium | Small-medium | Small-large |
| Efficiency, bits per package size | Low | Medium | Medium | Medium-high |
| Extra costs | Spare diodes | Programmer | Programmer, UV eraser | Mask charge |
| Power supplies | +5 V | +5 V to run; +12 V or more to program | +5 V, -9 V; +48 V to program | +5 V |
| Cost of programmer | Nothing | Inexpensive | Somewhat costly | Inapplicable |

Fig. 14.5.1--Some Considerations When Choosing Type of ROM to Be Used



microcomputer
design

SEC. 14.6 THE ROMIN OPTION

14.6.1 Flexible Memory Referencing There are two basic ways in which to load one of the 8008's internal index registers from memory. The first is to use the *LrI* instructions. These instructions are good mainly for handling constants stored in ROM as part of the program, and do not constitute a very flexible method for loading memory. The second way is to use the *LrM* instructions. These load the register *r* with the contents of the location in memory addressed by the H and L registers. This method is more flexible, but may still be somewhat cumbersome because the H and L registers must constantly be manipulated.

The improved instruction set designed into the 8080 microprocessor allows the A register to be loaded from memory locations which are addressed either by the B and C registers, or by the D and E registers, in a manner similar to the use of the H and L registers. Although these added instructions can be used only to load the A register, the added flexibility is a great advantage when moving a block of data. One pair of registers (e.g. D and E) points to where data is being picked up, and the other pair of registers (e.g. H and L) points toward the RAM location where the data is being placed.

With the 8008 this flexibility is not automatically available. Several options are available, however, to help make up for this deficiency. The *RAM-PAGE* option described in Chapter 13 is often helpful in small systems, since that option eliminates having to manipulate the H register when addressing RAM. But *RAM-PAGE* is no help in systems requiring more than one page of RAM.

Another useful design idea for increasing memory-addressing flexibility in an 8008 system is the *ROMIN* option. Essentially, ROM is treated as an input port, and a conditional input approach allows the A register to address the memory.

14.6.2 Implementing the ROMIN Option With the *ROMIN* option, a system may reference memory in either of two ways. The first is through the normal method: using the *LrM* or *LrI* instructions in conjunction with the H and L registers. The second is by using input (*INP*) instructions. While 8008 systems are usually designed so that memory may be referenced only during *PCI* (instruction fetch) and *PCR* (memory read) cycles, systems with the *ROMIN* option also permit memory to be read during *PCC* (I/O command) cycles.



microcomputer
design

SEC. 14.6 THE ROMIN OPTION (cont'd)

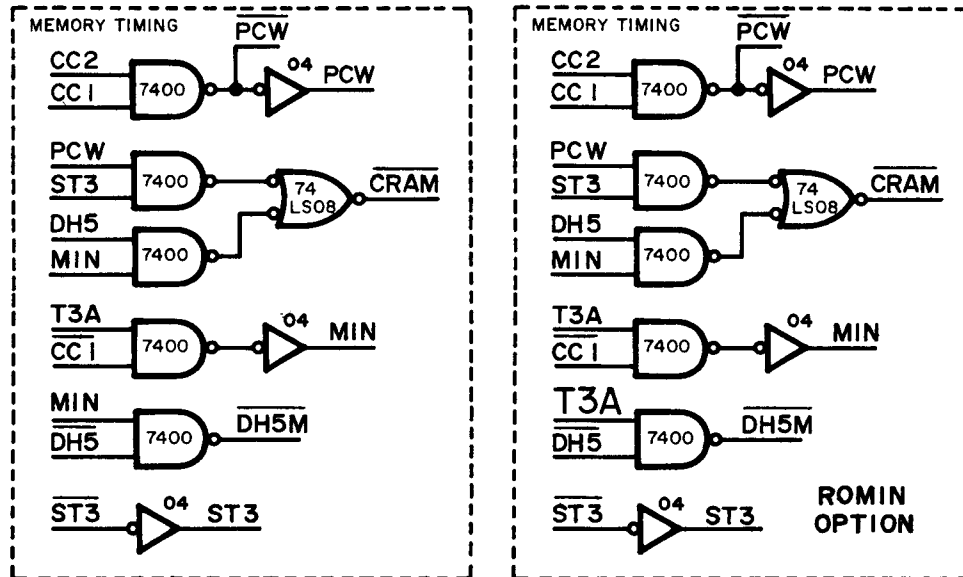


Fig. 14.6.1--Original MIKE 4 Memory Timing; ROMIN Option Modification

The memory timing circuitry for the MIKE 4 (see Chapter 26) has been reprinted in Figure 14.6.1. For comparison, the circuit has been modified for the *ROMIN* option. Note how easily *ROMIN* may be implemented. Only one wiring change has been made.

In the original circuit, $\overline{DH5M}$ ($\overline{DH5}$ modified) is generated by NANDing $\overline{DH5}$ with \overline{MIN} . \overline{MIN} is a timing signal which is active (i.e., high) during PCI-T3A and PCR-T3A times. $\overline{DH5M}$, in turn, is used to enable ROM. (See Chapter 26 for elaboration.) Thus ROM may be enabled during PCI cycles (ROM as source of program instructions) or PCR cycles (ROM as source of data read from memory).

With the *ROMIN* option, the $\overline{DH5M}$ signal which enables ROM is created using T3A, rather than \overline{MIN} . T3A is active not only during PCI and PCR cycles, but also during PCC cycles. (As explained in Chapter 5, the T3A signal is disabled during PCW cycles.) This change permits ROM to be read during input instructions (whence *ROMIN*).

SEC. 14.6 THE ROMIN OPTION (cont'd)

It turns out that INP 000, INP 001, INP 002, and INP 003 will read ROM using the above circuit, because of the bit combinations of DH5, DH4, and DH3 which may occur. If the resultant limitation in the use of input instructions is overly stringent, the designer might expand the input port array with the conditional input concept (Chapter 8).

A memory map is shown in Figure 14.6.2. Note that the chart shows that the four input instructions reference four pages in ROM.

| PAGE NUMBER | USAGE | PAGE NUMBER | USAGE | PAGE NUMBER | USAGE | PAGE NUMBER | USAGE |
|-------------|-------|-------------|-------|-------------|--------|-------------|--------|
| 077 | RAM | 057 | RAM | 037 | ROM #3 | 017 | NO ROM |
| 076 | | 056 | | 036 | (OPT.) | 016 | HERE |
| 075 | | 055 | | 035 | | 015 | |
| 074 | | 054 | | 034 | | 014 | |
| 073 | | 053 | | 033 | | 013 | |
| 072 | | 052 | | 032 | | 012 | |
| 071 | | 051 | | 031 | | 011 | |
| 070 | | 050 | | 030 | | 010 | |
| 067 | | 047 | | 027 | ROM #2 | 007 | ROM #0 |
| 066 | | 046 | | 026 | (OPT.) | 006 | |
| 065 | | 045 | | 025 | | 005 | INP 2 |
| 064 | | 044 | | 024 | | 004 | |
| 063 | | 043 | | 023 | | 003 | INP 1 |
| 062 | | 042 | | 022 | | 002 | |
| 061 | | 041 | | 021 | | 001 | INP 0 |
| 060 | | 040 | | 020 | | 000 | |

Fig. 14.6.2--Memory Map for MIKE 4 with ROMIN Option

14.6.3 Programming with ROMIN The *ROMIN* option permits an input instruction to address memory. The high-order memory address (DH5 through DH0) is defined by the code for the input instruction itself, which (in binary form) is 01 00M MM1 (where MMM defines which one of the eight input instructions is being executed). Since the DH0 bit is always logic one, only odd-numbered pages of memory may be referenced by a *ROMIN* input instruction. The low-order memory address bits are simply set up in the A register before executing the input instruction. This is possible because, as with all I/O instructions, the A register is transferred to the DL register during PCC-T1 time.

SEC. 14.6 THE ROMIN OPTION (cont'd)

PURPOSE OF PROGRAM: LOAD CONTENTS OF MEMORY AT LOCATION 003125
INTO A REGISTER

| METHOD #1 | METHOD #2 (ROMIN) |
|------------|-------------------|
| LHI 003 | LAI 125 |
| LLI 125 | INP 001 |
| <u>LAM</u> | <u> </u> |
| (5 bytes) | (3 bytes) |

Fig. 14.6.3--Simple ROMIN Program Comparison



microcomputer
design

SEC. 15.1 DIRECT MEMORY ACCESS

Regardless of how fast a microprocessor or minicomputer may be, there is some high-speed peripheral which requires data at a rate which is too fast for the CPU, or which takes up too much of the CPU's time. *Direct memory access (DMA)* can effectively increase the speed of the computer in handling blocks of data, and is therefore very useful in microcomputer systems where a fast peripheral puts a strain on the capabilities of the microprocessor.

A computer with DMA can write data into memory, or read from it, without separate input or output instructions for each byte. For example, a peripheral may be connected to DMA hardware, with the DMA circuitry under control of the CPU. A typical instruction to the DMA controller might be "read in 32 bytes from the first sector of the floppy disc, and place them in memory, starting at location 007000." After the microprocessor gives this command to the DMA controller, it continues to execute its normal flow of instructions. The DMA system provides a flag (input bit) which the CPU may interrogate periodically to find out whether the job has been completed. Another alternative is to have the DMA controller create an interrupt when its job is done.

It is not the purpose of this chapter to describe all of the various DMA techniques which the designer may develop. Instead, the ways of obtaining direct access to memory in 8008 and 8080 microcomputers are described.

SEC. 15.2 DMA WITH THE 8080

The address bits on the 8080 chip use three-state output circuitry. The DMA controller is connected to the HOLD terminal of the 8080, as shown in Figure 15.2.1. When the HOLD line is brought high, the CPU will acknowledge with a logic one on the HLDA output. The CPU address and data bus will be floating in the high-Z state by the end of the next ϕ_2 pulse after HLDA goes high. Once the 8080 address lines are floating, the address lines coming from the DMA controller may be enabled. This circuit allows the DMA system to gain access to both the memory address bus and the memory input and output data.

The 471 data sheet, near the end of this book, includes basic information on the 8080 hold function (Sec. 1.9).



microcomputer
design

SEC. 16.2 INITIAL INTERRUPT (cont'd)

In the 8080, an interrupt is not used to initialize the CPU. Instead, the RESET input is used; this terminal clears only the 8080 PC register. All other internal registers must be initialized through software. (See the 471 data sheet near the end of the book, Sec. 1.7.)

SEC. 16.3 HOW THE INTERRUPT IS USED

The program which the microcomputer enters through the initial interrupt, which contains the instructions normally executed by the microcomputer in carrying out its principal functions, is called the *mainline program*. When an interrupt occurs, the microprocessor finishes its current instruction, and then allows an extra instruction to be inserted (*jammed in*). This extra instruction is usually a RESTART instruction which *calls* a subroutine in memory; that is, the CPU jumps from its location in the mainline program to the location where the subroutine is stored. The interrupt subroutine is said to *service* the interrupt which caused that subroutine to be called. For example: typing a key on a keyboard may cause an interrupt, which calls an interrupt subroutine for processing keyboard characters. The interrupt subroutine *services* the keyboard by inputting the character typed, and storing it into a list of typed characters in RAM. Then the subroutine returns to the mainline program. Depending on the design of the system, either the mainline program, or another interrupt routine, picks up the characters stored in RAM for further processing later on.

The use of the microprocessor's interrupt capability is an important element in the overall design of the system. Whether interrupts are used at all, or one interrupt level is used, or a number of interrupt levels are used, depends on the application for which the microcomputer is intended. An example of the choices involved is illustrated by the two approaches for adding a keyboard input to a microcomputer which are discussed in this book. In Chapter 21, the microprocessor periodically checks

SEC. 16.3 HOW THE INTERRUPT IS USED (cont'd)

for new keyboard data, and a FIFO provides some temporary keyboard data storage. This approach avoids some of the complications of dealing with interrupts. In Chapter 26, the *MIKE 4* microcomputer has a similar keyboard input, but each new keyboard character interrupts the microcomputer. Chapter 17 gives several design examples for interrupt systems, concentrating on the means of saving status during interrupts. Note in these examples that the system design frequently involves tradeoffs between software complexity and added hardware. The interrupt feature is often an important element in the design.

SEC. 16.4 SYNCHRONIZING INTERRUPT REQUESTS (8008)

The 8008's interrupt line is strobed into two different parts of the CPU's internal circuitry. The interrupt strobe takes place on the falling edge of $\phi 1$. If the interrupt signal changes state shortly before that time, one section of the CPU might recognize the request, and another part not. For this reason 8008 interrupts must be synchronized with external circuitry to $\phi 2$, or to the rising edge of $\phi 1$.

The 8080 contains its own internal interrupt synchronization.

SEC. 16.5 SIMPLE INTERRUPTS

One example of a simple interrupt system is a microcomputer where an interrupt is recognized only when the CPU is in the STOPPED state. This is suitable when the interrupt request need not be serviced immediately when the demand arises. Even in very complex systems, of course, an interrupt will not be serviced immediately, if a higher priority interrupt is already being processed.

If the main line program can be interrupted only at certain points during its execution, the problems associated with having to save internal microprocessor status, during execution of the interrupt, are minimized. (See Chapter 17 on saving status.)

In Figure 16.5.1, part (2), a flip-flop is connected between an interrupt source and the interrupt terminal of the CPU. An interrupt request will be passed on to the CPU only when the CPU halts before the request was received. In an 8008 system, the HALT condition is decoded in the state decoder circuitry (Ch. 5) as a string of pulses, produced by $\phi 2$ or $\phi 1$; these pulses will permit the request to be passed on very shortly after it occurs. In an 8080 system, the signal HLTA (halt acknowledge) could be combined with PH2T to produce a similar pulse train for use in this circuit.



SEC. 16.5 SIMPLE INTERRUPTS (cont'd)

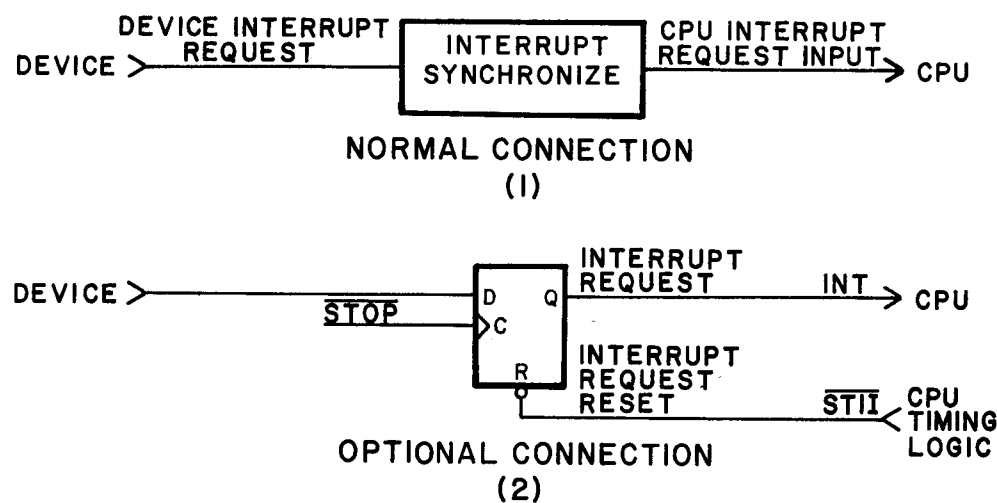


Fig. 16.5.1--Flip-Flop Prevents Interrupt from Being Served Until a HALT Instruction is Executed

The CPU acknowledges that it has been interrupted with an INTERRUPT REQUEST RESET signal. The INTA signal is used with the 8080; in an 8008, STII is used.

Note that in an 8008 system, the STOP strobe is related to $\phi 2$ of the 8008 clock, avoiding the interrupt race problem mentioned above.

SEC. 16.6 INTRODUCTION TO PRIORITY INTERRUPT SYSTEMS

A microcomputer which is able to recognize interrupts from more than one source is called a *multiple interrupt* system. A system with two or more interrupt sources generally requires a method for assigning priorities as to which interrupt request should be acted upon first. A *priority interrupt system* arranges multiple interrupts in a hierarchy so that each interrupt has a certain level of importance.

Each interrupt is assigned to a given *priority level*, and when a program is being executed as the result of a particular interrupt, the microcomputer is said to be *on* that interrupt level.

SEC. 16.6 INTRODUCTION TO PRIORITY INTERRUPT SYSTEMS (cont'd)

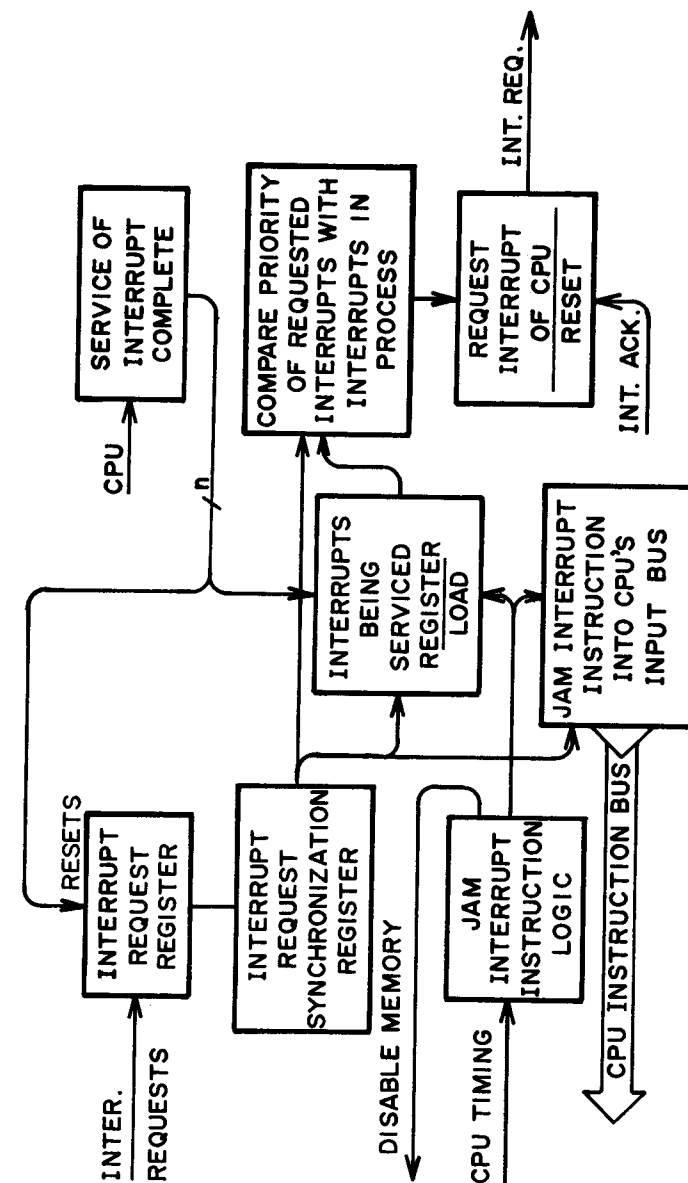


Fig. 16.6.1--Block Diagram of Priority Interrupt System

SEC. 16.6 INTRODUCTION TO PRIORITY INTERRUPT SYSTEMS (cont'd)

In the examples given in this chapter, interrupt level number 0 has the highest priority; levels with larger numbers have successively lower priorities. If the microcomputer is executing a program on interrupt level 2, a new interrupt on levels 1 or 0 should be recognized--the program should jump to the higher-priority interrupt (returning to interrupt level 2 later on). A level 2 interrupt cannot, however, be interrupted by level 3 or 4 interrupts, or by any other lower-priority requests. The system is designed so that a new interrupt on the same level as that already being executed will *not* be recognized.

The basic parts of a priority interrupt system are shown in Figure 16.6.1. Each element is described below.

SEC. 16.7 INTERRUPT REQUEST REGISTER

The original source of an interrupt may be an interval timer, a simple pushbutton switch, or a peripheral device. The *interrupt request* signals are fed into an *Interrupt Request Register*, an array of latches--one for each interrupt input. The purpose of this register is to store interrupt requests temporarily, since the microprocessor may not be able to service any given interrupt request immediately. Each interrupt latch is reset when the CPU finishes servicing that particular interrupt level.

A design for an Interrupt Request Register is shown in Figure 16.7.1. The register is made up of D flip-flops, one for each interrupt level. Though the drawing shows only two such latches, eight are required for a full eight-level priority interrupt system (four 7474 packages). Each flip-flop may be set on the rising edge of an interrupt request pulse (labeled REQ 0, REQ 1, etc.). Each is *reset* by an active-low *RET* signal which indicates that the microprocessor is *returning* from that interrupt level, having finished executing the designated subroutine. Note that MR also *sets* flip-flop #0; this is the only one so connected; see Sec. 16.12.

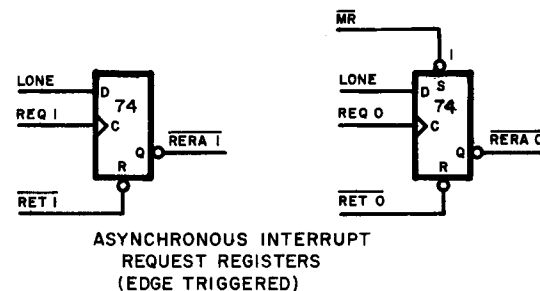


Fig. 16.7.1--Edge-Triggered Interrupt Request Register



SEC. 16.7 INTERRUPT REQUEST REGISTER (cont'd)

An asynchronous Interrupt Request Register triggered by negative pulses is shown in Figure 16.7.2. Again, only two latches are shown; more are required for a full-scale priority interrupt system. An eight-level system requires eight flip-flops (two 74279 packages). Note that half of the flip-flops in the 74279 package have a second reset terminal, which may be connected to a master reset signal, thereby reducing the number of instructions required at *power-on* to initialize the system. Note also that flip-flop #0 is *set* by MR, not reset, to provide the initialization interrupt.

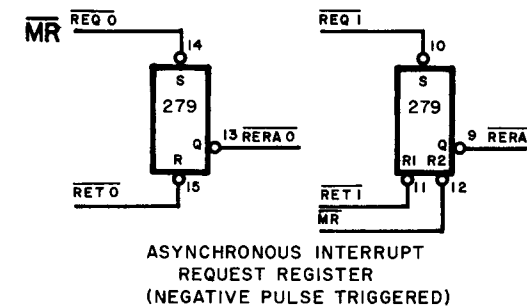


Fig. 16.7.2--Negative-Pulse Interrupt Request Register

SEC. 16.8 INTERRUPT REQUEST SYNCHRONIZATION REGISTER

The flip-flops within the Interrupt Request Register may be set at any random time. To prevent race conditions from occurring in the rest of the priority interrupt circuitry, an *Interrupt Request Synchronization Register* is required.

The least complicated kind of synchronization register is a strobed latch with sufficient bit capacity for the number of interrupt levels being handled. An eight-bit example is the 74273 in Figure 16.17.1 below.

SEC. 16.9 PRIORITY ENCODERS

A system with two or more interrupt sources generally requires a method for assigning priorities as to which interrupt request should be acted upon first. Since the heart of a *priority interrupt* system is a *priority encoder*, this device is introduced here. The easiest



SEC. 16.9 PRIORITY ENCODERS (cont'd)

way to understand the function of a priority encoder is to see how it may be connected so as to reverse the action of an ordinary decoder. Figure 16.9.1 shows a 74138/3205 three-to-eight decoder with its outputs connected to the inputs of a 74148/9318 priority encoder.

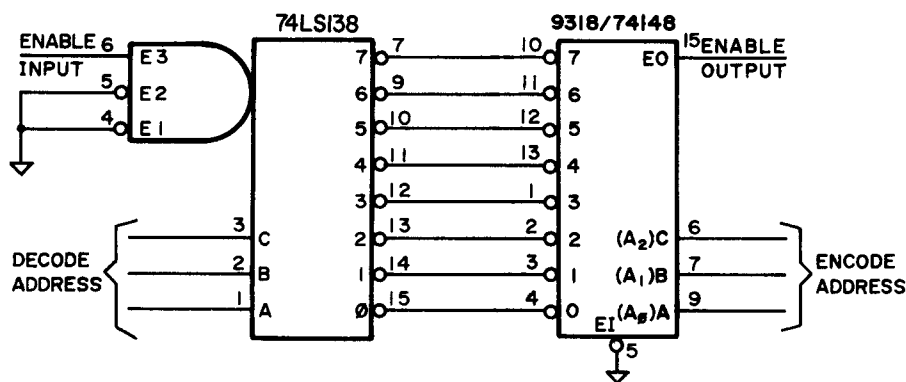


Fig. 16.9.1--Priority Encoder Reverses the Action of Decoder

When the 74138 is enabled, one and only one of its eight output terminals is low. The 9318 detects this condition, and outputs the same three-bit address that appeared at the 74138 inputs. The 9318 ENABLE OUTPUT terminal will be active (high) when the 74138 ENABLE INPUT terminal is a logic one. And, when none of the 74148's input lines is active (low), the ENABLE OUTPUT terminal will be disabled (low).

The manufacturers usually show the 74148/9318 with both its inputs and its outputs as active low. The notation in Figure 16.9.1 shows active-low inputs and active-high outputs. As a consequence, the usual input numbering is reversed: 7 for 0, 6 for 1, etc. Though both notations are correct, the one used here is more convenient for the circuits shown in this chapter. The proper pin numbers are given to avoid confusion.

A priority encoder does more than simply reverse the functions of a decoder. A priority encoder is usually connected to circuitry that permits more than one of the encoder's inputs to be active simultaneously--unlike the circuit of Figure 16.9.1 (where only one 74138 decoder output can go low at once). Thus, the 74148/9318 assigns a priority among

SEC. 16.9 PRIORITY ENCODERS (cont'd)

the possible input codes. The output address will correspond to the highest-priority active input. The lower-numbered inputs have the highest priority. If for example the input line labeled 0 is brought low, the output address will be 000 regardless of the state of the other input lines. Figure 16.9.2 illustrates this feature by using the symbol X to denote "don't care" input conditions.

| INPUTS | | | | | | | | OUTPUTS | | | | COMMENTS |
|--------|---|---|---|---|---|---|---|---------|---|---|----|------------------------------------|
| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | C | B | A | EO | |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | NO INPUT ACTIVE LOWEST PRIORITY |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | |
| X | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | |
| X | X | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | |
| X | X | X | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | |
| X | X | X | X | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | |
| X | X | X | X | X | 0 | 1 | 1 | 1 | 0 | 0 | 1 | |
| X | X | X | X | X | X | 0 | 1 | 1 | 0 | 0 | 1 | |
| X | X | X | X | X | X | X | 0 | 1 | 0 | 0 | 1 | |
| X | X | X | X | X | X | X | 0 | 0 | 0 | 0 | 1 | |

Fig. 16.9.2--Truth Table for Priority Encoder

SEC. 16.10 PRIORITY REGISTERS

Another useful element in priority interrupt schemes is the priority register. As contrasted to the priority encoder, the priority register does not encode its inputs (produce a binary code representing the number of the highest priority active input). Instead, it merely gates its inputs according to their priority, allowing only the highest-priority active input signal to pass through to its outputs. An example is the 74278, as shown in Figure 16.10.1.

SEC. 16.10 PRIORITY REGISTERS (cont'd)

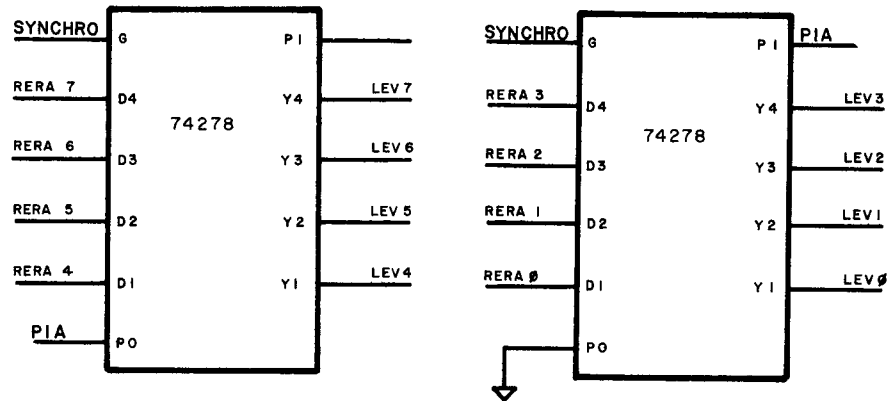


Fig. 16.10.1--Eight-Bit Prioritized Interrupt Request Synchronization Register

Of the cascaded-pair's eight outputs (LEV7 through LEV0), no more than one may be active at a time: the highest-priority output whose corresponding input is activated. In other words, if the highest-priority input signal (D1 on the 74278 to the right of the diagram) is high, it is passed through unaffected. The second-highest-priority output (Y2 on the right-hand 74278) is true if its input signal (D2) is true and Y1 is false. Since the registers are cascaded, the left-hand 74278 outputs are inactive unless the other 74278 enables the chip with a high PIA signal.

PRIORITY INPUT FROM LAST STAGE P0
 HIGHEST PRIORITY $Y1 = D1 \cdot \overline{P0}$
 $Y2 = D2 \cdot \overline{Y1}$
 $Y3 = D3 \cdot \overline{Y2}$
 LOWEST PRIORITY $Y4 = D4 \cdot \overline{Y3}$

PRIORITY OUTPUT TO NEXT STAGE $P1 = \overline{Y4}$

Fig. 16.10.2--Priority Register Logic Equations

The 74278 also incorporates a latching function. The input data values are latched up by the SYNCHRO signal, and thus the circuit in Figure 16.10.1 constitutes a *Prioritized Interrupt Request Synchronization Register*.



SEC. 16.11

INTERRUPTS BEING SERVICED REGISTER

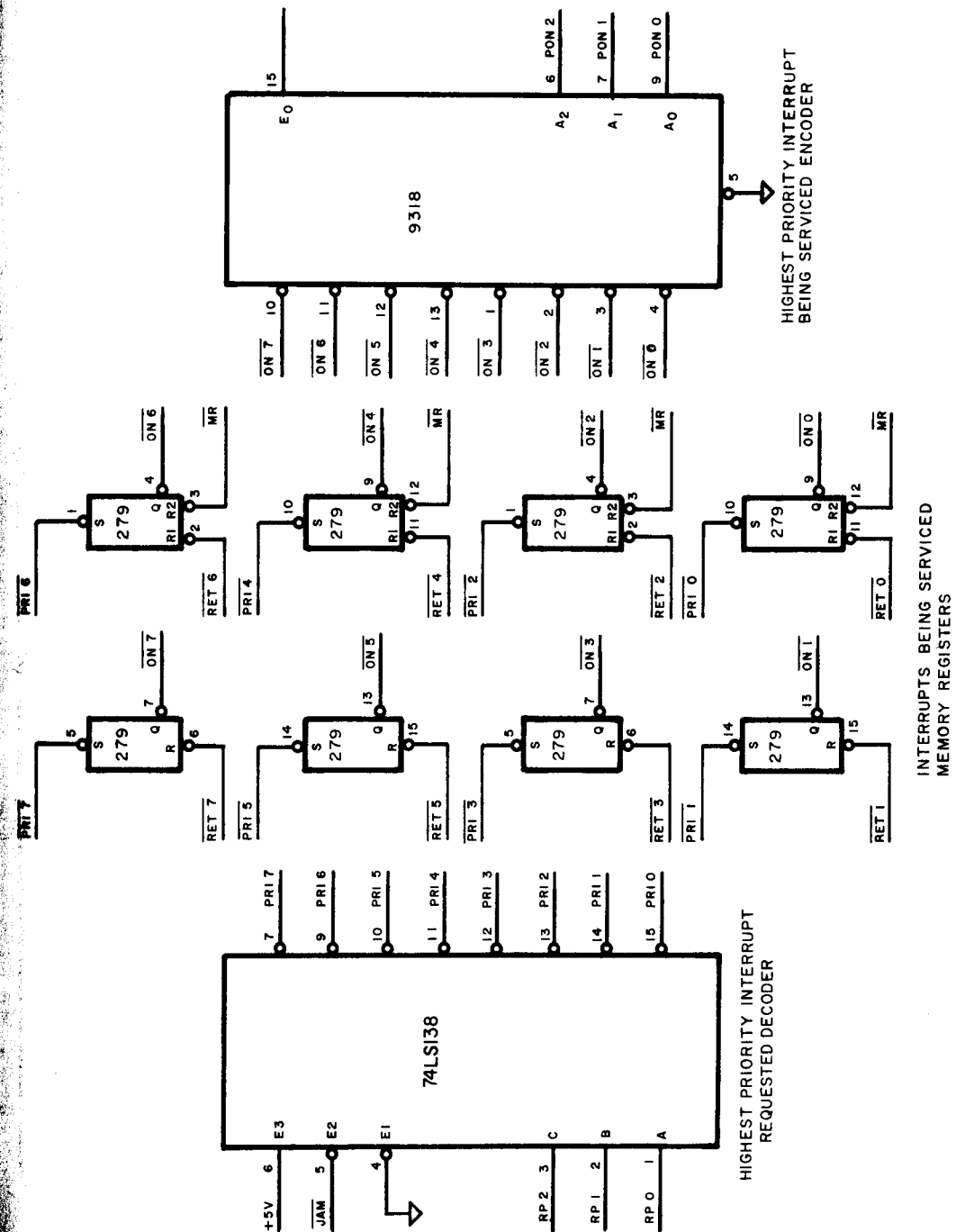


Fig. 16.11.1--Interrupts Being Serviced Register

SEC. 16.11 INTERRUPTS BEING SERVICED REGISTER (cont'd)

As stated above, at any given time several interrupt levels may be in process of being serviced. For example, the microcomputer might have begun servicing interrupt level 7, when an interrupt request on level 4 was received. The system must remember that both levels 4 and 7 are active, so that when the highest-priority interrupt subroutine is completed, the CPU can return to and finish all the lower-level interrupts. It is not adequate to truncate the system by combining the functions of the *Interrupts Being Serviced Register* and the *Interrupt Request Register*, because this would prevent the system from distinguishing readily between new interrupt requests and interrupts already in progress. The result would be lost time and erroneous results.

In its simplest form, the Interrupts Being Serviced Register is made up of an array of flip-flops, similar to the Interrupt Request Register discussed in Sec. 16.7 above.

Figure 16.11.1 (center) shows such a register in the form of two 74279 packages (eight latches). These latches are loaded as follows. The three inputs at the left of the schematic--*RP2*, *RP1*, and *RPO*--derive from a 9318 priority encoder (not shown), which in turn is connected to an Interrupt Request Synchronization Register (Sec. 16.8). Thus *RP2* through *RPO* represent a three-bit binary code for the highest-priority interrupt request received. When the microprocessor begins to service a new high-priority interrupt level, it creates the *JAM* signal (described later), here used to strobe the Interrupts Being Serviced Register.

The outputs of the Interrupts Being Serviced Register are in turn priority-encoded by a 9318, as shown to the right in Figure 16.11.1. Only four ICs are required by this circuit.

SEC. 16.12 PRIORITY COMPARATOR

The *Priority Comparator* continuously compares the interrupt level being serviced, with the interrupt requests which have been received. Whenever an interrupt request is received which is higher in priority than that currently being serviced, the system sends an interrupt request signal directly to the microprocessor.

An ordinary digital comparator may be used for this function. See for example the 93L24s at work in Figure 16.16.1 (center) and Figure 16.17.1 (center).

Note that when the microcomputer is first turned on, it should recognize an interrupt on level zero so as to carry out its initialization scheme. Thus the Priority Comparator should, at power-on, receive an interrupt request on level zero. Also, the priority interrupt system must *not* think it is *already* on interrupt level zero, or no interrupt

SEC. 16.12 PRIORITY COMPARATOR (cont'd)

pulse would be transmitted to the CPU.

Thus, the $ON\emptyset$ flip-flop in the interrupt level being serviced register (Sec. 16.11) must be *reset* by the master reset signal. Also, the master reset signal must generate an interrupt request to (*i.e.*, *set*) the zero-level flip-flop in the interrupt request register (Sec. 16.7).

SEC. 16.13 INTERRUPT JAM LOGIC

When the Priority Comparator strobes the CPU's INTERRUPT terminal with an interrupt request, the microprocessor responds with an interrupt acknowledgement signal--*INTA* for the 8080, *STI* for the 8008. The priority system jams in an instruction which causes the CPU to jump to an interrupt subroutine. In microcomputers based on the 8080 or 8008, the instruction is usually a RST (RESTART) instruction.

Two such schemes are shown in the three- and eight-level priority interrupt systems below (Figure 16.16.1 and 16.17.1). The instruction jammed in is a RESTART *N* instruction, where *N* is the interrupt level that is just beginning to be serviced. This instruction causes the CPU to jump to location 0000N in split octal notation, where a suitable interrupt subroutine is stored. The circuitry shown is for the 8008.

SEC. 16.14 NUMBERED RETURN INSTRUCTIONS

When a given interrupt subroutine is complete, the interrupt system logic must recognize this fact and clear out the appropriate latches in the registers which keep track of that interrupt level. Since subroutines generally end with RETURN instructions, a suitable technique is to decode the execution of RETURN instructions by the microprocessor, assigning unique numbered RETURN instructions to each interrupt level. That is, the very last instruction executed on interrupt level 3 is a *RET3* instruction. This instruction is decoded using a technique described in Chapter 11 above.


The *RET7* signal is used to reset the level 7 latches in both the Interrupt Request Register, and the Interrupts Being Serviced Register. *RET6* resets the latches for interrupt level 6; and so forth.

The *RET \emptyset* instruction is the last instruction in the power-on initialization subroutine, which takes place on interrupt level \emptyset . The normal RETURN instruction--which is the same as *RET \emptyset* --should be avoided until initialization is complete. Since interrupt level 0 is normally used *only* for initialization, an interrupt request for level 0 will not



SEC. 16.14 NUMBERED RETURN INSTRUCTIONS (cont'd)

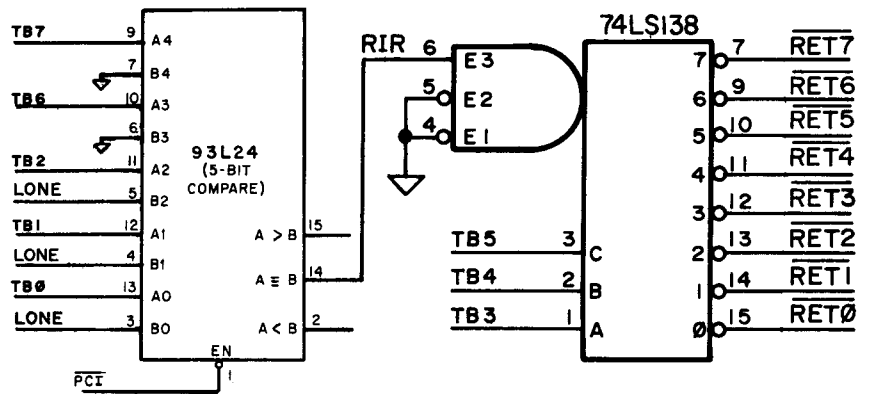occur afterwards. After this point, the RET or RET0 instruction may be utilized freely for normal subroutine returns. Note that this part of the interrupt system cannot be used with the 8080 microprocessor, which does not have numbered return instructions.



RETURN INSTRUCTION RECOGNITION

NUMBERED RETURN INSTRUCTION DECODER

SEC. 16.15 AN ADDRESSABLE LATCH AS AN INTERRUPT REGISTER

Figure 16.15.1 shows an Interrupts Being Serviced Register which combines several of the functions discussed above. The register itself is a 9334 eight-bit addressable latch. It is addressed from either of two sources, as selected by a 74158 multiplexer. Any one bit within the 9334 may be set by the priority-encoded interrupt request address, RP2 through RP0. This can occur only when the IRP (interrupt request present) signal is high (see this signal in Figures 16.16.1 and 16.17.1). A 9334 latch bit may be reset by the execution of the appropriate numbered RETURN instruction, whose address appears on three lines of the microcomputer output bus, TB5 through TB3. This in turn can happen only when the RIR (return instruction recognized) signal is high (Figure 16.14.1.)

The outputs from the Interrupts Being Serviced Register are priority-encoded by a 9318. This circuit accomplishes a respectable portion of the functions of a priority interrupt system with only three ICs.

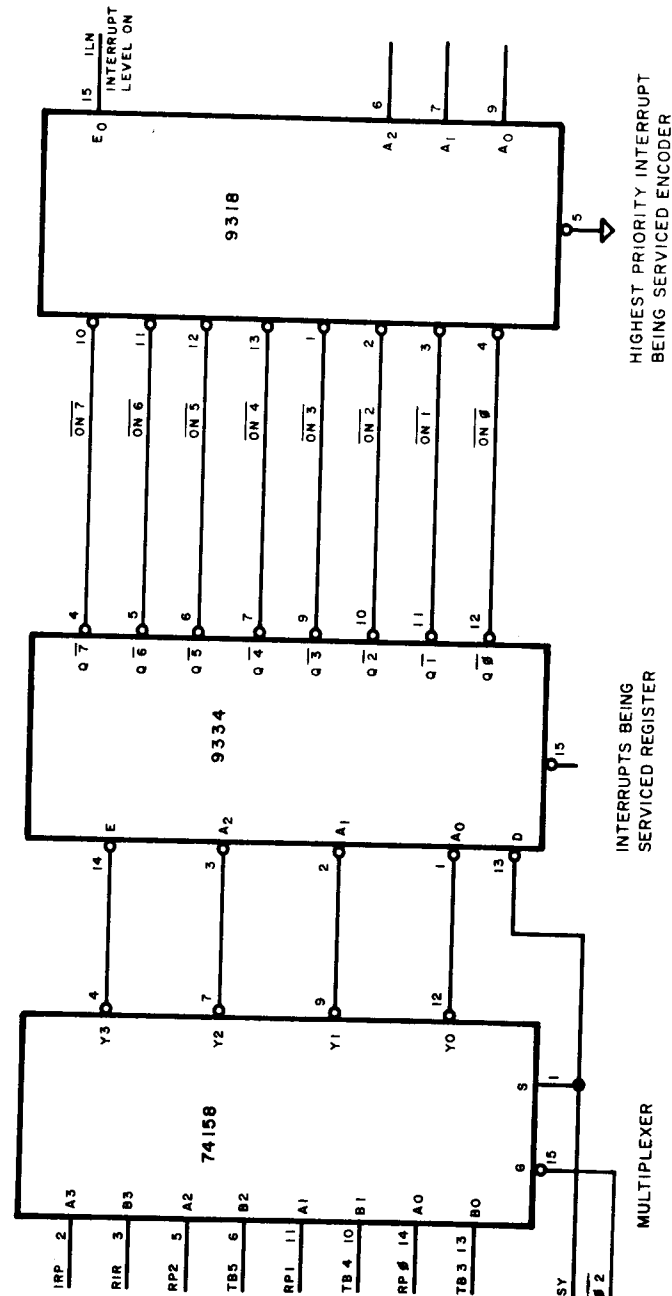


Fig. 16.15.1--Interrupts Being Serviced Register: Multiplexer Sets and Resets Addressable Latch



SEC. 16.16 THREE-LEVEL PRIORITY INTERRUPT SYSTEM

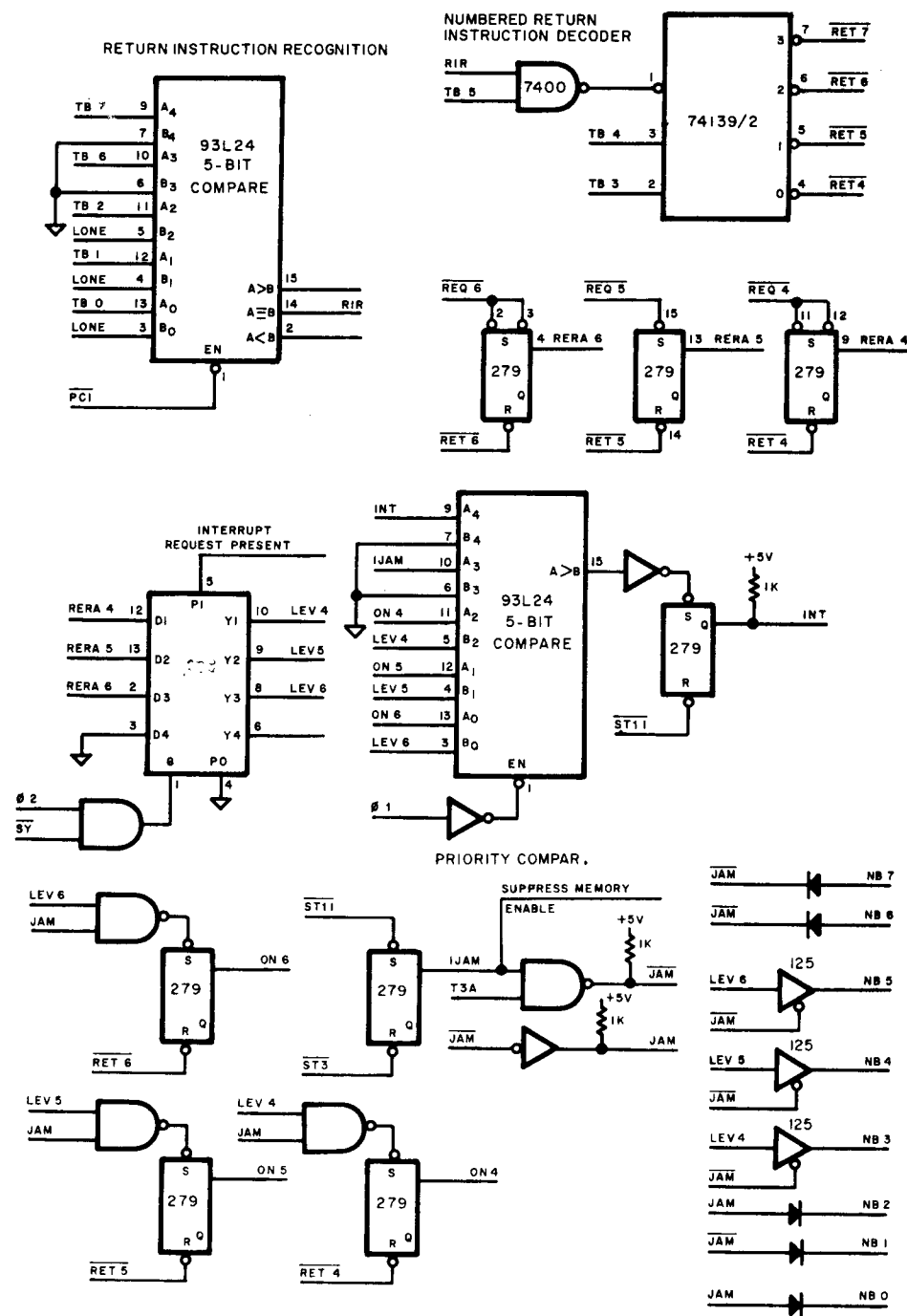


Fig. 16.16.1--3-Level Priority Interrupt System

SEC. 16.16 THREE-LEVEL PRIORITY INTERRUPT SYSTEM (cont'd)

The circuit for a three-level priority interrupt system is shown in Figure 16.16.1. This design uses many of the elements discussed in the previous sections of this chapter.

A 93L24 five-bit comparator is connected so as to recognize numbered RETURN instructions. The number of the RETURN instruction is decoded using one side of a 74139 dual decoder; only four such instructions are employed: RET7, RET6, RET5, and RET4. The three interrupt request inputs take the form of negative-pulse signals fed to the SET terminals of three 74279 set-reset flip-flops, whose outputs are marked RERA6, RERA5, and RERA4. These make up an asynchronous Interrupt Request Register.

The outputs from these flip-flops are connected to a 74278 priority register, where they are both synchronized by $\phi 2$ and \overline{SY} , and prioritized. The outputs of this register go, in turn, to the Priority Comparator and three NAND gates which feed the \overline{ON} flip-flops in the lower left-hand corner of the diagram. The second 93L24 comparator checks to see whether the requested interrupt is of a higher priority than any interrupt level already on. If it is, then the INT flip-flop is set, which requests an interrupt of the 8008 CPU. When the CPU acknowledges the interrupt, with an $\overline{ST1}$ strobe, the IJAM flip-flop is set. This prepares the JAM gate to jam the appropriate RESTART (RST) instruction onto the input bus (NB7 through NB0) at the next T3A time. In order to suppress the output of the Priority Comparator during the interrupt and jam sequence, the INT and IJAM signals are fed into the 93L24's two high-order bits (A4 and A3). This prevents the occurrence of multiple interrupts during the interrupt sequence.

Three 74125 three-state buffers are used to enable the LEV (interrupt level) bits into the RST jam instruction. The diodes provide the remaining constant bits of the RST instruction. (Recall that the octal code for the RST instruction is $\overline{ON}5$, where N is the level number: Chapter 11.)

The $\overline{ST3}$ strobe resets the IJAM flip-flop and terminates the interrupt sequence.

SEC. 16.17 FULL EIGHT-LEVEL PRIORITY INTERRUPT SYSTEM

The schematic for a full eight-level priority interrupt system for the 8008 is shown in Figure 16.17.1. The circuit can readily be modified for the 8080.

The eight-bit Interrupt Request Register consists of D flip-flops. This register provides rising-edge clock inputs (REQ0-REQ7), useful in avoiding problems related to pulse width and multiple interrupts.



SEC. 16.17 FULL EIGHT-LEVEL PRIORITY INTERRUPT SYSTEM (cont'd)

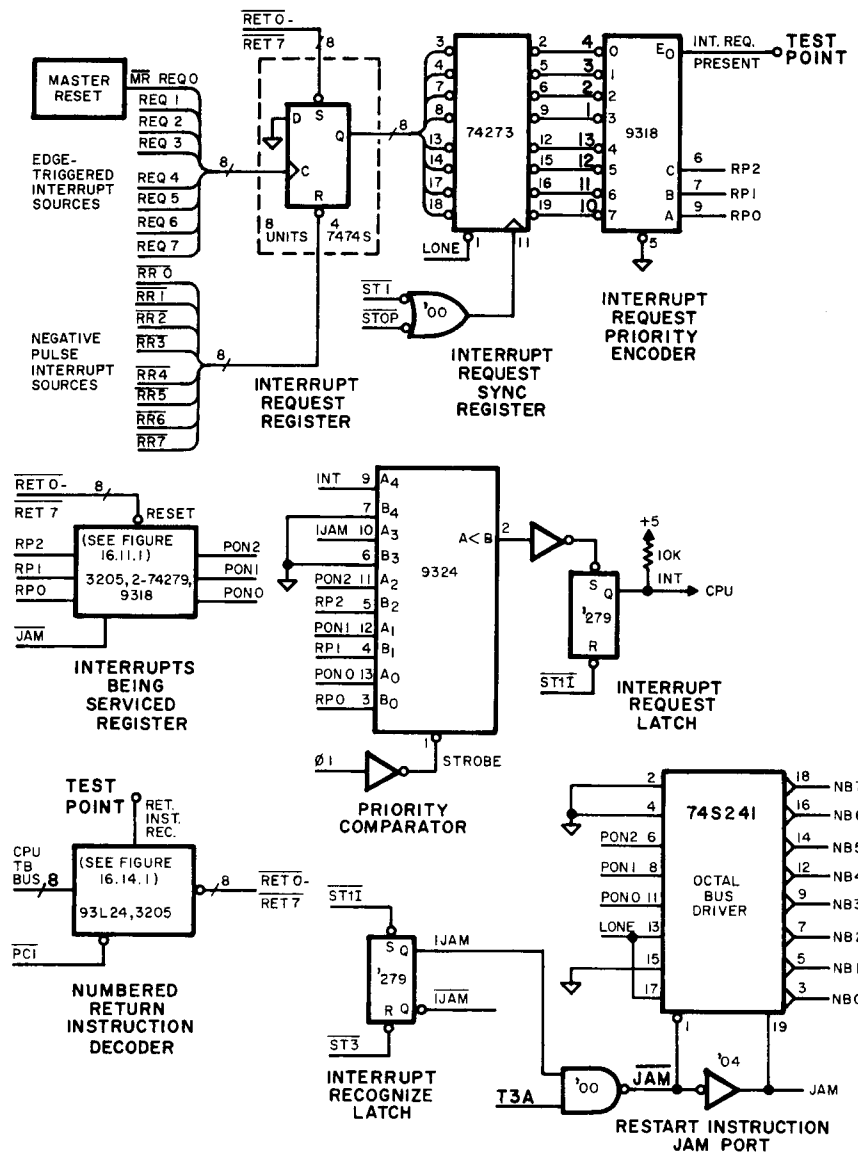


Fig. 16.17.1--An Eight-Level Priority Interrupt System



SEC. 16.17 FULL EIGHT-LEVEL PRIORITY INTERRUPT SYSTEM (cont'd)

The highest-priority interrupt request, level 0, is assigned to the master reset function. The register also allows for negative-pulse-triggered interrupt request signals (RRO-RR7), for added flexibility.

The output of the priority encoder must be stabilized before it can be considered valid for subsequent processing. For this reason, a 74273 Interrupt Request Synchronization Register is used. This octal latch is strobed from STI, or, if the CPU has hit a HALT instruction, from the repetitive STOP pulse train. In either case, the signals reaching the priority encoder can change only at a time which is related to PHASE TWO of the CPU clock: $STI = SY \cdot \phi 2 \cdot T1$; $STOP = STOPPED \cdot SY \cdot \phi 2$.

The remainder of the eight-bit priority interrupt system is similar to the three-bit example above. One difference is that a 74S241 octal bus driver is used to jam the RST instruction onto the CPU input bus.

SEC. 16.18 DAISY-CHAIN INTERRUPT SYSTEM

Another way of configuring a priority interrupt system is to employ a daisy-chain structure. The block diagram for a four-level daisy-chain interrupt system is shown in Figure 16.17.1.



Fig. 16.18.1--Daisy-Chain Interrupt Structure

Each member of the chain can block interrupt requests coming from a lower-priority member of the chain. At the same time, each level can block interrupt-acknowledge signals returning from the CPU, so that lower-priority daisy levels will not think that their interrupt requests have reached the CPU, and will keep trying. Since daisy level 0 is closest to the CPU logic, it is the highest-priority interrupt level. This kind of structure is used for interrupts in the Fairchild F-8 micro-processor chip set.

A diagram for one stage of such a system appears in Figure 16.18.2.

The interrupt-acknowledge signal need not necessarily be daisy-chained. It could be a number on the bus combined with a strobe signal. Such variations are left to the imagination of the designer.



 


Fig. 16.18.2 --One Stage of Daisy Chain Interrupt System



In many microcomputers, the CPU must be able to service an interrupt at any random point during the execution of the mainline program. The CPU's internal registers and flag bits might have any of the possible combinations of values at the time when the interrupt instruction is received. The content of the registers and flags, taken together at any particular time, is called the *machine status*, or simply *status*. If the mainline program is to proceed normally when the interrupt subroutine ends, the interrupt subroutine must *save status* as it begins, and *restore status* before returning control to the mainline program.

The 8080 makes status saving relatively easy. (See Chapter 23, Sec. 23.11, for a practical example.) However, the 8008's structure and instruction set require a number of special considerations. This chapter is devoted to the software and hardware necessary to enable the 8008 to save status during interrupts.

The 8008 has a number of registers on the chip. These include the PC register stack, the seven index registers, and the four flags--all discussed in the following sections.

17.2 THE PROGRAM COUNTER STACK

There are eight PC (*program counter*) registers in the 8008's internal PC register stack. When a subroutine is called by the microprocessor's program, the program counter goes up one level in the stack. This stack will overflow if subroutines are nested too many times. It must be remembered, therefore, that a subroutine interrupt uses at least one level in the stack, and if the software includes too many nested subroutines, the PC register stack may overflow.

Given that overflow is avoided, no special care need be taken to save the status of the PC register during an interrupt, since the PC stack pointer does the saving and restoring automatically. The RST (*restart*) instruction jammed in by the interrupt *pushes* the program counter by pointing up one level in the PC stack, thus saving the main line program location in the register below. The interrupt subroutine ends with an RET (*return*) instruction, which *pops* the PC register by pointing down one level in the stack to where the main line program location was stored.



SEC. 17.3 INDEX REGISTERS

The seven general-purpose index registers of the 8008, the A, B, C, D, E, H, and L registers, may be in use by the main line program when an interrupt occurs. The interrupt subroutine either must leave the contents of any given register unchanged, or must *save* the register, use it, then *unsave* or *restore* the register before returning to the main line program. If only a few registers are to be used during the interrupt subroutine, then only those registers need be saved and unsaved. The configuration of hardware and software that will be necessary to save status during interrupts depends therefore on the complexity of the interrupt subroutine. If a register is not used in the main line program it is, of course, not necessary to save it in the interrupt subroutine.

SEC. 17.4 FLAGS (CONDITION FLIP-FLOPS)

The 8008 has four internal flip-flops which store *flag* bits set during the execution of arithmetic and logic instructions. These four flags are C (*carry*), P (*parity*), Z (*zero*), and S (*sign*). The 8008 manual describes how these flags are set and tested by various instructions.

The parity of a word in the 8008 is based on the *eight-bit* result of an arithmetic or logic instruction. (This point is not described fully in current editions of the 8008 manual.) Even though the carry flag may be affected by the same instruction, the carry bit is not used in calculating the value of the parity bit. If the number of logical ones in the eight-bit result is even, then the parity is even, and the parity flag will be set to a one (logic true). If the number of ones is odd, the parity flag will be reset to zero. If the eight-bit result is all zeros, ie, there are zero ones, this is considered even parity, and the parity flag will be set.

Of the sixteen combinations of four bits, only ten flag combinations are really possible due to the logical constraints on the flags. For example, if the zero flag is set, the parity must be even, and therefore the parity flag must also be set. If the sign flag is set, the zero flag cannot be set. Figure 17.4.1 shows all combinations of the four 8008 flags, both possible and impossible.

SEC. 17.4 FLAGS (CONDITION FLIP-FLOPS) (cont'd)

| C P Z S | DESCRIPTION OF WORDS* | NO. OF WORDS* |
|---------|--|---------------|
| 0 0 0 0 | Half the positive numbers except for zero; no carry | 63 |
| 0 0 0 1 | Half the negative numbers; no carry | 64 |
| 0 0 1 0 | <i>Impossible: if zero flag is set, the parity flag must also be set</i> | 0 |
| 0 0 1 1 | <i>Impossible: if zero flag is set, the parity flag must also be set</i> | 0 |
| 0 1 0 0 | Half the positive numbers; no carry | 64 |
| 0 1 0 1 | Half the negative numbers; no carry | 64 |
| 0 1 1 0 | Zero; no carry | 1 |
| 0 1 1 1 | <i>Impossible: if sign flag is set, zero flag cannot be set</i> | 0 |
| 1 0 0 0 | Half the positive numbers except zero; with carry | 63 |
| 1 0 0 1 | Half the negative numbers, with carry | 64 |
| 1 0 1 0 | <i>Impossible: if zero flag is set, the parity flag must also be set</i> | 0 |
| 1 0 1 1 | <i>Impossible: if zero flag is set, the parity flag must also be set</i> | 0 |
| 1 1 0 0 | Half the positive numbers, with carry | 64 |
| 1 1 0 1 | Half the negative numbers, with carry | 64 |
| 1 1 1 0 | Zero; with carry | 1 |
| 1 1 1 1 | <i>Impossible: if sign flag is set, zero flag cannot be set</i> | 0 |

*A word is defined here as a unique combination of eight bits in the accumulator plus the carry bit. There are 512 possible words. The right-hand column shows the number of words which correspond to each combination of flags, and the middle column describes those words.

Fig. 17.4.1--The Sixteen Combinations of Flags, Including Six Combinations Which are not Possible



SEC. 17.5 STATUS-SAVING TECHNIQUES

There are two basic methods for saving status during interrupts: the first uses software, and the second uses hardware. Often the two techniques are combined to produce the most efficient design for the application.

The major disadvantage to the software approach is that the extra instructions take time to execute--time which in some systems just may not be available. The drawback of the hardware technique is the extra cost that the additional parts add to a system. In either case, the designs described in the following sections should aid the engineer in developing an efficient system to meet his needs. In keeping with the aim of this book, to be a practical guide, the latter sections of this chapter give solutions to *specific* design problems.

SEC. 17.6 SOFTWARE TECHNIQUES

17.6.1 General Constraints Without any additional hardware, it is not possible to save *all* of the registers and flags with the 8008 instruction set. The theoretical limit for systems using 256 bytes of RAM (the *RAM-PAGE* option discussed in Chapter 13) is to save all four flags and six out of the seven index registers with software alone. With more than a page (256 bytes) of RAM in the system, only five out of the seven registers may be saved with software alone.

The most efficient method of saving more than one index register requires setting up the address registers (H and L, or just L with the *RAM-PAGE* option) and storing each register through a sequence of LMr and INL instructions. Since the INL instruction modifies the flags, it is necessary to save flags *before* this sequence of instructions can be used. But in order to save the flags, the program must use at least the A register, in order to determine the status of the flags, and it must use at least the L register if the results are to be stored in RAM. This series of constraints implies that a status-saving program requires three parts.

17.6.2 Three-Part Program *Part one* must save the H and L registers and load them with an address in RAM where the A register is to be stored. *Part one* usually ends with an LMA instruction, which saves the A register in RAM.

SEC. 17.6 SOFTWARE TECHNIQUES (cont'd.)

Part two determines the status of those flags to be saved. Flags not used by the main line program need not be saved. Near the end of *part two*, the A register contains all of the information required to restore the flags later on. *Part two* ends with INL and LMA instructions, which store the status of the flags in RAM to be retrieved later. The INL instruction can be used here, for the first time, because the flag status has already been determined, and the fact that the INL instruction may change the flags no longer matters.

Part three saves all of the other registers used by *both* the main line program and the interrupt subroutine. Naturally, if the main line program never uses the C register, for example, the interrupt subroutine need not save it. On the other hand, if the interrupt subroutine does not use the C register, it would not be necessary to save it even if the main line program did use it. Again, the INL instruction can now be used since *part two* already saved the flag conditions.

Note: in the examples given in this chapter, all arabic numerals are in octal unless otherwise specified.

17.6.3 Saving Status, Part One An example of *part one* is shown in Figure 17.6.1:

```
LDH     SAVE H REGISTER IN D REGISTER.
LEL     SAVE L REGISTER IN E REGISTER.
LHI 040 POINT TO RAM LOCATION. .
LLI 370 . .USED FOR SAVING A REGISTER.
```

Figure 17.6.1--Save Status with Software, Part One

In Figure 17.6.1, it is assumed that the main line program does *not* use the D and E registers, but *does* use the H and L. The D and E registers are therefore used to save the H and L registers, so that they may be loaded with an address in RAM where the A register may be saved.



SEC. 17.6 SOFTWARE TECHNIQUES (cont'd)

17.6.4 *Saving Status, Part Two* An example of part two appears in Figure 17.6.2:

```

SAV LAI 000  ASSUME ZERO FLAG IS SET.
      JTZ SAVC IF TRUE, GET CARRY BIT.
      LAI 060  ASSUME SIGN BIT IS ZERO (POSITIVE WORD).
      JFS SAVC IF TRUE, GET CARRY BIT.
      LAI 300  SIGN BIT WAS SET.
SAVC RAR      GET CARRY BIT.
      JTP SAVW JUMP IF PARITY IS EVEN.
      XRI 001  SET PARITY ODD.
SAVW INL     POINT TOWARDS NEXT RAM BYTE.
      LMA      SAVE FLAG WORD.

```

Figure 17.6.2--Save Status with Software, Part Two

In this example of *part two*, the status of all four flags is packed into one eight-bit word and stored into memory. This word is arranged in a way that allows the restoration of flags with a simple two-instruction program. A step-by-step description of how flags are saved and restored using this program appears in Figure 17.6.3. The instructions appear to the left of the figure. The ten possible combinations of flags appear at the top, both in octal form, and broken down into the four binary flag bits. The ten columns of the figure show how the program affects each of the ten combinations, instruction by instruction.

The three-digit numbers in the columns in Figure 17.6.3 are in a notation which conveys *nine* bits of information, that is, the eight bits which make up the contents of the A register, plus the carry bit. Values of 400 or above represent a set carry flag. Each three-digit number reflects the contents of the A register (plus carry flag) *after* the instruction shown at the left of that row has been executed.



SEC. 17.6 SOFTWARE TECHNIQUES (cont'd)

| ALL FLAGS | | 00 | 01 | 04 | 05 | 06 | 10 | 11 | 14 | 15 | 16 |
|-------------|---|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| CARRY | C | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| PARITY | P | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| ZERO | Z | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| SIGN | S | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| SAV LAI 000 | | 000 | 000 | 000 | 000 | 000 | 400 | 400 | 400 | 400 | 400 |
| JTZ SAVC | | 000 | 000 | 000 | 000 | 000 | 400 | 400 | 400 | 400 | 400 |
| LAI 060 | | 060 | 060 | 060 | 060 | | 460 | 460 | 460 | 460 | |
| JFS SAVC | | 060 | 060 | 060 | 060 | | 460 | 460 | 460 | 460 | |
| LAI 300 | | ↓ | 300 | ↓ | 300 | ↓ | ↓ | 700 | ↓ | 700 | ↓ |
| SAVC RAR | | 030 | 140 | 030 | 140 | 000 | 230 | 340 | 230 | 340 | 200 |
| JTP SAVW | | 030 | 140 | 030 | 140 | 000 | 230 | 340 | 230 | 340 | 200 |
| XRI 001 | | 031 | 141 | ↓ | ↓ | ↓ | 231 | 341 | ↓ | ↓ | ↓ |
| SAVW INL | | 031 | 141 | 030 | 140 | 000 | 231 | 341 | 230 | 340 | 200 |
| LMA | | 031 | 141 | 030 | 140 | 000 | 231 | 341 | 230 | 340 | 200 |
| UNSAV LAM | | 031 | 141 | 030 | 140 | 000 | 231 | 341 | 230 | 340 | 200 |
| ADA | | 062 | 302 | 060 | 300 | 000 | 462 | 702 | 460 | 700 | 400 |
| CARRY | C | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| PARITY | P | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| ZERO | Z | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| SIGN | S | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| ALL FLAGS | | 00 | 01 | 04 | 05 | 06 | 10 | 11 | 14 | 15 | 16 |

Fig. 17.6.3--Saving Flags with Software Illustrated for All Ten Possible Flag Combinations



SEC. 17.6 SOFTWARE TECHNIQUES (cont'd)

The program has finished *saving* flags at the point where the dotted line appears, after the LMA instruction. Note that the content of the A register at this point is different for each of the ten flag combinations. This value is stored in memory. At this point comes part three of the status-saving program, which saves further registers; then comes the main body of the interrupt subroutine.

17.6.5 *Saving Status, Part Three* An example of *part three* of the status-saving procedure is shown in Figure 17.6.4.

```

INL    POINT TOWARDS NEXT RAM LOCATION.
LMB    SAVE THE B REGISTER.
INL    POINT TOWARDS NEXT RAM LOCATION.
LMC    SAVE THE C REGISTER.
INL    MOVE THE RAM POINTER AGAIN.
LMD    SAVE THE H REGISTER (FROM PART ONE).
INL    MOVE THE RAM POINTER AGAIN.
LME    SAVE THE L REGISTER (FROM PART ONE).

```

Figure 17.6.4--Saving Status with Software, Part Three

In Figure 17.6.4, note that the H and L registers are saved indirectly by saving the D and E registers. The H and L registers were loaded into the D and E registers previously, in part one.

A number of locations of RAM must be set aside to save registers and flags. The following registers are being used in this generalized example (Figure 17.6.5):

SEC. 17.6 SOFTWARE TECHNIQUES (cont'd)

| PAGE | BYTE | DESCRIPTION |
|------|------|-----------------|
| 040 | 370 | SAVE A REGISTER |
| 040 | 371 | SAVE FLAGS |
| 040 | 372 | SAVE B REGISTER |
| 040 | 373 | SAVE C REGISTER |
| 040 | 374 | SAVE H REGISTER |
| 040 | 375 | SAVE L REGISTER |

Fig. 17.6.5--RAM Locations Used in Saving Registers and Flags

17.6.6 *Interrupt Subroutine* After part three of the status saving procedure described above has taken place, the main line program status has been saved in RAM. The next part of the interrupt subroutine performs the functions for which the interrupt was intended by the designer. If, for example, the interrupt was caused by a key having been pressed on a Teletype, then the Teletype data might be shifted in, and the resultant character stored in a RAM buffer for subsequent processing by the main line program.

In any case, once the main body of the interrupt subroutine has been executed, it is necessary to restore the status saved in the three parts of the status-saving routine described above.

The restore program is also broken up into three parts. Since the last things saved are the first things restored, the three parts of the restore program are numbered inversely, *three, two, one*.

17.6.7 *Unsaving Status, Part Three* The first part of the program to restore status is *part three*. It unsaves the L, H, C, and B registers. Notice that this is the reverse of the order in which they were saved in Section 17.6.5 above.

A generalized example of unsaving status, part three, is given in Figure 17.6.6.



SEC. 17.6 SOFTWARE TECHNIQUES (cont'd)

```

LHI 040 POINT TO THE LOCATION WHERE . .
LLI 375 . . L REGISTER WAS SAVED.
LEM LOAD E REGISTER WITH SAVED L.
DCL POINT TO H REGISTER SAVE LOCATION.
LDM LOAD D REGISTER WITH SAVED H.
DCL POINT TO C REGISTER SAVE LOCATION.
LCM RESTORE C REGISTER.
DCL POINT TO B REGISTER SAVE LOCATION.
LBM RESTORE B REGISTER.

```

Figure 17.6.6--Unsave Status with Software, Part Three

The E and D registers are used as temporary storage for the original L and H register values, as was done in the third and first parts of the status-saving program.

17.6.8 *Unsaving Status, Part Two* Part two of the unsaving status program restores flags in a manner which corresponds to the way they were treated in the second part of the save routine. An example of a flag *restoring* program which works with the flag *saving* instructions shown in Section 17.6.4 is shown in Figure 17.6.7:

```

DCL POINT TOWARDS FLAG BYTE.
LAM PICK UP FLAG INFORMATION.
ADA RESTORE ALL FLAGS.

```

Figure 17.6.7--Unsave Status with Software, Part Two

The DCL instruction points to the location in memory where the flag-saving word was stored. The LAM instruction *unsaves* the flag-saving word from memory. The ADA instruction adds the A register to itself. This doubling of the A register is equivalent to shifting every bit left one place. The bit which was in bit A₇ is shifted into the carry bit. The A₆ bit becomes the sign bit, A₇, and sets the sign flag accordingly. Because all other bits have been paired so as not to affect parity, the parity is determined by the A₀ bit alone, as it is shifted into the A₁ position.

SEC. 17.6 SOFTWARE TECHNIQUES (cont'd.)

Since ADA is an arithmetic operation, the flags are now set according to the values of the octal results shown. The new flag values are shown at the bottom of Figure 17.6.3, bit-by-bit and in octal form, and correspond exactly with the original status of the flags.

The reader might find it helpful to study Figure 17.6.3, and convince himself that the flags are indeed saved and restored properly.

17.6.9 *Unsaving Status, Part One* Part one of the unsaving status program corresponds to part one of the saving status procedure. The DCL instruction may not be used in pointing to memory, because the flags have just been restored (paragraph 17.6.8) and must not be disturbed. A program example is given in Figure 17.6.8. Rather than using the two-byte LLI 370, a DCL (one byte) could be used if it were placed *before* the ADA instruction in Figure 17.6.7. See the examples at the end of this chapter.

```

LLI 370 POINT TOWARDS SAVED A REGISTER.
LAM RESTORE A REGISTER.
LLE RESTORE L REGISTER.
LHD RESTORE H REGISTER.
RET RETURN TO MAIN LINE PROGRAM.

```

Figure 17.6.8--Unsave Status with Software, Part One

17.6.10 *Summary* The restoration of status is now complete, and the interrupt subroutine returns to the main line program.

If the preceding generalized discussion seems complex to the reader, it is suggested that he read over the specific examples given near the end of this chapter.

SEC. 17.7 SAVING REGISTERS WITH HARDWARE

17.7.1 *General* Hardware is used to save status during interrupts in systems where software-only schemes are too restrictive or too time-consuming.

An example: the LIFO register design described in Chapter 12 may be used to save as many registers as might reasonably be desired. The LIFO may be used by more than one subroutine, and may even be used with subroutines which call themselves without losing any status information.

17.7.2 *One-Byte LIFO* Figure 17.7.1 shows a circuit which saves the A register with an OUTPUT X instruction, then reads the saved data back into the A register with an INPUT Y instruction. This circuit requires only one chip, the new TI 74S374, an eight-bit latch with three-state output circuitry. The 'S374 comes in a 20-pin *Skinny-DIP* package on standard 0.3-inch row-to-row centers. Alternately, the Intel 8212 IC may be used--another octal latch with three-state outputs, this one in a larger 24-pin package. And finally, the octal latch could be implemented with a separate octal latch, like the 74273, connected to an input multiplexer or to a discrete three-state buffer.

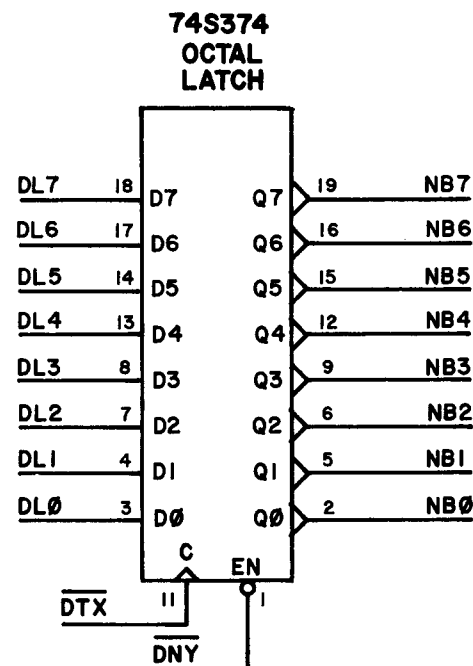


Figure 17.7.1--Saving A Register with One Instruction, Unsaving with One

SEC. 17.8 SAVING FLAGS WITH HARDWARE

Flag-saving hardware is needed mainly in microcomputers which utilize interrupts and cannot afford the time to save flags through software. They are also used in general-purpose designs which display the flags on front-panel lamps.

The designer must consider both the hardware and software needed by the system before building flag-saving hardware into his circuit. Even if such a circuit is included, it is frequently unnecessary to save all of the flags.

In communications applications, and in other systems where byte-manipulation techniques are used, the Carry and Parity flags might never be used in the main line program. In that case, all flags can be used within the interrupt subroutine, so long as it cannot itself be interrupted.

SEC. 17.9 LATCHING UP THE FLAGS

17.9.1 *Hardware* During the T₄ state of memory cycle two of each INPUT instruction, the 8008 outputs the flags on the CPU bus. The Carry flag (C) appears on bit D3, Parity (P) on D2, Zero (Z) on D1, and the Sign flag (S) on bit D0. Flag-saving hardware is usually designed to latch up the flags during only one of the eight available INPUT instructions. In the examples that follow, INPUT 7 is designated as the flag-saving instruction, and the associated input strobe signal is $\overline{DN7}$.

The technique then is to latch up the information on the four low-order bits of the CPU bus during the first T₄ state after every $\overline{DN7}$ strobe.

Specific flag-saving designs can be implemented using the many TTL chips available. Figures 17.9.1 and 17.9.2 illustrate some possible designs using some of the convenient integrated circuits.

SEC. 17.9 LATCHING UP THE FLAGS (cont'd)

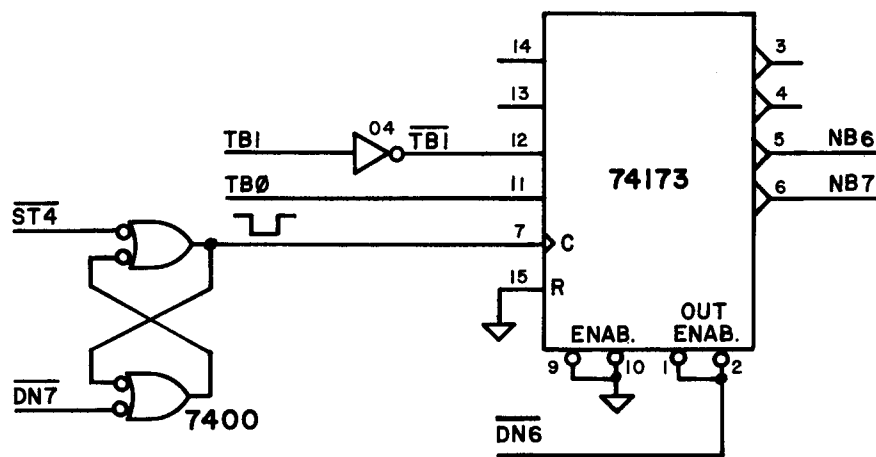


Figure 17.9.1--Save Sign and Zero Flags with a Few Chips

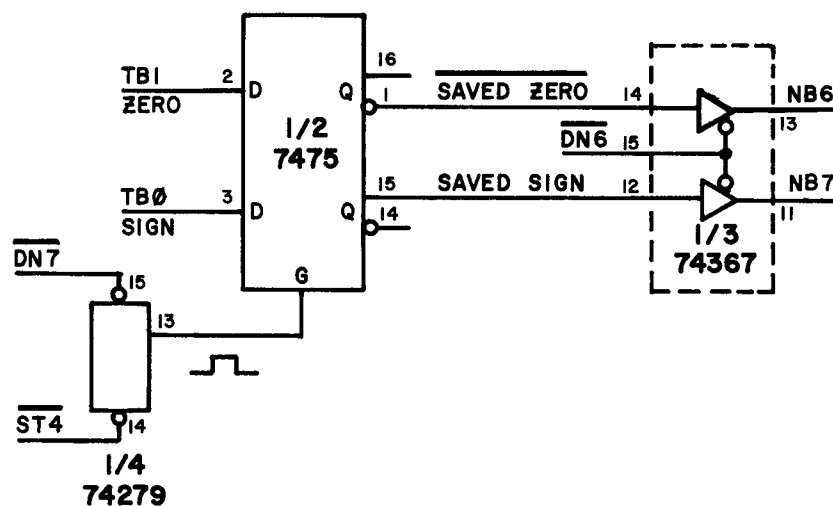


Figure 17.9.2--Another Way to Save the Same Two Flags

SEC. 17.9 LATCHING UP THE FLAGS (cont'd)

17.9.2 *Software* The program to save and unsave flags using the hardware in the preceding paragraphs is shown in Figure 17.9.3. This example assumes that the system uses only 256 bytes of RAM (the *RAM-PAGE* option introduced in Chapter 13), and that the system does not have hardware push-pop options. The main line program does not use the E register.

```

INTR LEL    SAVE L REGISTER IN E.
LLI 370    POINT TO SAVE A REGISTER LOCATION.
LMA        SAVE A REGISTER
INP 007    SAVE FLAGS.
INL        POINT TO SAVE H REGISTER LOCATION.
LMH        SAVE H REGISTER.

```

Main Body of Interrupt Program may use all Flags and A, L, H registers.

```

INP 006    GET SAVED FLAG BITS.
NDI 300B   RESTORE FLAGS S AND Z.
LAI 040    POINT TO SAVED . .
LLI 370    . . A REGISTER LOCATION.
LAM        RESTORE A REGISTER.
LLI 371    POINT TO SAVED H REGISTER.
LHM        RESTORE H REGISTER.
LLE        RESTORE L REGISTER.
RET        RETURN TO MAIN LINE.

```

Figure 17.9.3--Software for Saving Status Using Above Hardware

In Figure 17.9.3, the SAVE FLAGS instruction (INP 007) not only saves the flags, but also destroys the A register as would any other input instruction. It is therefore necessary to save the L register, set it up, and save the A register before executing the INP 7 instruction. Once the flags are saved, then the INL instruction, which could change the flags, can be used.

The INP 7 instruction should not, in general, be used in the main body of the interrupt program, lest the saved flags be lost. As an academic exercise, the reader might want to write a program which *does* uses INP 7 within the body of the interrupt program. The program uses two instructions, plus the INP 7 instruction, and avoids destroying the saved flags. However, since any input instruction could have been used it is best to choose one which is not needed in the interrupt subroutine.

SEC. 17.9 LATCHING UP THE FLAGS (cont'd)

The circuit of Figure 17.9.1 is a little more flexible than that of Figure 17.9.2 because the same input strobe could be used for both saving and unsaving flags. The second time the input instruction is executed, it will destroy the flags--but not until *after* the previously-saved information has been read into the microcomputer's input bus. This is because the clock (C) stores information in the 74173 in Figure 17.9.1 at ST4 time, whereas the information has already been read at T3A time. The T3A enable pulse always occurs before the ST4 strobe.

The circuit in Figure 17.9.1 is clocked with a logic signal which is normally high, but goes to zero at the beginning of the DN7 pulse, which corresponds closely to the T3A pulse. The clock signal returns to logic one at the beginning of the ST4 pulse. It is at this time that the flag information is loaded into the 74173's flip-flops.

The circuit in Figure 17.9.2 differs in the fact that the enable input, G, receives a positive pulse. The G input is the complement of the clock pulse used in the circuit of Figure 17.9.1. The 7475 latches begin following the inputs as soon as the enable line goes high, and latches (holds) the information that is on the inputs when the G line goes low at the beginning of the ST4 strobe. The fact that the outputs start following the inputs at the beginning of T3A time (DN7 time) means that the same input instruction cannot successfully read out the data *before* it changes, as was possible in the previous example.

SEC. 17.10 SAVING ALL FOUR FLAGS WITH HARDWARE

17.10.1 Hardware The circuit shown in Figure 17.10.1 saves all four flags in hardware. It uses a 74175 quad flip-flop to store the four bits of information. The clock for this circuit is developed like the negative pulse for Figure 17.9.1 above. The "Restore Flags Input Port" shown in Figure 17.10.1 consists of either a three-state buffer, or a multiplexer input port.

SEC. 17.10 SAVING ALL FOUR FLAGS WITH HARDWARE (cont'd)

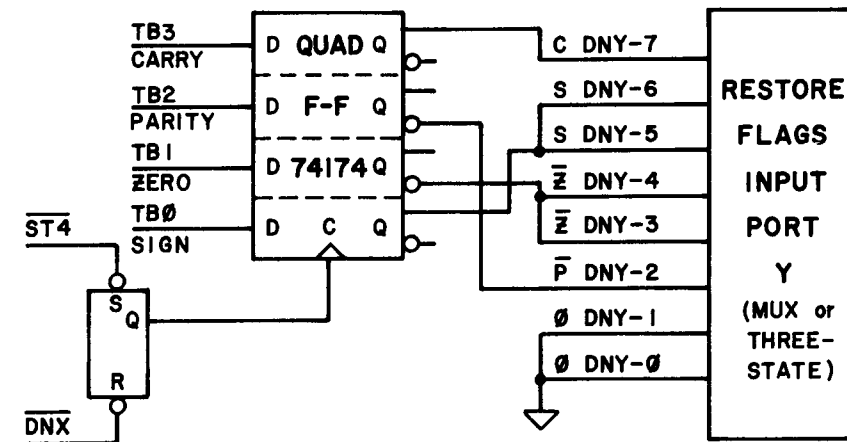


Figure 17.10.1--Quad Flip-Flop Saves All Four Flags

The bits representing the Sign flag (S) and the complement of the Zero flag (\bar{Z}) are entered into the input twice so that they will not disturb the parity of the input word, as established by the saved Parity (P) flag.

The resultant input word (INPUT Y) may be represented as follows:

| | | | | | | | | |
|------------|---|---|---|-----------|-----------|-----------|-------------|-------------|
| BIT NUMBER | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| CONTENTS | C | S | S | \bar{Z} | \bar{Z} | \bar{P} | \emptyset | \emptyset |

Figure 17.10.2--Values of Bits Stored in Hardware

SEC. 17.11 SAVING FOUR FLAGS, BUS STRUCTURED HARDWARE (cont'd)

In this circuit, an EXCLUSIVE OR gate, such as one quarter of a 7486 TTL device, helps perform the required logical manipulations of the flag values. The bit loaded into the 3D input on the 74173 is compensated so that the sign and zero bits will not disturb the parity bit.

17.11.2 *Software* The program used for saving and restoring flags is as follows:

```

INP X   SAVE FLAGS
-----
INP Y   GET FLAG WORD
NDI 360 MASK OUT LOW-ORDER BITS
ADA    RESTORE FLAGS

```

Figure 17.11.2--Instructions for Saving and Restoring Four Flags

The chart in Figure 17.11.3 shows how each of the ten possible flag combinations is stored in the four-bit latch. The values of the four bits are manipulated from the original flag values, as shown. The following symbol denotes the EXCLUSIVE OR operation: \oplus . The results in the A register after the ADA instruction are shown in the following column, and the flags that result from this instruction are shown at right.

SEC. 17.11 SAVING FOUR FLAGS, BUS STRUCTURED HARDWARE (cont'd)

| ORIGINAL FLAGS | STORED IN LATCHES | | | | AFTER ADA INSTRUCTION | RESTORED FLAGS |
|-------------------|-------------------|----|----------------|-----------|--------------------------|-------------------|
| | 1D | 2D | 3D | 4D | | |
| C P Z S | C | S | $P\oplus(S+Z)$ | \bar{Z} | C 7 6 5 4 3 2 1 0 | C P Z S |
| 0 0 0 0 | 0 | 0 | 0 | 1 | 0 0 0 1 0 0 0 0 0 | 0 0 0 0 |
| 0 0 0 1 | 0 | 1 | 1 | 1 | 0 1 1 1 0 0 0 0 0 | 0 0 0 1 |
| 0 1 0 0 | 0 | 0 | 1 | 1 | 0 0 1 1 0 0 0 0 0 | 0 1 0 0 |
| 0 1 0 1 | 0 | 1 | 0 | 1 | 0 1 0 1 0 0 0 0 0 | 0 1 0 1 |
| 0 1 1 0 | 0 | 0 | 0 | 0 | 0 0 0 0 0 0 0 0 0 | 0 1 1 0 |
| 1 0 0 0 | 1 | 0 | 0 | 1 | 1 0 0 1 0 0 0 0 0 | 1 0 0 0 |
| 1 0 0 1 | 1 | 1 | 1 | 1 | 1 1 1 1 0 0 0 0 0 | 1 0 0 1 |
| 1 1 0 0 | 1 | 0 | 1 | 1 | 1 0 1 1 0 0 0 0 0 | 1 1 0 0 |
| 1 1 0 1 | 1 | 1 | 0 | 1 | 1 1 0 1 0 0 0 0 0 | 1 1 0 1 |
| 1 1 1 0 | 1 | 0 | 0 | 0 | 1 0 0 0 0 0 0 0 0 | 1 1 1 0 |

Fig. 17.11.3--Four Flag Bits Manipulated, Stored, Unsaved

17.11.3 *Saving Three Flags Only* If the parity bit is not used, the OR and XOR gates may be omitted from the circuit of Figure 17.11.1, and the remaining flags will be saved and restored properly. In that case, the software would have to be changed to mask out what would have been the parity bit: NDI 320 would replace the NDI 360 in Figure 17.11.2.



SEC. 17.12 STATUS-SAVING SYSTEM, EXAMPLE I

Note: in this and the following sections, examples are given of practical status-saving systems, based on the information presented in all of the preceding sections of this chapter, both software and hardware.

17.12.1 *Description* The first status-saving example is for a fully-developed 8008-based microcomputer which has more than 256 bytes of RAM, and a main line program which uses all of the flags and registers. Therefore all are saved. Figure 17.12.1 is a STATUS USAGE CHART whose basic format is repeated, for comparison purposes, in the remaining sections of this chapter.

| USE \ STATUS | REGISTERS | | | | | | FLAGS | | | | PROGRAM COUNTER STACK REGISTERS | |
|---------------------------|-----------|---|---|---|---|---|-------|---|---|---|---------------------------------------|---|
| | A | B | C | D | E | H | L | C | P | Z | | S |
| USED IN MAIN LINE PROGRAM | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | |
| USED IN INTERRUPT PROGRAM | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | |

Figure 17.12.1--Status Usage Chart, Example I

17.12.2 *Hardware* To make this system possible, the hardware contains a register connected to the OUTPUT 16 and INPUT 6 ports, and a second register connected to the OUTPUT 17 and INPUT 7 ports.

17.12.3 *Interrupt Subroutine Restrictions* The interrupt subroutine can use all index registers and flags. There are eight total program counter stack registers available, and both the main line program, and the interrupt program, must use at least one PC register apiece. This leaves six additional PC stack levels which can be distributed between the main line program and the interrupt program, according to the demands of the software. The boxes in the chart above are left blank to be filled in by the user.

17.12.4 *Software Required* The remaining figures in this section show the software needed for saving and unsaving status using this design example.

SEC. 17.12 STATUS-SAVING SYSTEM, EXAMPLE I (cont'd)

```

OUT 16  SAVE A REGISTER IN HARDWARE.
LAL
OUT 17  SAVE L REGISTER IN HARDWARE.
LAH
LLI 000  SET L RAM SAVE.
LHI 040  SET H RAM SAVE.
LMA     SAVE H REGISTER.

```

Figure 17.12.2--Example I: Saving Status, Part 1, A, H, L Registers

```

LAI 000  ASSUME ZERO.
JTZ SAVC IF TRUE GET CARRY BIT.
LAI 060  ASSUME POSITIVE.
JFS SAVC IF TRUE GET CARRY BIT.
LAI 300  SIGN FLAG WAS SET.
SAVC RAR GET CARRY BIT.
JTP SAVF JUMP IF PARITY IS EVEN.
XRI 001  SET PARITY ODD.
SAVF INL POINT TOWARD NEXT RAM BYTE.
LMA     SAVE FLAG WORD.

```

Figure 17.12.3--Example I: Saving Status, Part 2, Flags

```

INL
LMB     SAVE B REGISTER.
INL
LMC     SAVE C REGISTER.
INL
LMD     SAVE D REGISTER.
INL
LME     SAVE E REGISTER.

```

RAM Locations used (assume RAM addressed at 040 000):

```

SAV DEF 0  SAVE H REGISTER BYTE.
DEF 0     SAVE FLAG WORD.
DEF 0     SAVE B REGISTER.
DEF 0     SAVE C REGISTER.
DEF 0     SAVE D REGISTER.
SAVE DEF 0 SAVE E REGISTER.

```

Figure 17.12.4--Example I: Saving Status, Part 3; B, C, D, E Registers



SEC. 17.12 STATUS-SAVING SYSTEM, EXAMPLE I (cont'd)

```

LHI      040
LLI      000
LEM      UNSAVE E
DCL
LDM      UNSAVE D
DCL
LCM      UNSAVE C
DCL
LBM      UNSAVE B

```

Fig. 17.12.5--Example I: Restoring Status, Part 3; B, C, D, E Registers

```

DCL
LAM      GET FLAG WORD.
DCL      POINT TOWARD H REGISTER.
ADA      RESTORE ALL FLAGS.

```

Fig. 17.12.6--Example I: Restoring Status, Part 2; Flags

```

LHM      RESTORE H REGISTER.
INP 7    GET SAVED L REGISTER.
LLA      RESTORE L REGISTER.
INP 6    RESTORE A REGISTER.
RET      RETURN TO MAIN LINE PROGRAM.

```

Fig. 17.12.7--Example I: Restoring Status, Part 1; A, H, L Registers

SEC. 17.13 STATUS-SAVING SYSTEM, EXAMPLE II

17.13.1 *Description* This microcomputer has only one page (256 bytes) of RAM and is designed in the manner described in the section in Chapter 13 on the *RAM-PAGE* option. The main line program uses only the Sign, Carry, and Zero flags, never testing the Parity flag. In addition, the main line program never uses the E register.

| STATUS USE | REGISTERS | | | | | | | FLAGS | | | | PROGRAM COUNTER STACK REGISTERS |
|---------------------------------|-----------|---|---|---|---|---|---|-------|-----|---|---|--|
| | A | B | C | D | E | H | L | C | P | Z | S | |
| USED IN MAIN LINE PROGRAM | ✓ | ✓ | ✓ | ✓ | | ✓ | ✓ | ✓ | (1) | ✓ | ✓ | |
| USED IN INTERRUPT PROGRAM | ✓ | ✓ | | | | ✓ | ✓ | ✓ | ↑ | ✓ | ✓ | |

Fig. 17.13.1--Status Usage Chart, Example II

17.13.2 *Hardware* No hardware save registers are needed in this example. Because the main line program does not use the E register, and the *RAM-PAGE* option is used, software alone is sufficient to save status.

17.13.3 *Interrupt Subroutine Restrictions* The interrupt subroutine can use only the A, B, H, and L registers. It always sets the Parity flag to logic one before returning to the main line program. (This is indicated graphically in the chart above.)

17.13.4 *Software Required* The following figures show the software needed for saving and unsaving status using this design example.

```

LEL      MOVE L TO E TEMPORARILY.
LLI SAVA
LMA      SAVE A REGISTER.

```

Fig. 17.13.2--Example II: Saving Status, Part 1; A and L Registers

SEC. 17.13 STATUS-SAVING SYSTEM, EXAMPLE II (cont'd)

```

LAI 000  ASSUME ZERO.
JTZ SAVC IF TRUE GET CARRY BIT.
LAI 060B ASSUME POSITIVE.
JFS SAVC IF TRUE GET CARRY BIT.
LAI 300B SIGN FLAG WAS SET.
SAVC RAR  GET CARRY BIT.
INL      POINT TOWARD RAM FLAG BYTE.
LMA      SAVE FLAG INFORMATION.

```

Figure 17.13.3--Example II: Saving Status, Part 2; C, Z, S Flags

```

INL
LMB      SAVE B REGISTER
INL
LMH      SAVE H REGISTER
RAM Locations used in saving status
SAVA DEF 0  SAVE A REGISTER BYTE.
SAVF DEF 0  SAVE FLAGS.
SAVB DEF 0  SAVE B REGISTER BYTE.
SAVH DEF 0  SAVE H REGISTER BYTE.

```

Figure 17.13.4--Example II: Saving Status, Part 3; B and H Registers

```

LHI SAVB
LLI SAVB
LBM

```

Figure 17.13.5--Example II: Restoring Status, Part 3; B Register

```

DCL      POINT TOWARD SAVF.
LAM      GET FLAG WORD.
DCL      POINT TOWARDS SAVED A REGISTER.
ADA      RESTORE S, C, + Z FLAGS, SET PARITY BIT TO ONE.

```

Figure 17.13.6--Example II: Restoring Status, Part 2; C, Z, S Flags

SEC. 17.13 STATUS-SAVING SYSTEM, EXAMPLE II (cont'd)

```

LAM      RESTORE A REGISTER.
LLI SAVH
LHM      RESTORE H REGISTER.
LLE      RESTORE L REGISTER.
RET      RETURN TO MAIN PROGRAM.

```

Figure 17.13.7--Example II: Restoring Status, Part 1: A, H, L Registers

The fact that the Parity bit is always set by the restore status routine in Figure 17.13.6 above implies that the occurrence of an interrupt can be detected by the main line program. A program which shows the normal way of waiting until after an interrupt has occurred before proceeding is shown below, in Figure 17.3.8:

```

HLT      WAIT FOR INTERRUPT BEFORE CONTINUING.

```

Figure 17.3.8--Example II: Main Line Program Waits for Interrupt

The main line program will halt until interrupted. After the interrupt, the program will continue with the instruction which follows the HLT.

The program in Figure 17.13.9 also provides a pause in the main line program while waiting for an interrupt, but at the same time, checks for a switch closure occurring on input 4, bit 7.

```

LAI 001  LOAD ODD PARITY WORD.
ORA      RESET PARITY FLAG
LOOP INP 4  GET INPUT 4 WORD.
RAL      MOVE BIT 7 TO CARRY.
CFC SWCH  CALL ROUTINE IF SWITCH IS CLOSED.
JFP LOOP  CHECK SWITCH AGAIN UNLESS INTERRUPT HAS OCCURRED.

```

Figure 17.13.9--Main Line Program Checks Switch While Awaiting Interrupt



SEC. 17.14 STATUS-SAVING SYSTEM, EXAMPLE III

17.14.1 *Description* In this simple system, the main line program does not use the D or E registers. It uses only the Sign and Zero flags.

| USE \ STATUS | REGISTERS | | | | | | FLAGS | | | | PROGRAM COUNTER STACK REGISTERS | | |
|---------------------------|-----------|---|---|---|---|---|-------|---|---|---|---------------------------------------|---|---|
| | A | B | C | D | E | H | L | C | P | Z | | S | |
| USED IN MAIN LINE PROGRAM | ✓ | ✓ | ✓ | | | | | ✓ | ✓ | | | ✓ | ✓ |
| USED IN INTERRUPT PROGRAM | ✓ | | | | | | | | | ✓ | ✓ | ✓ | ✓ |

Fig. 17.14.1--Status Usage Chart, Example III

17.14.2 *Hardware* No special hardware functions are added.

17.14.3 *Interrupt Subroutine Restrictions* The interrupt subroutine uses only the A register; it may use all four flags.

17.14.4 *Software Required* See the remaining figures in this section.

```
LEA    SAVE A REGISTER.
```

Fig. 17.14.2--Example III: Saving Status, Part 1; A Register

```
LAI 000  ASSUME ZERO.
JTZ SAVZ  PUT AWAY IF ZERO.
LAI 060  ASSUME POSITIVE.
JFS SAVZ  PUT AWAY IF POSITIVE.
LAI 300B SET NEGATIVE.
SAVZ LDA  SAVE FLAG WORD IN D REGISTER.
```

Fig. 17.14.3--Example III: Saving Status, Part 2; Z, S Flags

SEC. 17.14 STATUS-SAVING SYSTEM, EXAMPLE III (cont'd)

(Not Needed.)

Fig. 17.14.4--Example III: Saving Status, Part 3

(Not Needed.)

Fig. 17.14.5--Example III: Restoring Status, Part 3

```
LAD    GET FLAG WORD.
ADA    RESTORE S, Z FLAGS.
```

Fig. 17.14.6--Example III: Restoring Status, Part 2; Z and S Flags

```
LAE    RESTORE A REGISTER.
RET    RETURN TO MAIN LINE PROGRAM.
```

Fig. 17.14.7--Example III: Restoring Status, Part 1; A Register

Example III shows how simple a status-saving procedure can be, when only the essential flags and registers are saved. It is important to use the simplest approach, whenever possible.

SEC. 17.15 STATUS-SAVING SYSTEM, EXAMPLE IV

17.15.1 *Description* The interrupt is caused by an interval timer.

The interrupt program is designed to test whether the transmit buffer is empty on a UART (Universal Asynchronous Receiver/Transmitter). If it is not empty, i.e., there is information ready for transmission, the interrupt routine returns to the main line program. If the UART transmit buffer is empty, the transmit buffer is loaded from a location in RAM, and the interrupt subroutine returns to the main line program.

The system has more than one page of RAM.

The UART transmit buffer empty flag is connected to the high-order bit of input port number 5. The main line program uses the Parity, Zero, and Sign flags, but never uses the Carry bit. The D and E registers are never used in the main line program.

| USE \ STATUS | REGISTERS | | | | | | FLAGS | | | | PROGRAM COUNTER STACK REGISTERS | |
|---------------------------------|-----------|---|---|---|---|---|-------|---|---|---|---------------------------------------|---|
| | A | B | C | D | E | H | L | C | P | Z | | S |
| USED IN MAIN LINE PROGRAM | ✓ | ✓ | ✓ | | | ✓ | ✓ | | ✓ | ✓ | ✓ | 5 |
| USED IN INTERRUPT PROGRAM | ✓ | | | | | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | 1 |

Figure 17.15.1--Status Usage Chart, Example IV

17.15.2 *Hardware* The UART is connected to the microcomputer input port as described above. No special hardware is needed for the specific purpose of saving or restoring status.

17.15.3 *Interrupt Subroutine Restrictions* The interrupt subroutine can use the A, H, and L registers, and all flags. It uses only one PC stack register.

SEC. 17.15 STATUS-SAVING SYSTEM, EXAMPLE IV (cont'd)

17.15.4 *Software Required* The first part of the interrupt subroutine (Figure 17.15.2) tests the UART TR buffer to see whether it is empty. If it is not empty, it returns to the main line program. This part of the program is very fast, yet it restores all necessary status before returning.

```

000 070   LEA       SAVE A REGISTER.
000 071   INP 005   GET TR EMPTY FLAG FROM UART.
000 072   RAL      MOVE FLAG INTO CARRY BIT, WITHOUT DISTURBING
                   P, Z, S FLAGS.
000 073   LAE      RESTORE A REGISTER.
000 074   RFC      RETURN IF TR BUFFER NOT EMPTY.

```

Fig. 17.15.2--Example IV: Saves, Unsave Status While Testing UART

In the main body of the interrupt program in Figure 17.15.3, the reader may, as an exercise, identify the instructions which save and unsave each needed register and flag, and compare these to the numbered steps in the preceding sections of this chapter.

SEC. 17.15 STATUS-SAVING SYSTEM, EXAMPLE IV (cont'd)

| LOCATION | INSTRUCTION | COMMENT |
|----------|-------------|--|
| 000 075 | LDH | SAVE H REGISTER. |
| 000 076 | LEL | SAVE L REGISTER. |
| 000 077 | LHI 040 | POINT TOWARD PAGE IN RAM. |
| 000 101 | LLI 370 | POINT TOWARD LOCATION IN PAGE. |
| 000 103 | LMA | SAVE A REGISTER. |
| 000 104 | LAI 000 | ASSUME ZERO. |
| 000 106 | JTZ 000125 | IF ZERO GO SAVE. |
| 000 111 | LAI 060 | ASSUME POSITIVE. |
| 000 113 | JFS 000120 | JUMP IF POSITIVE. |
| 000 116 | LAI 300 | SIGN FLAG WAS SET. |
| 000 120 | JTP 000125 | JUMP IF PARITY IS EVEN. |
| 000 123 | XRI 001 | SET PARITY ODD. |
| 000 125 | INL | POINT TOWARD NEXT RAM BYTE. |
| 000 126 | LMA | SAVE FLAG WORD. |
| 000 127 | INL | LOCATION OF BUFFER POINTER (040 372). |
| 000 130 | LLM | |
| 000 131 | INH | PAGE CONTAINING TRANSMIT BUFFER. |
| 000 133 | LAM | GET NEXT CHARACTER TO TRANSMIT. |
| 000 134 | ORA | SET FLAGS. |
| 000 135 | JTZ 000152 | ZERO MEANS BUFFER EMPTY, GO RESTORE STATUS AND EXIT. |
| 000 140 | OUT 015 | OUTPUT NEW CHARACTER TO UART. |
| 000 141 | XRA | LOAD ZERO TO A REGISTER. |
| 000 142 | LMA | NOTE CHARACTER HAS BEEN TRANSMITTED. |
| 000 143 | DCH | POINT TOWARD . . . |
| 000 144 | LLI 372 | . . . BUFFER POINTER. |
| 000 146 | LAM | GET BUFFER POINTER. |
| 000 147 | ADI 001 | INCREMENT POINTER. |
| 000 151 | LMA | REPLACE POINTER. |
| 000 152 | LHI 040 | POINT TOWARD . . . |
| 000 154 | LLI 371 | . . . SAVED FLAGS. |
| 000 156 | LAM | GET FLAG WORD. |
| 000 157 | DCH | POINT TOWARD SAVED A REGISTER. |
| 000 160 | ADA | RESTORE FLAGS. |
| 000 162 | LAM | RESTORE A REGISTER. |
| 000 163 | LHD | RESTORE H REGISTER. |
| 000 164 | LLE | RESTORE L REGISTER. |
| 000 165 | RET | RETURN TO MAIN-LINE PROGRAM. |


Figure 17.15.3--Main Body of Interrupt Program, Including Saving, Restoring Status

SEC. 18.1 INTERVAL TIMERS

Two types of interval timer are discussed in this chapter. The first is used to interrupt the microprocessor. The second is connected to an input port, so that the microcomputer can find out what time it is by executing an input instruction. Either interval timer may be preset to a given value with an output instruction.

SEC. 18.2 INTERRUPT INTERVAL TIMER

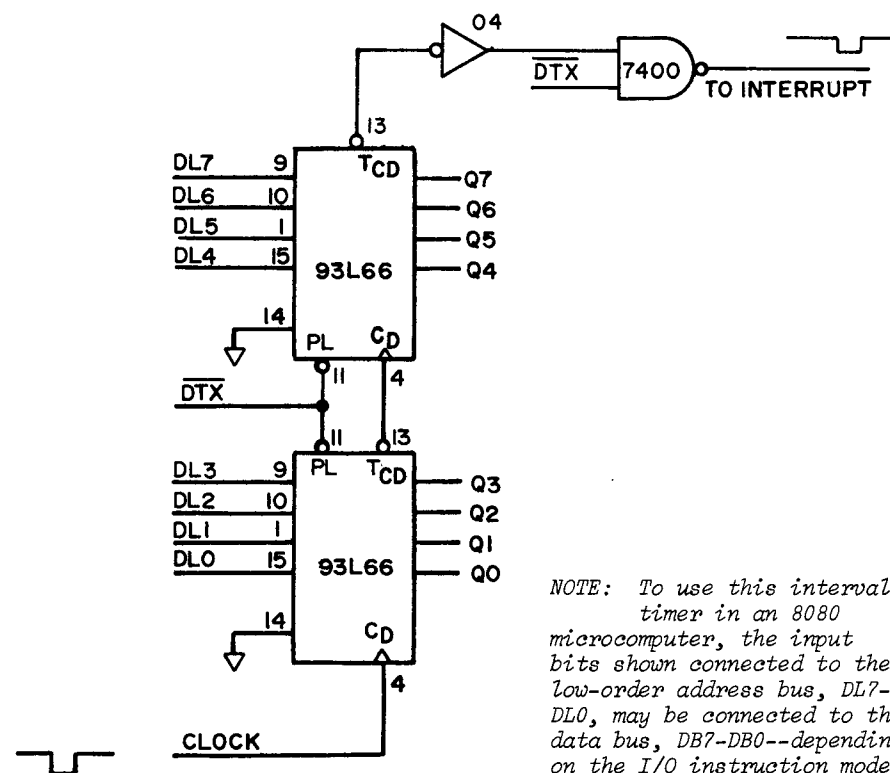An eight-bit presetable interval timer requiring only two integrated circuits is shown in Figure 18.2.1. Its only output is the underflow (borrow) terminal, which is connected to an interrupt port of the CPU. (See 16 on interrupts generally.) The NAND gate avoids the possibility of a false interrupt occurring during the parallel load.



NOTE: To use this interval timer in an 8080 microcomputer, the input bits shown connected to the low-order address bus, DL7-DL0, may be connected to the data bus, DB7-DB0--depending on the I/O instruction mode being used. See Chapter 7.

Fig. 18.2.1--Presetable Interval Timer Interrupts CPU When Counters Underflow

SEC. 18.2 INTERRUPT INTERVAL TIMER (cont'd)

The counters may be loaded to any desired eight-bit value with an output instruction. The output strobe, \overline{DTX} , enables the counters' active-low PARALLEL LOAD (PL) terminals. The clock causes the counters to decrement towards zero, and at the clock time following the counters' having reached an all-zero count, the BORROW terminal goes low. Figure 18.2.2 shows the number 005 (octal) being loaded into the interval timer, and an interrupt strobe being generated six clock periods later. The counter outputs, labeled Q7 through Q0 in Figure 18.2.1, need not be connected to the microprocessor at all. In this example, they are used only to illustrate circuit timing in Figure 18.2.2.


 


Fig. 18.2.2--Counters Loaded with 005; Count to Zero; Cause Interrupt

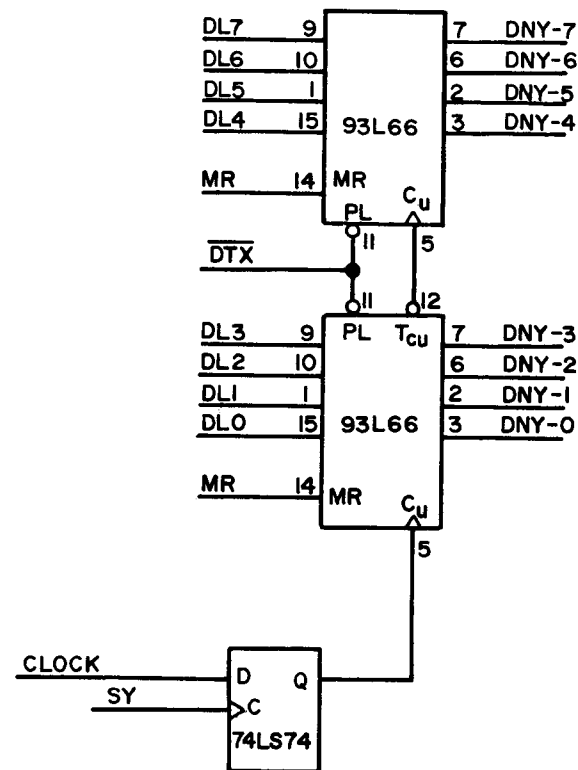

SEC. 18.3 TIMERS FOR INPUT PORTS

18.3.1 MULTIPLEXER INPUTS Another approach to interval timer design is to require the microcomputer to read the time by executing an input instruction. Figure 18.3.1 shows a circuit with TTL outputs suitable for use with an eight-bit microcomputer with a multiplexer input structure. (Input designs: see Chapter 8.) Like the circuit in the previous section, the microcomputer can preset this timer by executing an *Output X* instruction, strobing the counters' PARALLEL LOAD terminals. Here the counters are connected to count up, and the timer's eight-bit output is connected to the input terminals of a multiplexer array. An *Input Y* instruction switches the multiplexer to the *DNY* position, and the setting of the interval timer is read by the microprocessor.



NOTE: To use this interval timer in an 8080 microcomputer, the input bits shown connected to the low-order address bus, DL7-DL0, may be connected to the data bus, DB7-DB0-- depending on the I/O instruction mode used. See Chapter 7.

In an 8080 system, use PH2T rather than SYNC-- which, in an 8080 system, stops in the hold mode.

Fig. 18.3.1--Interval Timer for Multiplexed Input



SEC. 18.3 TIMERS FOR INPUT PORTS (cont'd)

It is necessary to ensure that the counters do not change state during an input instruction, or else the CPU might garble its input data. The appropriate method for doing this depends on the speed of the clock pulse and on whether the clock can be related conveniently to the timing pulses already available within the microcomputer. In Figure 18.3.1, a relatively low-speed clock is connected to the D input of a D-type flip-flop. In the circuit shown, the clock signal derives from the SYNC (SY) signal developed in the main timing circuitry of an 8008 microcomputer.

When the repetition rate of the SY signal (4.0 μ s for a standard 8008 clock) is orders of magnitude higher than the clock source, the slight jitter caused by the asynchronous relationship between the clock and the SYNC signal is negligible. But the circuit can be made synchronous by deriving the low-speed clock from the main timing oscillator.

The clock is gated through a D-type flip-flop, using a synchronization signal from the CPU to assure stable counter outputs during data transfer onto the microcomputer bus. In Figure 18.3.1, the rising-edge positive pulse, needed by the 93L66 to count, can appear only when the input clock signal has just changed from zero to one, and SY goes high. This occurs at the beginning of T3A time, as the input cycle begins. In an 8080 microcomputer, the signal PH2T (the clock signal) may be used in place of SY. This signal occurs even when the CPU is in the hold mode, unlike SY.

18.3.2 Bus-Structure Inputs The interval timer in Figure 18.3.2 is designed to output directly onto the microprocessor input bus. The counters used are therefore three-state devices. The DM8554s shown are binary (sixteen-count) devices; the DM8552, a pin-compatible decimal (BCD) counter, could also be used. These types include internal latches between the counters and the output stages. When the TE (*transfer enable*) pin is low, the outputs cannot change. This pin is strobed by a timing signal derived from the microprocessor, to make sure that the outputs do not change while the interval timer is driving the microcomputer bus.

In the circuit of Figure 18.3.2, a synchronized clock signal (CLKS) is developed by the same flip-flop circuit discussed in a previous section.

SEC. 18.3 TIMERS FOR INPUT PORTS (cont'd)

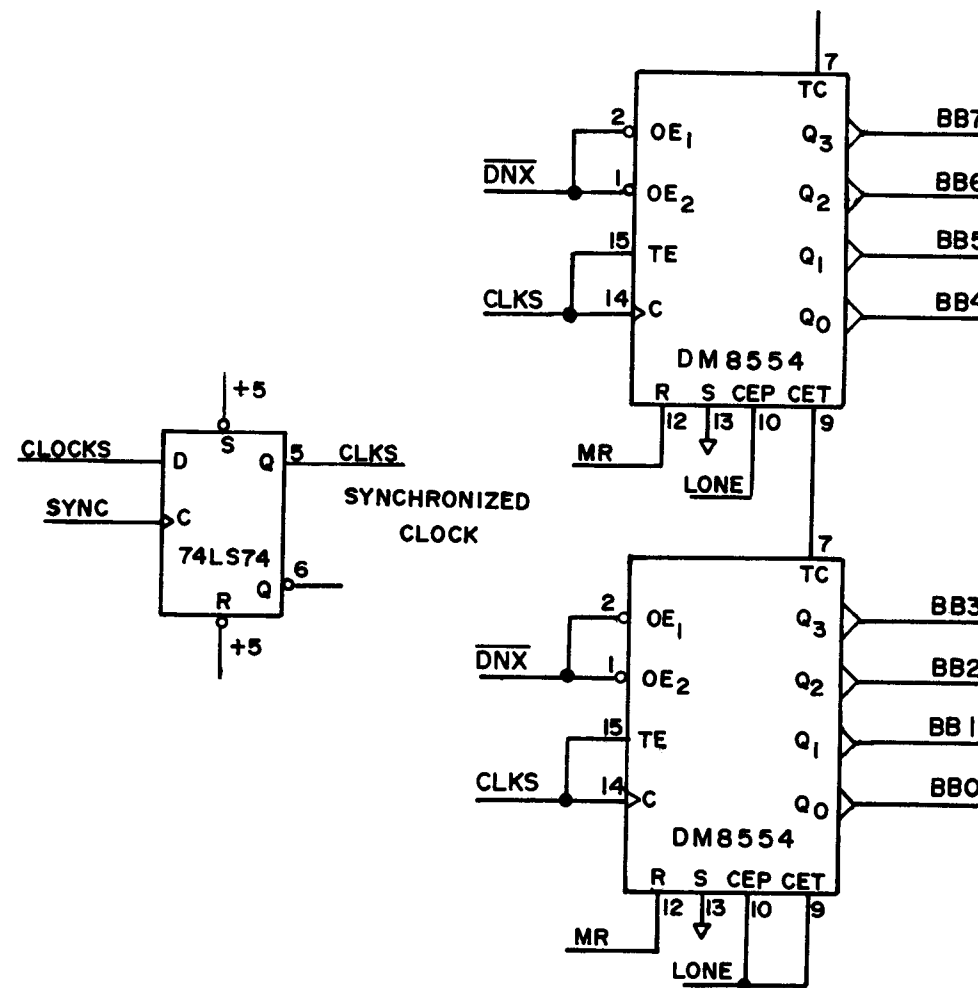


Figure 18.3.2--Timer for Use with Bus-Structured Inputs



SEC. 18.3 TIMERS FOR INPUT PORTS (cont'd)

 


Figure 18.3.3--Timing Diagram for Figure 18.3.2 (8008 System)

Figure 18.3.3, the timing diagram for Figure 18.3.2, shows the low-order bit from the timer being loaded onto the low-order line of the microcomputer data bus (BBO). The instruction cycle designations, and timing signals generally, are for an 8008 system. The counter may change states (count) at the beginning of the DNX enable signal. However, the TTL counter is much faster than the MOS CPU, and the count will settle down on the bus long before the CPU transfers the information from its data bus to its internal b register.

With the 8080, the PH2T signal should be used instead of SYNC. In an 8080 system, the SYNC signal is suspended during hold operations.

Note that, unlike the two preceding designs, the interval timer of Figure 18.3.2 cannot be preset using a microcomputer output instruction. If this feature is desired in an interval timer connecting to the CPU input bus, the circuit of Figure 18.3.1 could be used, interposing three-state buffers between the 93L66 and the bus.



SEC. 18.4 CLOCKS FOR INTERVAL TIMERS

The microcomputer itself needs a clock to drive its main timing circuitry, as discussed in Chapter 5 above. In many cases the same clock can do double duty by driving the interval timer. The frequency count-down inherent in the microcomputer main timing logic can be utilized by using a signal like $\phi 1$ or $\phi 2$. Further time division will require precounters.

SEC. 18.5 PRECOUNTERS

In many cases, the interval timer must develop signals several orders of magnitude slower than those available either from the main timing logic, or from a separate crystal oscillator using a small, reasonably-priced crystal. If accuracy is not a prime concern, of course, a multivibrator based on a timer IC like the 555 could be used. But usually a precounter is more suitable, inserted between a fast signal source in the main timing logic and a presettable interval timer circuit of the type shown earlier in this chapter.

A precounter can be cleared or reset by the same signal (or its complement) used to strobe the presettable stages, in order to assure a predictable pulse interval.



SEC. 19.1 DIGITAL DISPLAYS

An increasing number of electronic products use digital displays to convey information to their operators. Several technologies are available: notably the cold-cathode discharge tube, typified by the Nixie tube trademarked by the Burroughs Corporation; the fluorescent tube; the liquid crystal display, which is coming into its own in low-power applications; and the light-emitting diode (LED) display. We limit discussion to LEDs, not because they are best in every application, but because they interface most easily with TTL circuitry. Cold cathode and fluorescent displays require high-voltage power supplies; liquid crystals require AC drive circuitry and are difficult to multiplex--and though these are not complex problems to surmount, they take us beyond the scope of this book. A small suitcase of valuable applications literature can easily be collected from the manufacturers of the displays and of the integrated circuits used to drive the displays.

SEC. 19.2 SEGMENT DECODERS

The standard method of driving a seven-segment LED display employs a segment decoder such as the 7447 or 9357 TTL IC. A four-bit binary-coded decimal (BCD) signal is presented to its inputs; the chip's active low outputs are connected through current-limiting resistors directly to the LED display. See Figure 19.2.1.

 


Fig. 19.2.1--Decoder Drives LED Display

In a microprocessor-based system the BCD input to the decoder usually derives from a latching device. The microprocessor executes an output instruction which strobes the latch and transfers the data on the output bus into the display. The digit displayed does not change until the next output instruction is executed. One method is to use separate latches and decoders, as shown below in Figure 19.2.2.

SEC. 19.2 SEGMENT DECODERS (cont'd)

A reduction in power consumption results when an LED display is pulse-modulated. For example, if an LED is operated with a 25% duty cycle, the peak current required for brightness equal to that obtained with a DC supply would apparently be four times the DC requirement. However, the human eye tends to respond to peak intensities, so that the required power for apparent equal brightness will be as much as 30% less than the DC value. A disadvantage: extra bypass capacitors may be required on the power supply to suppress switching transients. A convenient method of achieving pulse modulation is to strobe the ripple-blanking input (RBI terminal) of the 7447 segment decoder, as shown in Figure 19.2.2.

This schematic also shows the connection of the ripple-blanking terminals of the 7447 decoders to suppress non-significant zeros. Thus the number 042,300 is displayed 42.3. The RBO (ripple-blanking output) terminals of the 7447s are connected to DTL-type circuitry within the decoders, so that open-collector buffers may be used (as shown) to pull these terminals low. A separate open-collector buffer is provided for each segment decoder, to allow a switching arrangement to change the position of the decimal point. Note that shifting the decimal point with this all-hardware approach might require a relatively complex switching arrangement.

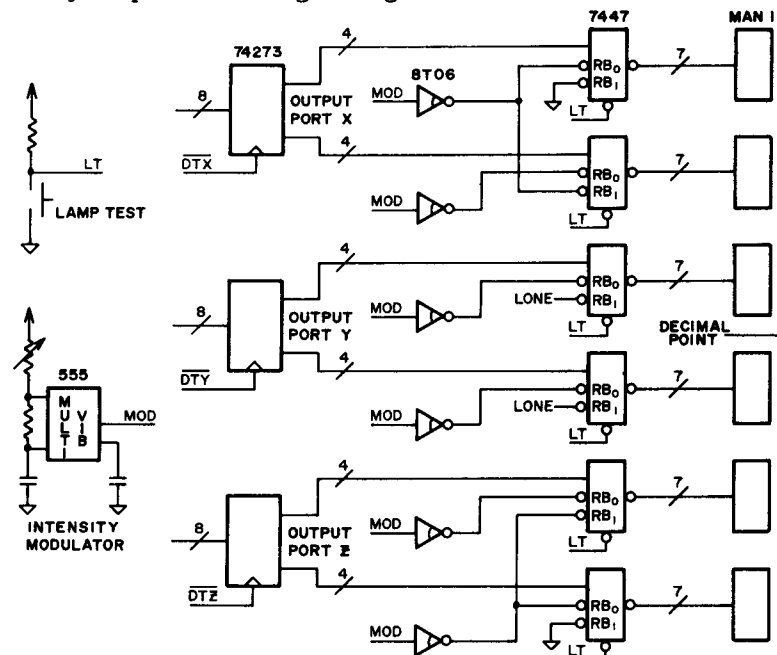


Figure 19.2.3--Zero-Suppression Using Hardware



microcomputer
design

SEC. 19.2 SEGMENT DECODERS (cont'd)

An integrated circuit which combines the latching and segment decoding functions is the 9368. This chip is utilized in the circuit for an octal display in Chapter 24, useful to the design engineer in developing and testing microcomputers. Note that the circuit shown there makes use of BCD decoders for octal display purposes simply by grounding the A3 input of the decoder.

SEC. 19.3 MULTIPLEXING

In a multi-digit system, a significant savings in gates results from multiplexing. The segment decoders are timeshared by switching rapidly between digits. A typical scheme is shown in Figure 19.3.1. This figure shows the display connected to the output circuitry of a microcomputer. Two digits are addressed at one time with the output instruction; the latches store their values and the displays remain stable until addressed again. Note that, with the 7447 decoder, a decimal 15 (1111) input blanks the digit. The digits can therefore be blanked, when power is first applied to the equipment, by incorporating a few instructions in the power-on initialization subroutine stored in the microcomputer's ROM. These instructions need only load the accumulator with all logic ones, and then output to the digital displays, two digits at a time. Blanking nonsignificant zeros with a few extra instructions is not overly difficult.

If the 7447's ability to produce a blank display with a binary 1111 input is not needed, it may be replaced with an 8T59 decoder, with active-high current-source outputs, and the anode driver transistors eliminated. The 8T59 produces a creditable hex display from a four-bit binary input (... 9, A, b, C, d, E, F).



microcomputer
design

SEC. 19.3 MULTIPLEXING (cont'd)

SEC. 20.1 SYSTEMS

The best way to introduce this chapter is to restate the reasons for designing with microprocessors in the first place, as opposed to random logic. First, the ease of changing a design to upgrade a machine or meet new requirements. Merely changing the software stored in the microcomputer's read-only memory (ROM), and adding a few input or output interface chips, can redefine the machine. Second, a related point: microprocessors allow a great deal of flexibility in systems design. The heart of the machine--the microcomputer proper--can be the common element in a whole family of related products. A variety of different peripheral devices can be added with minimal extra design time or hardware.


Let us assume that the designer is working with a family of computer peripherals--CRT display, printer, send/receive terminal, etc.--based on a microprocessor. The microcomputer itself consists of the microprocessor, the auxiliary chips necessary for timing and input/output selection, ROM to store the programs, at least a minimal configuration of RAM for temporary data storage, and some general-purpose input and output interface chips. All of this fits on one printed circuit board. On separate boards go the components needed for the specialized functions of the machine: motor controls, deflection amplifiers, modems, etc. The same microcomputer board plugs into each of the final machines, and the ROM needed to store the appropriate instructions is plugged into a socket on this board.

SEC. 20.2 COST-EFFECTIVE MODULARITY

The goal is now to optimize the microcomputer design around the modular systems concept. Almost all of the logic needed to add a keyboard to the system, for example, should be located on the keyboard, and when a keyboard is not used with the microcomputer, almost none of the cost of that device should be included in the basic system. This design principle we call *cost-effective modularity*.

The development of an efficient bus structure for interfacing with peripheral devices requires the designer to pay attention not only to the current requirements of the system, but to potential changes and new interconnections in the future. Typically the pressure on the design engineer is such that he hardly has time to design a prototype, debug it, document it, and turn it over to the production department. Designing for optimum flexibility may seem like a luxury. But the engineer who develops a microcomputer which does not require extensive redesign for every new application, should find his work well appreciated.

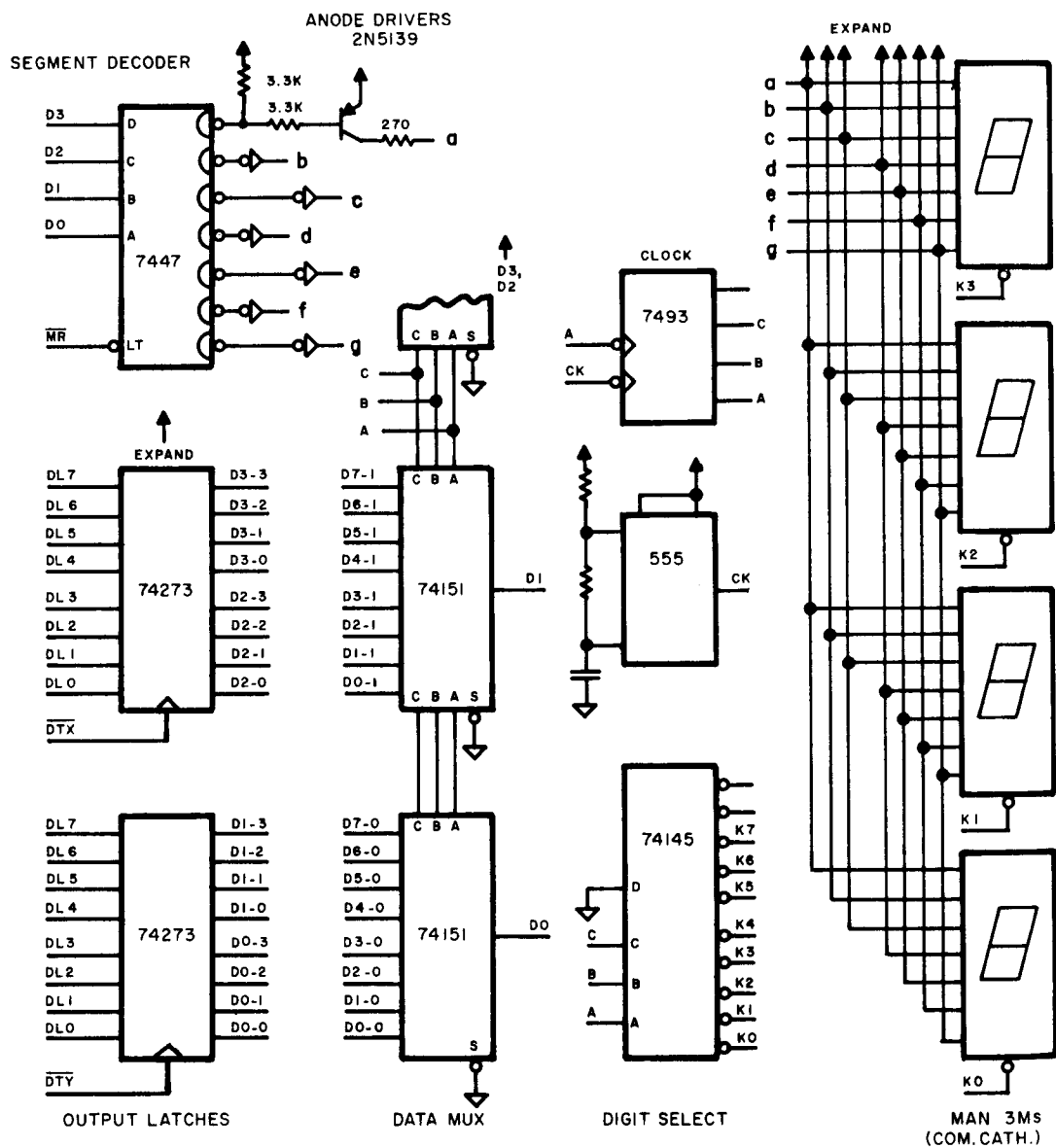The first step is to simplify the microcomputer's hardware--to recapitulate briefly from various sections of this book. One important



NOTE: In an 8080 microcomputer, output data may derive from the DB bus, rather than the DL bus: see Chapters 7, 9.

Figure 19.3.1--Multiplexed LED Display



SEC. 20.2 COST-EFFECTIVE MODULARITY (cont'd)

goal is to simplify microcomputer input and output selection. The standard method uses digital multiplexers, like those of the 74151 series. Thus for a eight-bit microprocessor with eight different input sources, the microcomputer would include the digital equivalent of an eight-pole, eight-throw switch. Up to sixty-four separate input lines could be needed to route data from the various inputs to the microprocessor. In a more complex system, extra multiplexers would be needed on the microcomputer board, and would take up space and power even when some of the input ports were not in use. And with TTL ICs, all multiplexer inputs which might not be connected in certain system configurations would need pull-up resistors. (Chapter 8 more fully describes these various input techniques.)

Modularity and flexibility are enhanced through use of a bus-structured system. The input devices are all connected through three-state integrated circuits to the same input bus, which leads directly to the input terminals of the microprocessor. Each three-state device is normally inactive and its output is floating--that is, its high-impedance state allows some other IC attached to the same bus to determine the logical state. Now only sixteen connections are needed--the eight input bus lines, and up to eight input strobe lines. This both simplifies the wiring on the microcomputer board, and minimizes the number of connections needed between the microcomputer and the other circuit boards in the machine. (This technique has been described more fully in Chapter 7.)

SEC. 20.3 AN EFFICIENT MICROCOMPUTER BUS STRUCTURE

An efficient bus structure for microcomputers is shown in Figure 20.3.1. Nearly all of the sections of the block diagram are described in detail in various sections of this book. Though the diagram shows external DH and DL address registers--as would be present in an 8008-based microcomputer--the structure is compatible with the 8080. A very similar design forms the basis of the modular micro series, as exemplified by the Model 471 CPU board, described near the end of this book.

20.3.1 Main Board/Peripheral Organization In this example, the system will be organized as follows--with control signals appropriate for an 8008 system:

- DH3 LOW during PCC I/O on main CPU board.
- DH3 HIGH during PCC I/O from a peripheral.
- DH5 LOW during PCI, PCR, PCW memory on main board.
- DH5 HIGH during PCI, PCR, PCW memory in peripherals.



SEC. 20.3 AN EFFICIENT MICROCOMPUTER BUS STRUCTURE (cont'd)

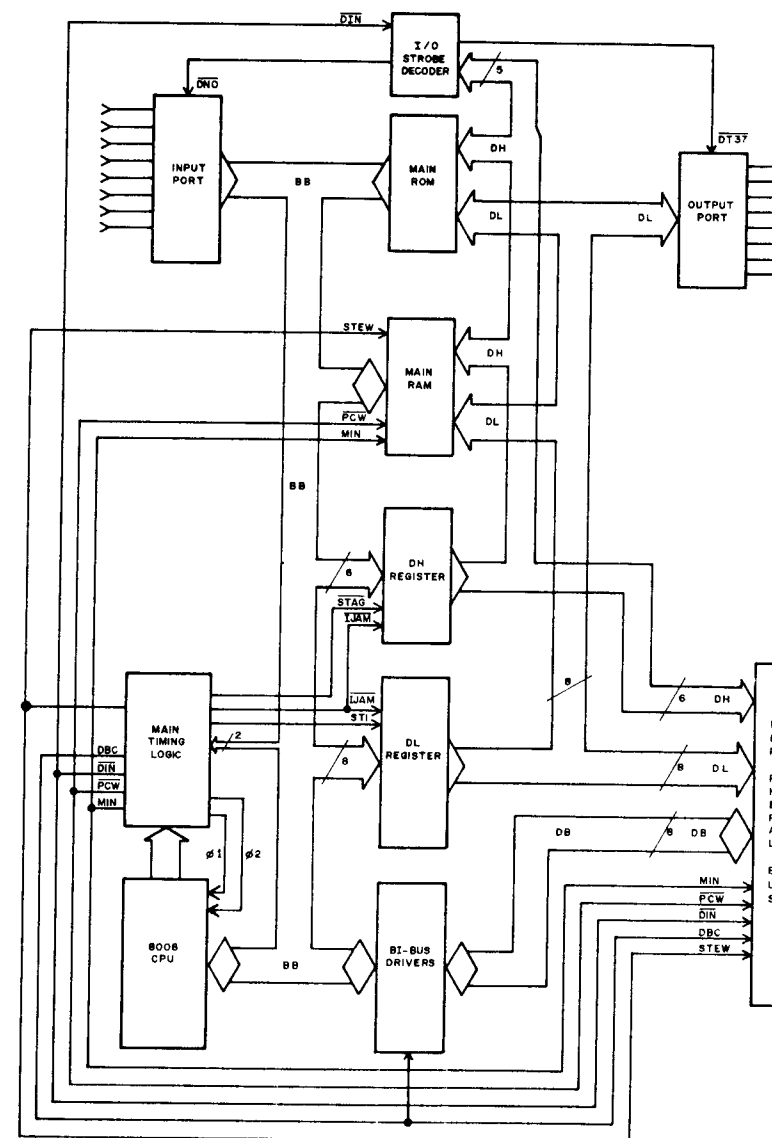


Fig. 20.3.1--An Effective 8008 Bus Structure for Peripheral Interfacing

SEC. 20.3 AN EFFICIENT MICROCOMPUTER BUS STRUCTURE (cont'd)

The above set of conditions for DH3 means that the following inputs and outputs can be used by various peripheral devices: OUT 36, 35, and 34; OUT 27, 26, 25, and 24; OUT 17, 16, 15, and 14; and INP 7, 6, 5, and 4. Each peripheral device develops its own strobe signals on board, using the peripheral strobe decoding techniques described in Chapter 7. Note the omission of OUT 37 above, which, as explained in Chapter 7, cannot readily be developed by the peripheral strobe decoder.

The remaining inputs and outputs may be used on the main CPU board. These include OUT 33, 32, 31, and 30; OUT 23, 22, 21, and 20; OUT 13, 12, 11, and 10; and INP 3, 2, 1, and 0. Since the strobes for OUT 37 and INP 0 cannot readily be developed on the peripheral boards, these two I/O ports may specifically be designated for use on the main CPU board--as shown in 20.3.1.

The constraints shown above for DH5 mean that the upper 8K of memory may be located on the peripheral boards, with the lower 8K of memory on the main CPU board. An example of a memory map which is consistent with this scheme is shown in Figure 20.3.2. Different configurations are possible, obviously.

| PAGE NO. | USAGE | PAGE NO. | USAGE | PAGE NO. | USAGE | PAGE NO. | USAGE |
|----------|---------|----------|----------|----------|-------|----------|-------|
| 077 | RAM, | 057 | PROM P#3 | 037 | MAIN | 017 | MAIN |
| 076 | PERI- | 056 | PROM P#2 | 036 | RAM | 016 | ROM |
| 075 | PERAL | 055 | PROM P#1 | 035 | | 015 | |
| 074 | #1 | 054 | | 034 | | 014 | |
| 073 | | 053 | | 033 | | 013 | |
| 072 | | 052 | | 032 | | 012 | |
| 071 | | 051 | | 031 | | 011 | |
| 070 | | 050 | | 030 | | 010 | |
| 067 | RAM P#3 | 047 | ROM P#4 | 027 | | 007 | |
| 066 | RAM P#2 | 046 | | 026 | | 006 | |
| 065 | RAM P#4 | 045 | | 025 | | 005 | |
| 064 | | 044 | | 024 | | 004 | |
| 063 | | 043 | | 023 | | 003 | |
| 062 | | 042 | | 022 | | 002 | |
| 061 | | 041 | | 021 | | 001 | |
| 060 | | 040 | | 020 | | 000 | |

Fig. 20.3.2--Memory Map for Peripheral System

20.3.2 Data Bus Control In order to realize the benefits of a bus-structured system, the system shown in Figure 20.3.1 includes a bidirectional bus driver, effectively extending the CPU's bidirectional bus (BB) and providing what is here labeled simply as the data bus (DB). An eight-bit bidirectional bus driver



microcomputer design

SEC. 20.3 AN EFFICIENT MICROCOMPUTER BUS STRUCTURE (cont'd)

made up of two 74S241 integrated circuits is shown in Figure 20.3.3. The left-hand part of the drawing shows each element of the IC, and the right-hand part of the drawing presents the same circuit element in a more convenient schematic notation. Though not shown in the diagram, each three-state driver and direction control gate in the 74S241 employs Schmitt trigger circuitry. (The bidirectional bus driver was introduced in Chapter 6 above.)

 


Fig. 20.3.3--Eight-Bit Bidirectional Bus Driver

The signal which controls the direction of the driver ICs is called the data bus control (DBC); it is normally high, driving outwards from the main CPU board to the peripheral boards. DBC should go low only when the CPU board is receiving data from the peripheral boards. This happens only at T3A time, during one of the following instruction cycles:



microcomputer design

SEC. 20.3 AN EFFICIENT MICROCOMPUTER BUS STRUCTURE (cont'd)

PCC--during an input instruction, where the input port has been assigned to the peripherals.

PCI--when the instruction address refers to a location in memory which is assigned to the peripherals.

PCR--when the CPU is reading memory from a location assigned to the peripherals.

Given the system organization defined above, a logic diagram for generating DBC is shown here:

 


Fig. 20.3.4--Gates for Developing DBC Signal

In the above figure, some simplification results from the fact that CCI is high only during PCI and PCR cycles. If the PCC signal is not already available on the main CPU board, it may be developed here by ANDing CC2 and CCI.

Note also in the figure above that the bidirectional bus driver is allowed to point inwards during *output* instructions, when the output port being addressed is assigned to the peripherals. This is permissible, as discussed in the section in Chapter 8 on developing input enable signals. During T3A time of an output instruction, the CPU itself is not receiving from the data bus anyhow.

20.3.3 Other Control Signals The other control signals shown in Figure 20.3.1 have all been discussed in other sections of this book. Specifically: \overline{DNO} , $\overline{DT37}$, and \overline{DIN} , in Chapter 7 (\overline{DIN} under peripheral strobe decoding techniques); MIN, in Chapters 14 and 26; \overline{LJAM} , in Chapter 16; \overline{PCW} , STEW, STI, $\phi 1$, and $\phi 2$, in Chapter 5.

SEC. 21.1 KEYBOARDS AND MICROCOMPUTERS

Many digital devices--especially computer peripherals like terminals, displays, and printers--use keyboards to receive information from human operators. The keyboard is currently the fastest, most reliable way for a person to enter information into a system for digital processing. As microcomputer technology develops, bringing digital machinery into more and more widespread use, the combination of a keyboard plus a microprocessor is already becoming quite common.

This design is based on a modular systems concept, as discussed in Chapter 6 and elsewhere in this book. In order to simplify input and output selection, the microcomputer employs bus-structured designs. Almost all of the logic needed to add a keyboard to the system should be located on the keyboard, and when the keyboard is not used with the microcomputer, almost none of that cost should be included in the basic system.

SEC. 21.2 THE KEYBOARD ENCODER

The MM5740 keyboard encoder has ten scan inputs and nine scan outputs. ["MOS Keyboard Encoding," Application Note AN-80, National Semiconductor Corp., 2900 Semiconductor Drive, Santa Clara, CA 95051. Also, data sheet for the MM5740 90-Key Keyboard Encoder.] Each key is assigned to a unique combination of one input and one output, for up to 90 keys. Each keyswitch is wired between a scan input and scan output, with a diode in series, as shown in Figure 21.1.1. On low-cost keyboards, the diodes may be omitted, but if the operator depresses three keys simultaneously, extraneous characters will be generated. The diodes block sneak signal paths and eliminate the "phantom key" effect.

Internal ring counters scan both the key matrix and an internal read-only memory (ROM) simultaneously. A depressed key results in a pulse which causes the ROM word for that key to be transferred into a one-character (nine-bit) output latch. With the MM5740AAE, a standard part, the output word will include the seven-bit ASCII code for the last character recognized. (Custom-encoded chips are available.) B8 is a parity bit, not used in this design; B9, the selective repeat bit, is discussed below.

SEC. 21.2 THE KEYBOARD ENCODER (cont'd)

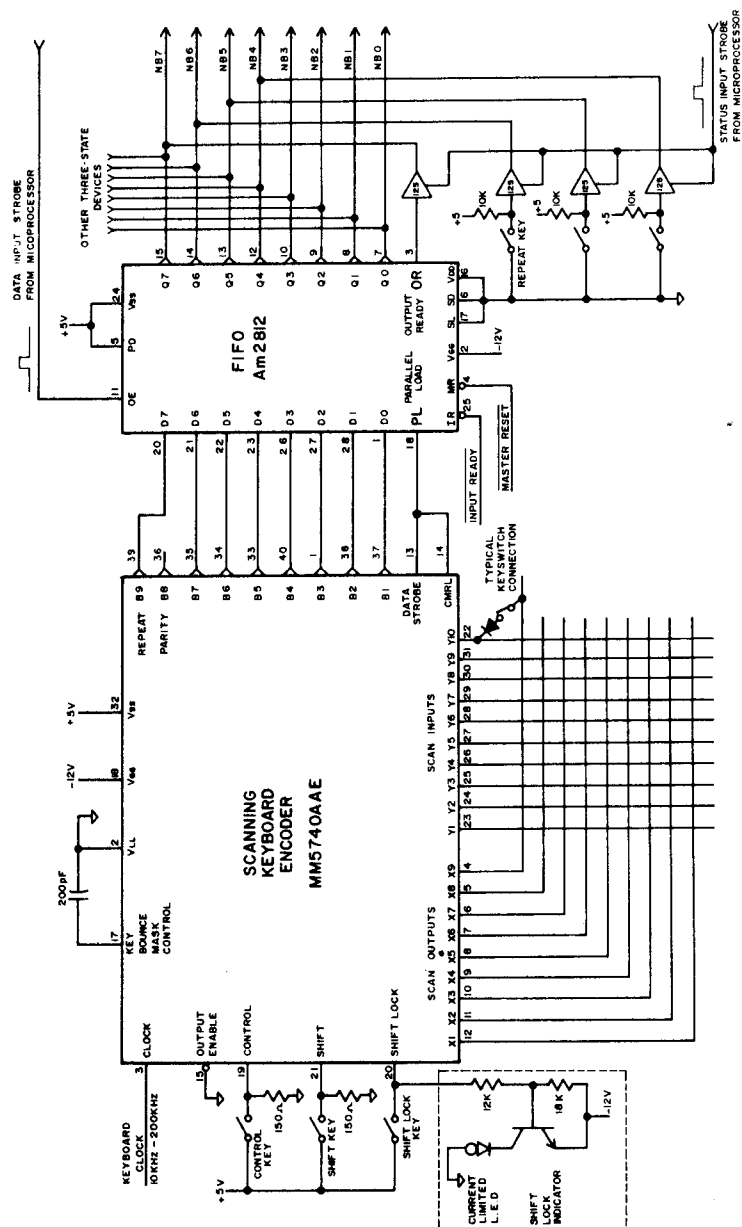


Fig. 21.2.1--Keyboard Interfaces with Microprocessor: Only Three Chips

SEC. 21.2 THE KEYBOARD ENCODER (cont'd)

Because a fast typist does not always release one key before hitting the next, the ideal keyboard responds only to key *closures*, without regard for how long each key is held down. The MM5740 implements this feature, *N-key rollover*, by feeding the key detect pulse into a 90-bit shift register and comparing the present status of each key with its condition the last time scanned. Only a transition from 0 to 1 (key closure) strobes the ROM word into the output latches.

Keyswitch contact bounce, which could cause unwanted repeated letters, is masked by initiating a delay of several milliseconds following detection of a depressed key, during which further closures are ignored. The capacitor shown at pin 17 produces the recommended delay.

The MM5740 requires an external clock oscillator in the 10- to 200 KHz range to drive the scanning counters. This signal is usually available elsewhere in the microcomputer--it can be derived from the microprocessor main timing circuit. Keyboard encoder chips which include clock oscillators, requiring only an external RC combination, are also available--though, so far, are less popular than the National MM5740: the S9021 [American Micro-Systems, 3800 Homestead Rd., Santa Clara, CA 95051]; the EA2000 [Electronic Arrays, 501 Ellis St., Mountain View, CA 94040]; and the KR2376-XX [Standard Microsystems, 35 Marcus Blvd., Hauppauge, NY 11787]. Each differs in features and performance.

In the MM5740, the shift, shift lock, and control mode keys are not scanned, but are sensed continuously by the encoder. In the circuit shown, a solid-state lamp displays the shift lock condition--instead of using mechanically interlocking shift and shift lock switches. Just as on an office typewriter, the operator removes the shift lock condition by stroking the shift key.

When the encoder recognizes a keystroke, it sets its DATA STROBE output to a logic one. This terminal is wired directly to the encoder's DATA STROBE CONTROL, an input terminal which resets the encoder output on the next falling edge of the keyboard clock. The data word is thus available at the encoder output for one keyboard clock period only, which allows the encoder to operate at maximum speed. However, if no more temporary storage were provided than the one character stored by the encoder, the microprocessor would have to test for keyboard data at a rapid rate, imposing unnecessarily severe restraints on its software.

SEC. 21.3 THE FIFO

The 2812 FIFO provides up to 32 characters of storage and made-to-order interfacing. ["Application of First-In First-Out Memories," John Springer, *Advanced Micro Devices*, 901 Thompson Place, Sunnyvale, CA 94086. Also, data sheet for the Am2812 32 x 8-Bit First-In First-Out Memory.] Its PARALLEL LOAD (PL) input is strobed by the encoder's DATA STROBE output, and loads a keyboard data word every time a keystroke is recognized. After a character is loaded into the FIFO, it bubbles down through the 32 positions until it reaches the output, or is stopped by a previous character. When there is at least one character stored in the FIFO, the 2812 OUTPUT READY signal will go to logic one. This signal is periodically tested by the microprocessor to see whether there is new data from the keyboard. With the 2812 providing buffer storage, the microprocessor needs to test for input data far less frequently.

The FIFO's PARALLEL DUMP (PD) control is permanently enabled by wiring it to +5 volts. But the parallel dump function is also internally gated with the OUTPUT ENABLE terminal, so that the first-received character will not be dumped until the OE terminal is activated. Thus a single strobe to the 2812 first reads the keyboard word into the microcomputer, and then dumps the word out of the FIFO, moving the next keyboard character into the output position. Figure 21.3.1 shows the timing. The delay (t_{oe}) between the leading edge of the DATA INPUT STROBE and the appearance of valid data on the microcomputer input bus is less than 40 ns for the 2812 (Figure 21.3.2).

The FIFO's registers are cleared out when power is first applied by a signal, MR, from the microcomputer's master reset circuit. This signal goes LOW for a fraction of a second and prevents the FIFO from taking on initial random states that could be interpreted as keyboard data.

SEC. 21.4 INPUT TO MICROPROCESSOR

The design discussed here is for an eight-bit microprocessor, like the 8008 or 8080, with bus-structured input circuitry. The input devices are connected together onto the same input bus, leading directly into the microprocessor's data input terminals. The input devices use three-state buffers.

SEC. 21.3 THE FIFO (cont'd)

 


Fig. 21.3.1--Scanning Keyboard Encoder Loads One Character into FIFO

 


Fig. 21.3.2--Inherent Bus Delay and Guaranteed Stability of Data During Transfer.



microcomputer
design



microcomputer
design

SEC. 21.4 INPUT TO MICROPROCESSOR (cont'd)

This system uses two input instructions for loading in information from the keyboard: STATUS INPUT and DATA INPUT. The microprocessor periodically does a STATUS INPUT instruction, sending a pulse down the STATUS INPUT STROBE line. This strobe activates a 74125 three-state buffer, which sends the FIFO's OR (*output ready*) bit onto the microprocessor bus, input bit 7 (NB7). The microprocessor tests this bit for the availability of keyboard data. If the bit is set to logic one, the microprocessor decides that keyboard data is ready, and then executes a DATA INPUT instruction. This instruction causes a strobe at the DATA INPUT STROBE line, which in turn activates the OE (*output enable*) terminal of the FIFO. Now the FIFO's three-state outputs are enabled, and the keyboard data word is impressed onto the microprocessor input bus.

The seven lower-order bits of the keyboard data word are the ASCII-encoded character. The high-order bit is the B9 output from the encoder, a selective repeat bit. The accomplishment of the repeating character function is one of the interesting features of this design.

SEC. 21.5 THE REPEAT FUNCTION

A repeating stroke--as for underlining and backspacing--could have been provided by connecting the MM5740 REPEAT terminal through a REPEAT keyswitch to an external 10-Hz clock. The MM5740AAE internal gating would allow repeated characters only when its selective repeat bit (B9) is logic one, as it is for X, the backspace, the hyphen, etc. However, this repeat circuit would require an external 10-Hz clock and therefore additional hardware.

In this design, B9 is simply connected to the high-order microprocessor input bus. The REPEAT switch is connected to the next most significant microprocessor bit through a 74125 three-state buffer. The repeat function can now be implemented through a few extra instructions in the microprocessor's programs. This technique obeys the first axiom in designing with microprocessors: software is better than hardware. Adding instructions to ROM is generally cheaper than adding chips.



microcomputer
design

SEC. 21.5 THE REPEAT FUNCTION (cont'd)

Two additional keyswitches can be used to enter data directly onto the microprocessor input bus, using the two remaining 74125 three-state buffers and the same STATUS INPUT instruction. These switches can be used for mode control or a variety of other functions.

Figure 21.5.1 shows a typical subroutine for testing for keyboard data, reading data into the microprocessor, and implementing the repeating character function.

| LABEL | INST. | ADDR. | COMMENTS |
|-------|-------|-------|--|
| CKKBD | INP | KBRDY | INPUT KEYBOARD DATA READY AND REPEAT SWITCH BITS. |
| | RAL | | ROTATE DATA READY BIT TO CARRY FLAG, REPEAT SWITCH BIT TO SIGN FLAG. |
| | RFC | | RETURN TO CALLER IF NO KEYBOARD DATA IS READY. |
| | INP | KDATA | INPUT KEYBOARD DATA. |
| | JFC | CHAR | GO PROCESS CHARACTER IF REPEAT SWITCH IS ON (CARRY = 0). |
| | NDI | 177B | MASK OUT SELECTIVE REPEAT (SIGN) BIT. |
| CHAR | | | <div style="border: 1px solid black; padding: 5px; margin: 5px 0;"> <p><i>Program to process characters-- will depend on the nature of the machine: terminal, display, printer, etc. 7-bit ASCII character is in A reg. If the sign bit is set, the repeat key is depressed AND the character is repeatable. Program must: save character and sign flag (eg, in B register) and come back to repeat the character so long as the switch is set; and, develop the appropriate repeat interval.</i></p> </div> |
| | JMP | CKKBD | CHECK FOR ANOTHER CHARACTER. |

Fig. 21.5.1--Typical 8008 Subroutine for Inputting Keyboard Data

Though the above program uses 8008 mnemonics, the 8080 version would be substantially identical. Translating: 8008 RFC = 8080 RNC; 8008 JFC = 8080 JNC.



microcomputer
design

SEC. 21.6 DOING IT WITH INTERRUPTS

Another method for interfacing a keyboard with the microprocessor should be mentioned here because it is often used: causing the FIFO's OR (*output ready*) signal to interrupt the microprocessor. In that case, the instructions for processing keyboard data would be part of the interrupt routine.

The microcomputer design shown in Chapter 26 contains a keyboard encoder which causes an interrupt when a key is struck.

SEC. 22.1 AN ANALOG INTERFACE SYSTEM FOR MICROCOMPUTERS

The microcomputer is, of course, a digital machine. In many applications, the microcomputer is called upon to sense continually varying analog inputs, or to provide an analog output signal. This chapter contains a brief introduction to simple analog circuitry suitable for interfacing with a microcomputer.

The system to be described receives analog input signals from up to eight channels; has provisions for adjusting the gain and bias of each channel manually for optimum digital resolution; and converts the analog signals to digital bytes for processing by the microcomputer. After digital processing, the microcomputer can reconvert the data to an analog output for analog measurements, control, or testing. This design is based on an actual instrument, a Data Multiplexer, which monitors physiological instrumentation (electrocardiograph, pressure transducers, etc.) in a medical laboratory; preprocesses the information; and dumps data periodically on demand into a large central computer.

SEC. 22.2 ANALOG INPUT AMPLIFIERS

The single-channel analog input amplifier shown in Figure 22.2.1 accepts a differential or single-ended analog input signal. The first stage is a conventional differential amplifier; the non-inverting input is connected to the output ground connection of the source instrument. This amplifier responds to the difference between the + and - inputs, which tends to cancel out ground loop noise. The 100 K ohm 10% resistor across the input terminals assures a zero stage output with open input terminals. The stage gain is -1.

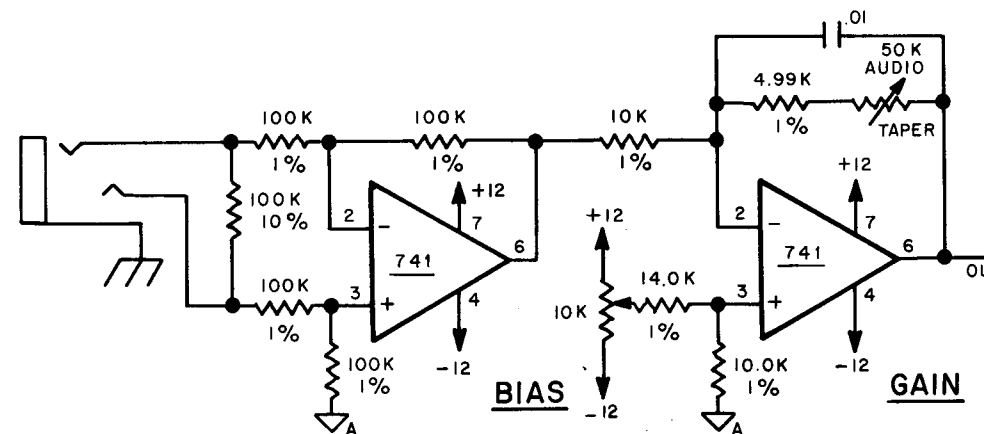


Fig. 22.2.1--Analog Input Amplifier with Gain and Bias Trimmers

SEC. 22.2 ANALOG INPUT AMPLIFIERS (cont'd)

The second stage has a gain control allowing manual adjustment in the range of -0.5 to -5. The inversion of the second stage restores the signal's original polarity. A second control biases the output voltage in the range of +5 to -5 volts. The output voltage range is limited to approximately +10 to -10 volts before clipping occurs.

The controls may be calibrated so that a given analog input voltage produces a standard digital result. Another mode of calibration is to adjust the controls so that the input voltage range corresponds closely to the range of the analog-to-digital (A/D) converter that follows. This leads to optimal digital resolution.

For example, assume that the A/D converter accepts voltages in the range of +5 to -5 volts (a 10-volt range). With the resistor values shown, this amplifier matches signals with peak-to-peak values of 2.0 to 20.0 volts to the converter. Signals with median values within plus or minus 5 volts of zero may be accommodated.

Note that once the analog gain settings are made for optimal resolution, further adjustments may be performed on the digital data using the microprocessor.

The capacitor shown causes the second op amp to function as a low-pass filter. Signals and noise above the frequency range of interest are kept out of succeeding stages. For this medical electronics application, a gradual rolloff is adequate. For some instrumentation, a higher-order active filter circuit may be required.

For an eight-channel system, eight of these dual op-amp circuits are required.

SEC. 22.3 ONE-CHANNEL TRACKING A/D CONVERTER

An effective A/D converter which is suitable for microcomputers needing only one analog input channel is shown in Fig. 22.3.1. Like many practical A/D designs, this circuit creates a trial eight-bit digital byte, and feeds it to a single-chip D/A converter (DAC). The analog result is compared to the analog input, and a digital error signal is used to readjust the trial digital byte.

This circuit is based on the MC1408L-8 DAC. (The 1508 is a device with military temperature ratings.) This DAC sinks between 0 and 2 MA of current, the amount being directly proportional to its eight-bit digital input.

SEC. 22.3 ONE-CHANNEL TRACKING A/D CONVERTER (cont'd)

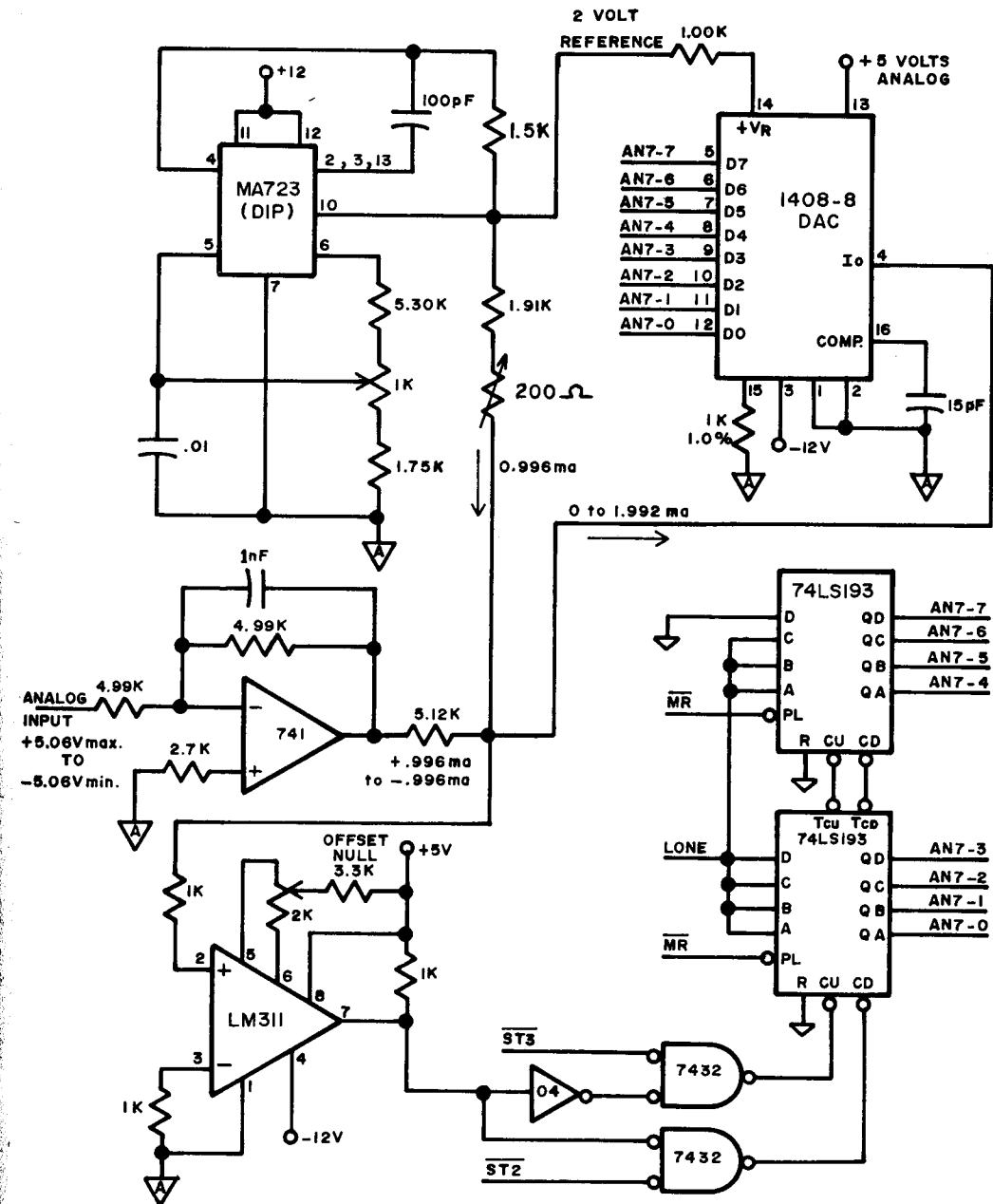


Fig. 22.3.1--Eight-Bit Tracking A/D Converter

SEC. 22.3 ONE-CHANNEL TRACKING A/D CONVERTER (cont'd)

The circuit shown in Figure 22.3.1 is configured so as to produce an eight-bit digital result in unsigned-magnitude binary code, with the polarity the inverse of the analog input. That is, an input voltage near +5 volts produces a digital result near 00000000, and an input voltage near -5 volts produces a digital result near 11111111. When this circuit is in use in an 8008 microcomputer, the result can be converted to two's complement notation with two instructions: INP 7; XRI 177. The first instruction inputs the A/D converter to the microcomputer. The second instruction complements all seven of the low-order bits, leaving the high-order bit in its original state. The correspondences between analog inputs and digital values are shown in Figure 22.3.2.

| ANALOG INPUT | | COUNT | A/D OUT | XRI 177 | COMPUTER |
|--------------|--------------|-------|----------|----------|----------|
| NOM. | RANGE | | | | |
| ERROR | $\geq +5.10$ | 255 | 11111111 | 10000000 | -128 |
| +5.08 | +5.06. +5.10 | 0 | 00000000 | 01111111 | +127 |
| +5.04 | +5.02. +5.06 | 1 | 00000001 | 01111110 | +126 |
| +5.00 | +4.98. +5.02 | 2 | 00000010 | 01111101 | +125 |
| | | ... | | | |
| +0.08 | +0.06. +0.10 | 125 | 01111101 | 00000010 | +2 |
| +0.04 | +0.02. +0.06 | 126 | 01111110 | 00000001 | +1 |
| 0.00 | -0.02. +0.02 | 127 | 01111111 | 00000000 | 0 |
| -0.04 | -0.06. -0.02 | 128 | 10000000 | 11111111 | -1 |
| -0.08 | -0.10. -0.06 | 129 | 10000001 | 11111110 | -2 |
| | | ... | | | |
| -5.00 | -5.02. -4.98 | 252 | 11111100 | 10000011 | -125 |
| -5.04 | -5.06. -5.02 | 253 | 11111101 | 10000010 | -126 |
| -5.08 | -5.10. -5.06 | 254 | 11111110 | 10000001 | -127 |
| ERROR | ≤ -5.10 | 255 | 11111111 | 10000000 | -128 |
| | | 256 | 00000000 | 01111111 | +127 |

Fig. 22.3.2--Analog Inputs, Digital Outputs for Tracking Design

SEC. 22.3 ONE-CHANNEL TRACKING A/D CONVERTER (cont'd)

Note that there are 256 possible levels of sink current through the DAC, corresponding to the possible combinations of its eight input bits, and that one of these levels is zero (all internal current switches turned off). This means that the maximum current sink possible is really 255/256 of 2.0 MA, or about 1.992 MA.

Consider the condition where there is a zero analog input. The voltage reference is adjusted for 2.00 V and the 200-ohm trimmer has been adjusted to provide a reference current of 0.996 MA flowing into the current node. Assume that the counters are properly tracking the input, and read 01111111. Of the DAC's eight internal current switches, all are on except for the high-order bit. The DAC sinks 127/256 of 2 MA, or about 0.992 MA. The current imbalance forces the node voltage to go slightly positive, and the comparator output becomes positive. The comparator signal is used to control the up/down counters.

As with any device connected to a microprocessor, the counters should not change state while inputting to the CPU. In this design, for the 8008, the counter clock input is gated by the microcomputer main timing signals. The counters may count *up* only when ST3 is low and the comparator output is high-- and may count *down* only when ST2 is low and the comparator output is low. The microprocessor input enable begins at T3A time, which occurs *after* ST2 and *before* ST3. This keeps the counter outputs stable during data transfer to the CPU.

Continuing with the example, the positive comparator output causes the counters to count *up* one step at the next ST3 time. Now the counters read 10000000. The DAC changes its current switches and now sinks 1.00 MA. Now the node voltage is slightly negative, and the comparator output goes negative. At ST2 time, the counters count down. Thus, as with any tracking A/D converter, the counters tend to oscillate around the true value.

However, in this design, the microcomputer sees a steady value. The CPU always reads during T3A time, after ST2. If the value is oscillating, the microcomputer sees only the *lower* of the two digital outputs from the counters. After the XRI 177 instruction has been executed, the CPU retains the more *positive* digital result--in this case, 00000000.

The 200-ohm current source trimmer, when adjusted properly, actually provides a bias current corresponding to one-half the least significant bit (1/2 LSB) of DAC sink current. This bias, taken together with the counter gating explained above, causes the converter to output a unique digital value for any given analog input with an accuracy of + or - 1/2 LSB.



SEC. 22.3 ONE-CHANNEL TRACKING A/D CONVERTER (cont'd)

This type of A/D converter can change its output value by only one count every clock period. Thus a tracking design is most suitable for continuous signals. When the instrument is turned on, or an analog input voltage applied, up to 256 clock periods may be required for the converter to start tracking the input. This time is reduced by half at power-on initialization by using the microcomputer master reset signal to load the counters to the 01111111 count.

The delay between the falling edge of the $\overline{ST2}$ signal, and the beginning of T3A time, is a little over 500 nanoseconds, in a system running at standard 8008 speed. This is plenty of time for the clock to increment or decrement the counters. The $\overline{ST2}$ is repeated during normal 8008 operations once every 20 microseconds, or more often, so that input signals into the kilohertz range may be sampled reliably. Note however that if the microprocessor program ever executes a halt (HLT) or wait instruction, the $\overline{ST2}$ strobe will not occur, and the A/D converter using this circuit would temporarily cease tracking its input. If software constraints are unacceptable, a slightly more complex clocking scheme will solve the problem.

The MCL408L-8 is rated to settle in 300 nanoseconds, typically, and the 311 comparator is also rated to operate within 300 ns.

Figure 22.3.2 shows that analog input voltages outside the converter's range will cause erroneous digital output values. There is a wraparound effect, whereby counting up from the highest counter output sets the counter at its *lowest* value. Now the DAC current is far from matching the analog input; but the digital feedback provided by the comparator will cause the counters to count *up* to try to balance the current node. As a result, when an overflow or underflow occurs, the counters must traverse all 256 counter values before the converters track again. Continuous inputs outside the voltage input limits will cause the converter to output a repetitive digital ramp signal. In a design where excessive input voltages are to be expected, the designer may need to include analog voltage clamps on the inputs, or a comparator which detects excessive deviations from 0 volts at the current node.

SEC. 22.4 SAMPLE/HOLD AND TRACK/HOLD

22.4.1 *Need for Hold Circuitry* If the A/D converter of the preceding section is to be expanded to handle two or more channels, several changes in the design are required. It is usually desirable to use only one DAC, because of the relatively high expense of this circuit element. It is also desirable to use only one microcomputer input port. This implies a system of analog switching. See the block diagram in Figure 22.4.1.

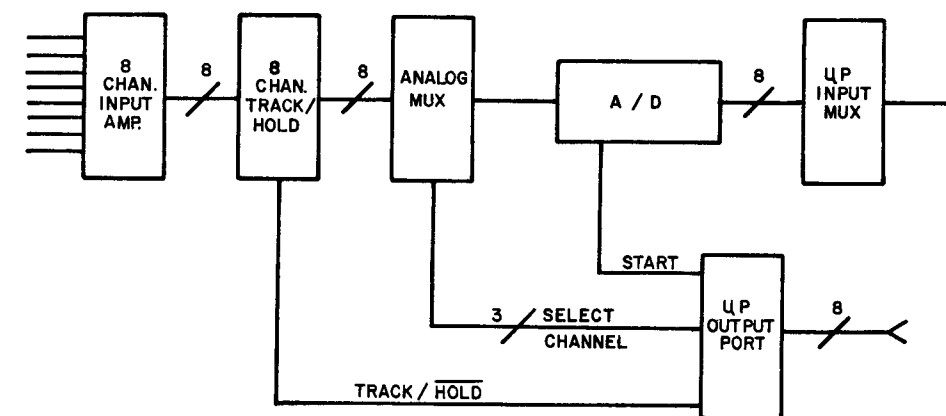


Figure 22.4.1--Block Diagram of Eight-Channel A/D Input System

Working backwards through the stages in the block diagram, the A/D converter requires an analog switch (multiplexer) to select the proper channel. The channel must have been selected for a short time before A/D conversion begins, and thus the converter is shown to be under control of one bit of a microprocessor output port. The multiplexer selects a channel as indicated by a three-bit selection code. The multiplexer in turn needs a steady input signal when processing a selected channel, thus the track/hold (or sample/hold) circuit.

22.4.2 *Track/Hold Circuitry* The circuit in Figure 22.4.2 is a practical track and hold design for eight channels. When the IH5012 FET is turned ON, through a LOW gating voltage, the junction between the two 10 K ohm precision resistors is effective connected to the inverting input of the 308 op amp. The op amp performs as a conventional inverting amplifier with a gain of -1. When the gating signal goes HIGH, the FET is turned off, and the op amp tends to maintain the charge on the 0.01

SEC. 22.4 SAMPLE/HOLD AND TRACK/HOLD (cont'd)

microfarad capacitor--a low-leakage device. A switching transistor is used to provide a gating signal referenced to +12 V, a level needed for reliable turnoff of the FET switches.

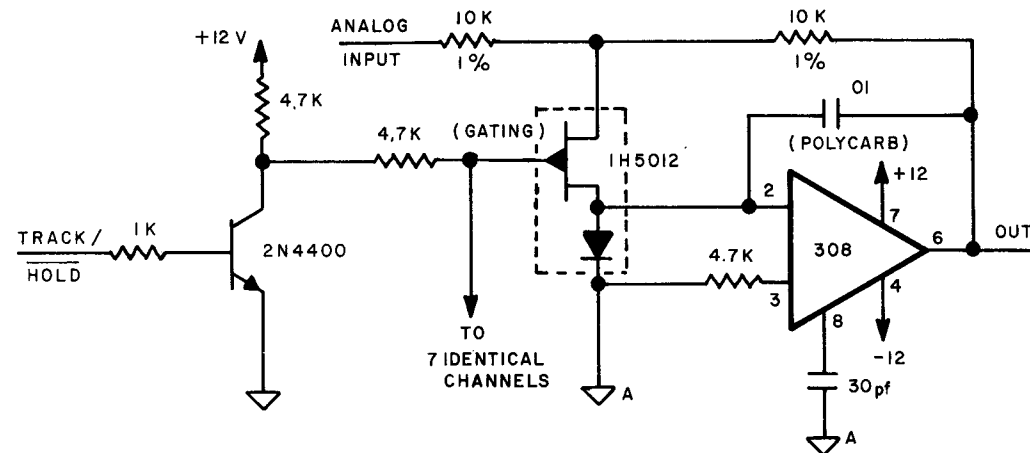


Fig. 22.4.2--Eight Channel Track and Hold

When the TRACK/HOLD signal is HIGH, the eight channels are all in TRACK mode, and remain so until the signal goes LOW. This contrasts to a sample/hold circuit, where a positive-going strobe would cause the FETs to turn on momentarily on the positive-going transition of the strobe, then return to HOLD mode automatically. Comparing operation of the two circuits, the track/hold circuit is normally in TRACK mode, and the output follows the input. A control signal places the amplifiers in HOLD mode for the purpose of initiating an A/D conversion. Then the amplifiers are normally returned to TRACK mode. The average voltage excursion of the amplifier output is relatively little. With the sample/hold design, the device is normally in the HOLD position, and the output is made to follow the input only when strobed; thus the average voltage excursion is greater.

Part (A) of Figure 22.4.3 shows how the low-order output bit of a conventional latching output port is used to gate the track/hold circuit of Figure 22.4.2. When an Output 7 instruction is executed, the low-order bit sets the track/hold mode (1 = track, 0 = hold), where it stays until the next Output 7 instruction. Part (B) shows an example of the pulse output technique of Chapter 9. The output is normally low (hold mode). When an Output 7 instruction is executed, with the low-order output bit set to 1, the one-shot is triggered. The one-shot is used to stretch the strobe so

SEC. 22.4 SAMPLE/HOLD AND TRACK/HOLD (cont'd)

that the capacitors in the hold circuits (Figure 22.4.2) have time to be charged or discharged to the newly sampled value. The Teledyne IH5012 FET switches need up to 500 nanoseconds settling time.

 


Fig. 22.4.3--Track/Hold, Sample/Hold Gating

SEC. 22.5 ANALOG MULTIPLEXER

The eight-channel analog multiplexer circuit of Figure 22.5.1 uses a 74145 decoder to select one of eight input channels. Three bits from output port 7--DT7-3, DT7-2, and DT7-1--are used to select the channel. The selected decoder output turns on the gate of a 5010 FET switch. The 741 op amp input circuitry includes a 10 K ohm, 1% resistor input resistor, connected to the selected analog input voltage. The feedback resistor is also a 10 K ohm resistor, with a matched FET switch (permanently turned on) in the feedback path for accurate gain and compensation. The output voltage is the inverse of the analog input voltage; gain is -1.

Note that in this and other schematics in this chapter, there is a separate ground return path for analog (A) and logic (L) signals. The noise caused by TTL switching transients will seriously upset low-current analog circuitry if present in the ground loops.

SEC. 22.5 ANALOG MULTIPLEXER (cont'd)

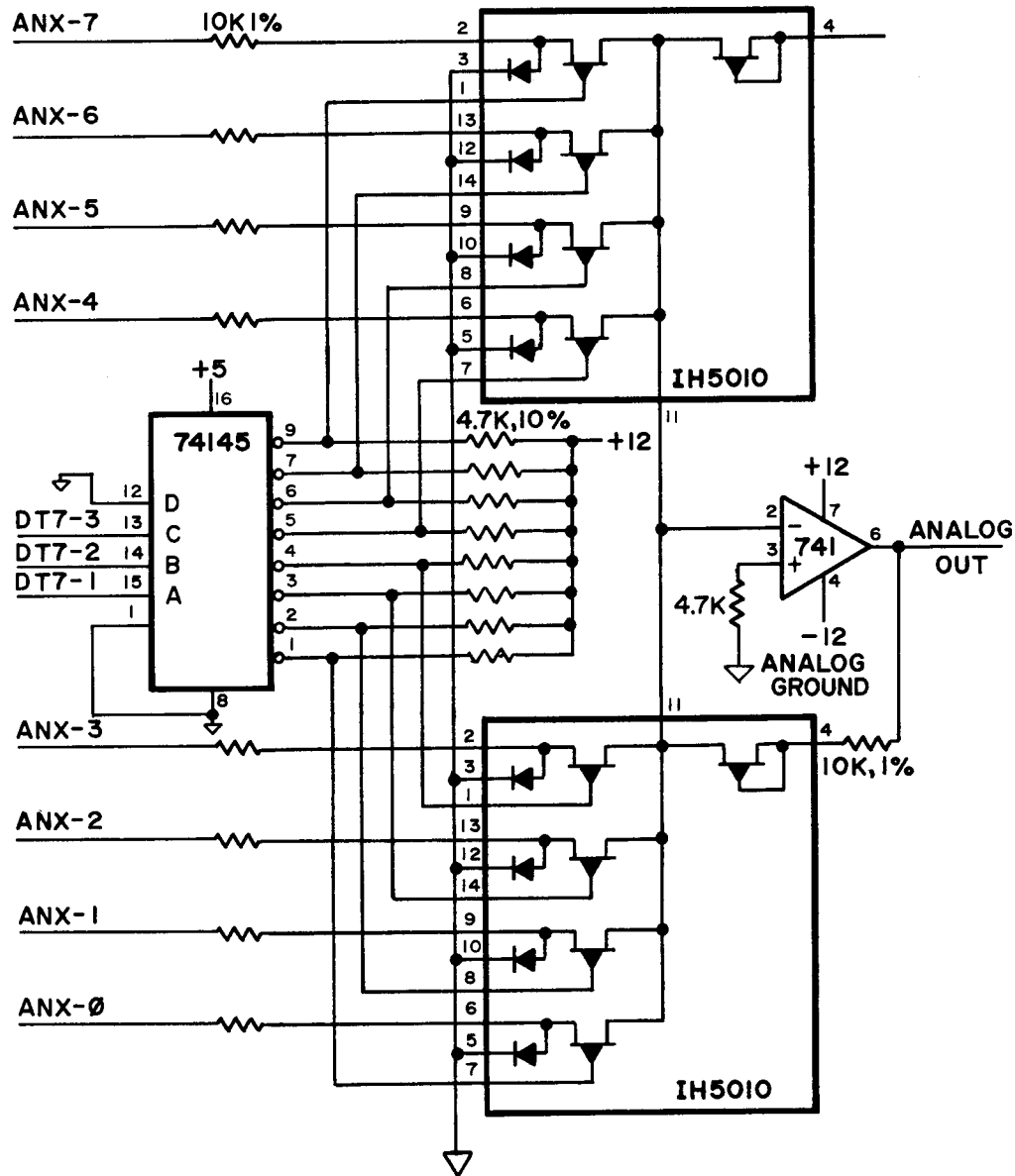


Figure 22.5.1--Eight-Channel Analog Multiplexer



SEC. 22.6 SUCCESSIVE APPROXIMATION A/D CONVERTER

The tracking A/D converter design discussed earlier in this chapter is not adequate in a multi-channel system, where the input signal is switched and therefore discontinuous. The successive approximation register (SAR) is capable of reaching an eight-bit resolution in eight clock periods, as opposed to a maximum of 256 for the eight-bit counter design. The attractiveness of the SAR is that it uses a nearly maximally efficient algorithm for reaching an eight-bit result in a digital feedback system. For details, see the applications memo "A Successive Approximation Register" published by Advanced Micro Devices.

Figure 22.6.1 should be considered an inset to Figure 22.3.1, where the AMD 2503 SAR replaces the two binary up/down counters. The TTL outputs of the 2503 are connected to the microcomputer's input multiplexers, and to the 1408-8 DAC. The comparator output is connected to the D (data) input of the SAR.

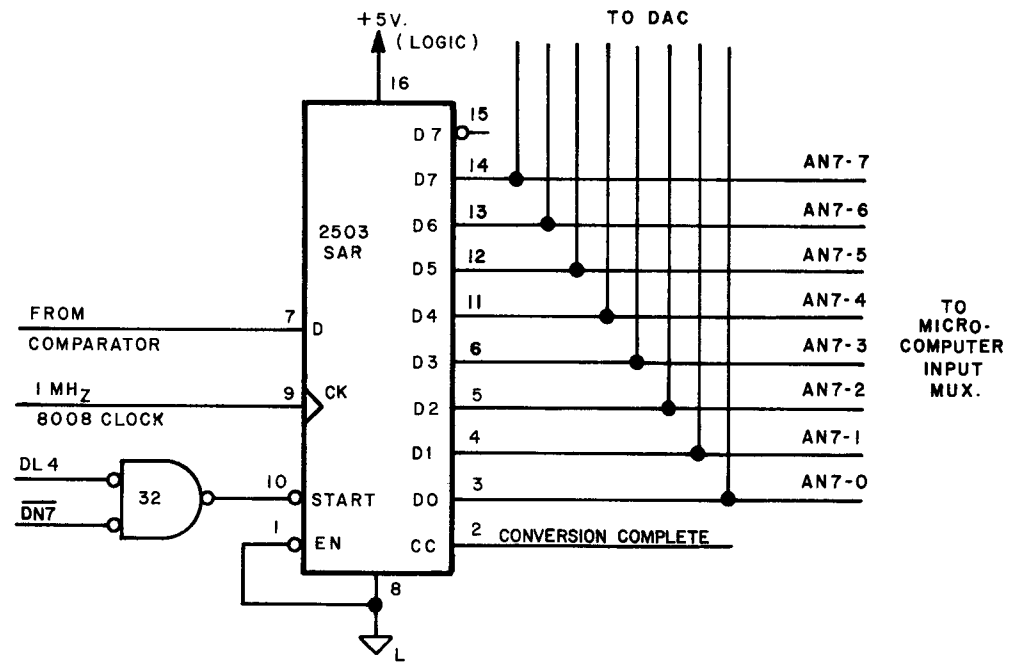


Fig. 22.6.1--SAR Replaces Counters in A/D Converter Circuit



SEC. 22.6 SUCCESSIVE APPROXIMATION A/D CONVERTER (cont'd)

The SAR is started with a conditional pulse output from the output 7 port (DT7-4 must be low). During the first clock period following the clock pulse, D7 is set low, with all other bits set high. This trial digital value is outputted to the DAC, and the comparator tells the SAR whether the analog input is greater or smaller than this trial value. At the beginning of the second clock cycle, D7 is set to the proper level, D6 is set low, and the remaining bits are set high. The trial comparison is repeated successively through D0.

The 2503 clock uses TTL input circuitry, imposing one standard TTL load on the signal source. It can operate at a frequency of more than 15 MHz, so that the conversion speed is effectively limited by the DAC and comparator. The 1408-8 DAC takes up to 300 nanoseconds, typically, and the 311 comparator takes about the same period of time. (For faster conversion, a 306 comparator has a delay of less than 50 ns.) Allowing one microsecond for each trial SAR value, the SAR can easily complete a conversion in less than the 20 microseconds standard 8008 instruction cycle time. Looking at the 8008 design example in Chapter 25, the designer could use the 1 MHz signal at the clock (C) input of the 7474 flip-flop in the main timing circuitry to drive the SAR clock.

The SAR provides a signal, conversion complete (\overline{CC}), that goes low at the end of the approximation cycle. This terminal is intended for applications where it is necessary to test for the availability of analog information. When, as here, the SAR is being driven synchronously by the microcomputer, testing this signal is unnecessary, since the conversion time is known in advance.

Pin 15 of the SAR, the complement of the most significant bit, can be used to output to the CPU, and provides an alternate means of achieving two's complement notation.

SEC. 22.7 D/A CONVERTER

A D/A converter circuit was presented earlier in this chapter--as part of the A/D designs. Figure 22.7.1 shows a basic D/A converter using the 1408L DAC and a 741 op amp. In order to preserve two's complement notation, the most significant bit is inverted digitally before being presented to the DAC. The eight-bit digital word to be converted derives from microcomputer output port 15 (not shown), and the +2 volt reference derives from a regulated supply such as the 723 circuit presented earlier in this chapter.

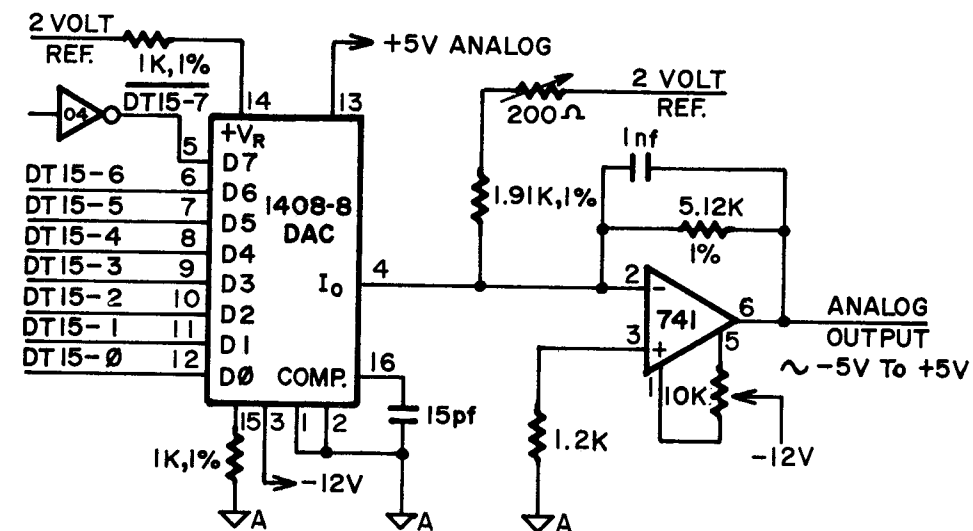


Fig. 22.7.1--Simple D/A Converter

In the medical electronics application for which this circuit was designed, the 741 op amp is adequately fast. Note that as the most significant bit changes at the input to the DAC, a relatively large current is switched reflecting the change of sign. This effectively limits the speed of the circuit still further. A more effective design for high-speed operation would omit the digital inverter at the DAC input (pin 5), and instead feed the current sink terminal for the most significant bit to the *non-inverting* input of a high-slew-rate op amp. This option is unavailable when designing around the 1408, with its single current sink terminal.

SEC. 22.8 MULTIPLE ANALOG OUTPUTS

Analog outputs may be multiplexed for the same reason that input multiplexers are used: to avoid the duplication of relatively expensive converters. Figure 22.8.1 shows a circuit in which eight sample/hold circuits receive an analog signal from a common DAC, like that shown in the previous section.

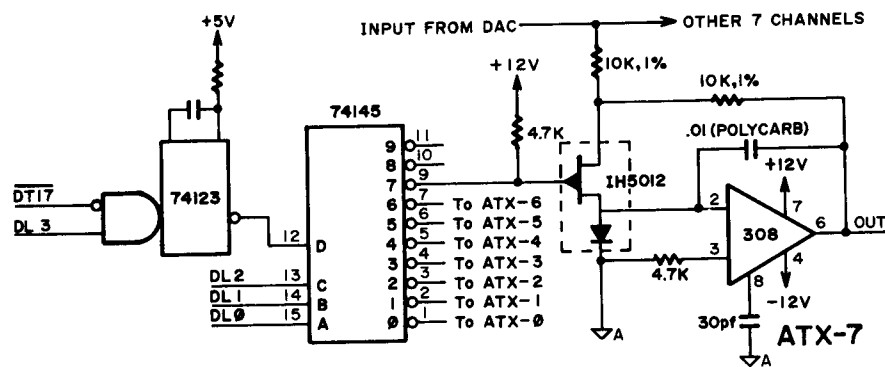


Fig. 22.8.1--Eight-Channel Sample/Hold Circuit Used for Output Multiplexing

The analog output channel is selected with a 74145 decoder, driven by the three low-order bits of an output port (here, Output 17). The next-higher-order bit--DT-17-3--must be high to cause an analog output sample signal to be generated; this allows the four remaining Output 17 bits to be used for other control purposes, without interfering with the analog output multiplexing circuitry. A one-shot stretches the output pulse for long enough to allow the 308 op amp to charge or discharge the hold capacitor.



SEC. 22.9 ANALOG RANGE SWITCHING

The resolution of an A/D converter can be improved by using (cont'd)

 


Fig. 22.9.1--Analog Range Switching Circuit

| OUTPUT RANGE | DT17-7 | DT17-6 | DT17-5 | DT17-4 | -5V | -4V | -3V | -2V | -1V | 0V | +1V | +2V | +3V | +4V | +5V |
|--------------|--------|--------|--------|--------|-----|-----|-----|-----|-----|----|-----|-----|-----|-----|-----|
|--------------|--------|--------|--------|--------|-----|-----|-----|-----|-----|----|-----|-----|-----|-----|-----|

 


Fig. 22.9.2--Digital Outputs Select Analog Ranges



SEC. 22.9 ANALOG RANGE SWITCHING (cont'd)

microcomputer-controlled gain and bias switching. Though this technique may be applied to analog output circuits, in general it is most useful for inputs. Figure 22.9.1 shows a circuit; Figure 22.9.2 shows how the output instruction controls the range of the circuit; and Figure 22.9.3 shows a typical program for use with the 8008.

PROGRAM FOR DRIVING FIGURE 22.8.1

```
LAB      GET DIGITAL VALUE.
OUT 015  OUTPUT ANALOG VOLTAGE.
LAI 017  SELECT ANA OUT & CHANNEL 7
OUT 017  DELIVER PULSE TO ATX-7 SAMPLE/HOLD
```

PROGRAM TO SELECT ANALOG INPUT FOR GAIN = 2

```
LAI 100  PREPARE AND..
OUT 017  ..SET GAIN OF 1
LAI 005  ANALOG INPUT #5
INP 007  CONVERT ANX-5
XRI 177  ADJUST FOR TWO'S COMPLEMENT
ADA      CARRY = POS. OR NEG.
JTC NEG  SIGN = ABSOLUTE VALUE OF NO.
ADA      CARRY = UPPER RANGE.
JTC A11  USE RANGE 11.
JTS A11
JMP A10
NEG XRI 377
ADA
JTC A12
JTS A12
A10 LAI 200 SEL. GAIN-SET & RANGE 10 (CENTER).
      JMP CONT (SEE FIG. 22.9.2)
A11 LAI 220 SEL. GAIN-SET & RANGE 11.
      JMP CONT
A12 LAI 240 SELECT GAIN-SET (BIT 3 = 0) AND RANGE 12.
CONT OUT 017
      LBA      SAVE GAIN & BIAS SETTING.
      LAI 005
      INP 007  INPUT WITH ADDED RESOLUTION.
```

COMMENTS:

```
USE RANGE 10 FOR VOLTAGE INPUT  $\pm 1.25$  V
USE RANGE 11 FOR VOLTAGE INPUT +1.25V TO
+5 VOLTS
USE RANGE 12 FOR VOLTAGE INPUT -5V TO -1.25 V
```

Fig. 22.9.3--Software for Analog Gain Selection

SEC. 23.1 SOFTWARE TRICKS

The usefulness of a microprocessor may be enhanced as much by good programming as by good hardware. Though the principal purpose of this book is to assist the designer with hardware, a number of simple programs are given in this chapter which can help the programmer perform the job quickly and with efficient use of ROM and RAM storage.

These subroutines have been written for the 8008. Some will help close the gap between the 8008 and the 8080, with its more versatile instruction set.

SEC. 23.2 CLEAR THE A REGISTER INSTRUCTION

XRA is an instruction which EXCLUSIVE ORs the content of the A register with itself, on a bit-by-bit basis. Since either 0 or 1 EXCLUSIVE-ORed with itself produces a result of zero, the whole A register will be cleared.

Since the EXCLUSIVE-OR instruction sets the flags, the status after the XRA instruction will be:

| | |
|------------|-----|
| A REGISTER | 000 |
| CARRY FLAG | 0 |
| SIGN FLAG | 0 |
| ZERO FLAG | 1 |
| PARTY FLAG | 0 |

SEC. 23.3 COMPLEMENT INSTRUCTION

XRI 377 will complement every bit in the A register. That is, each bit which had been a one will become a zero, and vice versa. In the 8080, the single-byte instruction CMA (complement the A register) provides this function. Note that (with either 8008 or 8080) the instruction XRI 017 complements the last four bits of the A register, leaving the other bits undisturbed.

SEC. 23.4 MULTIPLE PRECISION ADD AND SUBTRACT

Both the 8080 and 8008 were designed to facilitate multiple-byte binary addition and subtraction. The 8080 has a sixteen-bit add instruction, namely DAD--a feature which the 8008 lacks. Since multiplication and division consist of additions and subtractions, it is not difficult to perform all four basic arithmetic functions.



SEC. 23.4 MULTIPLE PRECISION ADD AND SUBTRACT (cont'd)

The following program is a two-byte add routine. The *first summand* is a 16-bit number whose low-order bits are in the A register and whose high-order bits are in the B register. The *second summand* is in the C and D registers as shown in Figure 23.4.1. After the execution of the program shown in Figure 23.4.2, the *sum* will reside in the A and E registers.

| | | |
|----------------|------------|-----------------------|
| FIRST SUMMAND | B REGISTER | A REGISTER |
| SECOND SUMMAND | D REGISTER | C REGISTER |
| SUM | C | A REGISTER E REGISTER |

Figure 23.4.1 The Use of the Registers in Performing a Double-Precision Addition.

| | |
|-----|--|
| ADC | ADD LOW ORDER BYTES, CREATE CARRY. |
| LEA | SAVE RESULT. |
| LAB | GET HIGH ORDER BYTE, FIRST SUMMAND. |
| ACD | ADD HIGH ORDER BYTE, SECOND SUMMAND, AND CARRY BIT FROM LOW ORDER BYTE ADDITION ABOVE. |

Figure 23.4.2 Four Single-Byte Instructions Perform Double-Precision Add.

The heart of this program is the ACD instruction which allows adding together *three* numbers simultaneously. The first number is in the A register (8 bits), the second number is in the D register (8 bits), and the third number is in the carry register (1 bit). The result of this addition is 9 bits: 8 bits in the A register and a ninth high order bit in the carry register. This ninth bit of the result is shown as *C* next to the sum in Figure 23.4.1. The result of adding two numbers may be either 16 bits, or 17 bits, depending on the size of the numbers added. If the carry bit of the result is discarded and only 16-bit numbers are used, it is possible to represent numbers between -32,768 and +32,767.

Note: The carry is referred to either as a one-bit register or as a flag depending on how it is being used. Both references are to the same actual flip-flop in the 8008 CPU, however.

The program shown in Figure 23.4.3 is used to subtract two 16-bit numbers. The *minuend* is in the B and A registers where the first summand was in Figure 23.4.1. The *subtrahend* is placed in the D and C registers and the *difference* ends up in the A and E registers.

SEC. 23.4 MULTIPLE PRECISION ADD AND SUBTRACT (cont'd)

| | |
|-----|--|
| SUC | SUBTRACT LOW ORDER BYTES, CREATE BORROW. |
| LEA | SAVE RESULT. |
| LAB | GET HIGH ORDER BYTE, MINUEND. |
| SBD | SUBTRACT HIGH ORDER BYTE, SUBTRAHEND, AND CARRY (BORROW) BIT FROM LOW ORDER SUBTRACTION ABOVE. |

Figure 23.4.3--Four Instructions Perform Double Precision Subtract in the 8008.

SEC. 23.5 INCREMENTING H AND L REGISTERS

In the 8080, INX H is a single-byte instruction which increments the register pair HL. INX B, INX D, and INX SP perform the same function for three other 8080 register pairs. With the 8008, the double-precision increment by one can be done with a few instructions. By storing these instructions at location 000050, the programmer can increment the HL register pair in the 8008 with the single instruction RST 050. The four-byte program is shown in Figure 23.5.1.

| | |
|------------|----------------------------------|
| LOC 000050 | |
| INL | INCREMENT L REGISTER |
| RFZ | RETURN IF NOT ZERO (NO OVERFLOW) |
| INH | INCREMENT H REGISTER |
| RET | RETURN TO CALLER |

Figure 23.5.1--Commonly-Used Subroutine for Incrementing H and L Registers in 8008 Microcomputer

Depending on the function of the microcomputer, there will be a number of commonly used subroutines. The *most* commonly used of these subroutines should be made to start at locations such as 000000, 000010 etc. so that they may be referenced by one-byte call instructions (RST). This reduces the amount of storage required for the ROM program. Less commonly used subroutines may be called using the three-byte CAL instruction.

SEC. 23.6 CLEAR RAM MEMORY

The program shown in Figure 23.6.1 clears RAM with a minimum of instructions in the shortest possible time. If the *RAM-PAGE* option is present in the system, the H register need not be loaded and the LHI 040 instruction may be eliminated.



SEC. 23.6 CLEAR RAM MEMORY (cont'd)

```

LHI 040    POINT TOWARD PAGE WHERE RAM IS TO BE CLEARED.
XRA        CLEAR A REGISTER.
LLA        CLEAR L REGISTER.
LOOP LMA   CLEAR MEMORY LOCATION.
INL        POINT TO NEXT LOCATION.
JFZ LOOP   LOOP UNTIL DONE.

```

Figure 23.6.1 Clear RAM to Zero Program

SEC. 23.7 INDEXED JUMP TABLE

An *indexed jump* instruction is one which causes the program to jump to one of several designated locations. Figure 23.7.1 shows a program which jumps to one of five locations, depending on the contents of the L register--which may take on values 0 through 4. Note that it is easiest to program index jump instructions if the jump table begins at the start of a new page in ROM.

PROGRAM INITIALIZATION, PERFORMED DURING POWER-ON INTERRUPT ONLY.

```

LHI 040
LLI 000
LMI 104    JUMP OPCODE
LLI 002
LMI 027    PAGE WHERE ROUTINES TO BE JUMPED TO ARE LOCATED

```

THE FOLLOWING JUMPS TO ROUTINES ACCORDING TO CONTENT OF L REGISTER.

```

LHI 020    POINT TOWARDS ROM TABLE.
LAM        PICK UP L PORTION FROM TABLE.
LHI 040    POINT TOWARDS RAM.
LLI 001    SECOND BYTE OF JUMP INSTRUCTION.
LMA        PLACE L PORTION IN JUMP INST.
JMP 040000 EXECUTE CONSTRUCTED JUMP INSTRUCTION IN RAM.

```

```

LOC 020000 START OF JUMP TABLE.
010        LOW PORTION OF ROUTINE 0 ADDRESS.
030        " " " " 1 "
075        " " " " 2 "
132        " " " " 3 "
375        " " " " 4 "

```

SEC. 23.7 INDEXED JUMP TABLE (cont'd)

```

LOC 027010
XXX        START OF ROUTINE 0
LOC 027030
XXX        START OF ROUTINE 1
LOC 027075
XXX        START OF ROUTINE 2
LOC 027132
XXX        START OF ROUTINE 3
LOC 027375
JMP 024000 JUMP TO START OF ROUTINE 4
LOC 024000
XXX        START OF ROUTINE 4

```

Fig. 23.7.1--Indexed Jump Program Causes Jump to Location Indicated by L Register

SEC. 23.8 INDEXED LOOPS

An *indexed loop* is a method of performing a repetitive function, such as in table lookups, or in performing an operation on a list of variables. The *DO LOOP* in Fortran is a commonly-used statement. Figure 23.8.1 shows a loop which performs some desired operation seven times, before continuing with the next portion of the program.

```

...
LBI 007    PERFORM 7 TIMES.
OPER XXX   SOME OPERATION.
DCB        COUNT DOWN.
JFZ OPER   LOOP UNTIL DONE.
...        CONTINUE WITH MAIN PROGRAM.

```

Fig. 23.8.1--Indexed Loop Using the B Register

SEC. 23.9 HARD HALT INSTRUCTION

The HLT (HALT) instruction stops a program from being executed only until an interrupt occurs.

The interrupt routine is executed, and then the main line program is free to continue, starting with the instruction following the HLT



SEC. 23.9 HARD HALT INSTRUCTION (cont'd)

instruction.

A HARD HALT instruction can be used to prevent execution of the main line program altogether. The designer may specify a HARD HALT to be executed when machine conditions indicate that a dramatic system failure has occurred. Only a power down cycle will permit the main line program to continue.

A HARD HALT usually consists of a JMP * instruction, which continually jumps to its own location. Many programmers prefer the two-instruction sequence shown in the figure below, which hard-halts with a JMP instruction, but also goes through the HLT state. This will cause the main timing logic to develop a STOPPED strobe, which can be used to light up a STOP lamp--either on the front panel of a console, or on the circuit board in prototype systems.

```
A HLT      HALT.
  JMP A    GO HALT AGAIN.
```

Fig. 23.9.1--Two-Instruction HARD HALT Sequence

If the microcomputer has a repetitive interrupt signal, in addition to any power-on interrupt present in the system--for example, from an interval timer, or from a peripheral device like a keyboard--the two-instruction HARD HALT sequence shown above will not prevent the execution of the associated interrupt subroutines. They will be executed, and then the program will re-enter the HARD HALT. To prevent the system from being interrupted, the interrupt port of the CPU must be disabled. With an 8080, a DI (disable interrupt) instruction at the beginning of the above routine will suffice. (Now only a RESET will end the HARD HALT.) With the 8008, a flip-flop can be added at the 8008 READY terminal; an OUTPUT X instruction is inserted at the beginning of the above instruction sequence, and the DTX strobe which is created resets the flip-flop, disabling the interrupt. The MASTER RESET signal would re-enable the interrupt by clearing the flip-flop.

SEC. 23.10 PUSH ALL REGISTERS

This section describes a system with associated software subroutines which is used to PUSH and POP all of the 8008's internal data registers. (A routine for the 8080 appears in Sec. 23.11 of this chapter.) When the PUSH subroutine is called, the current contents of all registers and flags are saved sequentially in

SEC. 23.10 PUSH ALL REGISTERS (cont'd)

RAM. When the POP subroutine is called, all registers and flags are restored to the exact status extant at the time when the PUSH subroutine was called.

The PUSH subroutine may be called a number of times, from any part of the program or its subroutines, just so long as the microprocessor's program counter (PC) stack is not overflowed. Each POP subroutine will restore the registers and flags as they were the *very last* time that the PUSH subroutine was called.

The hardware required includes two temporary data storage registers, referred to as TEM 7 and TEM 6 in the programs. TEM 7 is loaded with an OUT 027 instruction and read with an INP 007 instruction; TEM 6 is loaded with an OUT 026 and read with an INP 006. Each register may be implemented with the design for a "one-byte LIFO" shown in Chapter 12 above. Page 040 in RAM is designated as storage for use by the push/pop stack.

The power-on initialization program should include the sequence in Figure 23.10.0, which initializes the PUSH/POP pointer before any PUSH or POP subroutine is called.

```
LHI 040  POINT TO STACK POINTER (HIGH).
LLI 000  POINT TO STACK POINTER (LOW).
LMI 001  INITIALIZE TO LOC 040001.
```

Fig. 23.10.1--Initialization Sequence Presets PUSH/POP Pointer

The program in Figure 23.10.2 is the PUSH routine, which saves registers and flags, and the program in Figure 23.10.3 is the POP routine which restores status.

PUSH ALL REGISTERS AND FLAGS

```
007000/ 155  OUT 026  A to TEM 6,
007001/ 306  LAL      GET L REGISTER.
007002/ 157  OUT 027  SAVE L IN TEM 7.
007003/ 305  LAH      GET H TO SAVE LATER.
007004/ 056  LHI 040  POINT AT STACK POINTER.
007006/ 066  LLI 000  POINT AT STACK POINTER.
007010/ 367  LLM      POINT TO STACK.
007011/ 370  LMA      PUSH H TO STACK.
007012/ 006  LAI 000  ASSUME ZERO FLAG IS SET.
```

Fig. 23.10.2--PUSH All Registers and Flags (cont'd on next page)



SEC. 23.10 PUSH ALL REGISTERS (cont'd)

| | | | |
|---------|-----|------------|----------------------------|
| 007014/ | 150 | JTZ 007021 | IF TRUE GET CARRY BIT. |
| 007017/ | 006 | LAI 060 | ASSUME SIGN BIT IS ZERO. |
| 007021/ | 120 | JFS 007026 | IF TRUE GET CARRY BIT. |
| 007024/ | 006 | LAI 300 | SIGN BIT WAS SET. |
| 007026/ | 032 | RAR | GET CARRY BIT. |
| 007027/ | 170 | JTP 007034 | JUMP IF PARITY IS EVEN. |
| 007032/ | 054 | XRI 001 | SET PARITY ODD. |
| 007034/ | 060 | INL | INCREMENT STACK POINTER. |
| 007035/ | 370 | LMA | PUSH FLAG WORD. |
| 007036/ | 060 | INL | INCREMENT STACK POINTER. |
| 007037/ | 371 | LMB | PUSH B REGISTER. |
| 007040/ | 060 | INL | INCREMENT STACK POINTER. |
| 007041/ | 372 | LMC | PUSH C REGISTER. |
| 007042/ | 060 | INL | INCREMENT STACK POINTER. |
| 007043/ | 373 | LMD | PUSH D REGISTER. |
| 007044/ | 060 | INL | INCREMENT STACK POINTER. |
| 007045/ | 374 | LME | PUSH E REGISTER. |
| 007046/ | 060 | INL | INCREMENT STACK POINTER. |
| 007047/ | 117 | INP 007 | GET L REGISTER FROM TEM 7. |
| 007050/ | 370 | LMA | PUSH L REGISTER. |
| 007051/ | 060 | INL | INCREMENT STACK POINTER. |
| 007052/ | 115 | INP 006 | GET A REGISTER FROM TEM 6. |
| 007053/ | 370 | LMA | PUSH A REGISTER. |
| 007054/ | 060 | INL | START OF NEXT PUSH. |
| 007055/ | 306 | LAL | GET NEW POINTER. |
| 007056/ | 066 | LLI 000 | POINT TO POINTER. |
| 007060/ | 370 | LMA | PUT AWAY NEW POINTER. |
| 007061/ | 115 | INP 006 | GET A REGISTER FROM TEM 6. |
| 007062/ | 007 | RET | RETURN TO CALLER. |

Fig. 23.10.2--PUSH All Registers and Flags

POP ALL REGISTERS AND FLAGS

| | | | |
|---------|-----|---------|-----------------------------|
| 007063/ | 056 | LHI 040 | POINT AT STACK POINTER. |
| 007065/ | 066 | LLI 000 | POINT AT STACK POINTER. |
| 007067/ | 307 | LAM | GET STACK POINTER. |
| 007070/ | 024 | SUI 010 | DECREMENT POINTER BY 8. |
| 007072/ | 370 | LMA | REPLACE POINTER. |
| 007073/ | 004 | ADI 007 | START AT END. |
| 007075/ | 360 | LLA | POINT AT END (SAVED A REG). |
| 007076/ | 307 | LAM | POP A REGISTER. |
| 007077/ | 155 | OUT 026 | A TO TEM 6. |
| 007100/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007101/ | 307 | LAM | POP L REGISTER. |
| 007102/ | 157 | OUT 027 | L TO TEM 7. |

Fig. 23.10.3 POP All Registers and Flags (cont'd on next page)

SEC. 23.10 PUSH ALL REGISTERS (cont'd)

| | | | |
|---------|-----|---------|------------------------------|
| 007103/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007104/ | 347 | LEM | POP E REGISTER. |
| 007105/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007106/ | 337 | LDM | POP D REGISTER. |
| 007107/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007110/ | 327 | LCM | POP C REGISTER. |
| 007111/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007112/ | 317 | LBM | POP B REGISTER. |
| 007113/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007114/ | 307 | LAM | POP FLAGS. |
| 007115/ | 061 | DCL | DECREMENT STACK POINTER. |
| 007116/ | 200 | ADA | RESTORE FLAGS. |
| 007117/ | 357 | LHM | POP H REGISTER. |
| 007120/ | 117 | INP 007 | GET L REGISTER FROM TEM 7. |
| 007121/ | 360 | LLA | RESTORE L REGISTER. |
| 007122/ | 115 | INP 006 | GET A REGISTER FROM TEM 6. |
| 007123/ | 007 | RET | RETURN, ALL STATUS RESTORED. |

Fig. 23.10.3--POP All Registers and Flags

Finally, Figure 23.10.4 shows the addresses in RAM where registers and flags are stored by the PUSH subroutine. Note that this system provides for up to eight push/pop levels if all of page 040 in RAM is used. Recall the constraint however that the microprocessor's program counter stack must not be overflowed.

| | | |
|---------|-----|--------------------------------|
| | | THE FOLLOWING IS RAM MEMORY |
| 040000/ | 001 | STACK POINTER |
| 040001/ | | H REGISTER SAVE |
| 040002/ | | F FLAGS SAVE |
| 040003/ | | B REGISTER SAVE |
| 040004/ | | C REGISTER SAVE |
| 040005/ | | D REGISTER SAVE |
| 040006/ | | E REGISTER SAVE |
| 040007/ | | L REGISTER SAVE |
| 040010/ | | A REGISTER SAVE |
| | | ABOVE USED ON FIRST PUSH LEVEL |
| | | |
| 040011/ | | H REGISTER SAVE |
| 040012/ | | F FLAGS SAVE |
| 040013/ | | B REGISTER SAVE |
| 040014/ | | C REGISTER SAVE |
| 040015/ | | D REGISTER SAVE |
| 040016/ | | E REGISTER SAVE |
| 040017/ | | L REGISTER SAVE |

Fig. 23.10.4--Address Assignments for PUSH/POP Storage of Registers and Flags in Memory (cont'd on next page)



SEC. 23.10 PUSH ALL REGISTERS (cont'd)

| | |
|---------|--|
| 040020/ | A REGISTER SAVE ABOVE USED ON SECOND PUSH LEVEL |
| 040021/ | H |
| 040022/ | F |
| 040023/ | B |
| 040024/ | C |

ET CETERA

Fig. 23.10.4--Address Assignments for PUSH/POP Storage of Registers and Flags in Memory

SEC. 23.11 8080 PUSH/POP INSTRUCTIONS

The 8080's PUSH and POP instructions represent one of the 8080's most significant improvements over the 8008. These single-byte instructions greatly facilitate saving CPU flag and register status.

Unlike the 8008, the 8080 does not have an internal program counter stack; instead it has a full 16-bit stack pointer, referencing any convenient area in external RAM memory, which becomes the CPU's program stack. This stack is addressable through various 8080 instructions, and can be used to store not only program counter values, but registers and flags as well.

For example, to store the B and C registers, a PUSH B instruction is executed. The following steps occur: the stack pointer is decremented by one; the B register is stored at this new location in RAM; SP is decremented again; and the C register is stored there. To restore the status of this register pair, a POP B instruction is executed, and the above process takes place in reverse. The C register is loaded from the RAM location designated by SP; SP is incremented; the B register is loaded from RAM; SP is incremented again.

The D and E registers also make up a register pair for these instructions (PUSH D, POP D), as do the H and L (PUSH H, POP H). The A register is pushed and popped together with a processor status word (PSW), which contains the 8080 flag values, as follows:

| | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|
| D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 |
| ----- | ----- | ----- | ----- | ----- | ----- | ----- | ----- |
| S | Z | 0 | AC | 0 | P | 1 | CY |

Fig. 23.11.1--8080 Flags Stored in Processor Status Word (PSW)

SEC. 23.11 8080 PUSH/POP INSTRUCTIONS (cont'd)

In the above figure, S is the sign bit, Z is the zero bit, AC is the auxiliary carry bit (used by the decimal adjust instruction), P is parity, and CY is carry. PUSH PSW pushes the A register first, then the status word--and for consistency with the PUSH B, PUSH D, and PUSH H instructions, should perhaps be called PUSH A. POP PSW pops the status word first, then the A.

These instructions clearly simplify the storing and restoring of the 8080's flags and data registers. In order to push (that is, save) the program counter, to preserve the memory address from which the program instructions are currently being fetched, it is necessary merely to execute CALL (or RESTART) instructions; and to pop the program counter, to restore the program location, a RETURN instruction is executed.

In short, a CALL instruction can be defined simply as a PUSH PC; JUMP instruction. A RESTART instruction is a specialized CALL instruction, referring to the first page in memory, and the same definition applies.

A RETURN instruction is simply a POP PC instruction.

An instruction sequence for saving 8080 flags and registers is shown in Figure 23.11.2.

| | |
|----------|------------------------|
| PUSH PSW | SAVE A REGISTER, FLAGS |
| PUSH B | SAVE B, C REGISTERS |
| PUSH D | SAVE D, E REGISTERS |
| PUSH H | SAVE H, L REGISTERS |

Fig. 23.11.2--Saving 8080 Flags, Registers

To restore 8080 status, the sequence in Figure 23.11.3 is used

| | |
|---------|---------------------------|
| POP H | RESTORE L, H REGISTERS |
| POP D | RESTORE E, D REGISTERS |
| POP B | RESTORE C, B REGISTERS |
| POP PSW | RESTORE FLAGS, A REGISTER |

Fig. 23.11.3--Restoring 8080 Flags, Registers

The 8080's power-on initialization program should set up the stack pointer to an area of RAM suitable for housing the stack. The instruction LXI SP (load immediate the stack pointer) is convenient.

As the previous section (23.10) and Chapter 17 demonstrate, it

SEC. 23.11 8080 PUSH/POP INSTRUCTIONS (cont'd)

is very cumbersome to save status with the 8080--so that the programmer usually plans that subroutines will destroy certain registers and flags, and makes suitable provisions. With the 8080, it is easy enough to save status that many programmers save and restore all registers and flags in every subroutine.

SEC. 24.1 TESTING MICROPROCESSORS

Complete testing of microprocessor chips is usually so complex that it is very difficult to design a general purpose tester which will check out all of the characteristics of the device. Instead, a two-part testing program is recommended.

The first step is to use a testing circuit for burning in the microprocessor. The test circuit uses a simple program which is sufficient to reject the majority of defective devices.

The final test is performed in a circuit identical to that in which the microprocessor is expected to operate. This tests the chip with the programs it will actually be required to execute. Unless the equipment being produced will need updating in the field--by reprogramming the ROM--the cost of an elaborate test program is probably not justified.

| | | | |
|-------------|---------|-------------|---------|
| 010000/ 015 | RST 010 | 010041/ 276 | CPL |
| 010001/ 000 | HLT | 010042/ 013 | RFZ |
| 010002/ 000 | HLT | 010043/ 006 | LAI 125 |
| 010003/ 000 | HLT | 010045/ 275 | CPH |
| 010004/ 000 | HLT | 010046/ 013 | RFZ |
| 010005/ 000 | HLT | 010047/ 250 | XRA |
| 010006/ 000 | HLT | 010050/ 274 | CPE |
| 010007/ 000 | HLT | 010051/ 013 | RFZ |
| 010010/ 006 | LAI 252 | 010052/ 006 | LAI 222 |
| 010012/ 310 | LBA | 010054/ 273 | CPD |
| 010013/ 321 | LCB | 010055/ 013 | RFZ |
| 010014/ 332 | LDC | 010056/ 006 | LAI 111 |
| 010015/ 343 | LED | 010060/ 272 | CPC |
| 010016/ 354 | LHE | 010061/ 013 | RFZ |
| 010017/ 365 | LLH | 010062/ 006 | LAI 244 |
| 010020/ 006 | LAI 125 | 010064/ 271 | CPB |
| 010022/ 310 | LBA | 010065/ 013 | RFZ |
| 010023/ 321 | LCB | 010066/ 006 | LAI 243 |
| 010024/ 332 | LDC | 010070/ 271 | CPB |
| 010025/ 343 | LED | 010071/ 023 | RFS |
| 010026/ 354 | LHE | 010072/ 033 | RFP |
| 010027/ 046 | LEI 000 | 010073/ 003 | RFC |
| 010031/ 036 | LDI 222 | 010074/ 005 | RST 000 |
| 010033/ 026 | LCI 111 | 010075/ 000 | HLT |
| 010035/ 016 | LBI 244 | ----- | |
| 010037/ 006 | LAI 252 | | |

Fig. 24.1.1--Sample 8080 Test Program



SEC. 24.1 TESTING MICROPROCESSORS (cont'd)

The *MIKE 1* circuit presented in Chapter 25 is quite suitable for 8008 testing. It uses only eight ICs in addition to the 8008, which would be inserted into a socket for testing.

A sample test program which may be employed for burning in 8008s with the *MIKE 1* is shown in Figure 24.1.1. This program tests register-to-register transfers and flag conditions. More complete test programs are available with the *MIKE 1*.

SEC. 24.2 DESIGNING FOR EASY TESTING

In a typical microcomputer, most system failures occur as the result of the breakdown of devices connected directly or indirectly to the microprocessor bus. Since the microprocessor controls most system functions, these failures ultimately cause incorrect instructions to be delivered to the CPU, and show up as deviations in the execution of the CPU's program. Although these failures may appear to have been caused by the CPU itself, actually the microprocessor itself tends to be one of the most reliable devices in a microcomputer.

Essential troubleshooting equipment includes instrumentation which allows the engineer or technician to visualize the microprocessor's software as it is actually being executed. This is covered in sections below.

The designer can help the serviceman by designing extra signals into the microcomputer for testing purposes. For example, an 8008 or 8080 microcomputer generally includes an I/O strobe decoder, as described in Chapter 7 and illustrated in Chapters 25 and 26. Frequently the decoder develops more strobes and enables than are actually used to control input and output ports. These extra decoder outputs may be designated as test signals and brought out to test points on the PC board. Say that there is no *Output 37* port, but that the *DT37* strobe is available. The *OUT 37* instruction is included at a crucial branch in the machine's programming. Then the repairman may probe the test point to determine whether the program is executing that stage in the program.

Test points for some of the microcomputer's more important signals should also be made readily accessible to the repairman. Some suggested connections are discussed in the following section.



microcomputer
design

SEC. 24.3 SIXTEEN-CHANNEL OSCILLOSCOPE DISPLAY

Without the proper equipment, it is often difficult to trace problems associated with microprocessors. This is true both in the design stages and in production.

The circuit described in this section allows sixteen channels of digital information to be displayed on a single-trace triggered-sweep oscilloscope. It provides a simple but very convenient method of debugging microcomputers equipped with interrupt capabilities.

Figure 24.3.1 shows a 16-channel display constructed with only three TTL and two CMOS integrated circuits. Shown connected to an 8008-based microcomputer, the design is applicable to an 8080. The circuitry contains an oscillator which is used to provide continuous repetitive interrupt signals to the microcomputer under test. The signal which indicates that the CPU has recognized an interrupt is connected to the oscilloscope's EXTERNAL SYNC input terminal. For an 8008, this signal is *STI1* (as shown); for an 8080, it would be *INTA*. The scope's VERTICAL INPUT terminal is connected to the output of the D/A converter. The oscilloscope screen displays sixteen lines of digital information; the appearance is very much like the timing diagrams which appear in various sections of this book. The top trace shows the state of *ST1*, the second of *ST2* and so forth down the screen.

The display is of the alternating-sweep type; that is, sixteen repetitions of the program are needed to display the sixteen channels.

The reader might at first feel that a sixteen-channel display would be too complex or confusing. However, with a little practice in the use of the horizontal position control on the 'scope, one can line up any desired instruction with the center vertical line on the graticule and read all of the microprocessor's state conditions quite easily.

Note also that the resistors in the D/A portion of the circuitry in Figure 24.3.1 are specified to display four groups of four lines each, thus making it easier to distinguish between traces on the screen. The 5% resistors shown produce satisfactory resolution on the screen. Theoretically, since this is a five-bit D/A converter, the resistors should have an accuracy of one part in 32 (3.1%) or better, but even a random selection of 10% resistors works well (values of 1 K, 2.2 K, 4.7 K, 10 K, 22 K). The four CMOS buffers in the D/A section may also be omitted—but this omission leads to a somewhat inferior (though still useful) display appearance. The buffers between the 74150 and the CPU data bus are necessary, however, at least with simple microcomputers with unbuffered data busses, to avoid overloading the CPU.

The oscillator section generates a signal which interrupts the microcomputer every few milliseconds. A resistor is connected from the PHASE 1 signal, developed by the 8008 main timing circuitry (Chapter 5), to the oscillator input in order to synchronize the interrupt clock with



microcomputer
design

SEC. 24.3 SIXTEEN-CHANNEL OSCILLOSCOPE DISPLAY (cont'd)

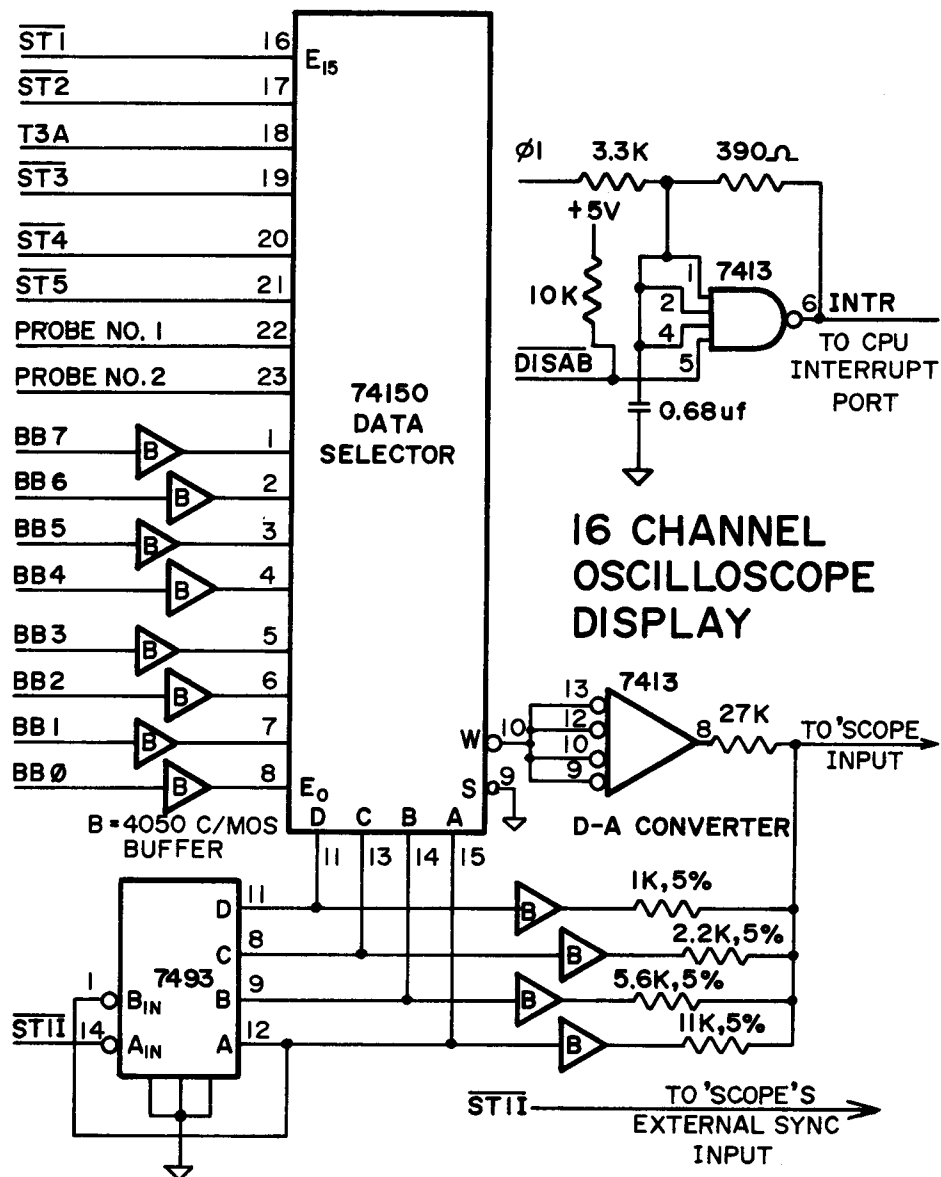


Fig. 24.3.1--Sixteen-Channel Display Draws Timing Diagrams on 'Scope



microcomputer
design

SEC. 24.3 SIXTEEN-CHANNEL OSCILLOSCOPE DISPLAY (cont'd)

the microcomputer and avoid the race condition which otherwise might occur (see Chapter 16). (This is unnecessary with an 8080 CPU.) When the microprocessor recognizes the interrupt, it generates an ST11 strobe, incrementing the 7493 counter and triggering the scope, causing the trace to begin moving from left to right.

The counter's four output bits are used both to control which one of the sixteen input channels is selected, and as inputs to the D/A converter. The four counter outputs constitute the high-order D/A inputs, and the resistors are weighted accordingly. Thus each time the counter increments, it selects a different input channel, and moves the trace up the screen one position.

The data on the selected channel moves through the 74150, is inverted to logic true state, and is connected as the fifth, low-order input bit to the D/A converter. As the trace moves from left to right, this data bit follows the input data on the selected channel, causing the trace to move up and down slightly and in effect drawing a logic timing diagram.

For an 8008, the suggested inputs to the 16-channel display include the eight 8008 output bus (TB) lines; ST1, ST2, T3A, ST3, ST4, and ST5; and two spares which may be connected by probes to signals under investigation. With an 8080, the six control signals might include PH2T, SYNC, DBIN, WR, STACK, and DLO.

The display circuitry should be connected to the microcomputer output bus, as specified above--rather than directly to the CPU bidirectional data bus (BB). This is because the 74150's TTL inputs will in most cases overload the BB bus. (See Chapter 6 on bus structures, Ch. 8 on loading.) When the microcomputer has no output bus, the 16-channel display should include its own low-power buffers to isolate the 74150 from the CPU bus. The 4050 hex CMOS buffers shown in the next section would be suitable for this purpose.

SEC. 24.4 OCTAL DATA DISPLAY

The sixteen-channel oscilloscope display presented above is useful for visualizing the logic state of each bit on the data bus, and elsewhere in the microcomputer, as the program is executed. Sometimes, however, it is more convenient to have the logical states on the data bus decoded, and presented in digital form. The circuit shown in Figure 24.3.1 performs these functions. It is useful in debugging programs, finding errors in new hardware designs, and finding faults on microcomputer cards in production.



microcomputer
design

SEC. 24.4 OCTAL DATA DISPLAY (cont'd)

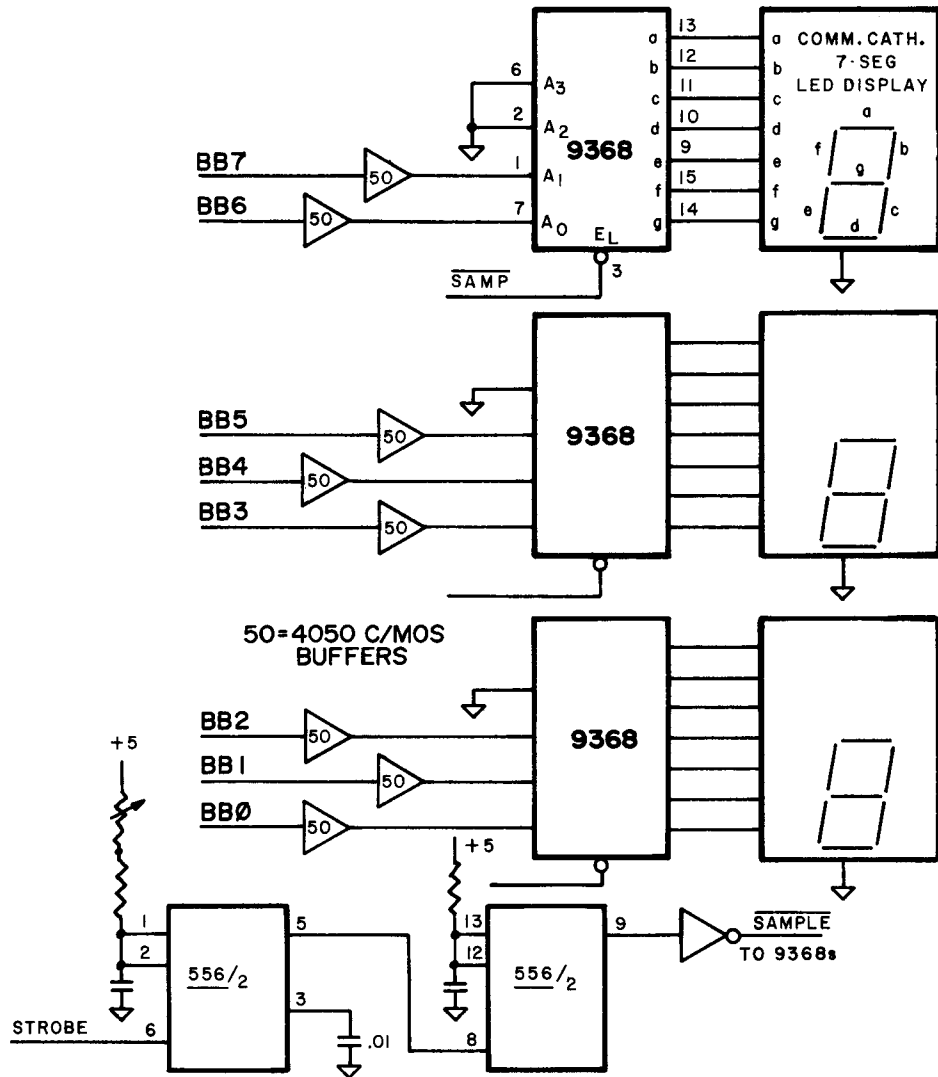


Fig. 24.4.1--Digital Display of Bus Data in Octal Form



microcomputer design

SEC. 24.4 OCTAL DATA DISPLAY (cont'd)

The potentiometer connected to the NE555's THRESHOLD terminal is used to vary the delay period. By moving the control gradually--a ten-turn pot is recommended--the user can make the display move through the program, displaying data on the bus step by step, in octal code.

If more than one interrupt signal is used in the microcomputer under test, additional gating should be provided so that only one particular interrupt will trigger the timer. Alternately, an input strobe, output strobe, or other regularly-executed signal may trigger the timer.

For example, it may be desired to display the bus data only at T3 time. This allows the operator to visualize the instruction codes, input data, memory read data, and memory write data--all of which appear on the data bus of either an 8080 or 8088 microcomputer at this time. Further, the operator may also need to step through the program one instruction cycle at a time. See Figure 24.4.2, an addition to the previous diagram. With the RUN/STEP switch in the STEP position, the 7408 continuously enables the 9368 latch/decoders. Each time the STEP pushbutton is depressed, the CPU READY terminal is enabled by the 7474 flip-flop. The FF is reset at the beginning of the next machine cycle, and the CPU re-enters the WAIT state at the next T3 time. The new T3 bus data is now displayed continuously. With switch in the RUN position, the octal data display operates as described for Figure 2.4.1. In an 8088 system, the signal resetting the flip-flop is (as shown) STI; for an 8080, ADV may be used.

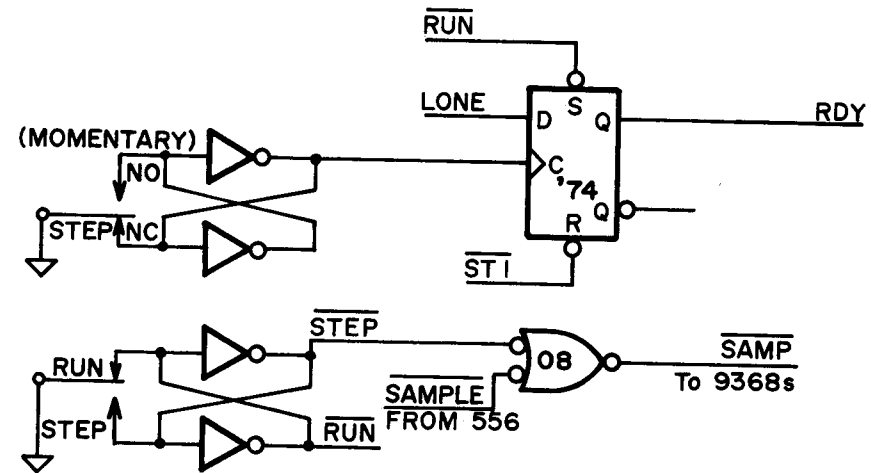


Fig. 24.4.2--Alternate Gating Circuit Displays Instructions Only



microcomputer design

SEC. 24.5 KEEPING THE READY LINE OPEN

In microcomputers based on either the 8080 or the 8008, the CPU's READY terminal is often unused in the final design. This may result when the microprocessor need not wait for slow memory or an external peripheral. Rather than returning this terminal directly to +5 volts, however, it is often better to connect the terminal through a 10 K ohm resistor to +5. This allows a technician or engineer to bring the terminal low when testing the device. When the computer employs an array of pullup resistors on the CPU data bus, the READY pullup resistor can be included in the same resistor package. A test clip can then be snapped over the resistor pack (or the CPU) to allow the operator to step through each instruction cycle.

SEC. 24.6 USING THE SELF-TRANSFER INSTRUCTIONS FOR TESTING

The *Output Any Register* option in Chapter 11 above allows the designer to output any CPU index register to a special output port with one single-byte instruction. The *self-transfer* instructions are decoded--in 8008 mnemonics, LAA, LBB, LCC, LDD, LEE, LHH, and LLL. With an 8080, these instructions are MOV A,A; MOV B,B; etc.

A useful testing technique is based on this concept. Self-transfer instructions are inserted by the programmer into the microcomputer's permanently-stored software (in ROM) at key points in the program. During normal operation, these instructions are NO-OP (no operation) instructions, and simply take up one instruction cycle of the microcomputer's time.

During testing, these instructions are decoded and visualized on a sixteen-channel oscilloscope display. A 93L24 comparator and a 74107 flip-flop (as shown in the *Output Any Register* circuit in Chapter 11) develop the SDT strobe pulse. This signal is used to locate the self-transfer instruction on the oscilloscope screen. One method is to connect one of the two extra display probes of the sixteen-channel display (described earlier in this chapter) to the SDT signal and look for the corresponding pulse on the screen, adjusting the oscilloscope's horizontal position and sensitivity controls for best visualization. The SDT strobe occurs at PCI-T4 time; at the same time, the designated index register appears on the data bus, and will be displayed on the eight lines at the bottom of the screen.

Another method is to use the $\overline{\text{SDT}}$ signal to strobe the oscilloscope display circuit (instead of ST11).

Note that an 8008 377 HALT instruction will be decoded using this technique. (The alternate 000 or 001 opcodes will not be detected). The 8080 HALT instruction (code 166) will always be detected as well.

SEC. 25.1 A NINE-CHIP MICROCOMPUTER

For applications requiring very little temporary data storage capacity, the RAM may be eliminated altogether. The 8008's seven internal index registers are available for temporary storage. A practical circuit, which can be used as an 8008 tester, is shown in Figure 25.1.1.

Introduced as the *MIKE 1*, this micro has been replaced by the *MIKE 2*, available from Martin Research.

25.5.1 Two-Phase Clock The two-phase clock required by the 8008 is generated with three inverters and a capacitor, using a circuit presented in Chapter 5. A 7474 flip-flop and two 7402 NOR gates (shown here as negative AND gates) make up the counter and decoder stages.

25.1.2 Strobe Decoding The strobes ST1, ST2, and so forth, are decoded by a 3205, as shown in Chapter 5. A set-reset flip-flop and an extra NAND gate generate the active-low T3A signal. T3A is not suppressed during PCW cycles, as usual, since there are no PCW cycles--there being no use for memory write (*LM*) instructions in a RAM-less machine.

A single 3205 decoder generates both I/O strobe/enable signals (*Chapter 7*) and memory chip-enable signals. This is done by feeding CCl (sometimes called *DH0*) to the decoder as one of the variables. When CCl is *low* at T3A time, either a PCI (instruction fetch) or PCR (memory read) cycle is being executed--so a PROM should be enabled. When CCl is *high* at T3A time, the cycle is a PCC (command) cycle, and an I/O strobe/enable signal should occur.

25.1.3 Memory Addressing The DL register is of conventional design, and is used to address low-order memory. The CC/DH register does not develop either CC2 or DH0, neither being necessary in this minimally configured microcomputer.

25.1.4 Interrupts The only interrupt signal provided for is the master reset signal created at power-on. A 7474 flip-flop is connected to the 8008's INTERRUPT terminal. A pushbutton START switch at the flip-flop's SET terminal is depressed by the operator at power-on, interrupting the CPU. This initial interrupt starts the microprocessor (*Chapter 16*).

The $\overline{\text{IJAM}}$ signal resets the CC-DH and DL registers to all-zero conditions. At the following PCI-T3 time, the CPU starts to execute an initialization subroutine stored in ROM, starting at memory location 000 000.



SEC. 25.2 USING THE CC-DH REGISTER AS A BUFFER (cont'd)

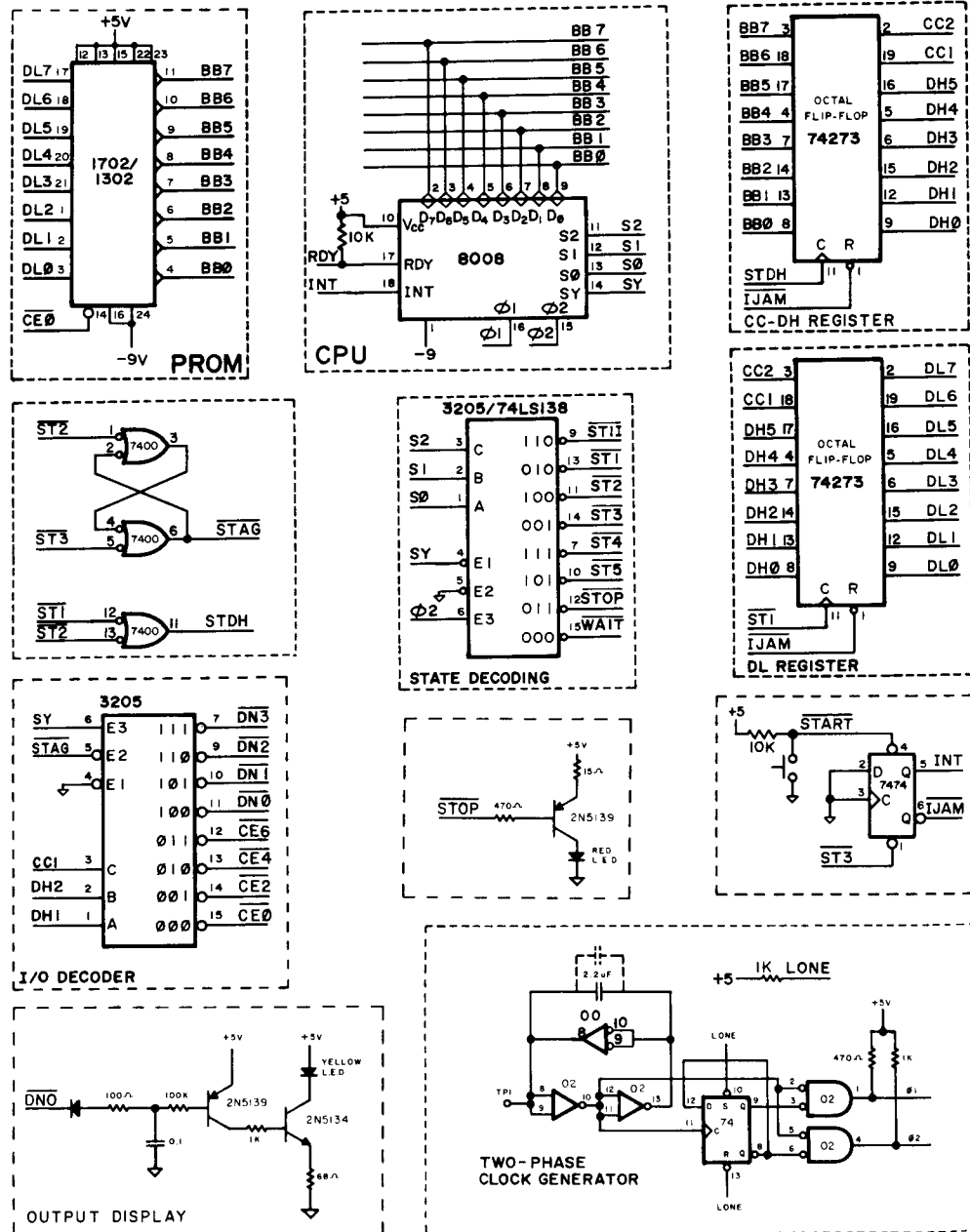


Fig. 25.2.1--Microcomputer Uses CC-DH Register as Data Bus Buffer

SEC. 25.2 USING THE CC-DH REGISTER AS A BUFFER (cont'd)

ST2 time, the CC-DH register is strobed again, and now this register contains its usual information.

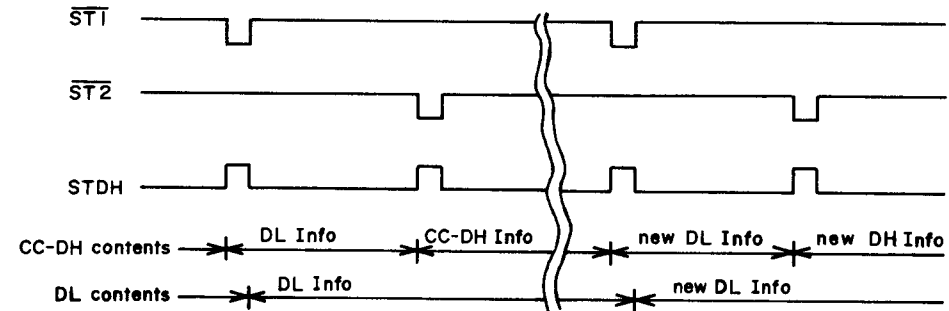


Fig. 25.2.2--Buffered DL Register Timing Diagram

One additional NAND gate is required to effect this scheme, in order to strobe the CC-DH register during both T1 and T2 times. The STDH strobe is active (high) both at ST1 and ST2 times. In Figure 25.2.1, the NAND gate which develops STDH is shown as a negative-OR gate.

In Figure 25.2.1, the circuit for MIKE 1 (shown in Figure 25.1.1) is modified to show this data buffering technique. All eight CC-DH bits are developed, and low-power Schottky devices are unnecessary, since only one 74273 receives from the BB bus. T3A is generated within the 3205, thus freeing up the additional required gate. And, since SY is fed directly to the 3205, a 7400 replaces the 74LS00 needed before.

SEC. 25.3 A TWENTY-DOLLAR MICROCOMPUTER

The circuit for an 8008 microcomputer which can be built for less than \$20.00 in OEM quantities is shown in Figure 25.3.1. It uses a 74S288 F/R/M for program storage (Chapter 14) and develops only two bits of the CC-DH register: CC1 and DH1. The two flip-flops that develop these bits serve as buffers for the respectively-numbered bits in the DL register. The remaining six bits of the DL register are obtained directly from the BB bus.

Another change which has been made in this circuit is that the STAG flip-flop has been eliminated. The T3A signal is generated, effectively, within the 3205 stroke decoder. The T3A signal is produced by



SEC. 25.3 A TWENTY-DOLLAR MICROCOMPUTER (cont'd)

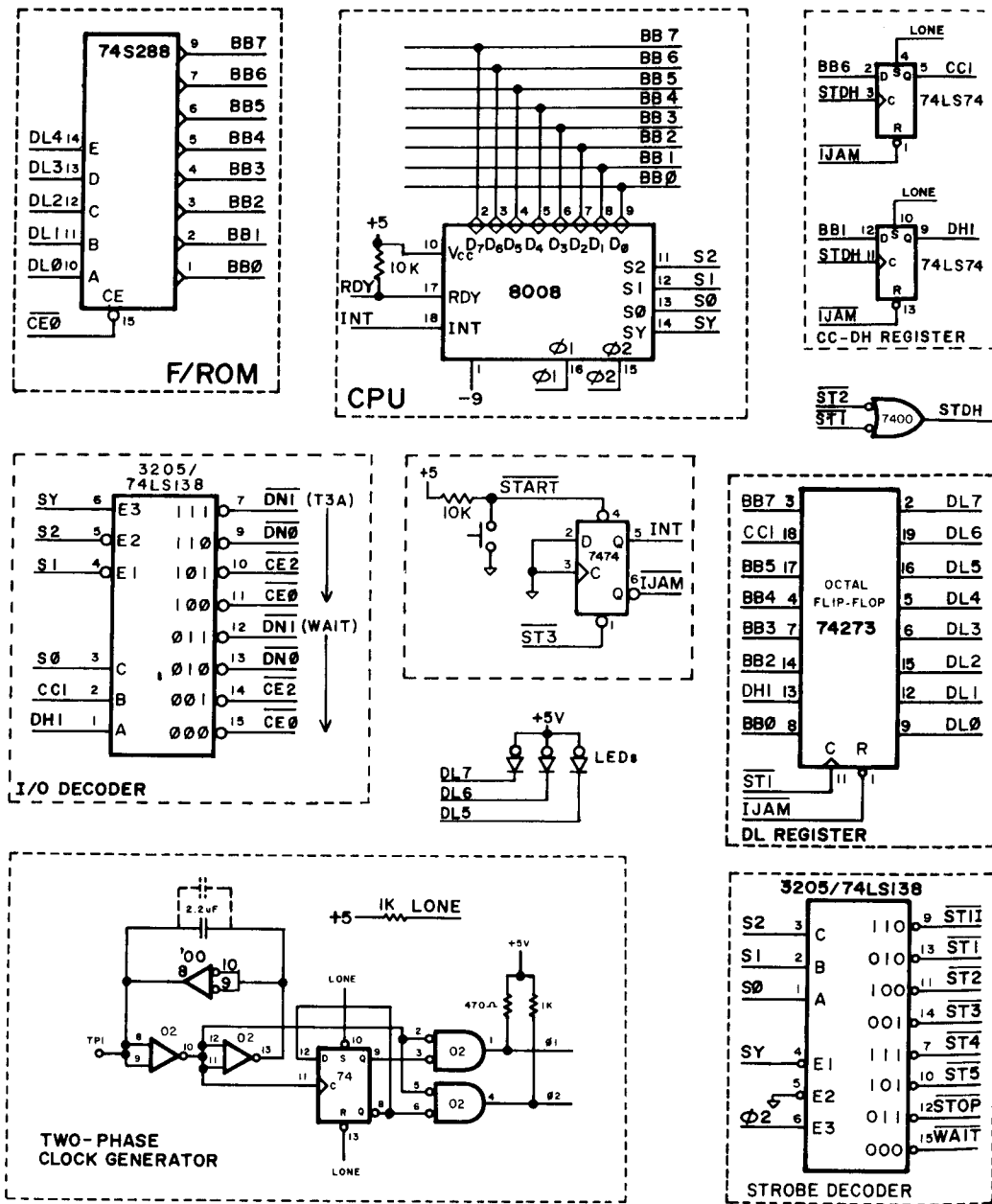


Fig. 25.3.1--Simple Microcomputer Under Control of a F/ROM

SEC. 25.3 A TWENTY-DOLLAR MICROCOMPUTER (cont'd)

connecting its constituent signals to the decoder: $T3A = \overline{S2} \cdot \overline{S1} \cdot S0 \cdot SY$. The 3205 combines these signals with CCI and DHI to produce two I/O strobes. (The race problems which ensue are not detrimental to the operation of the microcomputer.)

Since the high-order DL register bits are not used for memory addressing, they may be used to drive current-limited LEDs. Unusual programming techniques are made possible. For example, the lamp connected to DL5 will be lit by a RESTART 010 instruction, and extinguished by a RESTART 050 instruction. And, since the DL5 bit is not used to distinguish between memory locations in the F/ROM, the program will fetch the instruction in location 010 of the F/ROM following either a RESTART 010 or a RESTART 050 instruction. A JUMP or CALL instruction will turn the DL5 lamp on or off.

SEC. 25.4 A SEVEN-CHIP MICROCOMPUTER

The microcomputer shown in Figure 25.4.1 uses fewer chips than the previous circuits, but is more costly because it contains 2048 bytes of ROM storage. This circuit combines various features of the previous schematics.

Perhaps the most novel feature of this circuit is its economical two-phase clock. Four inverters from a 4449 hex CMOS inverter IC generate Φ1 and Φ2. Note that the values of the RC parts may easily be changed to create an asymmetrical (skewed) clock, should this be desired.



SEC. 25.4 A SEVEN-CHIP MICROCOMPUTER (cont'd)

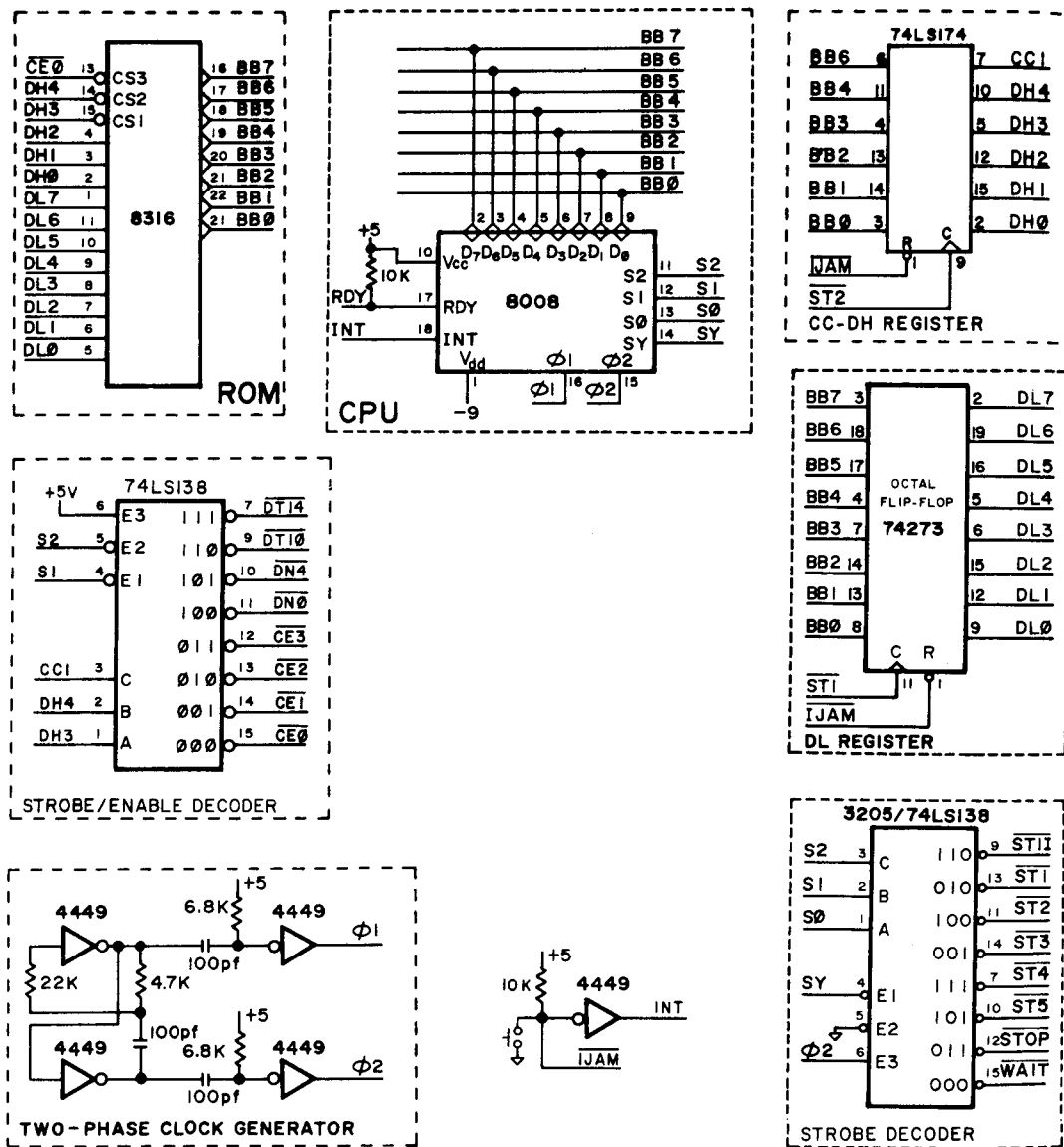


Fig. 25.4.1--Seven-Chip Microcomputer with 2048 Bytes of ROM

SEC. 26.1 A NINETEEN-CHIP 8008-1 MICROCOMPUTER

This chapter describes a microcomputer design example called the MIKE 4. This microcomputer includes a full ASCII keyboard, and has 2048 bytes of ROM. The design also includes 256 bytes of RAM, and is organized in accordance with the RAM-PAGE option (described in Chapter 14) for easy memory addressing and more flexible interrupt handling. MIKE 4 has one eight-bit output port, and one six-bit input port (in addition to the keyboard). Five extra enable/strobe lines are developed, allowing the user to add input and output ports with little difficulty. The MIKE 4 is useful in applications requiring accurate and consistent timing, since it uses a crystal-controlled clock.

The remaining sections of this chapter describe the operation of the MIKE 4. Though unique features are described, a full description of every function is not provided here, to avoid duplication with the foregoing chapters of this book. Instead, the reader is referred to the relevant chapters.

SEC. 26.2 THE MICROPROCESSOR

The schematic for the MIKE 4 in Figure 26.2.1 shows an 8008-1 microprocessor. This selected device provides an instruction cycle time of 12.5 microseconds--the time needed to execute an instruction, such as IAB, which uses all five internal processor states (T1 through T5). A standard 8008 may be substituted if the 12.8 MHz crystal is replaced with an 8.0 MHz crystal, without any other circuit changes. The instruction cycle time would then be 20.0 microseconds.

| CRYSTAL FREQ. (MHz) | phi1 FREQ. (KHz) | SY FREQ. (KHz) | STATE TIME (us) | INST. CYCLE TIME* (us) | COMMENTS |
|---------------------------|------------------------|----------------------|-----------------------|---------------------------------|---------------------------------------|
| 8.0 | 500 | 250 | 4.0 | 20.0 | Standard 8008 speed. |
| 10.0 | 625 | 312.5 | 3.2 | 16.0 | Many if not most 8008s run this fast. |
| 12.8 | 800 | 400 | 2.5 | 12.5 | 8008-1 speed. |

*Instruction cycle time for five states (T1 - T5)

Fig. 26.2.1--Crystal Frequencies, Timing, 8008 Speeds



SEC. 26.2 THE MICROPROCESSOR (cont'd)

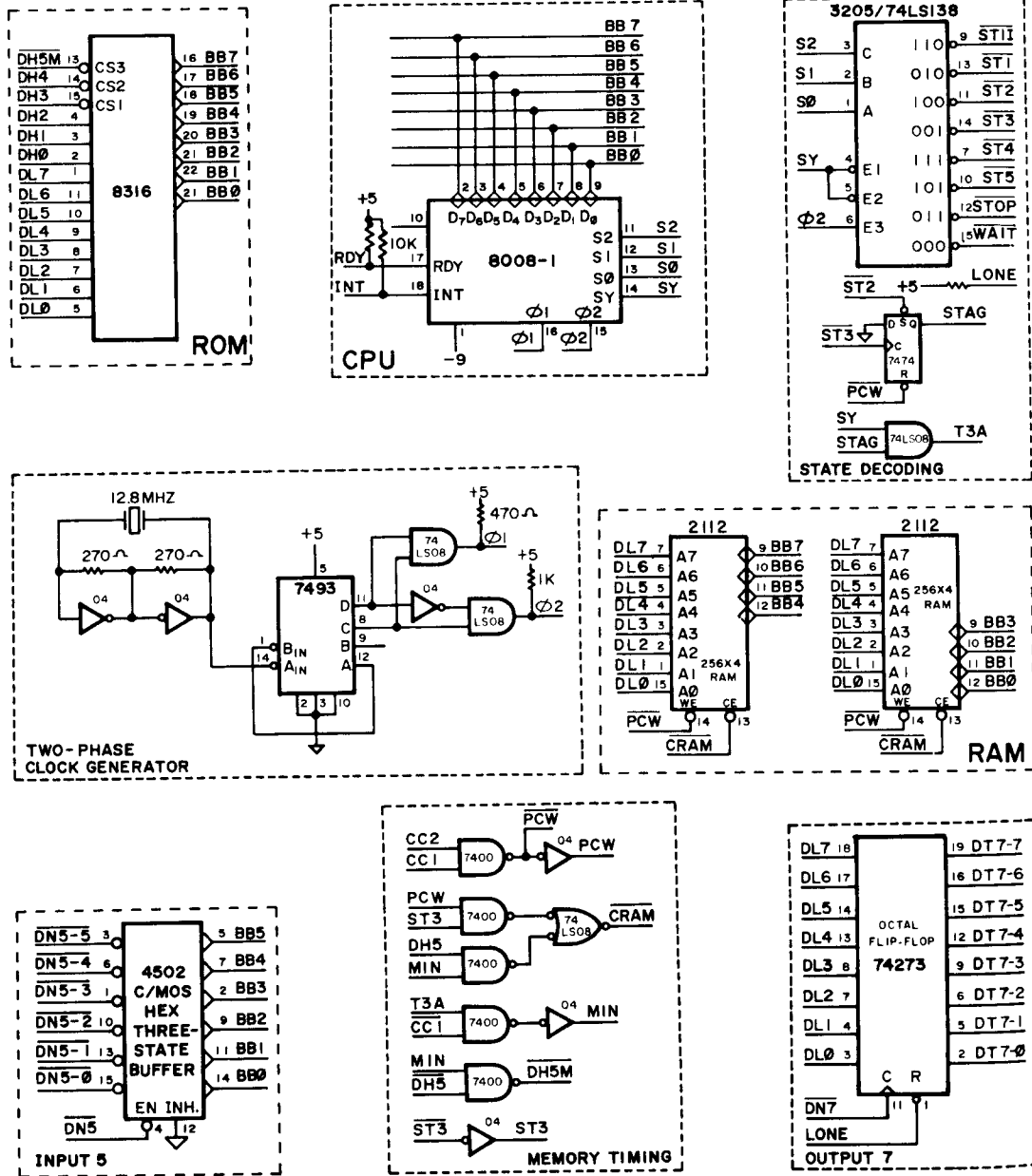


Fig. 26.2.2--The MIKE 4, a 19-Chip Microcomputer (Part 1)

SEC. 26.2 THE MICROPROCESSOR (cont'd)

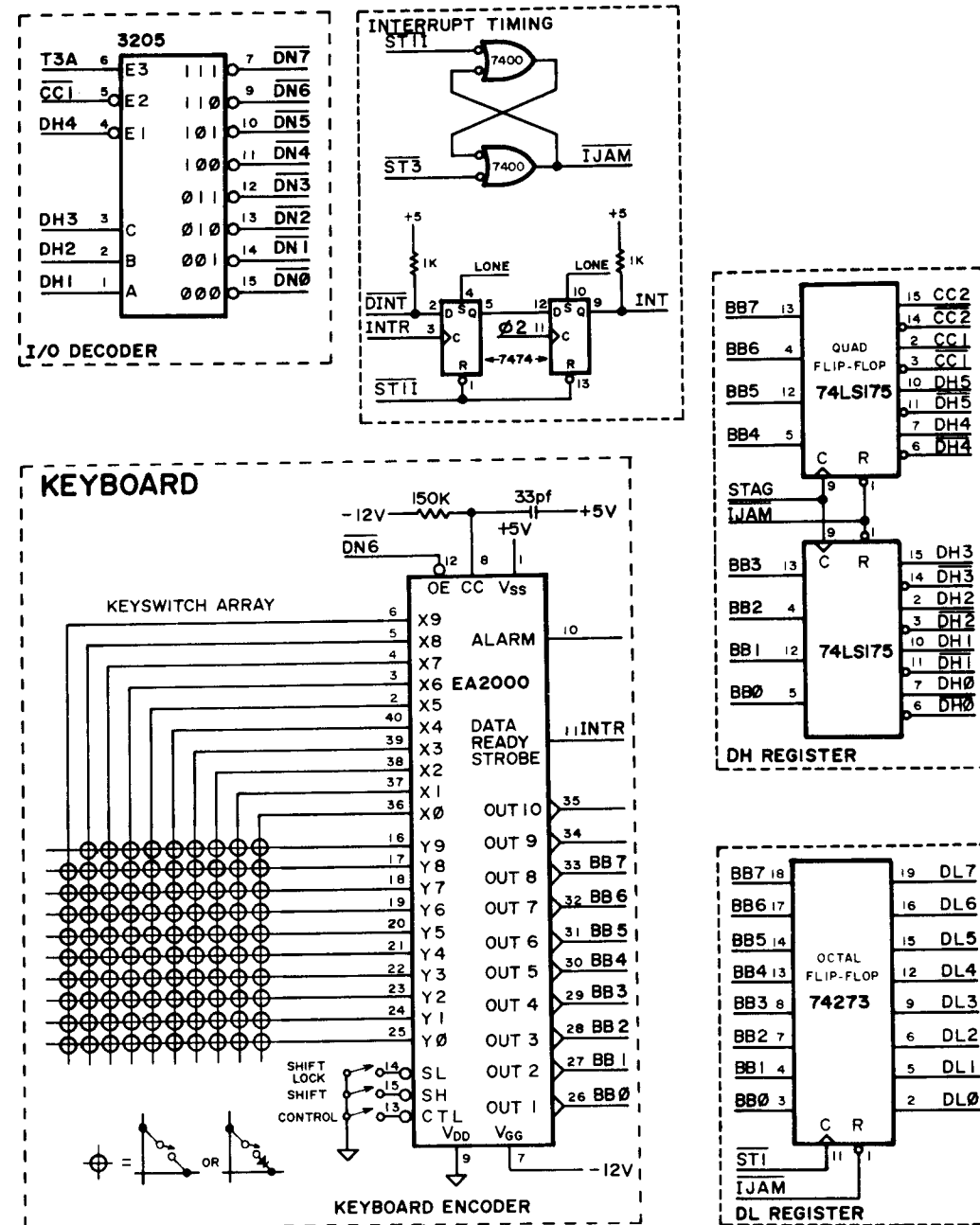


Fig. 26.2.2--The MIKE 4, a 19-Chip Microcomputer (Part 2)

SEC. 26.2 THE MICROPROCESSOR (cont'd)

The 8008 bidirectional data bus, BB7 through BB0, is connected directly to the ROM, DH and DL register data inputs, keyboard encoder outputs, and the *Input 5* input port. Note the use of low-power Schottky devices for some of these functions, so that the total load on the 8008 data bus remains within specified limits. These parts allow the circuit to function without data bus buffering. (See Chapter 6 on bus structures, Chapter 8 on input load considerations.)

SEC. 26.3 MAIN TIMING

The crystal oscillator produces a 12.8 MHz signal which is divided by 16 by the 7493 binary counter. The two 74LS08 AND gates combine the 800 KHz and 1.6 MHz signals from the counter to produce $\phi 1$ and $\phi 2$. The 1 K ohm pullup resistors make sure that these signals meet the 3.5-volt CPU logic high input requirements. The CPU further divides $\phi 2$ by two, producing the SYNC (SY) signal, a 400-KHz (2.5 microsecond) state cycle time. Thus a five-cycle instruction takes 12.5 microseconds with the 8008-1, as stated above.

SEC. 26.4 STATE DECODING

A 3205 (74LS138) 3-to-8 decoder connected to the CPU is used to produce eight strobe/enable signals. The decoder is strobed by $\phi 2$ and SYNC, which produces signals valid during the middle of each state--T1, T2, T3, etc.--thus greatly simplifying the development of strobe and enable signals used for activating inputs and outputs (Chapter 5).

The 3205 is chosen not only for its functional convenience but because its low-power inputs do not overload the drive power of the CPU.

Also developed are several special-purpose signals. The STAG pulse begins in the middle of T2 time (at ST2 time) and ends in the middle of T3 time (at ST3 time). The 7474 flip-flop that develops STAG is reset by PCW, which suppresses the development of STAG during memory write (PCW) instruction cycles.

The T3A signal is developed ANDing STAG and SYNC from the CPU. This produces a signal which goes high late in T2 time, and low in mid-T3 time (end of SYNC). T3A is used primarily to enable input devices to drive the CPU data bus, and is also used as an output strobe (Chapter 9).

$\overline{DH5M}$ (that is, $\overline{DH5}$ modified) is produced by NANDing MIN and $\overline{DH5}$. Note the conditions for $\overline{DH5M}$ to go low: (1) DH5 must be low and (2) CC1 must be low (3) at T3A time. $\overline{DH5M}$ is used to enable ROM memory.

SEC. 26.5 DH AND DL REGISTERS

A 74273 eight-bit latch serves as the DL register. It is strobed at ST1 time and cleared to all-zeros during interrupts by the IJAM signal.

Two 74LS175s make up the DH register. Their low input currents prevent overloading of the BB bus, which is already driving the DL register (about 0.625 TTL load). These chips provide complementary outputs which are needed in the microcomputer, and they are strobed by the rising edge of STAG (in other words at the beginning of ST2 time). Like the DL register, the DH register is cleared out during interrupts by IJAM.

As always in the 8008 microcomputer, the DH and DL registers are used to address memory (Chapter 13). In addition, the DL register temporarily stores output data during output instructions (Chapters 7, 9).

SEC. 26.6 RAM AND ROM MEMORY

This microcomputer has one page (256 bytes) of RAM memory, made up of two 2112 256 x 4 RAMs. Memory is organized according to the RAM-PAGE option (discussed in detail in Chapter 13). Memory write instructions automatically reference RAM memory without setting up the H register, as implied by the memory enabling signals discussed above. Only the eight low-order memory address bits are used; note the connection of the 2112s to the DL register bus.

A memory read instruction references RAM *only* if DH5 is high. That is, all thirty-two high-order memory page addresses, 077 through 040, point to this one page of RAM. This is of great convenience in programming (as outlined in Chapter 13). For an illustration, see the Mike 4 memory map in Figure 26.6.1.

This design provides for one 8316 2048 x 8 ROM, occupying pages 007 through 000. The ROM is addressed during memory read cycles when DH5 is low. The $\overline{DH5M}$ signal combines this condition with T3A, thus strobing the ROM at the correct time for the CPU to receive input data on the BB bus. This ROM is addressed when DH5, DH4, and DH3 are all low. Other ROMs may be added using other combinations of DH4 and DH3, but DH5 must always be low to avoid conflict with RAM addresses.

See Chapter 14 above for an alternate version of this MIKE 4 memory map, where the ROM-IN option allows access to ROM through input instructions.



SEC. 26.6 RAM AND ROM MEMORY (cont'd)

| PAGE NUMBER | USAGE | PAGE NUMBER | USAGE | PAGE NUMBER | USAGE | PAGE NUMBER | USAGE |
|-------------|-------|-------------|-------|-------------|--------|-------------|--------|
| 077 | RAM | 057 | RAM | 037 | ROM #3 | 017 | ROM #1 |
| 076 | | 056 | | 036 | (OPT.) | 016 | (OPT.) |
| 075 | | 055 | | 035 | | 015 | |
| 074 | | 054 | | 034 | | 014 | |
| 073 | | 053 | | 033 | | 013 | |
| 072 | | 052 | | 032 | | 012 | |
| 071 | | 051 | | 031 | | 011 | |
| 070 | | 050 | | 030 | | 010 | |
| 067 | | 047 | | 027 | ROM #2 | 007 | ROM #0 |
| 066 | | 046 | | 026 | (OPT.) | 006 | |
| 065 | | 045 | | 025 | | 005 | |
| 064 | | 044 | | 024 | | 004 | |
| 063 | | 043 | | 023 | | 003 | |
| 062 | | 042 | | 022 | | 002 | |
| 061 | | 041 | | 021 | | 001 | |
| 060 | | 040 | | 020 | | 000 | |

Fig. 20.6.1--Memory Map for MIKE 4

SEC. 26.7 I/O STROBE/ENABLE DECODING

A second 3205 decoder is used to produce the eight signals $\overline{DN7}$ through $\overline{DN0}$. This decoder is enabled only at T3A time of an input/output (I/O) instruction (PCI cycle) when CC2 = 0 and CC1 = 1. The resultant enable signals are, in the schematic, used to activate the keyboard encoder ($\overline{DN6}$), and activate the six-bit input port ($\overline{DN5}$). The *Input 7* instruction is used as a strobe for the *output port*, see below. The remaining enable and strobe signals, $\overline{DN4}$ through $\overline{DN0}$, can be used for input/output expansion. (However care must be taken not to overload the CPU data bus.)

SEC. 26.8 INPUT PORT

A six-bit input port is available for accepting digital data from the outside world. Made of a 4502 three-state MOS buffer, this input is accessed by performing an *Input 5* instruction. Note that the 4502 has inverting inputs. Note also that all of the *input devices* on the CPU bidirectional data bus (BB7 through BBO) are MOS ICs. None should have trouble driving the 8008 to the required logic high input voltage of 3.5 volts. If a TTL three-state buffer (with non-inverting inputs) were used--such as the 74367--there would be no assurance that any given part would meet the 3.5-volt specification. An array of 22 K ohm

SEC. 26.8 INPUT PORT (cont'd)

pullup resistors would have to be added to the BB bus to use either the 74367 or the new eight-bit TTL three-state buffer, the 74S240.

SEC. 26.9 KEYBOARD ENCODER

The *MIKE 4* includes a full ASCII keyboard. The Electronic Arrays EA 2000 keyboard encoder can handle up 99 keys, with facilities for shift and control modes. The chip has a ten-by-ten scanning matrix; only the 99th position (X9, Y9) may not be used. Operation is similar to the National keyboard encoder described in more detail in Chapter 21 above.

In this design, when a key closure is detected, the encoder's DATA READY STROBE signal goes high, causing an interrupt to be requested of the microprocessor. The CPU handles the processing of the ASCII-encoded keyboard word as part of an interrupt subroutine. This subroutine contains an *Input 6* instruction, which is used to get the keyboard data. The $\overline{DN6}$ strobe enables the encoder's three-state outputs, transferring the keyboard data word directly onto the CPU data bus.

The EA2000 contains its own internal clock, whose speed is determined by the external RC components shown in the diagram.

SEC. 26.10 INTERRUPT FUNCTION

An interrupt request generated by the keyboard encoder sets a 7474 flip-flop. At the rising edge of the next $\phi 2$ signal, an associated 7474 flip-flop is also set. This provides the interrupt synchronization necessary to avoid a race condition (as discussed in Chapter 16).

When the CPU recognizes an interrupt, it substitutes a T1I cycle for the next T1 state. The microcomputer's state decoding stage decodes this state, producing the ST1I strobe at T1I time. This signal sets the two-gate set-reset flip-flop shown in the *Interrupt Timing* section of the *MIKE 4* schematic, causing the \overline{IJAM} signal to go low.

The \overline{IJAM} signal is used to reset the CC-DH and DL registers to an all-zero condition. In effect, the memory address is now 000 000. At the PCI-T3 time that follows, the CPU will fetch the instruction from memory location 000 000. This location contains a RST 010 which forces a call to a subroutine, starting at location 000 010, used for processing keyboard data.



SEC. 26.10 INTERRUPT FUNCTION

As usual at the end of an interrupt subroutine, a *RETURN* instruction causes the CPU to return to the memory location being processed at the time when the interrupt was received.

The initial interrupt required to start the microprocessor is provided by tapping any keyboard key.

SEC. 26.11 THE MODULAR MICRO SERIES

Martin Research has introduced a series of microcomputer modules, including the 8008-based *MIKE 2* and the 8080-based *MIKE 3*. A computer based on the Z-80, the *MIKE 3*, was being introduced as this book to press. Though prototyped, the *MIKE 4* discussed in this chapter is not currently available.

The *modular micro* series uses a universal bus structure, compatible with standard eight-bit microprocessors, similar to that discussed in Chapter 20 of this book. Another useful feature is the single-PROM MONITOR program provided with each microcomputer system. More elaborate software packages--such as the *MONITOR 8* operating system for the 8008, and the *MONITOR 80* for the 8080-- are also available (or in development).

Schematics, circuit descriptions, and software listings appear in the *MIKE 2 MANUAL*, *MIKE 3 MANUAL*, and so forth. For details, contact Martin Research.

NEW FROM MARTIN RESEARCH...



As the microprocessor revolution continues, microcomputers find their way into an ever-widening variety of applications. Our *silver box*--a versatile industrial control package-- is a case in point, since it puts high-power computer technology to work in a low-cost controller.

Other new products :

- The new *DEBUG* version of the 8080-based *MIKE 3*, a low-cost development system with single-step and 32-channel oscilloscope display
- New special-purpose boards in the *modular micro* series: a serial communications board; a battery-backed power supply; and a control interface module


MODULAR MICROS...

The *modular micros* from Martin Research provide all the advantages of microprocessor technology. These versatile printed circuit modules communicate via a bus structure, compatible with:

- The *MIKE 3* series, based on the industry standard 8080
- The *MIKE 2*, based on the 8008-- for small industrial controllers
- The new *MIKE 8*, based on the Z80 from Zilog/Mostek--combining the best features of the 8080 and 6800

MODULARITY...

Our design philosophy: *cost-effective modularity*. The CPU board, housing the microprocessor, provides the basic control signals needed for the system. Then, each memory, I/O, or peripheral interface board contains all the logic unique to its special function. Nearly all the costs associated with a keyboard, for example, are on that keyboard module--and the user does not pay for it until a keyboard is needed. Still, the bus structure is designed for complete flexibility, allowing the full potential of the microprocessor to be put to work as new functions are added.

 

THE MIKE 3...

The *MIKE 3* typifies the *modular micro* approach. An optimal small system, yet fully expandable. The AT813 is a three-board system, based on the Model 471 CPU board, with an 8080A microprocessor. (For complete description, see page 4.) The system comes with a Model 420 Console board, featuring a calculator-style keyboard and six fully-decoded LED digits. The third board is a Model 423 PROM/RAM board, with 512 bytes (½K) of RAM and a versatile MONITOR program in a PROM. The MONITOR allows the user to program the computer with the keyboard, visualizing the results on the LED digits. (The 423 board has capacity for up to 1K of RAM and 2K of PROM.) An ideal small system for prototyping and for educational use, the AT813 lists for only \$395.00, fully assembled and tested.

NEW DEBUG SYSTEM!

Martin Research takes pride in announcing the AT814, a *MIKE 3* computer featuring a powerful but low-cost diagnostic package. Designed for use in development, trouble-shooting, and educational applications, the 814 is one of the most powerful basic development systems available today.

DEBUG PROM...

This software package supplements the *MIKE 3 MONITOR* by allowing the user to step through programs one instruction at a time, using the console keyboard. Unlike the step/run switch on other computers, however -- which simply deactivates the CPU between instructions--the *DEBUG PROM* maintains full processor activity. After executing each instruction, the user can inspect the status of every data register in the computer--any desired memory location (including the program stack) and the 8080's internal registers and flags! Or, the user can set a breakpoint at any desired location, even a point in PROM or ROM memory.

32-Channel Scope Display

The 32-Channel Microprocessor Data Display allows the user to inspect all important computer signals on an external single-trace, triggered sweep oscilloscope, 16 channels at a time. When a switch on the Model 472 Debug Board is pressed, the 16 address lines are displayed; otherwise, the data bus and selected control signals appear on the scope. Two probes on the 472 board may be used to trace any desired signals in the computer.

The AT814 comes with the 472 Debug board (with space for custom interface circuitry), 471 CPU board (with 8080A), console board, and 423 PROM/RAM board (MONITOR and *DEBUG* PROMs, and ½K of RAM). Fully assembled and tested, the AT814 lists for \$495.00.

A similar *MIKE 8* system, for the Z80, is available. Contact us for prices.



microcomputer
design



modular micros




martin research



The *FOUR KILOBYTE RANDOM ACCESS MEMORY* is a member of the family of modular microcomputers from Martin Research. Consisting of 4,096 eight-bit bytes of memory storage (for a total of 32,768 bits), this 4K RAM is fully compatible either with an 8080 system--the *MIKE 3*--or with an 8008 system--the *MIKE 2*. Featuring static memory devices, the 405 includes full memory address decoding, with user-programmable addresses. An optional WAIT circuit on the board allows the user to accommodate slow RAM chips to a fast CPU. The board requires a single +5 volt supply, and uses standard 50-pin connectors for plug-in interfacing with the *MIKE 3/MIKE 2* bus.

SPECIFICATIONS

| | |
|--------------------|--|
| <i>Speed</i> | 450 nanoseconds access time is standard for 4K RAMs purchased from Martin Research. This speed is suitable both for our 8080 system (<i>MIKE 3</i>) and for the 8008 (<i>MIKE 2</i>). |
| <i>Power</i> | Requires +5 volt supply, regulated $\pm 5\%$. Typical current requirement for full complement of 4K, using 32 type 2102A-4 RAM chips, 1.0A. |
| <i>Interfacing</i> | Connects directly to the modular micro bus with fifty-pin connectors. Memory address is user-selectable using jumpers on the board. |
| <i>Mechanical</i> | Standard size for Martin modular micro family: 5.5 by 7.0 inches (140 by 178 mm). Printed circuit boards are manufactured by commercial PC houses to meet professional standards, with plated-through holes, solder-mask protection of traces on the solder side of the board, and silkscreened part outlines for ease in assembly and repair. |

 


The 420 Console Board consists of a calculator-type keyboard and a six-digit display. In a typical modular micro system, the keyboard is used to program the microcomputer, and the bright, large (0.3-inch) digits are used to display data and memory addresses.

The keyboard may also be used for any other data input function, and the digits for any other display purpose--under control of the microcomputer. The keyboard is simply an input port, and the display, a set of output ports. The digit drivers will display data in octal, decimal, or hexadecimal (0-9 and A-F) formats.

A significant advance over older console designs--where banks of switches and lights are hardwired into the system control circuitry--the 420 keyboard/display reflects state-of-the-art systems design, as used in the latest generation of small computers.

PHOTO: Closeup shows bright digits, 20 keys

 

SPECIFICATIONS

Keyboard interface:

The numerals 0-9, and six special-function keys, are electronically interpreted in hexadecimal and make up microcomputer input port 006. Two more control keys interface as additional bits in input 006. The remaining two keys are related to the system interrupt function.

Display interface:

The six LED digits are driven by microcomputer output ports 015, 016, and 017. The 420's decoders display the numerals 0 through 9, and the hexadecimal numbers from A through F, thus: A, b, C, d, E, F.

System interface:

Board connects directly to the *modular micro* bus with standard fifty-pin connectors. Includes bus drivers for adequate drive power in expanded systems.

Power:

Requires a single +5 volt supply, $\pm 5\%$, 950 MA.


The 423 PROM/RAM BOARD is a basic memory component for computer systems in the modular micro family. The 423 has room both for 2K of programmable read-only memory (PROM), and for 1K of random access memory (RAM). Typically the PROM is used for storage of programs essential to system operation--such as the MIKE 3 or MIKE 2 Monitors. The RAM is for storing user's programs, for temporary data storage during program execution, and for storing CPU register status during subroutine and interrupt handling.

An optional WAIT circuit on the board allows the user to accommodate slow memory chips to a fast CPU. In addition, the memory address of each block of PROM and RAM is user-selectable. Both architecture and control structure of the 423 make it suitable for interfacing with a variety of modular micro systems.

SPECIFICATIONS

| | |
|------------------------|--|
| <i>Memory Capacity</i> | Up to 2K bytes of PROM: uses up to eight type 1702A, 256 by 8 reprogrammable memory devices. Up to 1K of RAM: up to eight type 2112 256 by 4 static RAM chips. |
| <i>Speed</i> | RAM, 800 ns select time; PROM, 900 ns select time (meets requirements of 8008-1 system without memory wait cycles). Faster memory chips available as options. |
| <i>Interfacing</i> | Connects directly to the modular micro bus with standard fifty-pin connectors. On-board bus drivers ensure adequate driving power for expanded systems. Typical page addresses: PROMs, pages 000 through 007; RAMs, pages 010 through 013. However, memory addresses are user-selectable using jumpers on the board. |
| <i>Power</i> | With 256 bytes each of PROM and RAM, requires +5 V, 380 MA; -9 V, 35 MA; regulated $\pm 5\%$. (-9 V can be derived from a -12 V supply using optional on-board diodes.) |

423

 

REV. A

The Model 424 Serial Communications Board interfaces a microcomputer with a wide range of peripheral devices. A typical use is to interface a *modular micro* system to a teletypewriter, CRT terminal, or data set.

The 424 converts the eight-bit parallel data format found within the microcomputer, to a serial bit stream that can be *transmitted* over a single pair of wires. The 424 also *receives* serial data from an external device, converting the serial format back to eight-bit bytes for use by the computer. The 424 permits locating the microcomputer remotely from the peripheral device, both simplifying interconnections by reducing the number of conductors required, and enhancing data transmission reliability at any distance.

The 424 can handle two completely independent terminals, each capable of both sending and receiving data simultaneously (*full duplex* mode). Data transmission need not be synchronous with microcomputer internal timing--thus simplifying interfacing--because the 424 makes use of IC UARTs (universal asynchronous receiver/transmitters). The speed of transmission (baud rate) is programmable, under control of microcomputer output instructions.

The microcomputer to which the 424 board is connected is effectively DATA TERMINAL EQUIPMENT (as contrasted with Data Communications Equipment) under the communications conventions which apply to serial data. The 424 is capable of meeting the principal requirements of RS-232-C, a widely-used serial data interchange standard ("*EIA Interface*"). The 424 may also be adapted for the 20-milliamp current loop (*neutral current* interface) found in the Model 33 Teletype, or to other teleprinters using 60 MA current loops.


Optical isolators may be inserted on the 424 board, when exceptional line distance or unusual ambient noise requires this optional feature.

A schematic for the 424-4 version appears on pages 3 through 8.

TABLE OF CONTENTS

| PART | DESCRIPTION | PAGE |
|--------|---------------------------------------|------|
| SEC. 1 | 424 VERSIONS AVAILABLE | 2 |
| SEC. 2 | SERIAL/PARALLEL INTERFACING | 2 |
| SEC. 3 | SOFTWARE FOR THE 424. | 14 |

424

 

REV. A

SEC. 1 424 VERSIONS AVAILABLE

The 424 board includes provisions for a number of different options and configurations. Some of these options are available in standard versions from Martin Research, to fit certain common functions. Unless otherwise requested, all 424 boards are assembled and tested for operation in *MIKE 3* systems (8080 processor) or *MIKE 8* systems (Z-80 processor). For operation in a *MIKE 2* system (8008 CPU), see Sec. 8 below.



| MODEL | DESCRIPTION AND COMMENTS |
|---------|--|
| AT424-2 | Interfaces to a single Model 33 Teletype. 20 MA current loop. Does not include a UART. Requires a routine in the micro's software for developing the appropriate printer timing. (See Sec. 7 below.) |
| AT424-3 | Interfaces to a single Model 33 Teletype. 20 MA current loop. Includes a UART and programmable baud rate generator. Microcomputer communicates with the TTY via parallel data, i.e., memory read/write instructions. |
| AT424-4 | Two-terminal interface; for one Model 33 TTY, 20 MA current loop, and one terminal with an EIA interface. Two UARTs; dual programmable baud rate generator. Can be modified for optoisolation (Sec. 6 below). |
| AT424-5 | Two-terminal interface; for one PR11000 printer, and one terminal with EIA interface. Otherwise similar to AT424-4. |
| AT424-6 | Two-terminal interface; for one PR11000 printer, and one terminal with EIA-style interface, including optoisolation on the input leads from the EIA terminal. Otherwise similar to AT424-4. |

SEC. 2 SERIAL/PARALLEL INTERFACING

This section gives a general overview of the purpose of the 424 board, to interface between a modular micro system and peripheral devices, using serial data transfers.

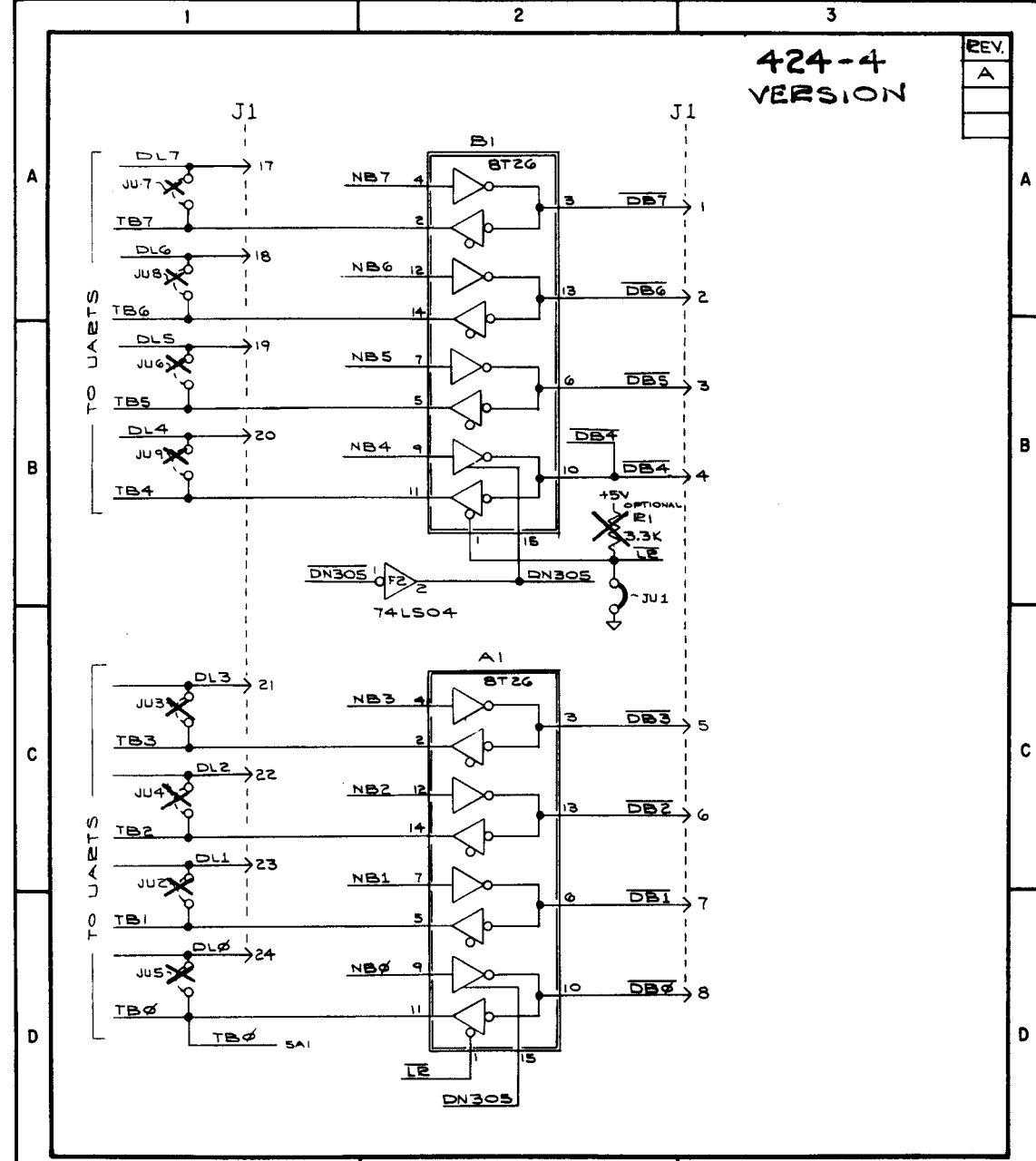 2.1 Serial versus Parallel Data transfers within the micro-computer generally take place eight bits at once, in *parallel*. However, it is convenient when interfacing with communications devices, such as teleprinters, to use a *serial* data format, where characters are sent one bit at a time, sequentially. This format potentially saves on connection costs, and also readily lends itself to transmission via radio link or telephone line (after conversion of electrical pulses to audio tones, by a modulator/demodulator, or *modem*).


The principal function of the 424 board is to convert parallel data to serial, for transmission to peripheral devices external to the microcomputer, and to receive serial data from these peripherals and convert it back to parallel data.




| |
|------|
| REV. |
| A |
| |
| |



424

 NOTE: PROPRIETARY INFORMATION. NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.
 DRAWN BY Boeck CHECKED BY DWK DRAWING NO. DS424 PAGE 3
 DATE 4-20-76 DATE 6-17-76




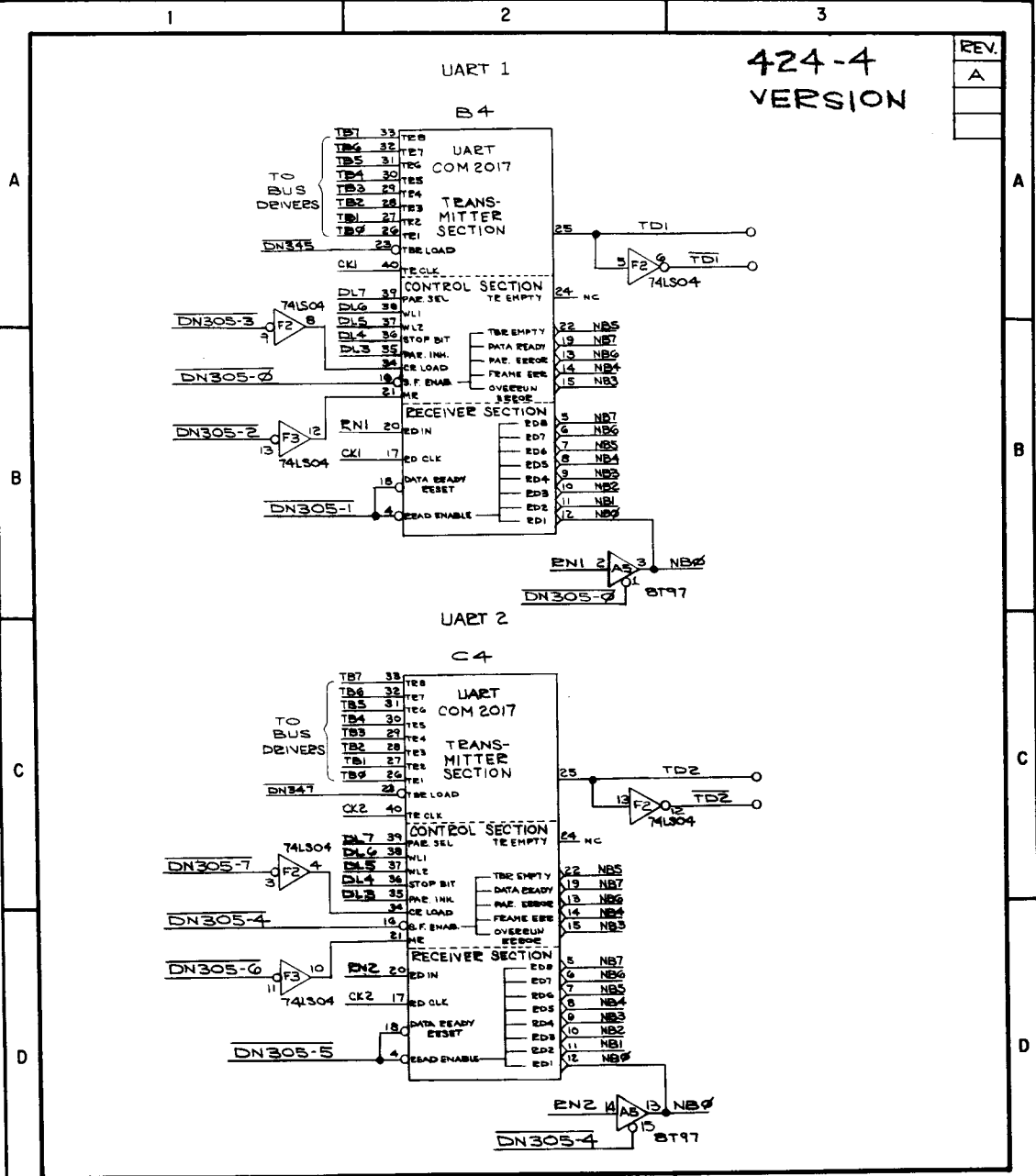

  NOTE: PROPRIETARY INFORMATION. NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.
 DRAWN BY *Roeck* CHECKED BY *DTX* DRAWING NO. DS 424 PAGE 4
 DATE 4-20-76 DATE 6-17-76




 NOTE: PROPRIETARY INFORMATION. NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.
 DRAWN BY *Amis* CHECKED BY *DTX* DRAWING NO. DS 424 PAGE 5
 DATE 3-13-76 DATE 6-17-76



424

SERIAL COMMUNICATIONS BOARD

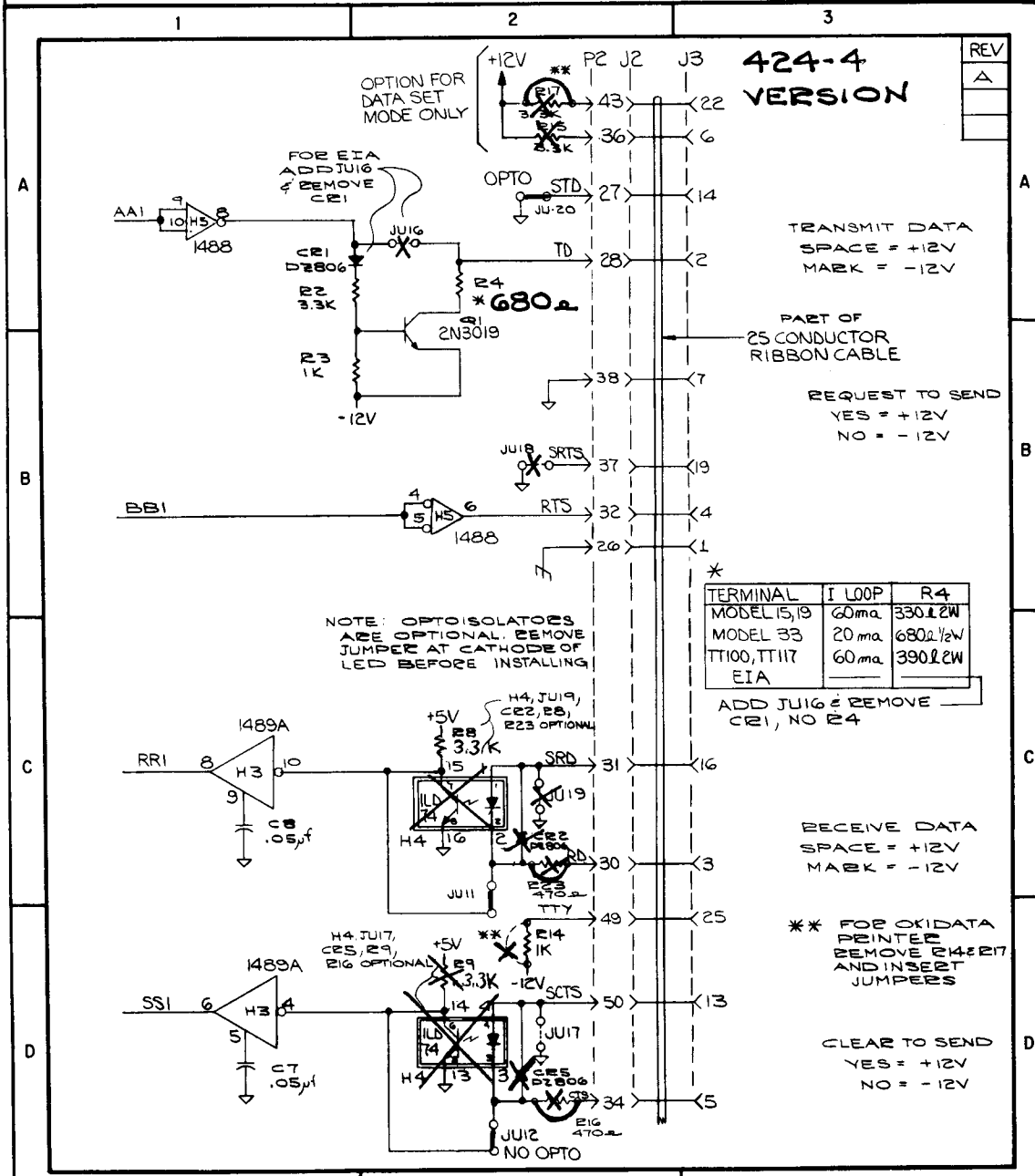


NOTE: PROPRIETARY INFORMATION. NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.

DRAWN BY *[Signature]* CHECKED BY *[Signature]* DRAWING NO. DS-424 PAGE 6

DATE 3-13-76 DATE 6-17-76

SERIAL COMMUNICATIONS BOARD


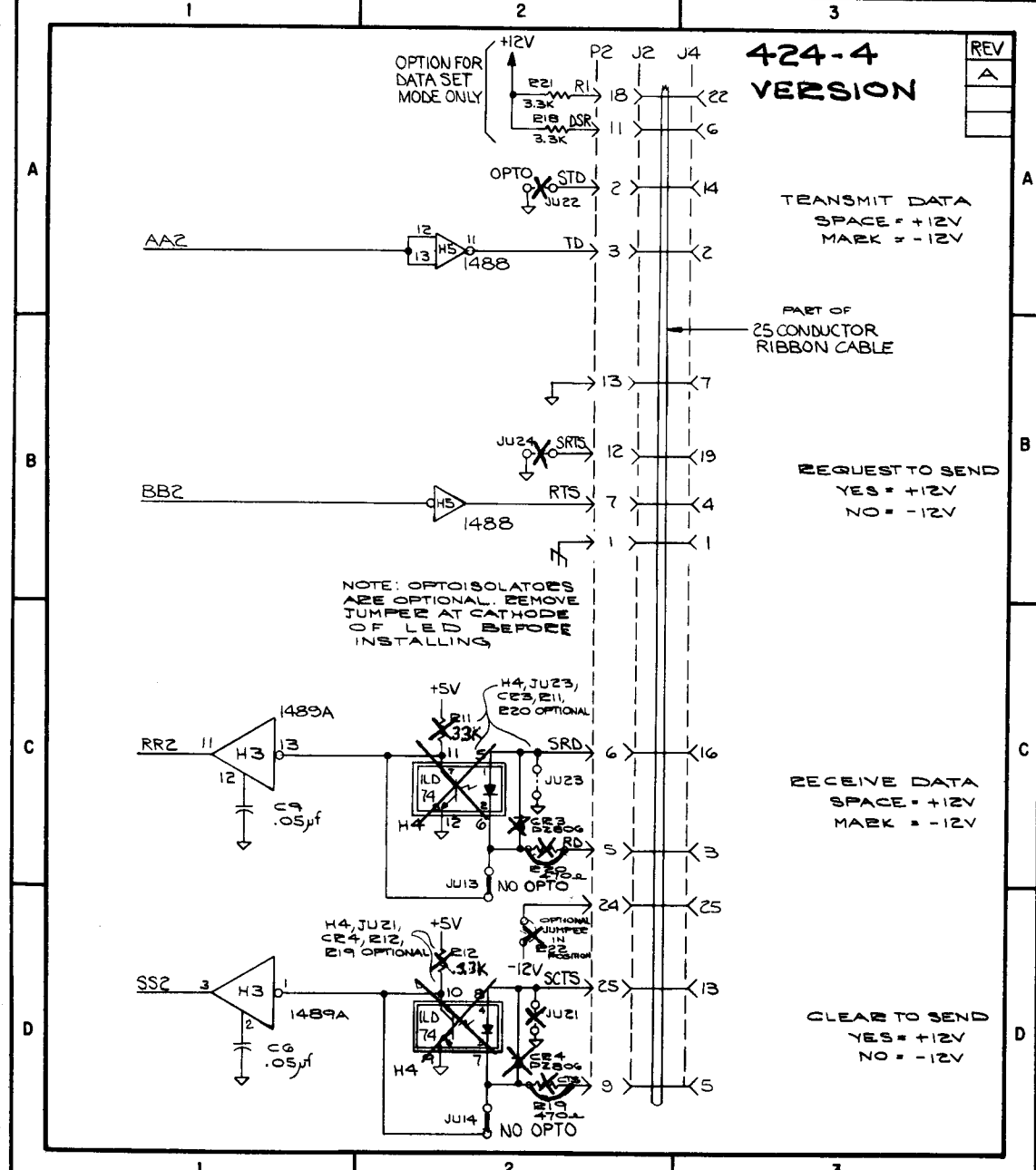


NOTE: PROPRIETARY INFORMATION. NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.


DRAWN BY *[Signature]* CHECKED BY *[Signature]* DRAWING NO. DS 424 PAGE 7

DATE 3-13-76 DATE 6-17-76

424

  


REV. A

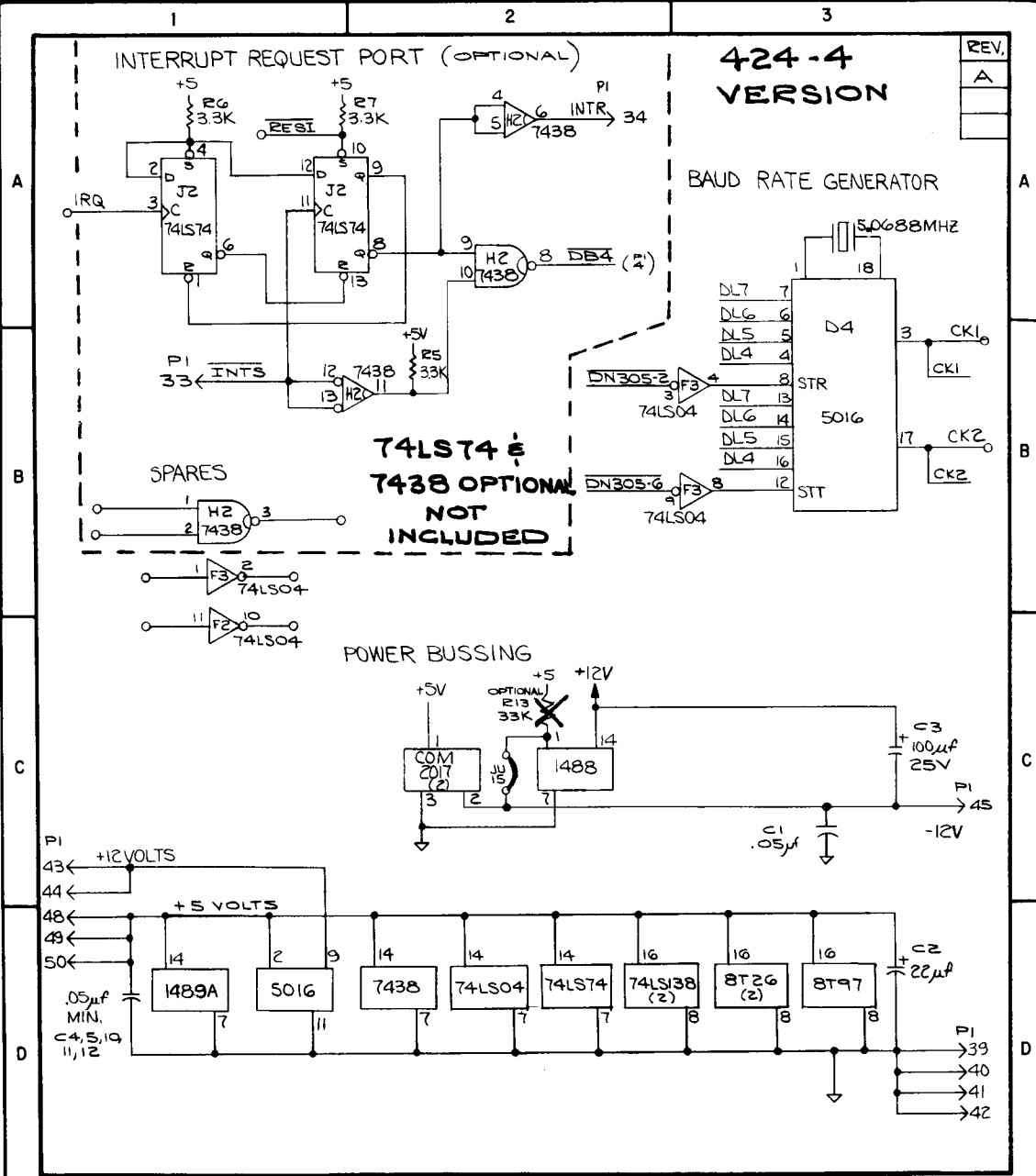

NOTE: PROPRIETARY INFORMATION NOT TO BE DISCLOSED WITHOUT EXPRESS WRITTEN PERMISSION.
DRAWN BY [Signature] CHECKED BY [Signature] DRAWING NO. DS 424 PAGE 8
DATE 3-13-76 DATE

EF4A

 

From the point of view of the microcomputer, the peripheral devices connected to the 424 board look like input/output ports, and can be addressed with ordinary memory read and write instructions. In other words, the 424 I/O ports are *memory-mapped*: each port is addressed as a designated *page* in the microcomputer's memory. (See Sec. 3 below for software considerations.)

From the point of view of the system, the microcomputer is a *data terminal* which transmits and receives data serially. *Start and stop bits* begin and end each character, which may be from five to eight bits long. The number of start and stop bits per character, as well as the number of bits per second (*baud rate*), are programmed by the microcomputer.

2.2 Serial Data Conventions Many computer peripheral devices now used in conjunction with microcomputers were originally designed for use in communications systems. For example, a TeletypeR Model 33 ASR (asynchronous send/receive) teletype-writer can be connected to a standard *modem* in order to transmit written messages over a telephone line. A standard has been developed by the Electronic Industries Association (EIA) on "Interface Between Data Terminal Equipment and Data Communication Equipment Employing Serial Binary Data Interchange," number *RS-232-C*. This standard is widely used not only in the communications field, but by computer peripheral manufacturers, so that equipment can readily be interconnected. Devices meeting this specification are commonly described as having an "EIA interface."


The Model 424 Serial Communications board is capable of meeting the principal requirements of *RS-232-C*, for connection to devices with an EIA interface. The 424 can also be modified for other serial data applications.

RS-232-C sets up specifications in three areas: serial data transfer format; connecting terminals; and electrical signals.

2.3 Serial Data Transfer Format In the example above--a teleprinter connected to a modem, for transmission of data through a telephone line--the teleprinter is considered a *data terminal*, and the modem, a *data set*. In a modular micro system, the microcomputer which includes the 424 board is the *data terminal*.

In accordance with the terminology of *RS-232-C*, the peripheral device connected to the 424 board would normally be a *data set*. When the serial data interchange is set up according to the full EIA standard, the data terminal and data set are connected with a 25-conductor cable. Approximately 20 of these signals are defined by the standard; most are specialized control signals. Figure 2.3.1 (following page) shows these signals, with a brief description of each. The far left-hand column (*EIA Conn.*) shows the conductor number assigned by the EIA standard.

424

 

REV. A

| EIA Conn. | | Ribbon Cable | | Signal Description | Signal Function | | | | | | (See Sec. 6) | | |
|-------------|-------------|--------------|-------------|--|-----------------|-------------|---------------|-------------|---------------|-------------|---------------|------------------|---------|
| J3 | J4 | P2/J2 | | | Grnd | Data | | Control | | Timing | | Return Path for: | |
| Terminal #1 | Terminal #2 | Terminal #1 | Terminal #2 | | | To Terminal | From Terminal | To Terminal | From Terminal | To Terminal | From Terminal | Signal | EIA Pin |
| 1 | 26 | 1 | | Protective Ground | X | | | | | | | | |
| 7 | 38 | 13 | | Signal Ground/Common Return | X | | | | | | | | |
| 2 | 28 | 3 | | Transmitted Data (TD) | | X | | | | | | | |
| 3 | 30 | 5 | | Received Data (RD) | | X | | | | | | | |
| 4 | 32 | 7 | | Request to Send (RTS) | | | | X | | | | | |
| 5 | 34 | 9 | | Clear to Send (CTS) | | | X | X | | | | | |
| 6 | 36 | 11 | | Data Set Ready (DSR) | | | X | X | | | | | |
| 20 | 39 | 14 | | Data Terminal Ready (DTR) | | | X | X | | | | | |
| 22 | 43 | 18 | | Ring Indicator (RI) | | | X | X | | | | | |
| 8 | 40 | 15 | | Received Line Signal Detector (RLSD) | | | X | X | | | | | |
| 21 | 41 | 16 | | Signal Quality Detector (SQD) | | | X | X | | | TSET | 15 | |
| 23 | 45 | 20 | | Data Signal Rate Selector (DSRD), Term. | | | | X | | | | | |
| 23 | 45 | 20 | | Data Signal Rate Selector (DSRD), Set | | | | X | | | | | |
| 24 | 47 | 22 | | Transm. Signal Element Timing (TSET), Term. | | | | | | X | | | |
| 15 | 29 | 4 | | Transm. Signal Element Timing (TSET), Set | | | | | X | | | | |
| 17 | 33 | 8 | | Receiver Signal Element Timing (RSET) | | | | | X | | TSET | 24 | |
| 14 | 27 | 2 | | Secondary Transmitted Data (STD) | | X | | | | | TD | 2 | |
| 16 | 31 | 6 | | Secondary Received Data (SRD) | X | | | | | | RD | 3 | |
| 19 | 37 | 12 | | Secondary Request to Send (SRTS) | | | | X | | | RTS | 4 | |
| 13 | 50 | 25 | | Secondary Clear to Send (SCTS) | | | X | X | | | CTS | 5 | |
| 12 | 48 | 23 | | Secondary Rec'd Line Signal Detector (SRLSD) | | | X | X | | | RLSD | 8 | |
| 9 | 42 | 17 | | (Reserved for testing) | | | | | | | | | |
| 10 | 44 | 19 | | (Reserved for testing) | | | | | | | | | |
| 11 | 46 | 21 | | (Unassigned by RS-232-C) | | | | | | | | | |
| 18 | 35 | 10 | | (Unassigned by RS-232-C) | | | | | | | | | |
| 25 | 49 | 24 | | Teletype 20 MA Current Return | | | | | | | | | Sec. 4 |

FIGURE 2.3.1-424 SERIAL DATA CONNECTIONS

REV. A

The first two connections shown in Fig. 2.3.1 are ground conductors; *Protective Ground* is normally connected to the equipment frame or chassis.

Transmitted Data (TD) is the conductor for serial data originated by the data terminal. It is received by the data set.

Received Data (RD) is the conductor for serial data received by the data terminal. It is transmitted by the data set.

It is possible to achieve a complete serial data interchange with only one shielded pair of wires--made up of one pair for *TD* and signal ground; another pair for *RD* and signal ground; and the shield connected to *Protective Ground*. This hookup would provide *full duplex* operation: the data terminal could transmit characters to the data set via the *TD* conductor, at the same time that it is receiving data from the data set via the *RD* conductor.

In many cases additional signals are necessary in order to properly synchronize data terminal and data set. For example, the *data set* may need to be able to signal the data terminal that it cannot receive data temporarily, since it is busy with some other task (e.g., dialing a new telephone number). Or, the data set may need to be able to originate a message, rather than leaving the data interchange under the sole control of the data terminal, as in the simplest system. The first four control signals shown in Fig. 2.3.1 (starting with *Request to Send*) are perhaps the most basic.

Data Set Ready (DSR) is a signal indicating that the data set is properly connected and ready to communicate.

Data Terminal Ready (DTR) is a signal indicating that the data terminal is ready to transmit or receive data.



Request to Send (RTS) is a signal from the data terminal indicating that it wishes to send information to the data set.

Clear to Send (CTS) is a signal from the data set indicating that it is ready to receive data, on the *TD* line.

Technically, under RS-232-C, the data terminal cannot transmit (via the *TD* line) unless all four of the above signals are active. In many of the applications contemplated by RS-232-C, moreover, even further control signals are required. For example, when a call is received by the data set, typically it sends the terminal a signal on the *Ring Indicator* line.

The EIA standard also provides for a *secondary data channel*, as shown in Fig. 2.3.1 (starting with *Secondary Transmitted Data*). This second data channel is typically used for remote terminal equipment; for back-up of the primary data channel to ensure reliability; or for transmission of data between data terminal and data set in a direction backwards to that of the primary channel.

424

  

REV. A

The precise method of control interface is specified not only by RS-232-C but by other communications standards. A full discussion is far beyond the scope of this data sheet. In practice, however, few microcomputer applications make use of all of the control signals specified by RS-232-C. In fact, the precise method of "hand-shaking" varies widely among terminals and peripherals which nominally make use of an "EIA interface." The Model 424 Serial Communications Board includes sufficient optional features and connections to allow most practical serial interface problems to be solved. The user will usually need to refer to the specifications of his equipment to develop the exact interface required.

2.4 EIA Connectors The 424 has provisions for two independent serial data channels, called *Terminal #1* and *Terminal #2*. Each is independently controlled by the microcomputer. The 25 EIA conductors for each terminal (50 conductors total) are brought out at the rear of the board at P2, a fifty-pin header. (In the most simple 424 application, hookup wires may be soldered directly into the 424 board at P2, replacing the header.)

The header, P2, is meant to receive a 50-pin transition connector, J2, into which have been crimped two separate 25-wire ribbon cables of the 3M Delta^R type. The other end of each of these two cables is crimped to a 25-pin female Delta-style EIA connector, which is in turn mounted to the wall of the microcomputer enclosure. These two EIA connectors are labeled J3 (for terminal #1) and J4 (for terminal #2).


Conductor assignments for P2/J2, J3, and J4 are shown in Figure 2.3.1 above.

The 424-4, -5, and -6 versions are provided with the fifty-pin header, P2. The 25-wire Delta ribbon cables must be added to the 424 assembly, as are the EIA connectors. The most convenient female EIA socket, for mounting on the microcomputer enclosure (J3 and J4), is the 3M Delta^R connector, which can be crimped onto the 25-conductor 3M Delta^R cable. An alternate socket, requiring soldering, is the Amphenol DB-25S.

Among suitable male EIA connectors, for plugging into J3 and J4, is Amphenol type DB-25P, plus type DB-51226-1 plastic hood for securing the connector onto an external 25-conductor round cable.

 2.5 EIA Electrical Signals Data and control signals in an EIA serial data system are normally generated from a ± 12 V supply. A circuit is considered *ON (Spacing)* when the signal voltage is greater than +3 volts, and *OFF (Marking)* when the voltage is more negative than -3 volts. Voltages in the transition region, between +3 and -3 volts, are undefined. DC line resistance is 3000 to 7000 ohms, and shunt capacitance is 2500 picofarads maximum. The signal must pass through the transition region in less than 1 millisecond, but the maximum rate of voltage change is 30 volts per microsecond.

EIA interface chips, the 1488 and 1489 (with associated shunt capacitors), are used on the 424 board to meet EIA electrical requirements.



REV. A

2.6 Serial Data Codes The code actually used by the computer and associated equipment in the serial data interchange is up to the user. Typical choices include ASCII, Baudot, EBCDIC, Correspondence, etc. The 424 board can be programmed for character lengths of five, six, seven, or eight bits. The number of start and stop bits, as well as the speed and parity bit convention, are also programmable. The choice is usually dictated by the equipment to be interfaced and the microcomputer software available. (For software details, see Sec. 3 below.)


2.7 Connecting One Data Terminal to Another Data Terminal A connection problem arises when two pieces of equipment are to be connected together which are both *data terminals*, neither being hooked up as a *data set*. This would be the case, for example, when connecting a microcomputer using a 424 board, to a CRT display set up as an EIA data terminal. If the usual EIA interconnecting cable were used, the *Transmitted Data (TD)* lead of each terminal would be connected together, and both would try to talk on the same lead. To solve the problem, the cable may be rewired such that the *Transmitted Data* lead from one terminal connects to the *Receive Data (RD)* lead of the other. This involves swapping the wires connected to pins 2 and 3 of the EIA connector, on *one* end of the cable.

This is only a partial solution, however, if other RS-232-C control signals are being used. For example, *Data Terminal Ready* for one terminal cannot usefully be connected to the *Data Terminal Ready* of the other. If however the *Data Terminal Ready* and *Data Set Ready* leads were interchanged on *one* end of the cable assembly, a useful interface would be achieved. Each terminal now effectively sees the other as a data set.

Leads to be exchanged, in order to set up an effective interface between two terminals, are shown in Fig. 2.7.1.

| SIGNAL ORIGINATED BY TERMINAL | CORRESPONDING SIGNAL RECEIVED BY TERMINAL |
|---|---|
| DATA TERMINAL READY (Pin 20) | DATA SET READY (Pin 6) |
| TRANSMITTED DATA (Pin 2) SECONDARY TRANSMITTED DATA (Pin 14) | RECEIVE DATA (Pin 3) SECONDARY RECEIVE DATA (Pin 16) |
| REQUEST TO SEND (Pin 4) SECONDARY REQUEST TO SEND (Pin 19) | CLEAR TO SEND (Pin 5) SECONDARY CLEAR TO SEND (Pin 13) |
| TSET (Term.) (Pin 24) REC. SIG. ELE. TIM. (Pin 17) | TSET (Set) (Pin 15) SIGNAL QUALITY DETECTOR (Pin 21) |

Fig. 2.7.1--SIGNALS TO BE EXCHANGED FOR CONNECTING ONE DATA TERMINAL TO ANOTHER DATA TERMINAL

 

REV. A

A recommended connection scheme to avoid confusion is as follows:

Data terminals use 25-pin EIA *female sockets* at their chassis enclosures.

Data sets (e.g., modems) use 25-pin EIA *male plugs* at their chassis enclosures.

To connect a *data terminal to a data set*, use a 25-conductor *extension cord*, consisting of a male EIA connector on one end, and a female at the other. (There are no wire reversals within the extension cord.)

To connect a *data terminal to a data terminal*, use a 25-conductor *adapter cord*, consisting of a male EIA connector at each end, with selected pairs of wires swapped at one end, as indicated in Fig. 2.7.1.

2.8 Adapting for Optical Isolation and Current Loop The EIA connection system needs modification to adapt the serial interface for a 20 MA current loop, for a Teletype^R machine. (See Sec. 4 below.)

To permit optoisolation of incoming signals, a return current path must be provided for each signal that is isolated. Typically, lesser-used conductors, such as the lead for *SECONDARY TRANSMITTED DATA*, are used. Referring to Fig. 2.7.1 above, the connector numbers for the *italicized* signals are typically used as return paths for the corresponding (Roman type) signals. (For details, see Sec. 6 below.)


SEC. 3 SOFTWARE FOR THE 424

The 424 board is controlled by program instructions executed by the microprocessor. These instructions perform two functions with respect to the 424: setting up the serial data format, and interchanging data. This section presents typical software instructions for these purposes. First, however, is a brief description of the input/output instructions used by the microcomputer in interfacing to the Serial Communications board.

 3.1 Memory-Mapped I/O Instructions The 424 board has been set up to make use of *memory-mapped I/O* instructions. In other words, microcomputer instructions which *write into memory* serve as *output* instructions, and *memory read* instructions are *input* instructions.

The 8080 microprocessor's regular input and output instructions, IN and OUT, cannot readily be used with the 424.

The 424 board has been assigned to three pages in memory: pages 305, 345, and 347 (in octal; C5, E5, and E7 in hex). As usual in the *modular micro* series, a *page* refers to a block of 256 eight-bit memory words which have the same high-order memory address. (In other words,



REV. A

DH7 through DH0 are the same.) When the 424 board is connected to the microcomputer, a memory write or memory read instruction referring to one of these page addresses will actually exchange information with the 424, rather than writing into RAM or reading from RAM or ROM.

Page 345 is used for *output data* from the microcomputer to *Terminal #1* on the 424 board. A memory write instruction addressed to page 345 will load up the UART on the 424 board in preparation for transmitting a serial character through Terminal #1. (The 424 hardware does not distinguish among the 256 memory words within page 345. In other words, the low-order memory address does not matter.)


Page 347 is used for *output data* from the microcomputer to Terminal #2 on the 424 board. It is similar in function to Page 345.

Page 305 is used for two purposes: for receiving *input data* from both Terminal #1 and Terminal #2, and for *outputting control words* which set up the baud rate; program the serial data format; and synchronize the microcomputer with the serial data hardware.

In order to permit a single memory page address to encompass these multiple functions, many of the individual memory locations within page 305 are assigned specific functions. In other words, the low-order memory address bits, DL7 through DL0, are effectively control characters which determine the purpose of the instruction which references this page. In general, the five address bits DL7 through DL3 are *set-up bits*, used to set up each terminal's baud rate, parity bit status, start/stop bit format, etc. The three low-order address bits, DL2, DL1, and DL0, are *function select bits*, and determine the purpose of the instruction which references page 305.

3.2 Function Selection Figure 3.2.1 illustrates how functions are selected by memory-mapped I/O instructions which address page 305 in memory. In general, the instruction reads from (or writes into) memory location 305 NNS, where S is an octal digit (0 through 7) which selects the function.

424

 

REV. A

| DL2 | DL1 | DL0 | EFFECTIVE MEMORY ADDRESS | FUNCTION PERFORMED | MEANING OF CONTROL (NN) BITS |
|-----|-----|-----|--------------------------|--|------------------------------------|
| 1 | 1 | 1 | 305 NN7 | Load Serial data format for Terminal #2. | See Figure 3.4.1 for format codes. |
| 1 | 1 | 0 | 305 NN6 | Reset UART #2. Load baud rate, Term. #2. | See Fig. 3.3.1 for baud rates. |
| 1 | 0 | 1 | 305 005 | Read a character from Terminal #2. | (None) See Sec. 3.6. |
| 1 | 0 | 0 | 305 004 | Read UART status flags, Terminal #2. | (None) See Sec. 3.5. |
| 0 | 1 | 1 | 305 NN3 | Load serial data format for Terminal #1. | See Figure 3.4.1 for format codes. |
| 0 | 1 | 0 | 305 NN2 | Reset UART #1. Load baud rate, Term. #1. | See Fig. 3.3.1 for baud rates. |
| 0 | 0 | 1 | 305 001 | Read a character from Terminal #1. | (None) See Sec. 3.6. |
| 0 | 0 | 0 | 305 000 | Read UART status flags, Terminal #1. | (None) See Sec. 3.5. |


FIGURE 3.2.1-SELECTING FUNCTIONS WITH MEMORY-MAPPED I/O INSTRUCTIONS

The *NN* designation in the memory address column in Fig. 3.2.1 is actually a pair of octal digits (00 through 37). The actual value of these digits is used in programming baud rate or serial data format, as explained below.

3.3 Selecting Baud Rate and Resetting UARTs When a memory-mapped I/O instruction is executed which references location 305 NN6 (for Terminal #2) or 305 NN2 (for Terminal #1), two functions are performed: first, the IC UART, which carries out serial to parallel data conversions, is initialized. Second, the baud rate (serial data transmission speed) is set up. The baud rate is programmed through four program bits, DL7 through DL4, and can range between 50 baud and 19,200 baud. See Figure 3.3.1.

In Figure 3.3.1, the 8080 instruction *LDA* is shown. This memory read instruction is normally used to load the 8080 A register from the contents of memory at the designated location. In this case, the instruction is used simply to initialize the UART and set up the baud rate, as shown. Any data which may end up in the 8080 A register at the end of the instruction should be disregarded.

Figure 3.3.1 also shows the period, in microseconds, which corresponds to each selected baud rate. The 424 can be used as a programmable interval timer which interrupts the microcomputer repetitively at a set interval. For details see Sec. 9 below.

 

REV. A

| TERMINAL #1 | TERMINAL #2 | BAUD RATE, BITS PER SEC. | INTERRUPT INTERVAL, MICROSECONDS |
|-------------|-------------|--------------------------|----------------------------------|
| LDA 305002 | LDA 305006 | 50 | 1250. |
| LDA 305022 | LDA 305026 | 75 | 833.3 |
| LDA 305042 | LDA 305046 | 110 | 568.2 |
| LDA 305062 | LDA 305066 | 134.5* | 464.7 |
| LDA 305102 | LDA 305106 | 150 | 416.7 |
| LDA 305122 | LDA 305126 | 300 | 208.3 |
| LDA 305142 | LDA 305146 | 600 | 104.2 |
| LDA 305162 | LDA 305166 | 1200 | 52.08 |
| LDA 305202 | LDA 305206 | 1800 | 34.72 |
| LDA 305222 | LDA 305226 | 2000* | 31.25 |
| LDA 305242 | LDA 305246 | 2400 | 26.04 |
| LDA 305262 | LDA 305266 | 3600 | 17.36 |
| LDA 305302 | LDA 305306 | 4800 | 13.02 |
| LDA 305322 | LDA 305326 | 7200 | 8.681 |
| LDA 305342 | LDA 305346 | 9600 | 6.510 |
| LDA 305362 | LDA 305366 | 19200* | 3.157 |


FIG. 3.3.1-8080 INSTRUCTIONS FOR LOADING BAUD RATE AND INTERRUPT INTERVALS

* NOTE: When baud rates of 134½, 2000, or 19,200 are selected, a slight error exists in the output frequency: +0.016% (134.5187 Hz); +0.253% (2005.0625 Hz); +3.125% (19,800 Hz), respectively.

 3.4 Selecting Serial Data Format A memory-mapped I/O instruction which references memory location 305 NN7 (for Terminal #2) or 305 NN3 (for Terminal #1) selects the serial data format necessary to interface with external data equipment. The *NN* above ranges from 00 to 37. See Figure 3.4.1.

Executing any memory read or write instruction which references a memory location shown in Fig. 3.4.1 will perform the designated function. The presence of the correct memory address, on the microcomputer address lines, is sufficient to select the serial data format.


The microcomputer *data* bus is inactive if the instruction is a memory write instruction; and though data may be transferred from the 424 into a CPU register, in the case of a memory read instruction, this data should be disregarded.



REV. A

| MEMORY ADDRESS | | CONTROL BIT | | | | | SERIAL DATA FORMAT | | |
|----------------|---------|-------------|-----|-----|-----|-----|--------------------|-----------|--------|
| TERM. 2 | TERM. 1 | DL7 | DL6 | DL5 | DL4 | DL3 | BITS/CHAR. | STOP BITS | PARITY |
| 305 377 | 305 373 | 1 | 1 | 1 | 1 | 1 | 8 | 2 | NONE |
| 305 367 | 305 363 | 1 | 1 | 1 | 1 | 0 | 8 | 2 | EVEN |
| 305 357 | 305 353 | 1 | 1 | 1 | 0 | 1 | 8 | 1 | NONE |
| 305 347 | 305 343 | 1 | 1 | 1 | 0 | 0 | 8 | 1 | EVEN |
| 305 337 | 305 333 | 1 | 1 | 0 | 1 | 1 | 6 | 2 | NONE |
| 305 327 | 305 323 | 1 | 1 | 0 | 1 | 0 | 6 | 2 | EVEN |
| 305 317 | 305 313 | 1 | 1 | 0 | 0 | 1 | 6 | 1 | NONE |
| 305 307 | 305 303 | 1 | 1 | 0 | 0 | 0 | 6 | 1 | EVEN |
| 305 277 | 305 273 | 1 | 0 | 1 | 1 | 1 | 7 | 2 | NONE |
| 305 267 | 305 263 | 1 | 0 | 1 | 1 | 0 | 7 | 2 | EVEN |
| 305 257 | 305 253 | 1 | 0 | 1 | 0 | 1 | 7 | 1 | NONE |
| 305 247 | 305 243 | 1 | 0 | 1 | 0 | 0 | 7 | 1 | EVEN |
| 305 237 | 305 233 | 1 | 0 | 0 | 1 | 1 | 5 | 1.5 | NONE |
| 305 227 | 305 223 | 1 | 0 | 0 | 1 | 0 | 5 | 1.5 | EVEN |
| 305 217 | 305 213 | 1 | 0 | 0 | 0 | 1 | 5 | 1 | NONE |
| 305 207 | 305 203 | 1 | 0 | 0 | 0 | 0 | 5 | 1 | EVEN |
| 305 177 | 305 173 | 0 | 1 | 1 | 1 | 1 | 8 | 2 | NONE |
| 305 167 | 305 163 | 0 | 1 | 1 | 1 | 0 | 8 | 2 | ODD |
| 305 157 | 305 153 | 0 | 1 | 1 | 0 | 1 | 8 | 1 | NONE |
| 305 147 | 305 143 | 0 | 1 | 1 | 0 | 0 | 8 | 1 | ODD |
| 305 137 | 305 133 | 0 | 1 | 0 | 1 | 1 | 6 | 2 | NONE |
| 305 127 | 305 123 | 0 | 1 | 0 | 1 | 0 | 6 | 2 | ODD |
| 305 117 | 305 113 | 0 | 1 | 0 | 0 | 1 | 6 | 1 | NONE |
| 305 107 | 305 103 | 0 | 1 | 0 | 0 | 0 | 6 | 1 | ODD |
| 305 077 | 305 073 | 0 | 0 | 1 | 1 | 1 | 7 | 2 | NONE |
| 305 067 | 305 063 | 0 | 0 | 1 | 1 | 0 | 7 | 2 | ODD |
| 305 057 | 305 053 | 0 | 0 | 1 | 0 | 1 | 7 | 1 | NONE |
| 305 047 | 305 043 | 0 | 0 | 1 | 0 | 0 | 7 | 1 | ODD |
| 305 037 | 305 033 | 0 | 0 | 0 | 1 | 1 | 5 | 1.5 | NONE |
| 305 027 | 305 023 | 0 | 0 | 0 | 1 | 0 | 5 | 1.5 | ODD |
| 305 017 | 305 013 | 0 | 0 | 0 | 0 | 1 | 5 | 1 | NONE |
| 305 007 | 305 003 | 0 | 0 | 0 | 0 | 0 | 5 | 1 | ODD |

FIGURE 3.4.1 -- MEMORY ADDRESSES FOR SELECTING SERIAL DATA FORMAT

 

REV. A

3.5 Synchronization In order to synchronize the microcomputer with the serial data hardware on the 424 board, selected memory read instructions can be executed which place *status flags* on the microcomputer's parallel data bus. Any memory read instruction referencing memory location 305 004 will input Terminal #2 status flags into the CPU. Reading from location 305 000 inputs status flags for Terminal #1.

The status flags appear on the microcomputer's data bus, as shown in Fig. 3.5.1.

| DATA BUS LINE | STATUS FLAG | COMMENTS |
|---------------|--------------------------|--|
| DB7 | DATA READY | 1 = ENTIRE CHARACTER RECEIVED AND IS READY TO BE READ BY CPU. |
| DB6 | PARITY ERROR | 1 = THE PARITY OF RECEIVED CHAR. DOES NOT AGREE WITH SELECTED PARITY |
| DB5 | TRANSMITTER BUFFER EMPTY | 1 = TRANSMITTER READY TO BE LOADED WITH A NEW CHARACTER TO BE SENT |
| DB4 | FRAME ERROR | 1 = CHARACTER RECEIVED WHICH LACKED STOP BIT IN PROPER POSITION |
| DB3 | OVER-RUN ERROR | 1 = NEW CHARACTER RECEIVED BUT OLD CHAR. NOT YET INPUTTED TO CPU |
| DB0 | (SERIAL INPUT DATA) | SERIAL INPUT BIT. MAY BE USED FOR TEST PURPOSES BY THE COMPUTER. |


FIGURE 3.5.1--STATUS FLAGS FOR SYNCHRONIZING SERIAL DATA TO CPU

Note the omission of DB2 and DB1 in Fig. 3.5.1; these data bus lines are not used for this purpose. DB0 carries the serial input data itself, before it has been converted to parallel format. While not a status flag, this bit can be checked by the CPU for test purposes.

3.6 Sending and Receiving Data When all of the initialization and hand-shaking discussed above has taken place through appropriate software instructions, the microcomputer can input and output serial data via the 424 board. Figure 3.6.1 includes typical software instructions for the 8080.

| FUNCTION | SOURCE OF DATA | DESTINATION | 8080 INSTRUCTION | |
|---------------------|----------------|-------------|------------------|-------------|
| | | | TERM. #2 | TERM.#1 |
| SEND A CHARACTER | CPU A REG. | SERIAL LINE | STA 347 000 | STA 345 000 |
| RECEIVE A CHARACTER | SERIAL LINE | CPU A REG. | LDA 305 005 | LDA 305 001 |

FIGURE 3.6.1--8080 INSTRUCTIONS FOR SENDING AND RECEIVING SERIAL DATA

 

REV. A

The programmer will recognize that there are a number of instructions for accomplishing the same results as those shown in the chart. For example, to send a character via Terminal #2, the following two 8080 instructions could be used: MVI B, 347. .STAX B. A character previously stored in the A register will be transferred to the 424 board.

If the data format selected involves a serial data word of fewer than eight bits, the corresponding data word on the microcomputer data bus is right-justified. That is, the low-order serial data bit always corresponds to DBO, the low-order line on the microcomputer's data bus. In *sending* a five-bit serial data word, for example, the 424 will disregard the three high-order bits on the microcomputer's data bus. Similarly, in *receiving* data from the 424, when five-bit serial data is being handled, the microcomputer software should disregard the three high-ordered bits read in on the computer's parallel data bus. Any unused data lines may take on either logical state.




The above text serves as a basic introduction to the 424 board, and to the question of interfacing a microcomputer to a serial data system.

A complete data sheet is provided to purchasers of the 424 Serial Communications Board. In addition to the preceding, it provides the following sections:

- SEC. 4 GENERAL CIRCUIT DESCRIPTION
- SEC. 5 INTERFACING TO THE PR11000 PRINTER: THE 424-5
- SEC. 6 ADDING OPTICAL ISOLATION: THE 424-6
- SEC. 7 ONE-BIT SERIAL OUTPUT: THE 424-2
- SEC. 8 ADAPTATION FOR THE 8008 MICROPROCESSOR (MIKE 2)
- SEC. 9 USING THE 424 AS AN INTERRUPT TIMER
- SEC. 10 CIRCUIT CONNECTIONS FOR 424 OPTIONS

APPENDICES

 - APP. A MODEL 33 TELETYPE MODIFICATIONS FOR COMPUTER CONTROL




REV. A

The 477 *DEBUG BOARD* is a special-purpose module in the *modular micro* series from Martin Research. Designed for use in development, trouble-shooting, and educational applications, the 477 supports the following:

A *32-Channel Scope Display* allows important microcomputer data and timing signals to be displayed on an external single-trace, triggered sweep oscilloscope. Timing diagrams of data, address, and control lines appear directly on the face of the scope.

 A photograph of an oscilloscope tracing generated by the Model 477 Debug Board appears at the right. Connected to a Model 471 CPU board, based on the 8080 microprocessor, the 32 channels include eight control and eight data lines (top of picture) and the sixteen address lines (bottom of photo).



A *Delayed Software Interrupt Port* provides a software-generated interrupt request signal for use in software-controlled single-step debugging of programs.


Also included: sockets for optional pull-up resistors on data, address, and control lines for use in multi-processor, DMA, and interrupt polling schemes. Breadboard space for seven 16-pin DIP ICs and one 14 pin DIP.

The Model 477 Debug Board is intended for use with the *MIKE 3* computer, based on the 8080 microprocessor, and with the *MIKE 8*, based on the Z 80.

The 477 plugs into the system's 50-conductor ribbon cable bus, like other boards in the modular micro series.

Order information: catalog AT477 includes an assembled and tested 477 board (less optional pullup resistor packs). The user must add an additional 50-pin transition connector, part number 1001, to the system's ribbon cable if an open position is not already available. Prices: AT477, \$89.00; 1001, \$6.00. (U.S. prices, subject to change without notice; standard order terms apply.) The 477 is also available as part of the *MIKE 3 DEBUG SYSTEM*, model AT814.

477

 

WHAT'S IN THE SILVER BOX?

We don't know!

...until you tell us.


The *silver box* is our name for this versatile industrial control package. What's inside depends on your application. Based on a modular micro CPU board, the *silver box* may include a specialized keyboard and display panel; one or more memory boards, as required; software tailored to the job; and circuitry for interfacing with your system.

The *silver box* computer is linked with electrical devices which control a process, or sense a condition, or display information about the system. Examples: switches and relays; motors—AC, DC, and stepping; pressure transducers; thermometers; remote terminals; high-speed printers—the variety is endless.

Some current *silver box* applications suggest its versatility: a time accounting machine; an industrial batching controller; a vehicle dispatching terminal; and a multi-home security system.

Why Microprocessors in Industrial Control?

- **Versatility**—Once your basic product has been micro-computerized, adding new functions entails plugging in another circuit board or a new programmable memory element (with modified instructions)—not a whole new design.
- **Low cost**—Microprocessor-based control systems are not only much more powerful than older versions based on relays, motorized timers, or previous generations of electronic logic (such as TTL)—they are actually *more economical* in more and more applications today. Almost uniquely in today's inflationary economy, microcomputers are growing less and less expensive per control function performed.

 

Available as
BLACK BOX (in
NEMA enclosure)
for adverse environments

Selected special features, for use with the *silver box*:

- **BATTERY-BACKED POWER SUPPLY**—A switching-regulator supply operating from 110/220 VAC, 50/60 Hz; includes a new sealed lead-acid battery pack, continuously charged when power is on. Allows system operation for 30 minutes or more after power loss; data retention for hours.
- **SERIAL COMMUNICATIONS BOARD**—The Model 424-4 converts eight-bit parallel microprocessor data format to serial data, allowing the computer to communicate with external devices over only one or several wires. With two UARTS, programmable baud rate, EIA or TTY voltage levels. Optoisolation is an optional extra. The 424-2 contains only the circuitry necessary to interface with an ordinary Teletype (w/o UARTS—but may be upgraded to a 424-4 merely by adding components).
- **CONTROL INTERFACE BOARD**—Interfaces between the microcomputer and industrial control circuitry. Drives standard solid-state relays; receives from switches, tachometers, etc., using high-impedance, noise-immune circuitry.

Putting Microprocessors into your Process...

A manufacturer using industrial control systems who is *not* looking at what microprocessors can do for him—will soon look like the manufacturer of a mechanical adding machine. Yet, only the largest companies can support a full-scale microcomputer development program—and even an all-out effort may take a year or more to put debugged circuit boards into production.

If this sounds like the problem your company faces, look into the *silver box* from Martin Research!

- Modular engineering ideal for expandable control systems.
- Prompt quotes on specialized system requirements.
- Fast turnaround on custom designs.
- Copies of PC board artwork, for your in-house production, available at reasonable cost.
- Full range of engineering services: consulting; production of key circuit boards; production of finished product.

OEMS... **THE SILVER BOX CAN CONTROL YOUR PROCESS!** Tell us your application, and we'll quote costs of a custom-engineered computer control system.

modular micros

martin research

The 471 CPU is a complete 8-bit central processor on a single printed circuit board. Based on the 8080A microprocessor, the 471 generates the essential control signals for a complete MIKE 3 microcomputer system.

The 471 supports the full capabilities of the 8080A microprocessor, including high speed--2.0 us instruction cycle--and memory addressing of up to 64K (65,536) bytes. The instruction set supports logical (Boolean), arithmetic, and bit-manipulating operations; the CPU can convert data to decimal (BCD) notation with a single instruction. Logical operations set flags which may be tested by conditional branch instructions to control program flow. For added convenience in memory addressing, six general-purpose internal registers may be addressed not only singly, but in pairs. There are also double-precision (16-bit) addition and increment/decrement instructions.

The 8080 stack pointer addresses external RAM memory, allowing for practically unlimited nesting of program subroutines. Through single-byte PUSH and POP instructions, registers, flags, and the program counter can be saved in the external stack, and restored later--greatly facilitating interrupt handling. The 471 includes circuitry for three interrupt levels, expandable to an eight-level prioritized interrupt system by adding an accessory circuit board. A digital timer restarts the computer automatically should the CPU fail to recognize interrupt requests for a set period.

Power bus drivers are included for driving expanded systems. However, control by the 8080A of the data and address busses may be suspended by a HOLD request, thereby allowing for direct memory access (DMA) or multi-processor operation.

The 471 includes a reliable crystal-controlled clock. Specialized control signals are developed on the CPU board and are present on the system bus to simplify expansion, by minimizing the extra interface circuitry needed on each new memory or input/output board. These signals not only include those required for 8080-type I/O instructions, but also support the 6800/6502 and 8008 I/O addressing modes. The 50-pin bus structure is compatible with these and other eight-bit processors, allowing the 471 to be used interchangeably with other CPU boards in interfacing to memory and accessory modules in the modular micro series.


While supporting all the potential of the powerful 8080A microprocessor, the Model 471 CPU board is a good example of the flexibility of the modular micro approach. Optimal for small systems--yet fully expandable.

APPLICATIONS

Industrial The flexible modular micro approach makes the Model 471 ideal for prototyping computers based on the 8080A microprocessor. The 471 is also attractive to the OEM for pilot runs and low-volume production, and can easily be adapted for specialized purposes. Ideal for a whole new generation of intelligent machines, including industrial controllers, computer peripherals, terminals, business machines, and many others.

Educational In design and packaging, the modular micro concept is well-suited for educational purposes. Used by university engineering and computer science departments in formal course work, and by engineers and programmers to keep up with the state of the art.

471

 

TECHNICAL DATA

SEC. 1 CIRCUIT DESCRIPTION

1.1 *Introduction* The 471 CPU board is based on the 8080 microprocessor. Normally the most complex element in a *MIKE 3* microcomputer, the CPU generates nearly all of the control signals which appear on the system's bus structure.

To form a working microcomputer, the 471 CPU board must be interfaced with memory storage. For example, the Model 423 PROM/RAM board includes space for PROM memory from which to read permanently-stored program instructions (such as the *MIKE 3* Monitor), and RAM memory for temporary data storage and for the push-pop stack. In addition, a complete micro-computer usually includes input/output boards for interfacing with keyboards, displays, printers, and other peripheral devices.


This circuit description conforms to the breakdown of the schematic diagram (beginning on page 4 of this data sheet), as follows:

- | | |
|---------------------------|-------------------------|
| 1.2 8080 CPU | 1.8 Interrupt Logic |
| 1.3 Bus Drivers | 1.9 Hold Circuitry |
| 1.4 Main Timing | 1.10 Wait Circuitry |
| 1.5 System Control Logic | 1.11 Indicator Lights |
| 1.6 I/O Instruction Modes | 1.12 Power Requirements |
| 1.7 Reset Circuitry | |

1.2 *8080 CPU* The 8080 is a microprocessor within a single integrated circuit. Based on 17-volt N-channel MOS technology, its 40-pin package includes terminals for an eight-bit bidirectional data bus, D7-D0; a sixteen-bit address bus, A15-A0; power supplies of +12 V, +5 V, and -5 V; and a variety of control signals. The 8080 requires an externally-generated two-phase clock (PH1 and PH2) driven to +12 V; all other control signals are at TTL voltage levels, between 0 and +5 volts.

Complete functional and electrical characteristics of the 8080 are provided in the manufacturers' manuals and spec sheets. Essential details are reprinted by Martin Research in data sheet DS2204. The reader should refer to these sources for an explanation of internal processor operations, and for detailed information on the 8080 instruction set. This data sheet focuses on the circuitry of the Model 471, a CPU board in the *modular micro* series from Martin Research.

NOTICE CONCERNING 8080 A VERSION - The 8080A is an improved version of the 8080, but is compatible with early 8080 devices. Changes implemented with the introduction of the 8080A include the following: a relaxation of the minimum clock input high voltage from +11.0 to +9.0 V; improved current sinking capabilities on output terminals, from 1.7 ma on the data bus (0.75 mA at other outputs) to 1.9 mA on all output terminals, measured at 0.45 V; and internal synchronization of the HOLD signal, avoiding the need for synchronizing circuitry outside the 8080.

 

SEC. 1.2 *8080 CPU* (cont'd.)

The 471 CPU board has been designed for use with the Intel C8080A, Advanced Micro Devices Am9080A, or NEC Microcomputers uPD8080A. The Texas Instruments TMS 8080, and early Intel C8080, will work with the 471 CPU board; however, please note the following. The 8224 clock driver circuit is not guaranteed to deliver PH1 and PH2 clock voltages of greater than +9.4 V, while the TMS 8080 and C8080 are specified to require +11.0 V. Lab tests by Martin Research indicate that in practice these components do interface successfully. Nevertheless, we cannot interpose a guarantee to that effect where the manufacturer's specifications fail to do so.

The NEC Microcomputers uPD8080A includes two features not found on other versions of the 8080: first, the DAA (decimal adjust accumulator) instruction successfully converts binary data to BCD after a subtraction instruction (as well as addition). Second, a MOV *r,r* (register-to-register transfer) instruction takes four (rather than five) machine cycles to execute. This last feature improves uPD8080A speed, but means that software is not 100% compatible with other 8080 processors. That is, slight differences in programming will be necessary in programmed timing loops which depend for accuracy on an exact count of machine cycles executed.


1.3 *Bus Drivers* Like other MOS microprocessors, the internal circuitry of the 8080A does not have the power to drive the large array of memory and other devices typically connected to the *modular micro* bus. For this reason, the 471 includes bus drivers both on the data bus and on the address bus.



The data bus driver stages include two type 8T26 inverting bus drivers. Data traveling on the *modular micro* data bus is inverted in computers using the 471 CPU board. Electrically, this improves system noise immunity. Accessory memory boards using PROM memory normally also use inverting bus drivers, so inversion of data when programming PROMs is unnecessary. In the case of RAM, there is no problem even when non-inverting bus drivers are used on the RAM board: if data is inverted when written into RAM, it is reinverted (and restored) when read back. Input and output data, however, is affected.

The DBIN signal, produced by the 8080A, indicates that the CPU is ready to read data from memory or an input device. Inverted by the system control logic (Sec. 1.5), DBIN activates the inward-pointing drivers of the two 8T26 ICs. The outward-pointing drivers are activated by SYNC and WR, both CPU-produced signals--the first indicating that machine status information is present on the bus. When neither pin 1 nor 15 is activated, the data terminals of the 8T26s are in a high-impedance state, and do not load the data bus.

The Address/Control Bus Driver stage includes four type 8T97 hex tri-state bus drivers. All 24 driver circuits are normally active, driving the 16-line *modular micro* address bus, as well as eight selected control lines. Only when the CPU has acknowledged a HOLD request are these drivers deactivated, allowing some device other than the 471 CPU board to control the system. Useful in DMA and multi-processor applications, this provision is discussed further in Sec. 1.9.


471

 

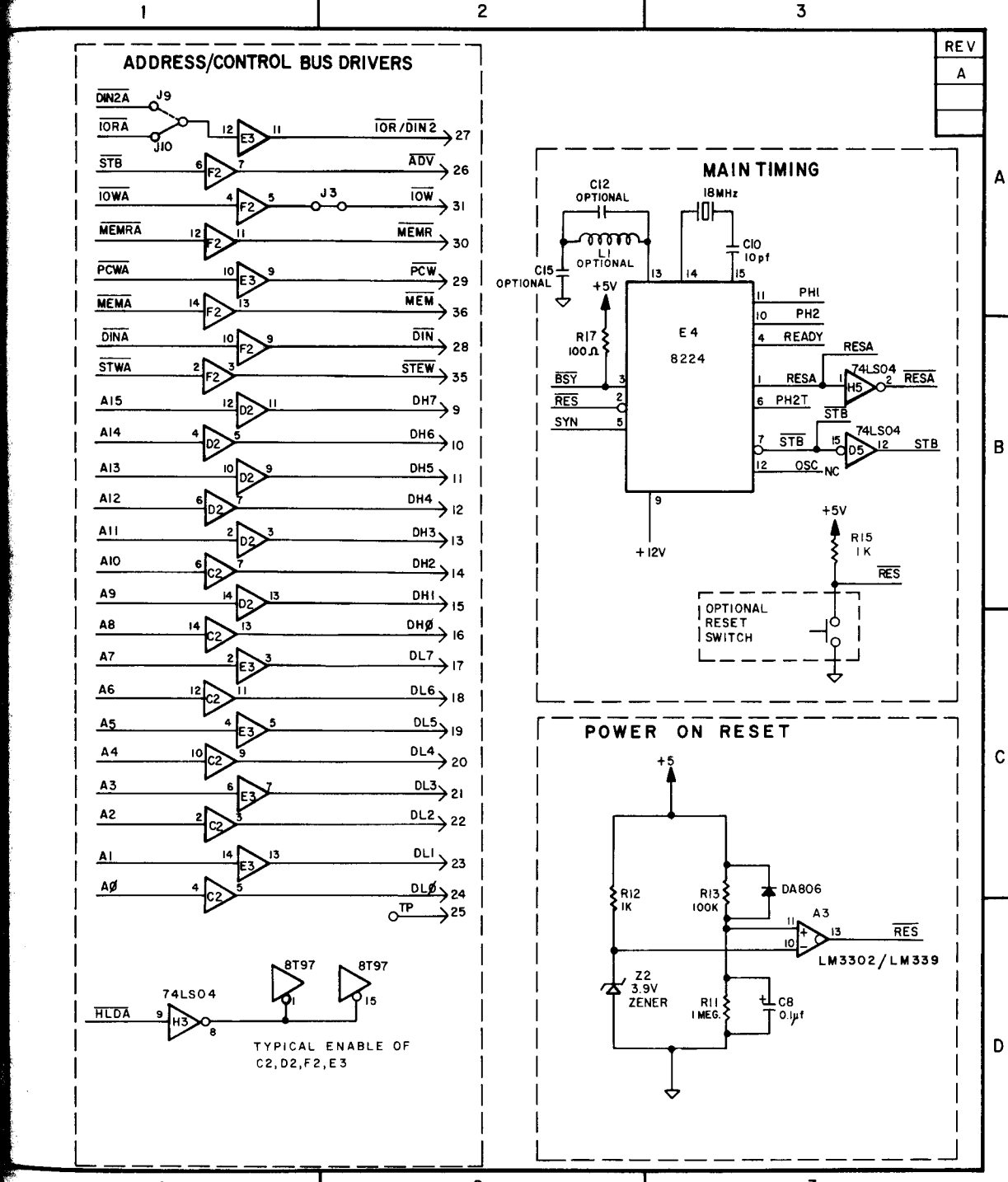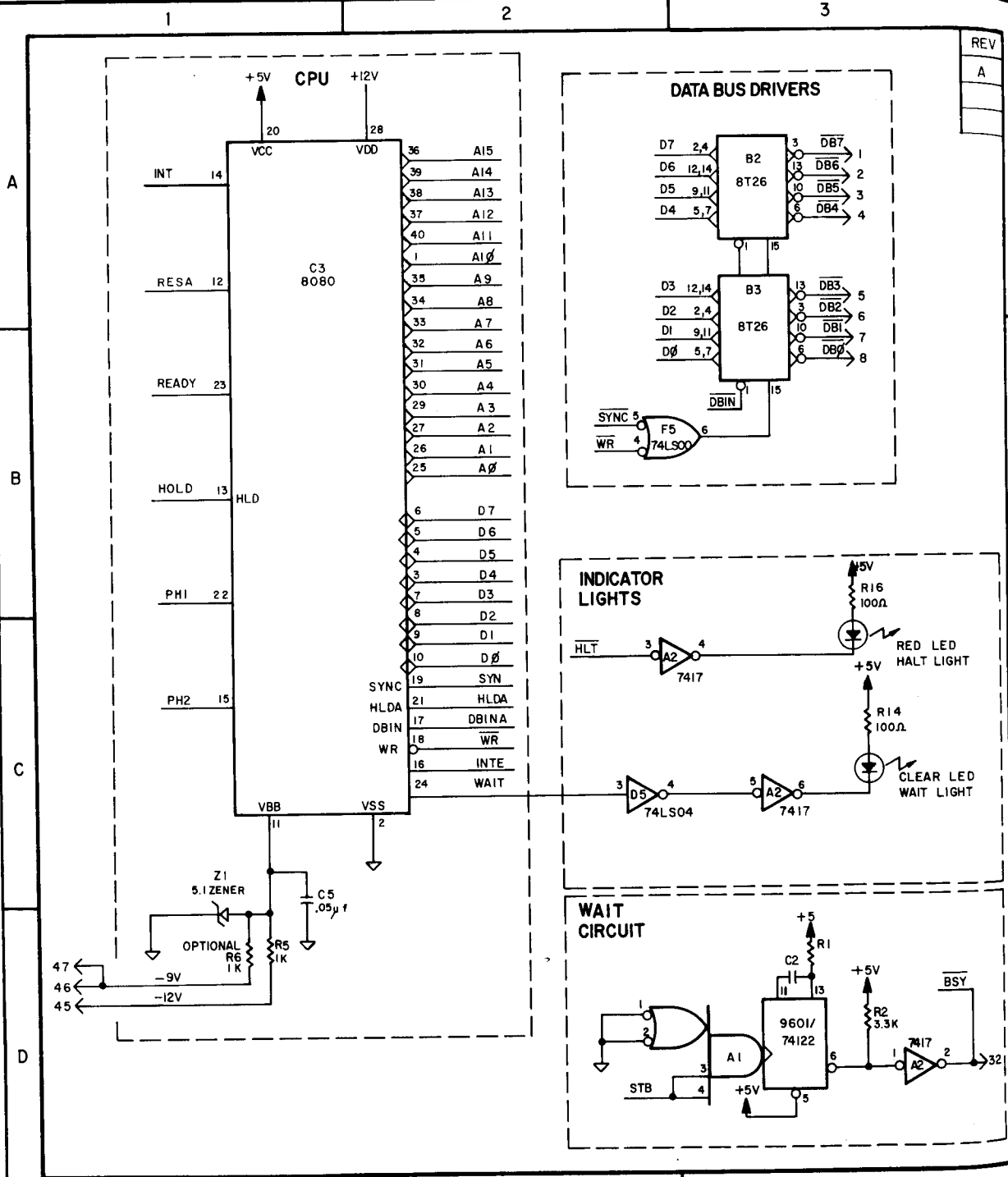



47

SYSTEM CONTROL LOGIC

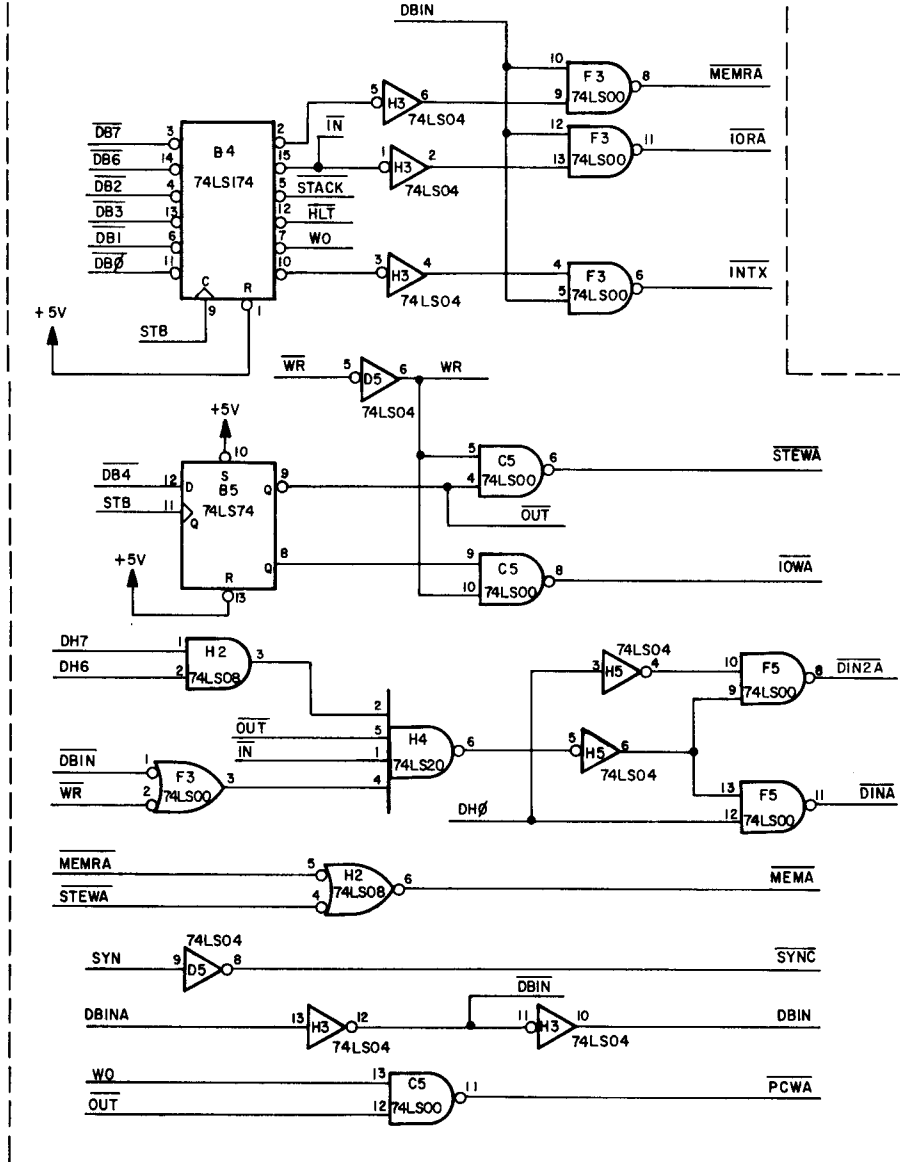

INTERRUPT LOGIC

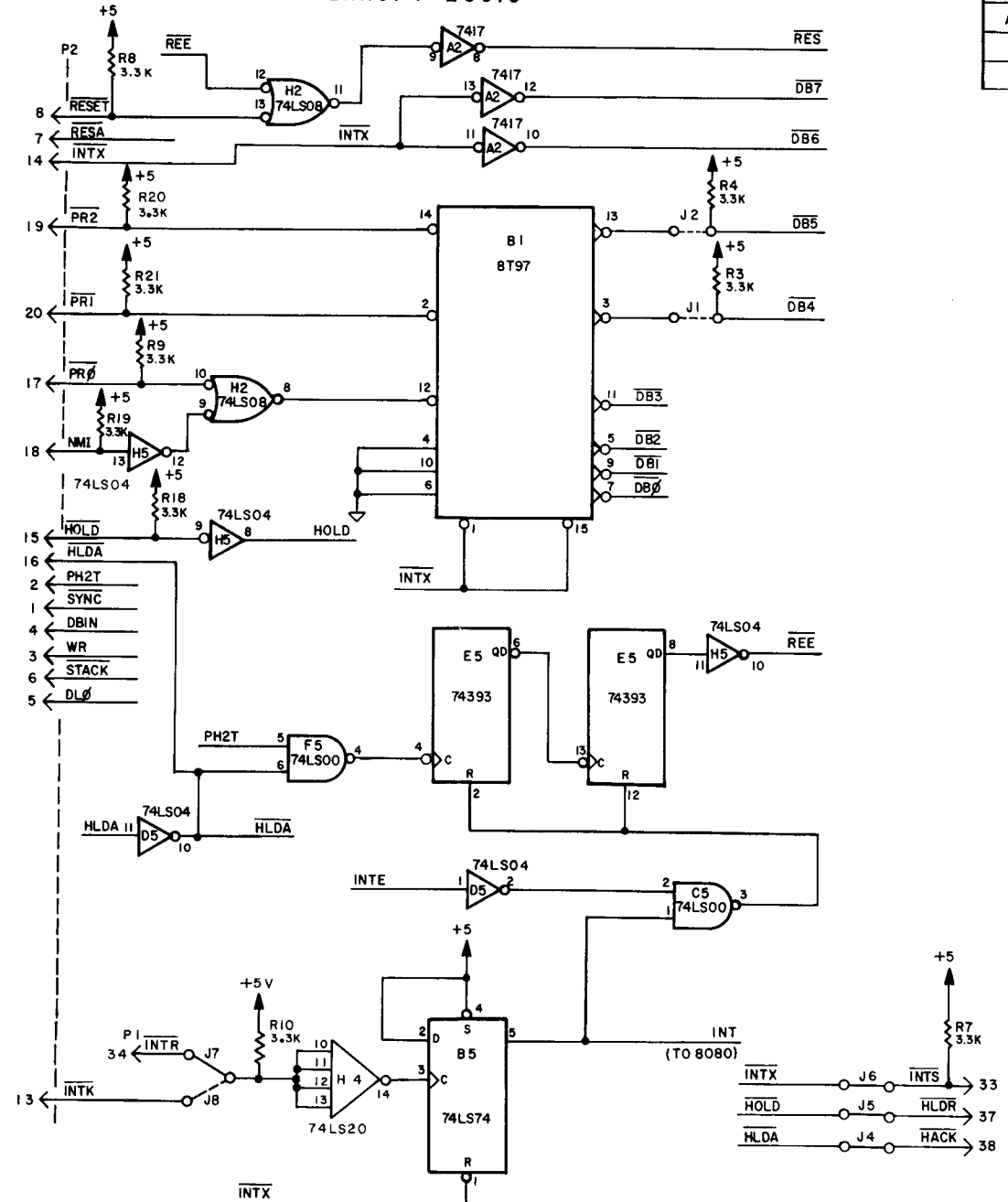

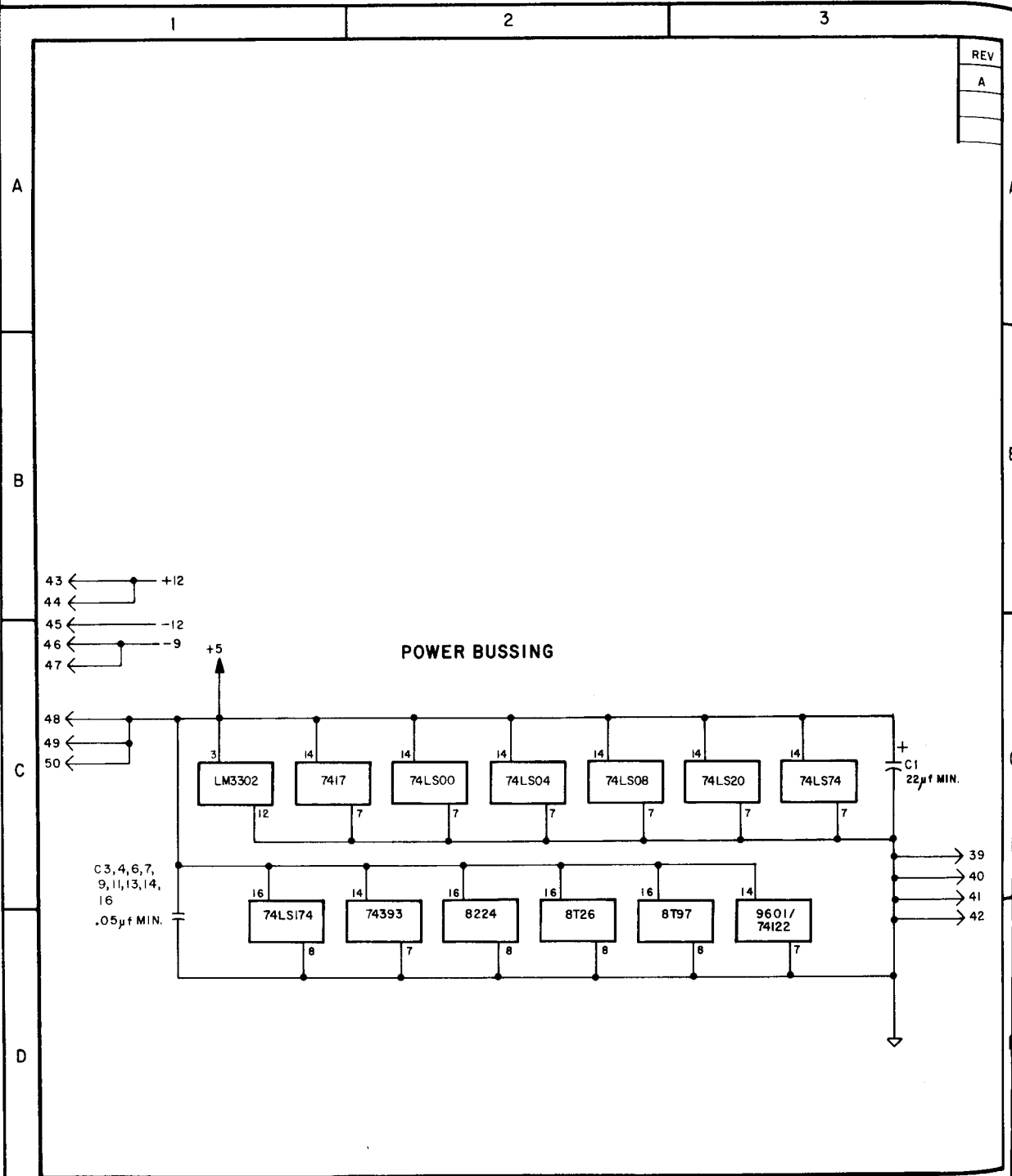

SEC. 1.3 BUS DRIVERS (cont'd.)

In the modular micro series, the 16 address lines are designated DH7 through DH0 (corresponding to A15 through A8 on the 8080 package), and DL7 through DLO (A7 through A0).

The 8T26s can sink up to 40 mA of current (about 25 standard TTL loads), and the 8T97s, up to 48 mA (about 30 standard TTL loads)--more than enough for most microcomputer systems. In addition, both bus driver types are assured of delivering a logic high input voltage of at least +3.5 V to the 8080 (at rated 8080 leakage currents), meeting the 8080 VIH specification of +3.3 V.

1.4 Main Timing The 8080 requires a two-phase clock referenced to +12 V. The standard 8080 requires a clock cycle time, tCY, ranging between 480 ns and 2.0 us; the 471 runs with a 500 ns clock cycle time, for an instruction cycle time of 2.0 us. An instruction cycle is defined for speed spec purposes as the time required for the 8080 to execute an instruction consisting of a single machine cycle consisting of four states, each state lasting one clock period. Actual instruction cycles vary in duration between four and 18 clock periods, depending on the instruction involved. The number of clock periods is further increased if the CPU is made to wait for slow memory.

The 471 CPU board uses a type 8224 clock generator/driver for supplying the 8080 with the required PH1 and PH2 signals. An 18.0 MHz crystal is connected to the 8224, whose internal oscillator produces an 18 MHz square wave (available at pin 12 for test purposes). An internal divide-by-nine counter produces two alternating positive pulses with a basic frequency of 2.0 MHz and an asymmetrical duty cycle (see Fig. 1.4.1). After passing through high-level drivers, these signals are connected directly to the 8080, as PH1 and PH2. A TTL version of PH2--PH2T--is also generated, and is available for system control purposes.


 


Fig. 1.4.1--Asymmetrical 8080 Clock

At press time, available high-speed versions of the 8080A (with maximum clock periods shown in nanoseconds) included Intel C8080A-2, Advanced Micro Devices Am9080A-2 (380); C8080A-1, Am9080A-1 (320); Am9080A-4 (250). The Intel 8224 can be used to generate 8080 clock signals up to a maximum frequency of 27 MHz (corresponding to a clock period down to 370 ns), which supports the 8080A-2. The Am8224 is specified to function with CPUs up to the 250 ns clock cycle speed. (These figures were those available at press time; new product releases were scheduled, and the reader should check for current specifications.)

471

 

SEC. 1.4 MAIN TIMING (cont'd.)

In order to permit the use of an overtone crystal which may be more economical at frequencies above 20 MHz—a tank circuit may be added, as shown by the optional parts connected to the 8224 in the 471 schematic. L1 and C12 are chosen for resonance at the overtone frequency, and C1 is an RF bypass capacitor.

The 8224 also supports three system control functions. First, it generates \overline{STB} , a *status strobe* occurring at the beginning of each 8080 machine cycle. \overline{STB} is used to strobe system control logic (Sec. 1.5), and is made up of SYN (an 8080 signal indicating the beginning of a machine cycle) and $\phi 1A$, which occurs "1 unit" before $\phi 1$ proper (referring to Fig. 1.4.1). Using $\phi 1A$ and incorporating this logic in the Schottky bipolar circuitry of the 8224 optimizes system speed. The 8224 circuitry also activates \overline{STB} during reset cycles.


The 8224 synchronizes the system reset signal at its \overline{RES} input with $\phi 2D$ of the clock (the rising edge of $\phi 2$), to provide the synchronization required by the 8080. (For more on the reset function, see Sec. 1.7 below.)

Finally, the 8224 synchronizes the microcomputer's \overline{BSY} line with $\phi 2D$ of the clock, again to meet 8080 internal timing requirements. (For more on use of the \overline{BSY} line for memory wait cycles, see Sec. 1.10.)

1.5 System Control Logic The 8080 is a synchronous device which follows certain intricate sequences in executing program instructions stored in memory. An *instruction cycle* is required for the execution of each instruction, with this time period subdivided into specialized cycles, as required in order to time-share the microprocessor's eight-bit data bus and sixteen-bit address bus. An instruction cycle consists of between one and four *machine cycles*, with the first always devoted to *fetching* the computer's program instruction from memory. The address bus selects the instruction location, and the data bus receives the memory word. In general, one additional machine cycle is necessary each time the instruction writes into or reads from memory or an I/O port. (For detailed information on processor cycles, the reader is referred to the 8080 data sheet, DS2204.)

Near the beginning of each machine cycle, the 8080 produces the signal SYNC, which is gated by the 8224 clock generator to produce the system strobe \overline{STB} . At \overline{STB} time, the 8080 data bus contains an eight-bit *status word* which defines the purposes of the machine cycle. The assignment of data bus bits is as follows:

| | | |
|----|----------------|---|
| D7 | MEMR | Memory to be read from |
| D6 | INP | Input data to be received |
| D5 | M ₁ | First byte of instruction to be fetched |
| D4 | OUT | Output data to be transmitted |

 

SEC. 1.5 SYSTEM CONTROL LOGIC (cont'd.)


| | | |
|----|-----------------|---|
| D3 | HLTA | CPU in the HALT state |
| D2 | STACK | Stack operation |
| D1 | \overline{WO} | Write into memory or output port (active low) |
| D0 | INTA | CPU acknowledges an interrupt request |

The system control logic on the 471 CPU board includes a 74LS174 hex latch and a 74LS74 D flip-flop. Both circuits are strobed by \overline{STB} (\overline{STB} inverted), latching up seven of the eight bits of the 8080 status word. (The M₁ bit is not used.) Note that the inputs to the latches derive from the inverted data bus, $\overline{DB7}$ through $\overline{DB0}$; the data terminals of the latches have been bubbled to indicate the active-low logic involved. Three of the resultant outputs are inverted and gated with \overline{DBIN} to produce \overline{MEMRA} , \overline{IORA} , and \overline{INTX} . \overline{DBIN} comes from the 8080 (through buffering inverters), and indicates that the 8080 data bus terminals are ready to receive from external circuitry. \overline{INTX} is used to read in an interrupt jam instruction, during interrupt cycles (Sec. 1.8). \overline{MEMRA} and \overline{IORA} are buffered by the Address/Control Bus Driver stage (Sec. 1.3) and are relabeled \overline{MEMR} and \overline{IOR} . Distributed via the *modular micro* bus to circuitry outside the 471 CPU board, these signals are used for enabling memory to be read from, and input ports to be read from (respectively).

The 8080 creates an enable signal called \overline{WR} , indicating that it has valid data on the data bus to be written either into memory or into an output port. To distinguish between these write operations, two NAND gates combine \overline{WR} (\overline{WR} inverted) with the status word bit OUT, which is latched up in the 'LS74 and is available both true and complemented at the flip-flop outputs. \overline{STEWA} (sometimes called \overline{MEMWA}) is active during memory write cycles, and \overline{IOWA} during output write cycles. Both are buffered by the Address/Control Bus Drivers and appear on the *modular micro* bus as \overline{STEW} and \overline{IOW} . Note that these are enable signals, valid only at the moment when the 8080 is transmitting data on its data bus.

The signal \overline{MEMA} is produced by ORing together \overline{MEMRA} and \overline{STEWA} , and after buffering, is available as \overline{MEM} on the *modular micro* bus. It is a combined strobe/enable signal, active during cycles referring to memory (read or write), at the moment when data is transferred between CPU and memory via the data bus.

The signal \overline{PCWA} indicates that a memory write cycle is in progress. Unlike the signals described above, it is not a strobe/enable signal—that is, it is *not* valid just at the moment when data is transferred on the data bus. Rather, \overline{PCWA} starts near the beginning of a memory write cycle and does not end until the next machine cycle begins. A NAND gate is used to gate \overline{WO} (a status bit indicating a memory or output write cycle) with \overline{OUT} , in such a way that \overline{PCWA} is active only when \overline{OUT} is inactive. After buffering, the signal is called \overline{PCW} , and is available on the *modular micro* bus. Typically, \overline{PCW} is used to control the R/W terminals of RAM memory. \overline{PCW} anticipates both \overline{STEW} and \overline{MEMR} , so that the read/write mode on the RAM can be set up before the strobe/enable signal activates data transfers with the CPU.

 

SEC. 1.5 SYSTEM CONTROL LOGIC (cont'd.)

Another signal useful in interfacing with memory is the status strobe, \overline{STB} , developed by the 8224 clock generator and discussed above. After buffering by the Address/Control Bus Driver stage, it is piped along the modular micro bus under the label \overline{ADV} , for address valid. As the name implies, when \overline{ADV} occurs the 8080A address lines have been loaded and are stable, indicating that the address bus may be used reliably in memory and I/O addressing. \overline{ADV} occurs early enough in the machine cycle that, should the ready line be pulled down at this time, the CPU will enter a wait state. (See Sec. 1.10.)


1.6 I/O Instruction Modes

1.6.1 Standard 8080 I/O Mode The \overline{IOR} and \overline{IOW} signals discussed above are used for strobing and enabling input and output ports, using the standard 8080 INP and OUT instructions. In either of these instructions the second byte is an eight-bit I/O port address, which appears on both the DH and the DL address lines of the microcomputer. The I/O circuitry must first be addressed by the DH or DL address lines; then the \overline{IOR} signal enables an input port (or \overline{IOW} strobes an output port) and the I/O data flows between the port and the 8080 accumulator (A register).

1.6.2 Memory-Mapped I/O A second mode of I/O addressing is commonly used—simply defining selected addresses in memory as I/O ports. Output ports are addressed by memory write instructions—strobed with the STEW (MEMW) strobe. Input ports are addressed by memory read instructions—enabled with MEMR signals. This memory-mapped I/O mode is that used in the 6800/6502 microprocessor series, and is attractive because of its universality. That is, the approach is basically compatible with any microcomputer, and a peripheral device with this kind of I/O port addressing circuitry can most likely be interfaced with few modifications to different microprocessors. This is especially true in the modular micro series, where the bus is compatible with various standard eight-bit processors. Another advantage is that the 8080A includes instructions for transferring data between memory and a number of CPU index registers, rather than just the A register (accumulator) as with I/O instructions proper. Since the computer's memory read/write signals are used in controlling memory-mapped I/O, no additional circuitry is required. Naturally the user must maintain a memory map, to make sure that memory and I/O port addresses do not overlap.

By predecoding some of the I/O address lines, producing a specialized I/O strobe/enable signal, the amount of I/O strobe decoding circuitry necessary on peripheral boards in the microcomputer can be reduced. (See Sec. 1.6.4.)

1.6.3 8008-Compatible I/O A third mode of I/O addressing is supported by the 471 CPU board, which derives the \overline{DINA} strobe/enable signal (as shown in the System Control Logic section of the schematic). This I/O addressing mode is used by the 8008 microprocessor, the 8080's predecessor, widely used in industrial controllers. An 8008 microcomputer—the MIKE 2—is available from Martin Research, and some boards in the modular micro series use the 8008 mode of I/O addressing. The fact that the 471 includes these features

 


SEC. 1.6 I/O INSTRUCTION MODES (cont'd.)

| I/O ADDRESS BITS | | | | | MEMORY PAGE USING \overline{DIN} | | EQUIVALENT 8008 INSTRUCTION | | MEMORY PAGE USING $\overline{DIN2}$ | |
|------------------|-----|-----|-----|-----|------------------------------------|-----|-----------------------------|------------|-------------------------------------|-----|
| DH5 | DH4 | DH3 | DH2 | DH1 | OCTAL | HEX | MNEMONIC | OCTAL CODE | OCTAL | HEX |
| 0 | 0 | 0 | 0 | 0 | 301 | C1 | INP 00 | 101 | 300 | C0 |
| 0 | 0 | 0 | 0 | 1 | 303 | C3 | INP 01 | 103 | 302 | C2 |
| 0 | 0 | 0 | 1 | 0 | 305 | C5 | INP 02 | 105 | 304 | C4 |
| 0 | 0 | 0 | 1 | 1 | 307 | C7 | INP 03 | 107 | 306 | C6 |
| 0 | 0 | 1 | 0 | 0 | 311 | C9 | INP 04 | 111 | 310 | C8 |
| 0 | 0 | 1 | 0 | 1 | 313 | CB | INP 05 | 113 | 312 | CA |
| 0 | 0 | 1 | 1 | 0 | 315 | CD | INP 06 | 115 | 314 | CC |
| 0 | 0 | 1 | 1 | 1 | 317 | CF | INP 07 | 117 | 316 | CE |
| 0 | 1 | 0 | 0 | 0 | 321 | D1 | OUT 10 | 121 | 320 | DO |
| 0 | 1 | 0 | 0 | 1 | 323 | D3 | OUT 11 | 123 | 322 | D2 |
| 0 | 1 | 0 | 1 | 0 | 325 | D5 | OUT 12 | 125 | 324 | D4 |
| 0 | 1 | 0 | 1 | 1 | 327 | D7 | OUT 13 | 127 | 326 | D6 |
| 0 | 1 | 1 | 0 | 0 | 331 | D9 | OUT 14 | 131 | 330 | D8 |
| 0 | 1 | 1 | 0 | 1 | 333 | DB | OUT 15 | 133 | 332 | DA |
| 0 | 1 | 1 | 1 | 0 | 335 | DD | OUT 16 | 135 | 334 | DC |
| 0 | 1 | 1 | 1 | 1 | 337 | DF | OUT 17 | 137 | 336 | DE |
| 1 | 0 | 0 | 0 | 0 | 341 | E1 | OUT 20 | 141 | 340 | EO |
| 1 | 0 | 0 | 0 | 1 | 343 | E3 | OUT 21 | 143 | 342 | E2 |
| 1 | 0 | 0 | 1 | 0 | 345 | E5 | OUT 22 | 145 | 344 | E4 |
| 1 | 0 | 0 | 1 | 1 | 347 | E7 | OUT 23 | 147 | 346 | E6 |
| 1 | 0 | 1 | 0 | 0 | 351 | E9 | OUT 24 | 151 | 350 | E8 |
| 1 | 0 | 1 | 0 | 1 | 353 | EB | OUT 25 | 153 | 352 | EA |
| 1 | 0 | 1 | 1 | 0 | 355 | ED | OUT 26 | 155 | 354 | EC |
| 1 | 0 | 1 | 1 | 1 | 357 | EF | OUT 27 | 157 | 356 | EE |
| 1 | 1 | 0 | 0 | 0 | 361 | F1 | OUT 30 | 161 | 360 | FO |
| 1 | 1 | 0 | 0 | 1 | 363 | F3 | OUT 31 | 163 | 362 | F2 |
| 1 | 1 | 0 | 1 | 0 | 365 | F5 | OUT 32 | 165 | 364 | F4 |
| 1 | 1 | 0 | 1 | 1 | 367 | F7 | OUT 33 | 167 | 366 | F6 |
| 1 | 1 | 1 | 0 | 0 | 371 | F9 | OUT 34 | 171 | 370 | F8 |
| 1 | 1 | 1 | 0 | 1 | 373 | FB | OUT 35 | 173 | 372 | FA |
| 1 | 1 | 1 | 1 | 0 | 375 | FD | OUT 36 | 175 | 374 | FC |
| 1 | 1 | 1 | 1 | 1 | 377 | FF | OUT 37 | 177 | 376 | FE |

Figure 1.6.1—8080 Memory Pages for 8008 I/O Instructions

471

 

SEC. 1.6.3 8008-COMPATIBLE I/O (cont'd.)

makes it very attractive in updating 8008 systems, especially when it is not desired to change peripheral I/O boards.

In the 8008 I/O mode, the I/O port address appears on five lines of the high-order memory address bus, namely DH5 through DH1. *Output* data appears on the low-order memory address, DL7-DL0. *Input* data is transmitted to the CPU via the data bus. When executed on an 8008, there are special single-byte input and output instructions; but with the Model 471 8080 CPU board, these 32 I/O ports are addressed with certain memory referencing instructions.

Referring to the circuitry which creates \overline{DINA} : this signal occurs when the 8080 data bus is ready to receive data (\overline{DBIN}) or transmit data (\overline{WR}); when the instruction is not a standard 8080 I/O instruction (\overline{OUT} and \overline{IN} must be high); and only when DH7 and DH6 are high, and DH0 is high. These conditions mean that any 8080 memory read/write instruction which references the odd-numbered pages in the upper one-fourth of memory can be used as an 8008-compatible I/O instruction. (See Figure 1.6.1.)

$\overline{DIN2A}$ is a variant of \overline{DINA} , differing only in that it is created when DH0 is low (rather than high). By using $\overline{DIN2}$, another set of 32 I/O ports can be addressed. Again, see Fig. 1.6.1.

The Address/Control Bus Driver stage converts \overline{DINA} to \overline{DIN} , and $\overline{DIN2A}$ to $\overline{DIN2}$, for use on the *modular micro* bus. Note that the user must choose between the extra 32 8008-compatible I/O ports (using the $\overline{DIN2}$ signal), and the standard 8080 input ports (using the \overline{IOR} signal), by wiring up *either* jumper 9 (J9) or J10. As the solid line indicates, factory-assembled boards are wired for \overline{IOR} .

To decode the strobe and enable signals for an 8008-compatible I/O port, circuitry on a peripheral board combines the \overline{DIN} or $\overline{DIN2}$ signal on the *modular micro* bus with the five address bits DH5 through DH1. Using a single 74LS138 (3205/8205), eight such strobe/enable signals can be produced by connecting the five DH bits in various combinations to the three select inputs, and to one active-low and one active-high enable input. (This technique is elaborated in the data sheet for a Universal I/O Kit, KT9001, and in Chapter 7 of *Microcomputer Design*.)

Several kinds of 8080 instructions may be performed using the 471 CPU board in order to address 8008-compatible I/O ports. These are indicated in Figure 1.6.2.

SEC. 1.6 I/O INSTRUCTION MODES (cont'd.)

| I/O PORT ADDRESS IS IN: | OUTPUT DATA IS IN: | 8080 INSTRUCTION EXECUTED: | OUTPUT DATA ENDS UP IN: | INPUT DATA ENDS UP IN: |
|-------------------------|----------------------|----------------------------|-------------------------|--------------------------------------|
| H | L | MOV A, M | OUTPUT PORT | A |
| B | C | LDAX B | OUTPUT PORT | A |
| D | E | LDAX D | OUTPUT PORT | A |
| 2ND INST. BYTE (PPP) | 3RD INST. BYTE (DDD) | LDA PPPDDD | OUTPUT PORT | A |
| 2ND INST. BYTE (PPP) | 3RD INST. BYTE (DDD) | STA PPPDDD | OUTPUT PORT | NO INPUT-- A REG. IS UNCHANGED |

Figure 1.6.2--8080 Instructions Referencing 8008-Compatible I/O Ports



Note that many of these 8080 instructions can be used as *combined* I/O instructions. Assume that a strobe decoder on a peripheral I/O board combines \overline{DIN} with some combination of DH5-DH1--say 00100, corresponding to octal memory page 311 (Fig. 1.6.1). The resulting signal is used to strobe an eight-bit latch, whose inputs are connected to the DL address bus. This is an output port--equivalent to 8008 Output Port 4. The same signal is used to enable an eight-bit bus driver, with inputs deriving from some eight-bit parallel data source, and tri-state driver outputs connected to the microcomputer data bus (8008 Input Port 4). The 8080 instruction LDA 311DDD is executed (where DDD is the output data). \overline{DIN} goes low; the H address 311 is decoded; both input and output ports are activated; the output data DDD ends up in the output port; and the input data is moved to the A register.

For example, the program . . .

```
LXI    B,311123
LDAX  B
```

. . .will output the octal value 123 to Output Port 4, and simultaneously load the A register with the data at Input Port 4. The instruction LDA 311123 would accomplish the same thing.

Note also that if the purpose of the instruction is to *input* data only, the low-order address need not set up. For example, the instruction LDAX B might be executed, with the input port address previously loaded into the B register, but any arbitrary data in the C.

  

SEC. 1.6 I/O INSTRUCTION MODES (cont'd.)

Finally, note that the use of these 8008-compatible I/O instructions is entirely optional. Any of the page addresses shown in Fig. 1.6.1 may instead be used for memory, activated by the normal 8080 memory signals (STEW, MEMR, etc.), and DIN may be ignored. As with other forms of memory-mapped I/O--of which this is a specialized version--the only constraint is that a given memory page address not be used for more than one purpose (memory or I/O port).

1.6.4 Memory-Mapped I/O with Predecoded Strobe One advantage of the 8008-compatible I/O mode discussed above is that there are only five I/O address lines, as opposed to eight with the 8080 mode and eight with the memory-mapped mode (if a whole page in memory is used for each I/O port; 16 lines if a single location in memory is assigned as an I/O port). This means that circuitry needed to produce I/O strobes, for activating input bus drivers and output latches on a peripheral circuit board, must combine eight or more I/O address lines, plus a control signal (IOR, IOW, MEMR, STEW). This circuitry will be cumbersome, especially if more than one I/O strobe/enable signal is needed on that board.

The user of the 471 CPU board can combine the advantages of several I/O address modes by using DIN (or DIN2) for memory-mapped I/O. To output data, the program executes a memory write instruction, and data is written into the output port; to input data, the program executes a memory read instruction, and data is read from the input port into the CPU. All of the various memory-referencing instructions of the 8080 may be used. So far, this is a description of memory-mapped I/O in general. The only differences are these: the I/O ports use \overline{DIN} (or $\overline{DIN2}$) instead of \overline{MEMR} or STEW; and the high-order memory address which references these I/O ports must be one which will cause \overline{DIN} (or $\overline{DIN2}$) to be produced. (See Fig. 1.6.1.)

With this I/O method, a single 74LS138 on a peripheral board will produce eight I/O strobe/enable signals, as described in Sec. 1.6.3 above.

1.7 Reset Circuitry When power is first applied to the 8080, its internal registers may take on any random values. To initialize the machine, the 8080 RESET terminal must be brought to a logic high level for at least three clock cycles. This resets the program counter to zero, and the 8080 will proceed to execute stored program instructions, starting at location zero. The reset signal also resets the 8080 interrupt flip-flop, disabling interrupts (as does an interrupt itself). An initial interrupt is unnecessary for starting the computer. However, if it is desired to make the CPU wait for an initial interrupt before proceeding with its mainline program, the two instructions EI (enable interrupt), HLT (halt) may be inserted starting at location zero. 8080 flags and registers other than the program counter and interrupt flip-flop are not affected by the reset pulse, but must be initialized as required through program instructions.

The Model 471 CPU board includes a Power On Reset circuit which senses the rising of the +5 volt power supply as power is applied, generating the signal RES. The LM3302/339 is capable of operation at supply voltages as low as +2.0 V. Until the +5 volt line reaches +3.9 V, the zener diode does not conduct, and the - input to the comparator receives the full power supply voltage.

SEC. 1.7 RESET CIRCUITRY (cont'd.)

The resistive voltage divider, R13/R11, provides the + comparator input with 9/10 of the power supply voltage; and since the - input exceeds the + input level, the comparator output goes low, activating RES. When the +5 volt line reaches about +4.3 volts, the voltage at the + comparator input finally begins to exceed the 3.9 V zener voltage, and the comparator goes high, remaining so as the +5 volt supply finishes charging up to a full +5.0 volts, $\pm 5\%$.

The \overline{RES} signal is connected to the 8224 clock generator, which synchronizes the reset request with 8080 timing (Sec. 1.4 above). The output of the 8224, RESA, is connected directly to the 8080A CPU.

Should the +5 volt line ever dip below about 4.3 V, the comparator will again go low, after a delay while C8 discharges--generating RES and resetting the computer. The delay will prevent short glitches on the power supply from causing a reset. But if the voltage drops much below 4.0 V, the diode (DA806) starts to conduct, discharging the capacitor more rapidly, and causing a reset.

Note that this reset circuit looks only at the +5 volt power supply. For reliable operation of the computer, the +12 V and -12 (or -9) V supplies, also powering the 8080, should come up if not before, at least very soon after the +5 volt power supply does.

An optional reset switch may be installed, allowing the user to reset the microcomputer manually. This provision is generally unnecessary in production versions of the 471 CPU board, but is useful in prototyping. Consider the following potential 8080 system failure: a DI (disable interrupt) instruction has been executed, in order to protect a subroutine which must not be interrupted (such as a critical timing loop or stack operation). Because of a software or hardware bug, a HLT (halt) instruction is executed. This condition is inescapable through interrupts, since the CPU has masked them out. Only a system reset will restart the computer.

As an additional protection against this failure mode, the 471 board incorporates a digital timer which automatically resets the 8080 if the CPU has masked interrupts (through a DI instruction) and fails to acknowledge interrupt requests for a set period. The timer consists of a 74393 dual divide-by-16 counter (see page 7, location C2). The 8080 has an output terminal labeled INTE (interrupt enable) which is high when interrupts are enabled. When the CPU is in the state where interrupts will be acknowledged, the inverted version of INTE causes a low input to a 74LS00 NAND gate, whose output is therefore high. This holds the 74393 reset (R) terminals at a high level, forcing the counter output bits to zero and inhibiting counting.

When interrupts are disabled, INTE goes low. If at the same time, an interrupt request has been received, but has not yet been acknowledged by the CPU, the 74LS74 interrupt request flip-flop output (B5, pin 5) is high. These conditions are combined by the NAND gate, and the 74393 reset signal is removed, allowing the counters to count. Clocked by PH2T, the 74393 counts once each 8080 clock cycle. If the CPU acknowledges a HOLD request (Sec. 1.9), HLDA goes low, inhibiting counting--but not resetting the 74393. If the CPU acknowledges an interrupt

SEC. 1.7 RESET CIRCUITRY (cont'd.)

request, then the counters are reset. But if 128 PH2T cycles have been clocked, the high-order 74393 output bit (pin 8) goes high. The signal which results (after inversion), \overline{REE} , causes a reset.

\overline{REE} is ORed with the signal \overline{RESET} , which originates from an optional interrupt control board (Sec. 1.8). A 7417 open-collector buffer is connected to the \overline{RES} line, which may also be pulled low by the power-on reset comparator and the optional reset switch.

The automatic reset circuit may be defeated by removing the 74393 counter from its socket, and connecting a wire jumper between pins 8 and 7 (ground) on the 74393 socket.

1.8 Interrupt Logic The 8080 fully supports external interrupt requests. A typical interrupt source is a peripheral input device (such as a keyboard) which inputs data relatively infrequently and unpredictably, but which must receive immediate priority when ready. Basically, the 8080 receives the interrupt request and issues an interrupt acknowledgment. External circuitry detects the acknowledgment, and jams in a special instruction, causing the CPU to jump to the appropriate interrupt subroutine. When this ends, the CPU returns to the mainline program at exactly the point where it was interrupted.

In many systems there are multiple interrupt sources. It is necessary therefore to provide means for decoding the source of an interrupt request, in order to make the CPU execute the appropriate interrupt instructions. The 471 includes on-board provisions for three interrupt levels. In addition, the essential interrupt control signals are routed to a 20-pin connector at the side of the board, shown as P2 on the 471 schematic. An optional interrupt control board may be connected here for expansion to an eight-level prioritized interrupt system.

The interrupt cycle begins when some device within the modular micro system pulls the \overline{INTR} line (pin 34) low. (Refer to page 7, location D1.) \overline{INTR} is connected through jumper J7 to a 74LS20 inverter stage. (J8 would replace J7 only if the optional interrupt board were installed.) The 74LS74 interrupt request flip-flop is clocked, causing the INT signal to go high. The INT signal is connected directly to the 8080, requesting an interrupt.

The 8080 contains an internal interrupt flip-flop, INTE (as mentioned above). Executing a DI (disable interrupt) instruction, resetting the computer, or performing an interrupt, will reset the INTE flip-flop and prevent the CPU from acknowledging further interrupts. To enable interrupts, an EI instruction must be executed. This sets the INTE flip-flop and permits the 8080 to recognize interrupts. The 8080 CPU does not itself save interrupt requests which were placed when interrupts were disabled. However, the 471 CPU board does, in the interrupt request flip-flop (a 74LS74: page 7, location D2 in the schematic).

When an interrupt is recognized, the 8080 enters a special interrupt instruction cycle. In the machine status word for the instruction fetch cycle appearing on the data bus at STB time, $\overline{DB0}$ will be 0. The system control logic detects this interrupt acknowledgment, and at \overline{DBIN}

SEC. 1.8 INTERRUPT LOGIC (cont'd.)

time, produces the signal \overline{INTX} (Sec. 1.5 above). This enable signal is used to jam the special interrupt instruction onto the data bus. It also resets the 74LS74 interrupt request flip-flop.

\overline{INTX} is connected to the inputs of two 7417 open-collector buffers, and to the enable terminals of an 8T97 hex tri-state buffer. The 7417s pull $\overline{DB7}$ and $\overline{DB0}$ to 0, and the 8T97 pulls $\overline{DB3}$ through $\overline{DB0}$ to 0. ($\overline{DB3}$ is pulled low because pin 12 of the 8T97 is normally low--unless the optional interrupt board pulls down the NMI line.) $\overline{DB5}$ and $\overline{DB4}$ are held high by pullup resistors R4 and R3 (which would be replaced by jumpers J2 and J1 only if the optional interrupt board were installed).

These conditions mean that the inverted data bus bits $\overline{DB7}$ through $\overline{DB0}$ read 00110000. Reverting, the data word seen by the CPU is 11001111, or 317 octal. This is the code for an 8080 RST 1 instruction, a single-byte call instruction which causes the CPU to jump to memory location 000010, pushing the program counter stack. Starting at this location, the user installs a program which contains the instructions necessary to carry out the purposes of the interrupt request. The interrupt routine ends with a RET (return) instruction, popping the PC stack and returning control to the mainline program.

The reader should note that, to avoid having the interrupt routine disturb the mainline program, any registers and flags used both by the interrupt and mainline programs should be saved as the interrupt routine begins (with PUSH instructions) and restored as it ends (with POP instructions).



The device requesting an interrupt may pull down the $\overline{DB5}$ and $\overline{DB4}$ data bus lines at \overline{DBIN} time, altering the interrupt jam instruction as shown in Figure 1.8.1.

| $\overline{DB5}$ | $\overline{DB4}$ | DATA | DATA | OCTAL | INSTRUCTION | RESTART ADDRESS |
|------------------|------------------|----------|----------|-------|-------------|-----------------|
| 1 | 1 | 00110000 | 11001111 | 317 | RST 1 | 000010 |
| 1 | 0 | 00100000 | 11011111 | 337 | RST 3 | 000030 |
| 0 | 1 | 00010000 | 11101111 | 357 | RST 5 | 000050 |
| 0 | 0 | 00000000 | 11111111 | 377 | RST 7 | 000070 |

Figure 1.8.1--Interrupt Jam Instructions

This interrupt system effectively provides three interrupt levels, though there are four possible jam instructions (Fig. 1.8.1). RST 1 is a general-purpose interrupt, where the interrupting device does not affect $\overline{DB5}$ or $\overline{DB4}$. Typically this is a low-priority interrupt. A second interrupt port pulls down $\overline{DB5}$, and a third, $\overline{DB4}$. Other data bus lines could be pulled low but will have no

471

  

SEC. 1.8 INTERRUPT LOGIC (cont'd.)

effect unless the system is provided with the optional eight-level interrupt board. Since a RST 7 interrupt jam instruction would result when *both* the $\overline{DB5}$ and $\overline{DB4}$ interrupt ports requested interrupts at the same time, it cannot be used unambiguously for a third interrupt port. Note also that if a RST 3, 5, or 7 occurs, it masks the possibility that a RST 1 interrupt might also have been requested.

In order to synchronize circuitry on peripheral boards with the CPU interrupt logic, the \overline{INTX} interrupt jam enable signal is connected through jumper J6 to \overline{INTS} on the *modular micro* bus (page 7, location D3). The device requesting an interrupt uses this signal to enable circuitry which pulls down the $\overline{DB5}$ and $\overline{DB4}$ data bus lines. A suitable circuit using only two ICs appears in Figure 1.8.2. (A kit of the parts shown, plus wirewrap sockets, is available from Martin Research as KT9008.)

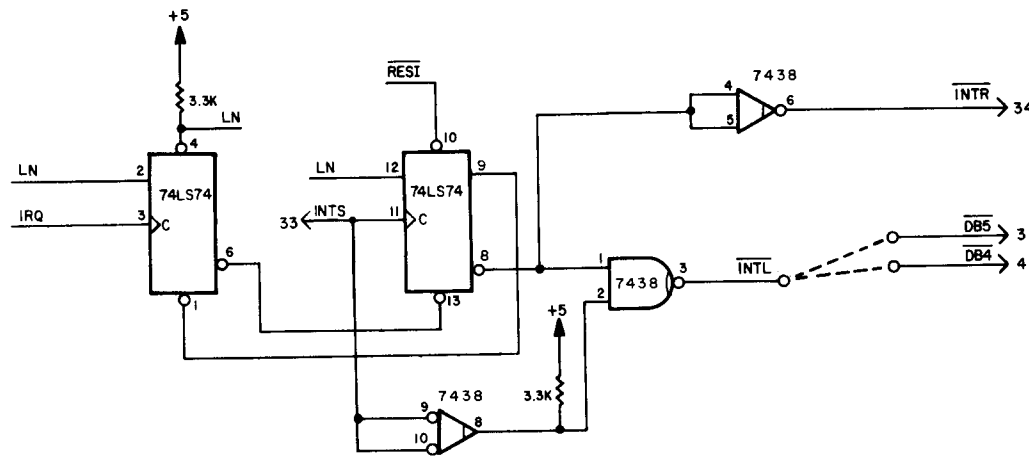


Figure 1.8.2--Interrupt Request Port

The device requesting an interrupt causes IRQ (interrupt request) to go high, setting the first 74LS74 flip-flop (pin 3). The \overline{Q} output of this flip-flop (pin 6) resets the second flip-flop (pin 13), causing its Q output (pin 9) to go low. This signal is fed back to the first FF reset terminal (pin 1), resetting the first FF. However, the second FF remains reset. With pin 8 high, the 7438 open-collector buffer connected to the \overline{INTR} line is activated, pulling \overline{INTR} low and requesting an interrupt from the 471 CPU board.

SEC. 1.8 INTERRUPT LOGIC (cont'd.)

The 471 acknowledges with an \overline{INTS} enable signal. When \overline{INTS} goes low, it activates a 7438 inverter stage (pins 9, 10, 8). This signal, combined with the high state remaining on the second FF \overline{Q} output (pin 8), activates a 7438 open-collector NAND gate (pins 1, 2, and 3), pulling down $\overline{DB4}$, $\overline{DB5}$, or neither, as required. When \overline{INTS} ends, going high, the second flip-flop is clocked (pin 11) and set. Pin 8 goes low, ending the \overline{INTR} interrupt request, and ending the interrupt jam on the $\overline{DB5}$ or $\overline{DB4}$ data bus line.

The signal $\overline{RES1}$, which sets the second flip-flop (pin 10), will (when low) disable the interrupt request port. If this signal is not used, it should be connected to logic one (LN).

Naturally the device requesting an interrupt would also have other circuitry for communicating with the CPU. If an input device, the restart instruction would cause the CPU to start executing input instructions addressing the appropriate input ports.


1.9 Hold Circuitry The 8080 includes provisions for suspending processor operations and allowing some other device to control the microcomputer's data and address busses. Shortly after the 8080 HOLD terminal is brought to a logic high level, the 8080 responds by deactivating its tri-state data and address bus drivers. The 8080 output terminal, HLDA, goes high, acknowledging the hold condition; the inverse of this signal, \overline{HLDA} , disables the Address/Control Bus Driver stages. Since the CPU ceases to create SYNC, \overline{DBIN} , or WR pulses, the data bus drivers are inactive as well. The 8080 leaves the hold mode when its HOLD input is returned to the logic low condition.

On the 471 CPU board, jumper J5 connects \overline{HOLD} to pin 37 on the *modular micro* bus. Jumper J4 connects the hold acknowledge signal, HLDA, to pin 38 on the microcomputer bus. (See page 7, location D3.) (These jumpers would be disconnected if the optional priority interrupt board were connected at P2; this board also provides extra DMA channels.)

To initiate a hold condition, a peripheral board pulls \overline{HLDR} low (pin 37). The CPU responds by pulling \overline{HACK} low (pin 38). Special circuitry on the peripheral board is then in control of the address bus, the data bus, and the eight control signals shown in the Address/Control Bus Driver section.

The A version of the 8080 CPU includes internal circuitry for synchronizing a hold request with CPU machine cycles. If an 8080 (original version) is used, the device requesting a hold must do the synchronizing. This is easily done on the peripheral board by gating the hold request circuitry with \overline{ADV} (address valid), pin 26 on the *modular micro* bus.

1.10 Wait Circuitry Inspection of the timing diagrams for the 8080 reveals that, operating with a 500 ns clock period, the CPU requires memory with an access time of about 650 ns. However, this is the ideal case, without allowing for delays in bus drivers, address decoders, and other adjunct circuitry in the microcomputer. Intel recommends that the access time of memory interfaced to the 8080 be in the range of 450 to 550 ns, or less. 550 ns is

 

SEC. 1.10 *WAIT CIRCUITRY* (cont'd.)

probably a safe figure, but the conservative designer may choose to specify memory with a 450 ns access time. 450 ns is Martin Research policy with regard to the Model 405 static 4K RAM board.

If slower memory is used, the 8080 must be made to wait for memory access. This is done by pulling the 8080 READY terminal low. When slow memory is addressed, special memory wait circuitry is triggered, pulling down the \overline{BSY} (busy) line on the *modular micro* bus. To synchronize wait requests with the 8080, \overline{BSY} is connected to the 8224 clock generator, which drives the 8080 READY terminal (Sec. 1.4).

Any peripheral device with slow memory can pull \overline{BSY} down and cause an extended wait period. The same provision may be used with slow I/O devices, during input and output instructions. Optional wait circuitry is a feature of several Martin Research circuit boards.


The 471 CPU board includes a wait circuit consisting of a 9601 or 74122 one-shot and a 7417 open-collector buffer. The one-shot is triggered by STB--a status strobe which comes sufficiently in advance of any read/write data transfer to guarantee that the CPU will enter the wait state. The \overline{Q} output (pin 6) goes low, activating the 7417 and pulling \overline{BSY} low.

The 9601 and 74122 are not identical, but both work in this circuit. They have very similar timing characteristics. The values of R1 and C2 determine the length of the wait cycle. In factory-assembled boards, R1 is 10K, and C2 is 270 pf, producing the required one-shot period of about 915 ns. The goal is to cause two memory wait cycles, which adds two clock cycles ($2 \times 500 \text{ ns} = 1.0 \text{ us}$) to the normal T3 state, adding to a total of 1.5 us. This compensates for memory with an access time as slow as 1.55 us.

For this CPU circuitry (8080 with 8224), to cause n wait states, the \overline{BSY} line should be pulled low (starting at the leading edge of STB) for the period $(n - 1/6) t_{cy}$, where t_{cy} is the clock cycle time. This formula allows enough latitude to permit using 10% tolerance R and C components.

Greater system speed will result if memory wait cycles occur only when necessary, when slow memory devices are being addressed. It is more efficient to install the wait circuitry on any memory (or I/O) board that requires it, and to use the minimum effective delay in every case. Then the memory wait circuit on the 471 CPU board is deactivated, simply by removing the one-shot from its socket.

1.11 *Indicator Lights* The 471 CPU board has two light-emitting diodes which indicate machine status. A red LED glows when memory wait cycles are being performed; the LED is driven by the 8080 WAIT output terminal, through an inverter and open-collector buffer.

 


SEC. 1.11 *INDICATOR LIGHTS* (cont'd.)

Another red LED glows when the 8080 is in the halt condition. The signal \overline{HLT} is derived by the system control logic (Sec. 1.5), driving the LED through a 7417. In order to end the halt, an interrupt must be requested (Sec. 1.8) or the machine must be reset. Recall that if the 8080 interrupt flip-flop is reset, it will not recognize interrupts, and only a reset will end the halt condition (Sec. 1.7).

 1.12 *Power Requirements* The model 471 board requires +12 V at 75 mA maximum, +5 V at 600 mA max., and -12 V at 7 mA. By removing the 1K resistor at R5 (see the CPU section of the schematic), and installing it as R6, the board may be operated from a -9 V supply rather than -12; the current drawn will be 4 mA.

Pins 39 through 50 on the *modular micro* bus are assigned to power supply connections.



This data sheet consists of reprints of literature published by the 8008 manufacturer, Intel Corporation. The 8008/8008-1 microprocessor is the heart of the central processing board of the MIKE 2, a microcomputer available from Martin Research. For replacement purposes, the 8008 is stocked as Part No. 2202, and the 8008-1 as P/N 2203.

SINGLE CHIP EIGHT-BIT PARALLEL CENTRAL PROCESSOR UNIT

- **Instruction Cycle Time** —
12.5 μ s with 8008-1 or 20 μ s with 8008
- **Directly addresses 16K x 8 bits of memory (RAM, ROM, or S.R.)**
- **Interrupt Capability**
- **48 Instructions, Data Oriented**
- **Address stack contains eight 14-bit registers (including program counter) which permit nesting of subroutines up to seven levels**


The 8008 is a single chip MOS 8-bit parallel central processor unit

This CPU contains six 8-bit data registers, an 8-bit accumulator, two 8-bit temporary registers, four flag bits (carry, zero, sign, parity), and an 8-bit parallel binary arithmetic unit which implements addition, subtraction, and logical operations. A memory stack containing a 14-bit program counter and seven 14-bit words is used internally to store program and subroutine addresses. The 14-bit address permits the direct addressing of 16K words of memory (any mix of RAM, ROM or S.R.).

The instruction set of the 8008 consists of 48 instructions including data manipulation, binary arithmetic, and jump to subroutine.


The normal program flow of the 8008 may be interrupted through the use of the INTERRUPT control line. This allows the servicing of slow I/O peripheral devices while also executing the main program.

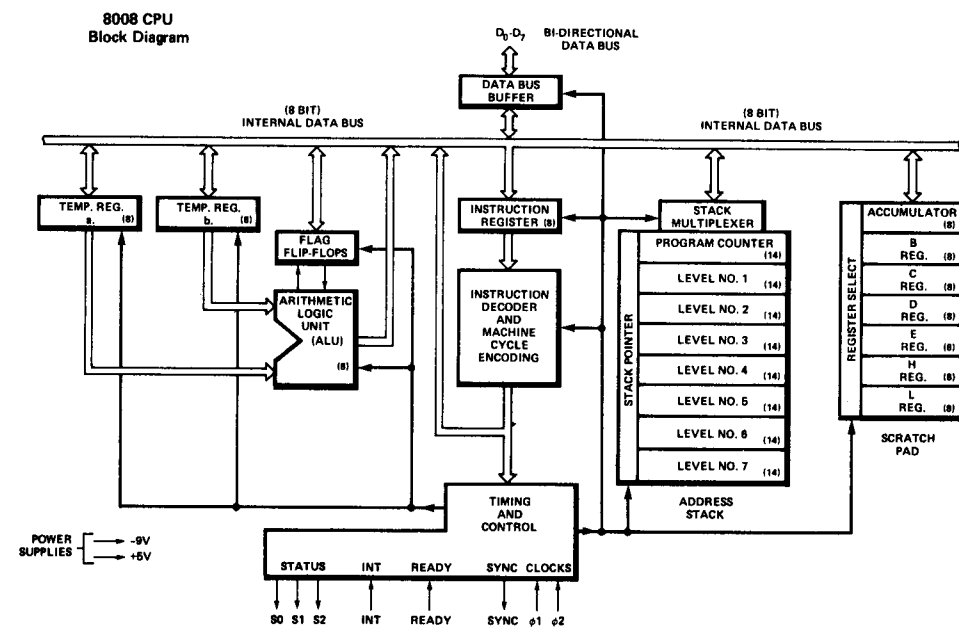The READY command line synchronizes the 8008 to the memory cycle allowing any type or speed of semiconductor memory to be used.



8008

8008 FUNCTIONAL PIN DESCRIPTION

 

D₀-D₇
BI-DIRECTIONAL DATA BUS. All address and data communication between the processor and the program memory, data memory, and I/O devices occurs on these 8 lines. Cycle control information is also available.

INT
INTERRUPT input. A logic "1" level at this input causes the processor to enter the INTERRUPT mode.

READY
READY input. This command line is used to synchronize the 8008 to the memory cycle allowing any speed memory to be used.

SYNC
SYNC output. Synchronization signal generated by the processor. It indicates the beginning of a machine cycle.

ϕ_1, ϕ_2
Two phase clock inputs.

S₀, S₁, S₂
MACHINE STATE OUTPUTS. The processor controls the use of the data bus and determines whether it will be sending or receiving data. State signals S₀, S₁, and S₂, along with SYNC inform the peripheral circuitry of the state of the processor.

V_{CC} +5V ±5%
 V_{DD} -9V ±5%

COPYRIGHT NOTICE

The information in this data sheet has been reprinted with the permission of the copyright holder, Intel Corporation. Copyright © 1973, 1974, 1975, Intel Corp.

PROCESSOR TIMING

The 8008 is a complete central processing unit intended for use in any arithmetic, control, or decision-making system. The internal organization is centered around an 8-bit internal data bus. All communication within the processor and with external components occurs on this bus in the form of 8-bit bytes of address, instruction or data. (Refer to the accompanying block diagram for the relationship of all of the internal elements of the processor to each other and to the data bus.)


A. State Control Coding

The processor controls the use of the data bus and determines whether it will be sending or receiving data. State signals S₀, S₁, and S₂, along with SYNC inform the peripheral circuitry of the state of the processor. A table of the binary state codes and the designated state names is shown below.

| S ₀ | S ₁ | S ₂ | STATE |
|----------------|----------------|----------------|---------|
| 0 | 1 | 0 | T1 |
| 0 | 1 | 1 | T11 |
| 0 | 0 | 1 | T2 |
| 0 | 0 | 0 | WAIT |
| 1 | 0 | 0 | T3 |
| 1 | 1 | 0 | STOPPED |
| 1 | 1 | 1 | T4 |
| 1 | 0 | 1 | T5 |

 B. Timing

Typically, a machine cycle consists of five states, two states in which an address is sent to memory (T1 and T2), one for the instruction or data fetch (T3), and two states for the execution of the instruction (T4 and T5). If the processor is used with slow memories, the READY line synchronizes the processor with the memories. When the memories are not available for either sending or receiving data, the processor goes into the WAIT state. The accompanying diagram illustrates the processor activity during a single cycle.



Basic 8008 Instruction Cycle

8008

The receipt of an INTERRUPT is acknowledged by the T11. When the processor has been interrupted, this state replaces T1. A READY is acknowledged by T3. The STOPPED state acknowledges the receipt of a HALT instruction.

Many of the instructions for the 8008 are multi-cycle and do not require the two execution states, T4 and T5. As a result, these states are omitted when they are not needed and the 8008 operates asynchronously with respect to the cycle length. The external state transition is shown below. Note that the WAIT state and the STOPPED may be indefinite in length (each of these states will be 2n clock periods). The use of READY and INTERRUPT with regard to these states will be explained later.

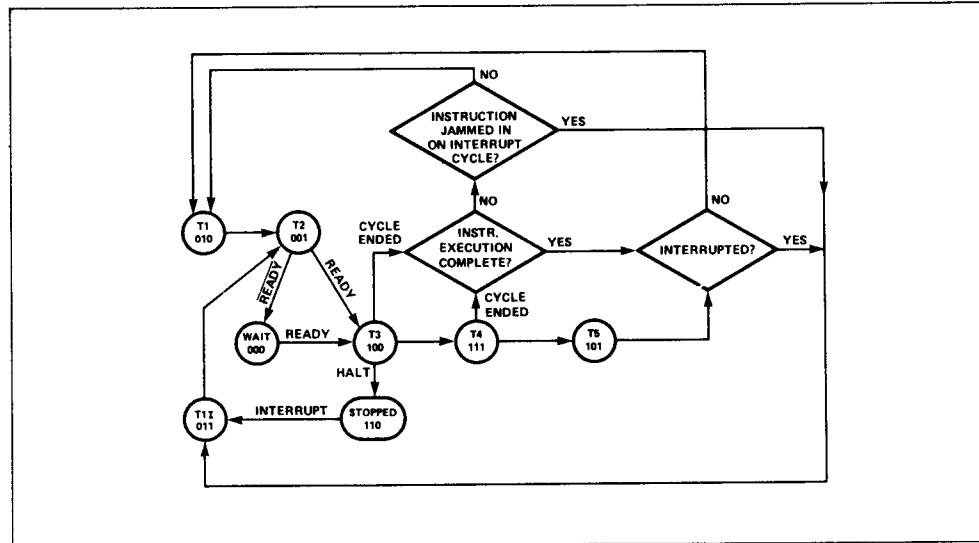


Figure 2. CPU State Transition Diagram

C. Cycle Control Coding

As previously noted, instructions for the 8008 require one, two, or three machine cycles for complete execution. The first cycle is always an instruction fetch cycle (PCI). The second and third cycles are for data reading (PCR), data writing (PCW), or I/O operations (PCC).

The cycle types are coded with two bits, D₆ and D₇, and are only present on the data bus during T2.

| D ₆ | D ₇ | CYCLE | FUNCTION |
|----------------|----------------|-------|---|
| 0 | 0 | PCI | Designates the address is for a memory read (first byte of instruction). |
| 0 | 1 | PCR | Designates the address is for a memory read data (additional bytes of instruction or data). |
| 1 | 0 | PCC | Designates the data as a command I/O operation. |
| 1 | 1 | PCW | Designates the address is for a memory write data. |

BASIC FUNCTIONAL BLOCKS

The four basic functional blocks of this Intel processor are the instruction register, memory, arithmetic logic unit, and I/O buffers. They communicate with each other over the internal 8-bit data bus.

A. Instruction Register and Control

The instruction register is the heart of all processor control. Instructions are fetched from memory, stored in the instruction register, and decoded for control of both the memories and the ALU. Since instruction executions do not all require the same number of states, the instruction decoder also controls the state transitions.

B. Memory

Two separate dynamic memories are used in the 8008, the pushdown address stack and a scratch pad. These internal memories are automatically refreshed by each WAIT, T3, and STOPPED state. In the worst case the memories are completely refreshed every eighty clock periods.

1. Address Stack

The address stack contains eight 14-bit registers providing storage for eight lower and six higher order address bits in each register. One register is used as the program counter (storing the effective address) and the other seven permit address storage for nesting of subroutines up to seven levels. The stack automatically stores the content of the program counter upon the execution of a CALL instruction and automatically restores the program counter upon the execution of a RETURN. The CALLs may be nested and the registers of the stack are used as last in/first out pushdown stack. A three-bit address pointer is used to designate the present location of the program counter. When the capacity of the stack is exceeded the address pointer recycles and the content of the lowest level register is destroyed. The program counter is incremented immediately after the lower order address bits are sent out. The higher order address bits are sent out at T2 and then incremented if a carry resulted from T1. The 14-bit program counter provides direct addressing of 16K bytes of memory. Through the use of an I/O instruction for bank switching, memory may be indefinitely expanded.

2. Scratch Pad Memory or Index Registers

The scratch pad contains the accumulator (A register) and six additional 8-bit registers (B, C, D, E, H, L). All arithmetic operations use the accumulator as one of the operands. All registers are independent and may be used for temporary storage. In the case of instructions which require operations with a register in external memory, scratch pad registers H & L provide indirect addressing capability; register L contains the eight lower order bits of address and register H contains the six higher order bits of address (in this case bit 6 and bit 7 are "don't cares").


C. Arithmetic/Logic Unit (ALU)

All arithmetic and logical operations (ADD, ADD with carry, SUBTRACT, SUBTRACT with borrow, AND, EXCLUSIVE OR, OR, COMPARE, INCREMENT, DECREMENT) are carried out in the 8-bit parallel arithmetic unit which includes carry-look-ahead logic. Two temporary registers, register "a" and register "b", are used to store the accumulator and operand for ALU operations. In addition, they are used for temporary address and data storage during intra-processor transfers. Four control bits, carry flip-flop (c), zero flip-flop (z), sign flip-flop (s), and parity flip-flop (p), are set as the result of each arithmetic and logical operation. These bits provide conditional branching capability through CALL, JUMP, or RETURN on condition instructions. In addition, the carry bit provides the ability to do multiple precision binary arithmetic.

D. I/O Buffer

This buffer is the only link between the processor and the rest of the system. Each of the eight buffers is bi-directional and is under control of the instruction register and state timing. Each of the buffers is low power TTL compatible on the output and TTL compatible on the input.

8008

 


BASIC INSTRUCTION SET

The following section presents the basic instruction set of the 8008.

 A. Data and Instruction Formats


Data in the 8008 is stored in the form of 8-bit binary integers. All data transfers to the system data bus will be in the same format.



DATA WORD


The program instructions may be one, two, or three bytes in length. Multiple byte instructions must be stored in successive words in program memory. The instruction formats then depend on the particular operation executed.

One Byte Instructions

 


OP CODE

Two Byte Instructions

 


OP CODE

 


OPERAND


Three Byte Instructions

 

OP CODE

 

LOW ADDRESS

 

HIGH ADDRESS*

TYPICAL INSTRUCTIONS

Register to register, memory reference, I/O arithmetic or logical, rotate or return instructions

Immediate mode instructions

JUMP or CALL instructions

*For the third byte of this instruction, D₆ and D₇ are "don't care" bits.

B. Summary of Processor Instructions

Index Register Instructions

The load instructions do not affect the flag flip-flops. The increment and decrement instructions affect all flip-flops except the carry.

| MNEMONIC | MINIMUM STATES REQUIRED | INSTRUCTION CODE D ₇ D ₆ D ₅ D ₄ D ₃ D ₂ D ₁ D ₀ | DESCRIPTION OF OPERATION |
|-----------------------------------|-------------------------|--|--|
| (1) L _r r ₂ | (5) | 1 1 D D D S S S | Load index register r ₁ with the content of index register r ₂ . |
| (2) L _r M | (8) | 1 1 D D D 1 1 1 | Load index register r with the content of memory register M. |
| LM _r | (7) | 1 1 1 1 1 S S S | Load memory register M with the content of index register r. |
| (3) L _r i | (8) | 0 0 D D D 1 1 0 B B B B B B B B | Load index register r with data B...B. |
| LMI | (9) | 0 0 1 1 1 1 1 0 B B B B B B B B | Load memory register M with data B...B. |
| IN _r | (5) | 0 0 D D D 0 0 0 | Increment the content of index register r (r ≠ A). |
| DC _r | (5) | 0 0 D D D 0 0 1 | Decrement the content of index register r (r ≠ A). |

Accumulator Group Instructions

The result of the ALU instructions affect all of the flag flip-flops. The rotate instructions affect only the carry flip-flop.

| | | | |
|-----------------|-----|------------------------------------|--|
| AD _r | (5) | 1 0 0 0 0 S S S | Add the content of index register r, memory register M, or data B...B to the accumulator. An overflow (carry) sets the carry flip-flop. |
| ADM | (8) | 1 0 0 0 0 1 1 1 | |
| AD _i | (8) | 0 0 0 0 0 1 0 0 B B B B B B B B | |
| AC _r | (5) | 1 0 0 0 1 S S S | Add the content of index register r, memory register M, or data B...B to the accumulator with carry. An overflow (carry) sets the carry flip-flop. |
| ACM | (8) | 1 0 0 0 1 1 1 1 | |
| AC _i | (8) | 0 0 0 0 1 1 0 0 B B B B B B B B | |
| SU _r | (5) | 1 0 0 1 0 S S S | Subtract the content of index register r, memory register M, or data B...B from the accumulator. An underflow (borrow) sets the carry flip-flop. |
| SUM | (8) | 1 0 0 1 0 1 1 1 | |
| SU _i | (8) | 0 0 0 1 0 1 0 0 B B B B B B B B | |
| SBr | (5) | 1 0 0 1 1 S S S | Subtract the content of index register r, memory register M, or data B...B from the accumulator with borrow. An underflow (borrow) sets the carry flip-flop. |
| SBM | (8) | 1 0 0 1 1 1 1 1 | |
| SBI | (8) | 0 0 0 1 1 1 0 0 B B B B B B B B | |

| MNEMONIC | MINIMUM STATES REQUIRED | INSTRUCTION CODE D ₇ D ₆ D ₅ D ₄ D ₃ D ₂ D ₁ D ₀ | DESCRIPTION OF OPERATION |
|-----------------|-------------------------|--|--|
| ND _r | (5) | 1 0 1 0 0 S S S | Compute the logical AND of the content of index register r, memory register M, or data B...B with the accumulator. |
| NDM | (8) | 1 0 1 0 0 1 1 1 | |
| ND _i | (8) | 0 0 1 0 0 1 0 0 B B B B B B B B | |
| XR _r | (5) | 1 0 1 0 1 S S S | Compute the EXCLUSIVE OR of the content of index register r, memory register M, or data B...B with the accumulator. |
| XRM | (8) | 1 0 1 0 1 1 1 1 | |
| XRI | (8) | 0 0 1 0 1 1 0 0 B B B B B B B B | |
| OR _r | (5) | 1 0 1 1 0 S S S | Compute the INCLUSIVE OR of the content of index register r, memory register m, or data B...B with the accumulator. |
| ORM | (8) | 1 0 1 1 0 1 1 1 | |
| ORI | (8) | 0 0 1 1 0 1 0 0 B B B B B B B B | |
| CP _r | (5) | 1 0 1 1 1 S S S | Compare the content of index register r, memory register M, or data B...B with the accumulator. The content of the accumulator is unchanged. |
| CPM | (8) | 1 0 1 1 1 1 1 1 | |
| CPI | (8) | 0 0 1 1 1 1 0 0 B B B B B B B B | |
| RLC | (5) | 0 0 0 0 0 0 1 0 | Rotate the content of the accumulator left. |
| RRC | (5) | 0 0 0 0 1 0 1 0 | Rotate the content of the accumulator right. |
| RAL | (5) | 0 0 0 1 0 0 1 0 | Rotate the content of the accumulator left through the carry. |
| RAR | (5) | 0 0 0 1 1 0 1 0 | Rotate the content of the accumulator right through the carry. |

Program Counter and Stack Control Instructions

| | | | |
|---------|-----------|---|---|
| (4) JMP | (11) | 0 1 X X X 1 0 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Unconditionally jump to memory address B ₃ ...B ₃ B ₂ ...B ₂ . |
| (5) JFc | (9 or 11) | 0 1 0 C ₄ C ₃ 0 0 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Jump to memory address B ₃ ...B ₃ B ₂ ...B ₂ if the condition flip-flop c is false. Otherwise, execute the next instruction in sequence. |
| JTc | (9 or 11) | 0 1 1 C ₄ C ₃ 0 0 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Jump to memory address B ₃ ...B ₃ B ₂ ...B ₂ if the condition flip-flop c is true. Otherwise, execute the next instruction in sequence. |
| CAL | (11) | 0 1 X X X 1 1 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Unconditionally call the subroutine at memory address B ₃ ...B ₃ B ₂ ...B ₂ . Save the current address (up one level in the stack). |
| CFc | (9 or 11) | 0 1 0 C ₄ C ₃ 0 1 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Call the subroutine at memory address B ₃ ...B ₃ B ₂ ...B ₂ if the condition flip-flop c is false, and save the current address (up one level in the stack). Otherwise, execute the next instruction in sequence. |
| CTc | (9 or 11) | 0 1 1 C ₄ C ₃ 0 1 0 B ₂ B ₂ B ₂ B ₂ B ₂ B ₂ X X B ₃ B ₃ B ₃ B ₃ B ₃ B ₃ | Call the subroutine at memory address B ₃ ...B ₃ B ₂ ...B ₂ if the condition flip-flop c is true, and save the current address (up one level in the stack). Otherwise, execute the next instruction in sequence. |
| RET | (5) | 0 0 X X X 1 1 1 | Unconditionally return (down one level in the stack). |
| RFc | (3 or 5) | 0 0 0 C ₄ C ₃ 0 1 1 | Return (down one level in the stack) if the condition flip-flop c is false. Otherwise, execute the next instruction in sequence. |
| RTc | (3 or 5) | 0 0 1 C ₄ C ₃ 0 1 1 | Return (down one level in the stack) if the condition flip-flop c is true. Otherwise, execute the next instruction in sequence. |
| RST | (5) | 0 0 A A A 1 0 1 | Call the subroutine at memory address AAA000 (up one level in the stack). |

Input/Output Instructions

| | | | |
|-----|-----|-----------------|--|
| INP | (8) | 0 1 0 0 M M M 1 | Read the content of the selected input port (MMM) into the accumulator. |
| OUT | (6) | 0 1 R R M M M 1 | Write the content of the accumulator into the selected output port (RRMMM, RR ≠ 00). |

Machine Instruction

| | | | |
|-----|-----|-----------------|---|
| HLT | (4) | 0 0 0 0 0 0 0 X | Enter the STOPPED state and remain there until interrupted. |
| HLT | (4) | 1 1 1 1 1 1 1 1 | Enter the STOPPED state and remain there until interrupted. |

NOTES:

- (1) SSS = Source Index Register } These registers, r_i, are designated A(accumulator-000),
DDD = Destination Index Register } B(001), C(010), D(011), E(100), H(101), L(110).
- (2) Memory registers are addressed by the contents of registers H & L.
- (3) Additional bytes of instruction are designated by BBBBBBBB.
- (4) X = "Don't Care".
- (5) Flag flip-flops are defined by C₄C₃: carry (00=overflow or underflow), zero (01=result is zero), sign (10=MSB of result is "1"), parity (11=parity is even).

8008


PROCESSOR CONTROL SIGNALS

A. Interrupt Signal (INT)

 1) INTERRUPT REQUEST


If the interrupt line is enabled (Logic "1"), the CPU recognizes an interrupt request at the next instruction fetch (PCI) cycle by outputting $S_0 S_1 S_2 = 011$ at T11 time. The lower and higher order address bytes of the program counter are sent out, but the program counter is not advanced. A successive instruction fetch cycle can be used to insert an arbitrary instruction into the instruction register in the CPU. (If a multi-cycle or multi-byte instruction is inserted, an interrupt need only be inserted for the first cycle.)

When the processor is interrupted, the system INTERRUPT signal must be synchronized with the leading edge of the ϕ_1 or ϕ_2 clock. To assure proper operation of the system, the interrupt line to the CPU must not be allowed to change within 200ns of the falling edge of ϕ_1 .



Recognition of Interrupt

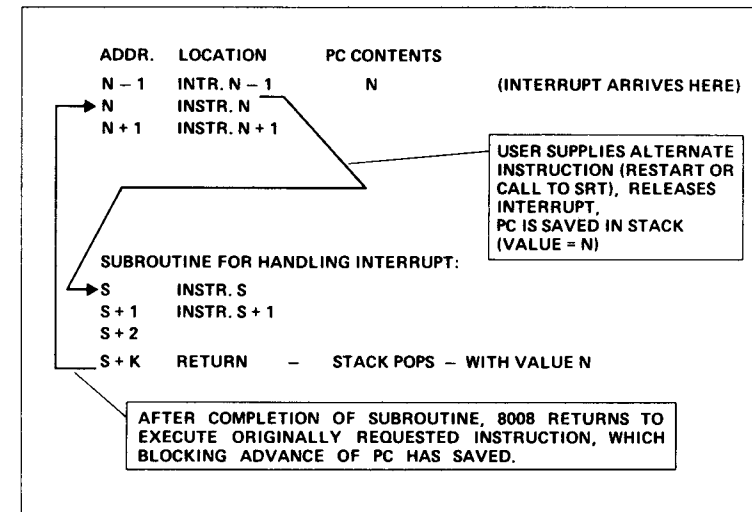If a HALT is inserted, the CPU enters a STOPPED state; if a NOP is inserted, the CPU continues; if a "JUMP to 0" is inserted, the processor executes program from location 0, etc. The RESTART instruction is particularly useful for handling interrupt routines since it is a one byte call.



8008 Interrupt

2) START-UP OF THE 8008

When power (V_{DD}) and clocks (ϕ_1, ϕ_2) are first turned on, a flip-flop internal to the 8008 is set by sensing the rise of V_{DD} . This internal signal forces a HALT (00000000) into the instruction register and the 8008 is then in the STOPPED state. The following sixteen clock periods after entering the STOPPED state are required to clear (logic "0") memories (accumulator, scratch pad, program counter, and stack). During this time the interrupt line has been at logic "0". Any time after the memories are cleared, the 8008 is ready for normal operation.

To reset the flip-flop and also escape from the stopped state, the interrupt line must go to a logic "1"; it should be returned to logic "0" by decoding the state T11 at some time later than ϕ_{11} . Note that whenever the 8008 is in a T11 state, the program counter is not incremented. As a result, the same address is sent out on two successive cycles.

Three possible sequences for starting the 8008 are shown on the following page. The RESTART instruction is effectively a one cycle call instruction, and it is convenient to use this instruction to call an initiation subroutine. Note that it is not necessary to start the 8008 with a RESTART instruction.

The selection of initiation technique to use depends on the sophistication of the system using the 8008. If the interrupt feature is used only for the start-up of the 8008 use the ROM directly, no additional external logic associated with instructions from source other than the ROM program need be considered. If the interrupt feature is used to jam instructions into the 8008, it would then be consistent to use it to jam the initial instruction.

The timing for the interrupt with the start-up timing is shown on an accompanying sheet. The jamming of an instruction and the suppression of the program counter update are handled the same for all interrupts.

8008

EXAMPLE 1:

Shown below are two start-up alternatives where an instruction is not forced into the 8008 during the interrupt cycle. The normal program flow starts the 8008.

| 8008 ADDRESS OUT | INSTRUCTION IN ROM | |
|-----------------------------|----------------------|-------------------------------------|
| 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | NOP (LAA 11 000 000) | } Entry Directly To Main Program |
| 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | NOP | |
| 0 0 0 0 0 0 0 0 0 0 0 0 0 1 | INSTR ₁ | |
| 0 0 0 0 0 0 0 0 0 0 0 1 0 | INSTR ₂ | |

| 8008 ADDRESS OUT | INSTRUCTION IN ROM | |
|-------------------------------|------------------------|---------------------------------|
| 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | RST (RST = 00 XYZ 101) | } A Jump To The Main Program |
| 0 0 0 0 0 0 0 0 X Y Z 0 0 0 0 | INSTR ₁ | |
| 0 0 0 0 0 0 0 0 X Y Z 0 0 0 1 | INSTR ₂ | |

EXAMPLE 2:

A RESTART instruction is jammed in and first instruction in ROM initially ignored.


| 8008 ADDRESS OUT | INSTRUCTION IN ROM | |
|-------------------------------|--|-----------------------|
| 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | INSTR ₁ (RST = 00 XYZ 101) | } Start-up Routine |
| 0 0 0 0 0 0 0 0 X Y Z 0 0 0 0 | INSTR _a | |
| 0 0 0 0 0 0 0 0 X Y Z 0 0 0 1 | INSTR _b | |
| ... | ... | |
| 0 0 0 0 0 0 0 0 n n n n n n | RETURN | } Main Program |
| 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | INSTR ₁ (INSTR ₁ executed now) | |
| 0 0 0 0 0 0 0 0 0 0 0 0 0 1 | INSTR ₂ | |

Note that during the interrupt cycle the flow of the instruction to the 8008 either from ROM or another source must be controlled by hardware external to 8008.

START-UP OF THE 8008

 
B. Ready (RDY)

The 8008 is designed to operate with any type or speed of semiconductor memory. This flexibility is provided by the READY command line. A high-speed memory will always be ready with data (tie READY line to V_{CC}) almost immediately after the second byte of the address has been sent out. As a result the 8008 will never be required to wait for the memory. On the other hand, with slow ROMs, RAMs or shift registers, the data will not be immediately available; the 8008 must wait until the READY command indicates that the valid memory data is available. As a result any type or any combination of memory types may be used. The READY command line synchronizes the 8008 to the memory cycle. When a program is being developed, the READY signal provides a means of stepping through the program, one cycle at a time.




ELECTRICAL SPECIFICATIONS

The following pages provide the electrical characteristics for the 8008. All of the inputs are TTL compatible, but input pull-up resistors are recommended to insure proper V_{IH} levels. All outputs are low-power TTL compatible. The transfer of data to and from the data bus is controlled by the CPU. During both the WAIT and STOPPED states the data bus output buffers are disabled and the data bus is floating.

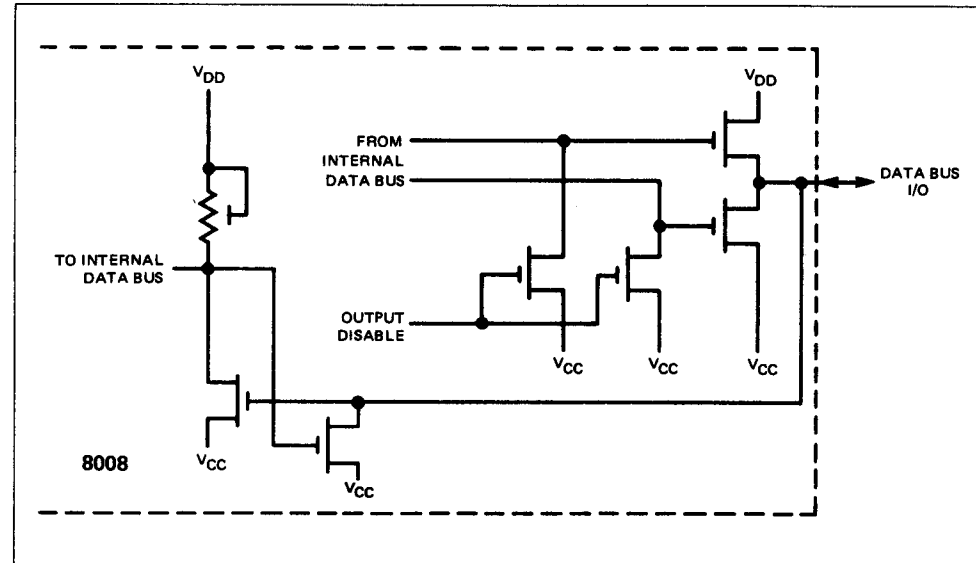

Data Bus I/O Buffer

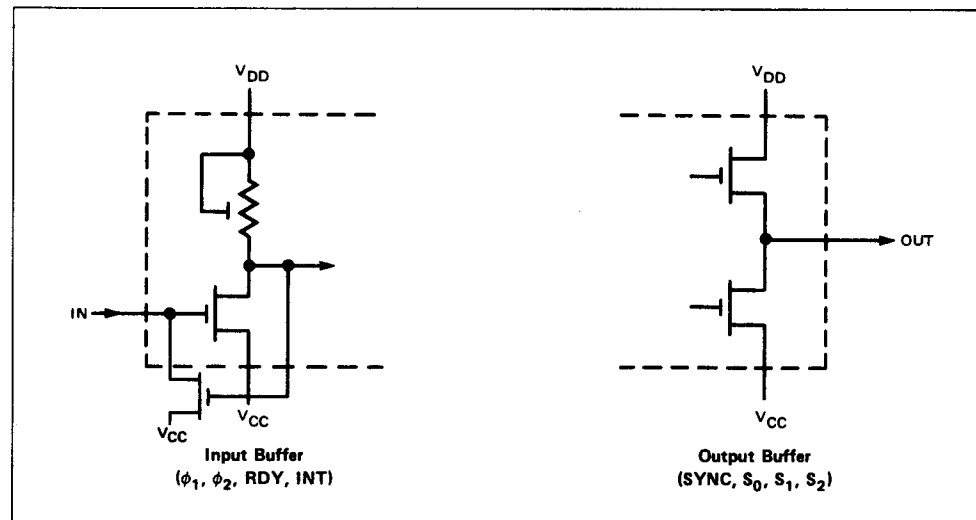

I/O Circuitry

8008

ABSOLUTE MAXIMUM RATINGS*

| | |
|---|-----------------|
| Ambient Temperature Under Bias | 0°C to +70°C |
| Storage Temperature | -55°C to +150°C |
| Input Voltages and Supply Voltage With Respect to V _{CC} | +0.5 to -20V |
| Power Dissipation | 1.0 W @ 25°C |

*COMMENT
Stresses above those listed under "Absolute Maximum Ratings" may cause permanent damage to the device. This is a stress rating only and functional operation of the device at these or any other condition above those indicated in the operational sections of this specification is not implied.

D.C. AND OPERATING CHARACTERISTICS

T_A = 0°C to 70°C, V_{CC} = +5V ±5%, V_{DD} = -9V ±5% unless otherwise specified. Logic "1" is defined as the more positive level (V_{IH}, V_{OH}). Logic "0" is defined as the more negative level (V_{IL}, V_{OL}).

| SYMBOL | PARAMETER | LIMITS | | | UNIT | TEST CONDITIONS |
|-----------------|--|----------------------|------|----------------------|------|---|
| | | MIN. | TYP. | MAX. | | |
| I _{DD} | AVERAGE SUPPLY CURRENT-OUTPUTS LOADED* | | 30 | 80 | mA | T _A = 25°C |
| I _{L1} | INPUT LEAKAGE CURRENT | | | 10 | μA | V _{IN} = 0V |
| V _{IL} | INPUT LOW VOLTAGE (INCLUDING CLOCKS) | V _{DD} | | V _{CC} -4.2 | V | |
| V _{IH} | INPUT HIGH VOLTAGE (INCLUDING CLOCKS) | V _{CC} -1.5 | | V _{CC} +0.3 | V | |
| V _{OL} | OUTPUT LOW VOLTAGE | | | 0.4 | V | I _{OL} = 0.44mA C _L = 200 pF |
| V _{OH} | OUTPUT HIGH VOLTAGE | V _{CC} -1.5 | | | V | I _{OH} = 0.2mA |

*Measurements are made while the 8008 is executing a typical sequence of instructions. The test load is selected such that at V_{OL} = 0.4V, I_{OL} = 0.44mA on each output.


A.C. CHARACTERISTICS

T_A = 0°C to 70°C; V_{CC} = +5V ±5%, V_{DD} = -9V ±5%. All measurements are referenced to 1.5V levels.

| SYMBOL | PARAMETER | 8008 | | 8008-1 | | UNIT | TEST CONDITIONS |
|---------------------------------|---|--------|------|--------|------|------|--|
| | | LIMITS | | LIMITS | | | |
| | | MIN. | MAX. | MIN. | MAX. | | |
| t _{CY} | CLOCK PERIOD | 2 | 3 | 1.25 | 3 | μs | t _R , t _F = 50ns |
| t _R , t _F | CLOCK RISE AND FALL TIMES | | 50 | | 50 | ns | |
| t _{φ1} | PULSE WIDTH OF φ ₁ | .70 | | .35 | | μs | |
| t _{φ2} | PULSE WIDTH OF φ ₂ | .55 | | .35 | | μs | |
| t _{D1} | CLOCK DELAY FROM FALLING EDGE OF φ ₁ TO FALLING EDGE OF φ ₂ | .90 | 1.1 | | 1.1 | μs | |
| t _{D2} | CLOCK DELAY FROM φ ₂ TO φ ₁ | .40 | | .35 | | μs | |
| t _{D3} | CLOCK DELAY FROM φ ₁ TO φ ₂ | .20 | | .20 | | μs | |
| t _{DD} | DATA OUT DELAY | | 1.0 | | 1.0 | μs | C _L = 100pF |
| t _{OH} | HOLD TIME FOR DATA BUS OUT | .10 | | .10 | | μs | |
| t _{IH} | HOLD TIME FOR DATA IN | [1] | | [1] | | μs | |
| t _{SD} | SYNC OUT DELAY | | .70 | | .70 | μs | C _L = 100pF |
| t _{S1} | STATE OUT DELAY (ALL STATES EXCEPT T1 AND T11) [2] | | 1.1 | | 1.1 | μs | C _L = 100pF |
| t _{S2} | STATE OUT DELAY (STATES T1 AND T11) | | 1.0 | | 1.0 | μs | C _L = 100pF |
| t _{RW} | PULSE WIDTH OF READY DURING φ ₂₂ TO ENTER T3 STATE | .35 | | .35 | | μs | |
| t _{RD} | READY DELAY TO ENTER WAIT STATE | .20 | | .20 | | μs | |


[1] t_{IH} MIN ≥ t_{SD} [2] If the INTERRUPT is not used, all states have the same output delay, t_{S1}.

TIMING DIAGRAM

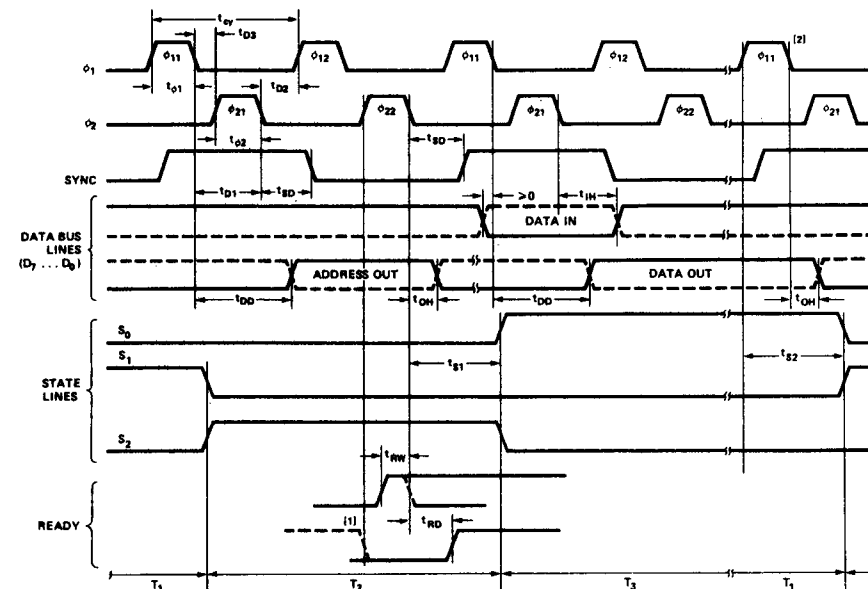


- Notes: 1. READY line must be at "0" prior to φ₂₂ of T₂ to guarantee entry into the WAIT state.
2. INTERRUPT line must not change levels within 200ns (max.) of falling edge of φ₁.

TYPICAL D.C. CHARACTERISTICS

 


8008

TYPICAL A.C. CHARACTERISTICS

 

CAPACITANCE f = 1MHz; T_A = 25°C; Unmeasured Pins Grounded

| SYMBOL | TEST | LIMIT (pF) | |
|------------------|--------------------------|------------|------|
| | | TYP. | MAX. |
| C _{IN} | INPUT CAPACITANCE | 5 | 10 |
| C _{DB} | DATA BUS I/O CAPACITANCE | 5 | 10 |
| C _{OUT} | OUTPUT CAPACITANCE | 5 | 10 |

 

8008 Photomicrograph With Pin Designations

This data sheet reprints literature published by Intel Corporation. The 8080A, part number 2204, is the heart of the MIKE 3 microcomputer from Martin Research.

ARCHITECTURE OF THE 8080 CPU

The 8080 CPU consists of the following functional units:

- Register array and address logic
- Arithmetic and logic unit (ALU)
- Instruction register and control section
- Bi-directional, 3-state data bus buffer

atically during every instruction fetch. The stack pointer maintains the address of the next available stack location in memory. The stack pointer can be initialized to use any portion of read-write memory as a stack. The stack pointer is decremented when data is "pushed" onto the stack and incremented when data is "popped" off the stack (i.e., the stack grows "downward").


The six general purpose registers can be used either as single registers (8-bit) or as register pairs (16-bit). The temporary register pair, W,Z, is not program addressable and is only used for the internal execution of instructions.

Registers:

The register section consists of a static RAM array organized into six 16-bit registers:

- Program counter (PC)
- Stack pointer (SP)
- Six 8-bit general purpose registers arranged in pairs, referred to as B,C; D,E; and H,L
- A temporary register pair called W,Z

Eight-bit data bytes can be transferred between the internal bus and the register array via the register-select multiplexer. Sixteen-bit transfers can proceed between the register array and the address latch or the incrementer/decrementer circuit. The address latch receives data from any of the three register pairs and drives the 16 address output buffers (A₀-A₁₅), as well as the incrementer/decrementer circuit. The incrementer/decrementer circuit receives data from the address latch and sends it to the register array. The 16-bit data can be incremented or decremented or simply transferred between registers.

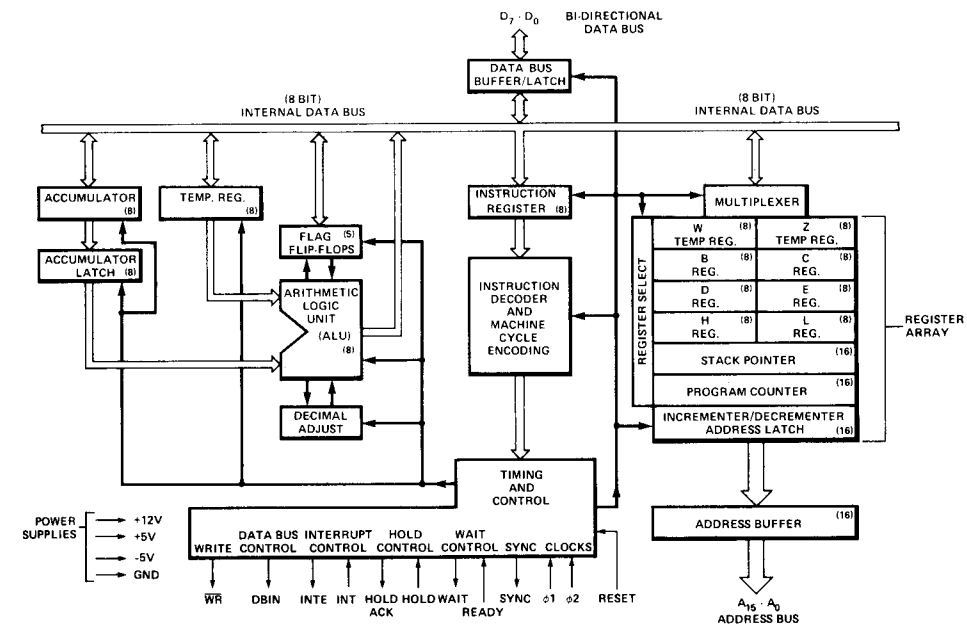

8080 CPU Functional Block Diagram

8080

Arithmetic and Logic Unit (ALU):

The ALU contains the following registers:

- An 8-bit accumulator
- An 8-bit temporary accumulator (ACT)
- A 5-bit flag register: zero, carry, sign, parity and auxiliary carry
- An 8-bit temporary register (TMP)

Arithmetic, logical and rotate operations are performed in the ALU. The ALU is fed by the temporary register (TMP) and the temporary accumulator (ACT) and carry flip-flop. The result of the operation can be transferred to the internal bus or to the accumulator; the ALU also feeds the flag register.

The temporary register (TMP) receives information from the internal bus and can send all or portions of it to the ALU, the flag register and the internal bus.

The accumulator (ACC) can be loaded from the ALU and the internal bus and can transfer data to the temporary accumulator (ACT) and the internal bus. The contents of the accumulator (ACC) and the auxiliary carry flip-flop can be tested for decimal correction during the execution of the DAA instruction.

Instruction Register and Control:

During an instruction fetch, the first byte of an instruction (containing the OP code) is transferred from the internal bus to the 8-bit instruction register.

The contents of the instruction register are, in turn, available to the instruction decoder. The output of the decoder, combined with various timing signals, provides the control signals for the register array, ALU and data buffer blocks. In addition, the outputs from the instruction decoder and external control signals feed the timing and state control section which generates the state and cycle timing signals.

Data Bus Buffer:

This 8-bit bidirectional 3-state buffer is used to isolate the CPU's internal bus from the external data bus (D₀ through D₇). In the output mode, the internal bus content is loaded into an 8-bit latch that, in turn, drives the data bus output buffers. The output buffers are switched off during input or non-transfer operations.


During the input mode, data from the external data bus is transferred to the internal bus. The internal bus is pre-charged at the beginning of each internal state, except for the transfer state T₃—described later.

THE PROCESSOR CYCLE:

An **instruction cycle** is defined as the time required to fetch and execute an instruction. During the fetch, a selected instruction (one, two or three bytes) is extracted from memory and deposited in the CPU's instruction register. During the execution phase, the instruction is decoded and translated into specific processing activities.

Every instruction cycle consists of one, two, three, four or five machine cycles. A **machine cycle** is required each time the CPU accesses memory or an I/O port. The fetch portion of an instruction cycle requires one machine cycle for each byte to be fetched. The duration of the execution portion of the instruction cycle depends on the kind of instruction that has been fetched. Some instructions do not require any machine cycles other than those necessary to fetch the instruction; other instructions, however, require additional machine cycles to write or read data to/from memory or I/O devices. The DAD instruction is an exception in that it requires two additional machine cycles to complete an internal register-pair add.

Each machine cycle consists of three, four or five states. A state is the smallest unit of processing activity and is defined as the interval between two successive positive-going transitions of the ϕ_1 driven clock pulse. The 8080 is driven by a two-phase clock oscillator. All processing activities are referred to the period of this clock. The two non-overlapping clock pulses, labeled ϕ_1 and ϕ_2 , are furnished by external circuitry. It is the ϕ_1 clock pulse which divides each machine cycle into states. Timing logic within the 8080 uses the clock inputs to produce a SYNC pulse, which identifies the beginning of every machine cycle. The SYNC pulse is triggered by the low-to-high transition of ϕ_2 .

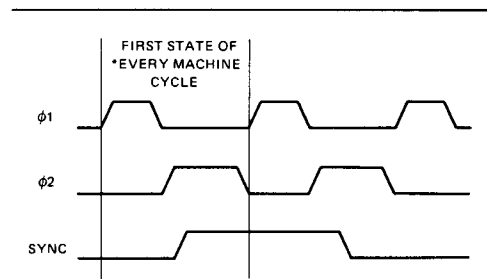

*SYNC DOES NOT OCCUR IN THE SECOND AND THIRD MACHINE CYCLES OF A DAD INSTRUCTION SINCE THESE MACHINE CYCLES ARE USED FOR AN INTERNAL REGISTER-PAIR ADD.

ϕ_1, ϕ_2 And SYNC Timing

There are three exceptions to the defined duration of a state. They are the WAIT state, the hold (HLDA) state and the halt (HLTA) state, described later in this chapter. Because the WAIT, the HLDA, and the HLTA states depend upon external events, they are by their nature of indeterminate length. Even these exceptional states, however, must

be synchronized with the pulses of the driving clock. Thus, the duration of all states are integral multiples of the clock period.

To summarize then, each clock period marks a state; three to five states constitute a machine cycle; and one to five machine cycles comprise an instruction cycle. A full instruction cycle requires anywhere from four to eighteen states for its completion, depending on the kind of instruction involved.

Machine Cycle Identification:

With the exception of the DAD instruction, there is just one consideration that determines how many machine cycles are required in any given instruction cycle: the number of times that the processor must reference a memory address or an addressable peripheral device, in order to fetch and execute the instruction. Like many processors, the 8080 is so constructed that it can transmit only one address per machine cycle. Thus, if the fetch and execution of an instruction requires two memory references, then the instruction cycle associated with that instruction consists of two machine cycles. If five such references are called for, then the instruction cycle contains five machine cycles.

Every instruction cycle has at least one reference to memory, during which the instruction is fetched. An instruction cycle must always have a fetch, even if the execution of the instruction requires no further references to memory. The first machine cycle in every instruction cycle is therefore a FETCH. Beyond that, there are no fast rules. It depends on the kind of instruction that is fetched.

Consider some examples. The add-register (ADD r) instruction is an instruction that requires only a single machine cycle (FETCH) for its completion. In this one-byte instruction, the contents of one of the CPU's six general purpose registers is added to the existing contents of the accumulator. Since all the information necessary to execute the command is contained in the eight bits of the instruction code, only one memory reference is necessary. Three states are used to extract the instruction from memory, and one additional state is used to accomplish the desired addition. The entire instruction cycle thus requires only one machine cycle that consists of four states, or four periods of the external clock.

Suppose now, however, that we wish to add the contents of a specific memory location to the existing contents of the accumulator (ADD M). Although this is quite similar in principle to the example just cited, several additional steps will be used. An extra machine cycle will be used, in order to address the desired memory location.

The actual sequence is as follows. First the processor extracts from memory the one-byte instruction word addressed by its program counter. This takes three states. The eight-bit instruction word obtained during the FETCH machine cycle is deposited in the CPU's instruction register and used to direct activities during the remainder of the instruction cycle. Next, the processor sends out, as an address,

the contents of its H and L registers. The eight-bit data word returned during this MEMORY READ machine cycle is placed in a temporary register inside the 8080 CPU. By now three more clock periods (states) have elapsed. In the seventh and final state, the contents of the temporary register are added to those of the accumulator. Two machine cycles, consisting of seven states in all, complete the "ADD M" instruction cycle.


At the opposite extreme is the save H and L registers (SHLD) instruction, which requires five machine cycles. During an "SHLD" instruction cycle, the contents of the processor's H and L registers are deposited in two sequentially adjacent memory locations; the destination is indicated by two address bytes which are stored in the two memory locations immediately following the operation code byte. The following sequence of events occurs:

- (1) A FETCH machine cycle, consisting of four states. During the first three states of this machine cycle, the processor fetches the instruction indicated by its program counter. The program counter is then incremented. The fourth state is used for internal instruction decoding.
- (2) A MEMORY READ machine cycle, consisting of three states. During this machine cycle, the byte indicated by the program counter is read from memory and placed in the processor's Z register. The program counter is incremented again.
- (3) Another MEMORY READ machine cycle, consisting of three states, in which the byte indicated by the processor's program counter is read from memory and placed in the W register. The program counter is incremented, in anticipation of the next instruction fetch.
- (4) A MEMORY WRITE machine cycle, of three states, in which the contents of the L register are transferred to the memory location pointed to by the present contents of the W and Z registers. The state following the transfer is used to increment the W,Z register pair so that it indicates the next memory location to receive data.
- (5) A MEMORY WRITE machine cycle, of three states, in which the contents of the H register are transferred to the new memory location pointed to by the W,Z register pair.

In summary, the "SHLD" instruction cycle contains five machine cycles and takes 16 states to execute.

Most instructions fall somewhere between the extremes typified by the "ADD r" and the "SHLD" instructions. The input (INP) and the output (OUT) instructions, for example, require three machine cycles: a FETCH, to obtain the instruction; a MEMORY READ, to obtain the address of the object peripheral; and an INPUT or an OUTPUT machine cycle, to complete the transfer.

8080

 

While no one instruction cycle will consist of more than five machine cycles, the following ten different types of machine cycles may occur within an instruction cycle:

- (1) FETCH (M1)
- (2) MEMORY READ
- (3) MEMORY WRITE
- (4) STACK READ
- (5) STACK WRITE
- (6) INPUT
- (7) OUTPUT
- (8) INTERRUPT
- (9) HALT
- (10) HALT • INTERRUPT

The machine cycles that actually do occur in a particular instruction cycle depend upon the kind of instruction, with the overriding stipulation that the first machine cycle in any instruction cycle is always a FETCH.

The processor identifies the machine cycle in progress by transmitting an eight-bit status word during the first state of every machine cycle. Updated status information is presented on the 8080's data lines (D₀-D₇), during the SYNC interval. This data should be saved in latches, and used to develop control signals for external circuitry. Table 2-1 shows how the positive-true status information is distributed on the processor's data bus.

Status signals are provided principally for the control of external circuitry. Simplicity of interface, rather than machine cycle identification, dictates the logical definition of individual status bits. You will therefore observe that certain processor machine cycles are uniquely identified by a single status bit, but that others are not. The M₁ status bit (D₅), for example, unambiguously identifies a FETCH machine cycle. A STACK READ, on the other hand, is indicated by the coincidence of STACK and MEMR signals. Machine cycle identification data is also valuable in the test and debugging phases of system development. Table 2-1 lists the status bit outputs for each type of machine cycle.

State Transition Sequence:

Every machine cycle within an instruction cycle consists of three to five active states (referred to as T₁, T₂, T₃, T₄, T₅ or T_W). The actual number of states depends upon the instruction being executed, and on the particular machine cycle within the greater instruction cycle. The state transition diagram in Figure 2-4 shows how the 8080 proceeds from state to state in the course of a machine cycle. The diagram also shows how the READY, HOLD, and INTERRUPT lines are sampled during the machine cycle, and how the conditions on these lines may modify the

basic transition sequence. In the present discussion, we are concerned only with the basic sequence and with the READY function. The HOLD and INTERRUPT functions will be discussed later.

The 8080 CPU does not directly indicate its internal state by transmitting a "state control" output during each state; instead, the 8080 supplies direct control output (INTE, HLDA, DBIN, WR and WAIT) for use by external circuitry.

Recall that the 8080 passes through at least three states in every machine cycle, with each state defined by successive low-to-high transitions of the ϕ_1 clock. Figure 2-5 shows the timing relationships in a typical FETCH machine cycle. Events that occur in each state are referenced to transitions of the ϕ_1 and ϕ_2 clock pulses.

The SYNC signal identifies the first state (T₁) in every machine cycle. As shown in Figure 2-5, the SYNC signal is related to the leading edge of the ϕ_2 clock. There is a delay (t_{DC}) between the low-to-high transition of ϕ_2 and the positive-going edge of the SYNC pulse. There also is a corresponding delay (also t_{DC}) between the next ϕ_2 pulse and the falling edge of the SYNC signal. Status information is displayed on D₀-D₇ during the same ϕ_2 to ϕ_2 interval. Switching of the status signals is likewise controlled by ϕ_2 .

The rising edge of ϕ_2 during T₁ also loads the processor's address lines (A₀-A₁₅). These lines become stable within a brief delay (t_{DA}) of the ϕ_2 clocking pulse, and they remain stable until the first ϕ_2 pulse after state T₃. This gives the processor ample time to read the data returned from memory.

Once the processor has sent an address to memory, there is an opportunity for the memory to request a WAIT. This it does by pulling the processor's READY line low, prior to the "Ready set-up" interval (t_{RS}) which occurs during the ϕ_2 pulse within state T₂ or T_W. As long as the READY line remains low, the processor will idle, giving the memory time to respond to the addressed data request. Refer to Figure 2-5.

The processor responds to a wait request by entering an alternative state (T_W) at the end of T₂, rather than proceeding directly to the T₃ state. Entry into the T_W state is indicated by a WAIT signal from the processor, acknowledging the memory's request. A low-to-high transition on the WAIT line is triggered by the rising edge of the ϕ_1 clock and occurs within a brief delay (t_{DC}) of the actual entry into the T_W state.


A wait period may be of indefinite duration. The processor remains in the waiting condition until its READY line again goes high. A READY indication must precede the falling edge of the ϕ_2 clock by a specified interval (t_{RS}), in order to guarantee an exit from the T_W state. The cycle may then proceed, beginning with the rising edge of the next ϕ_1 clock. A WAIT interval will therefore consist of an integral number of T_W states and will always be a multiple of the clock period.

Instructions for the 8080 require from one to five machine cycles for complete execution. The 8080 sends out 8 bit of status information on the data bus at the beginning of each machine cycle (during SYNC time). The following table defines the status information.

STATUS INFORMATION DEFINITION

| Symbol | Bit | Definition |
|-----------------|----------------|--|
| INTA* | D ₀ | Acknowledge signal for INTERRUPT request. Signal should be used to gate a restart instruction onto the data bus when DBIN is active. |
| \overline{WO} | D ₁ | Indicates that the operation in the current machine cycle will be a WRITE memory or OUTPUT function ($\overline{WO} = 0$). Otherwise, a READ memory or INPUT operation will be executed. |
| STACK | D ₂ | Indicates that the address bus holds the pushdown stack address from the Stack Pointer. |
| HLTA | D ₃ | Acknowledge signal for HALT instruction. |
| OUT | D ₄ | Indicates that the address bus contains the address of an output device and the data bus will contain the output data when WR is active. |
| M ₁ | D ₅ | Provides a signal to indicate that the CPU is in the fetch cycle for the first byte of an instruction. |
| INP* | D ₆ | Indicates that the address bus contains the address of an input device and the input data should be placed on the data bus when DBIN is active. |
| MEMR* | D ₇ | Designates that the data bus will be used for memory read data. |

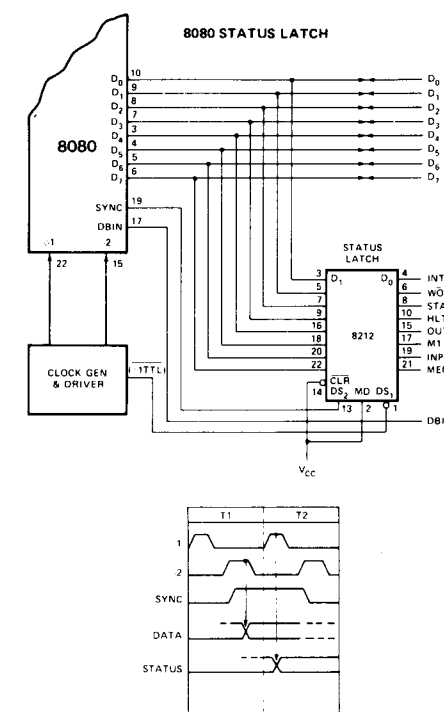
*These three status bits can be used to control the flow of data onto the 8080 data bus.



STATUS WORD CHART

| DATA BUS BIT | | TYPE OF MACHINE CYCLE | | | | | | | | | |
|----------------|-----------------|-----------------------|---|---|---|---|---|---|---|---|---|
| | | ① | ② | ③ | ④ | ⑤ | ⑥ | ⑦ | ⑧ | ⑨ | ⑩ |
| D ₀ | INTA | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| D ₁ | \overline{WO} | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| D ₂ | STACK | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| D ₃ | HLTA | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| D ₄ | OUT | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| D ₅ | M ₁ | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| D ₆ | INP | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| D ₇ | MEMR | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |

Table 2-1. 8080 Status Bit Definitions

 

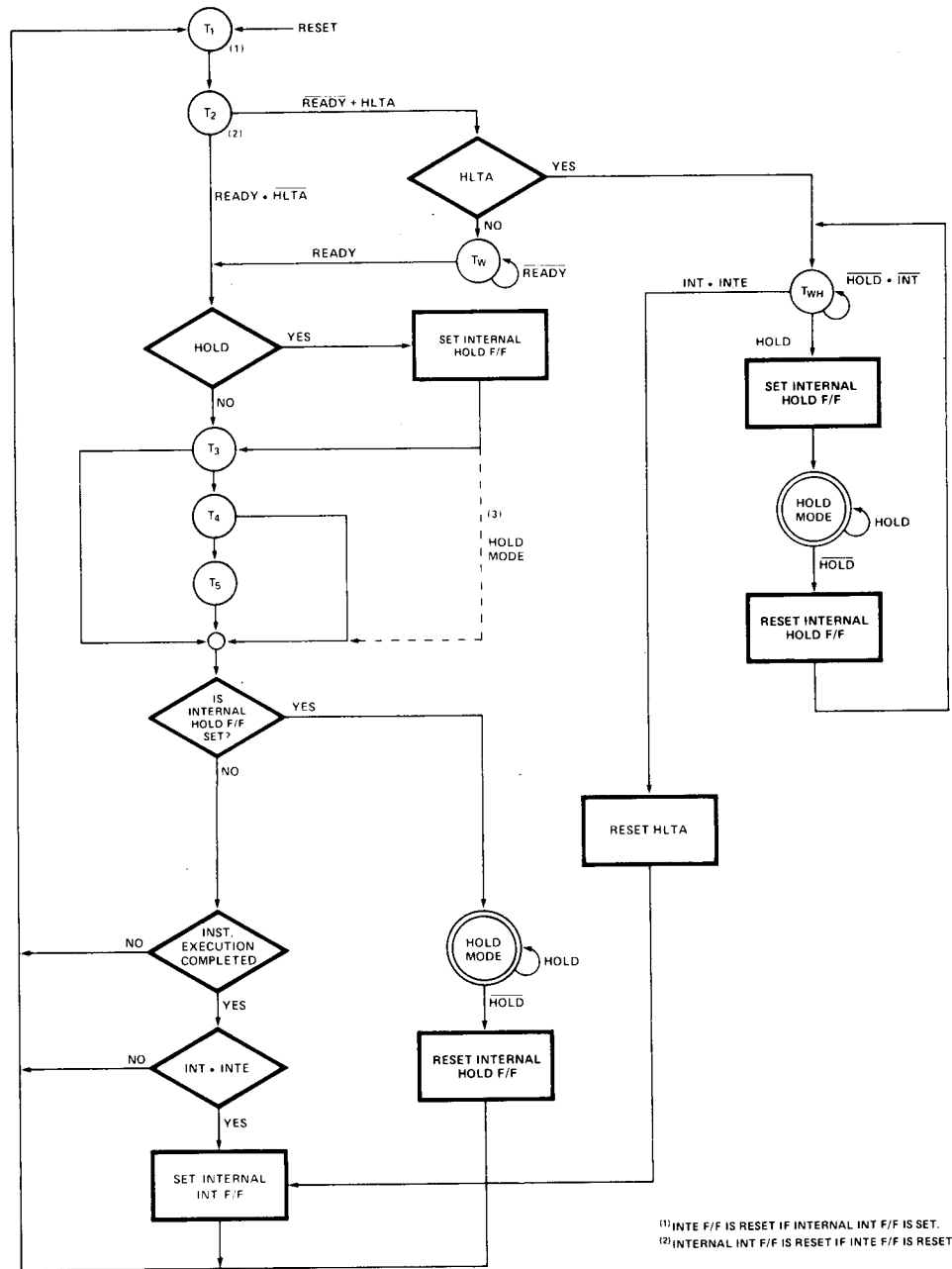


Figure 2-4. CPU State Transition Diagram


The events that take place during the T₃ state are determined by the kind of machine cycle in progress. In a FETCH machine cycle, the processor interprets the data on its data bus as an instruction. During a MEMORY READ or a STACK READ, data on this bus is interpreted as a data word. The processor outputs data on this bus during a MEMORY WRITE machine cycle. During I/O operations, the processor may either transmit or receive data, depending on whether an OUTPUT or an INPUT operation is involved.

Figure 2-6 illustrates the timing that is characteristic of a data input operation. As shown, the low-to-high transition of ϕ_2 during T₂ clears status information from the processor's data lines, preparing these lines for the receipt of incoming data. The data presented to the processor must have stabilized prior to both the " ϕ_1 -data set-up" interval (t_{DS1}), that precedes the falling edge of the ϕ_1 pulse defining state T₃, and the " ϕ_2 -data set-up" interval (t_{DS2}), that precedes the rising edge of ϕ_2 in state T₃. This same

data must remain stable during the "data hold" interval (t_{DH}) that occurs following the rising edge of the ϕ_2 pulse. Data placed on these lines by memory or by other external devices will be sampled during T₃.

During the input of data to the processor, the 8080 generates a DBIN signal which should be used externally to enable the transfer. Machine cycles in which DBIN is available include: FETCH, MEMORY READ, STACK READ, and INTERRUPT. DBIN is initiated by the rising edge of ϕ_2 during state T₂ and terminated by the corresponding edge of ϕ_2 during T₃. Any T_W phases intervening between T₂ and T₃ will therefore extend DBIN by one or more clock periods.

Figure 2-7 shows the timing of a machine cycle in which the processor outputs data. Output data may be destined either for memory or for peripherals. The rising edge of ϕ_2 within state T₂ clears status information from the CPU's data lines, and loads in the data which is to be output to external devices. This substitution takes place within the

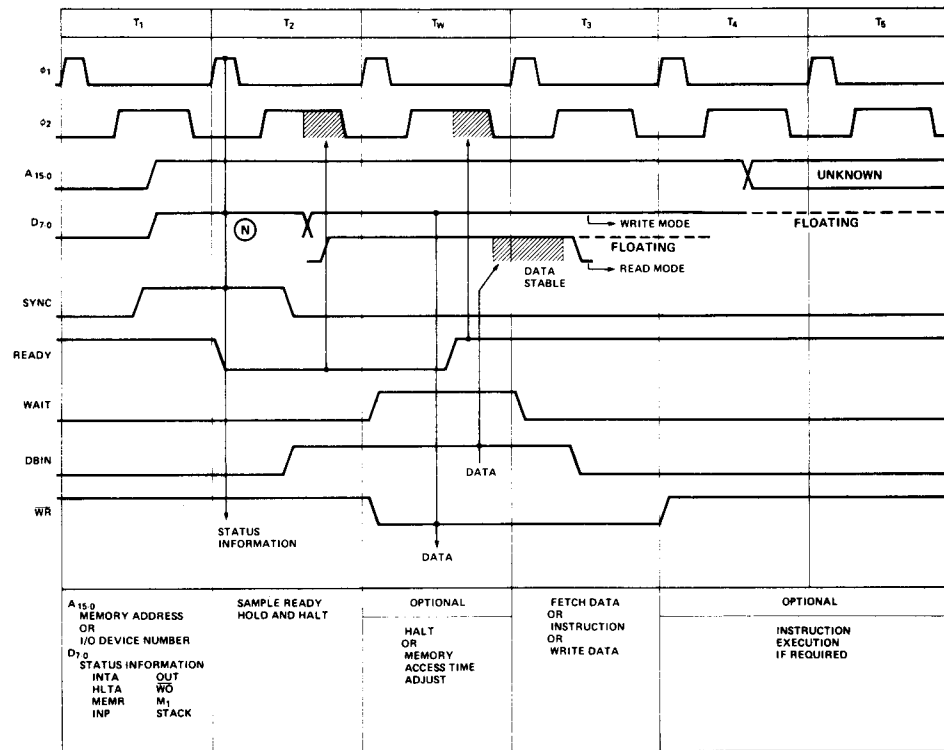

NOTE: (N) Refer to Status Word Chart

Figure 2-5. Basic 8080 Instruction Cycle

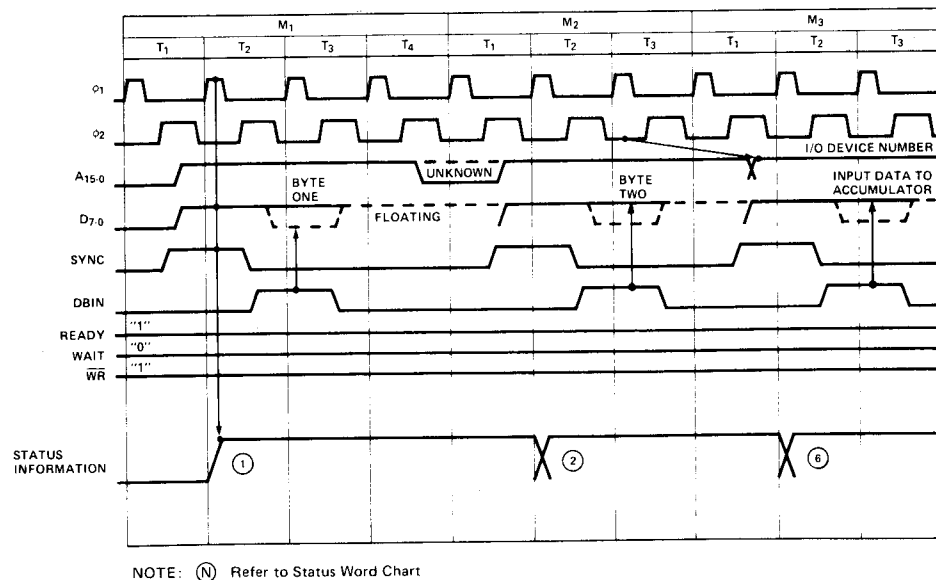


Figure 2-6. Input Instruction Cycle

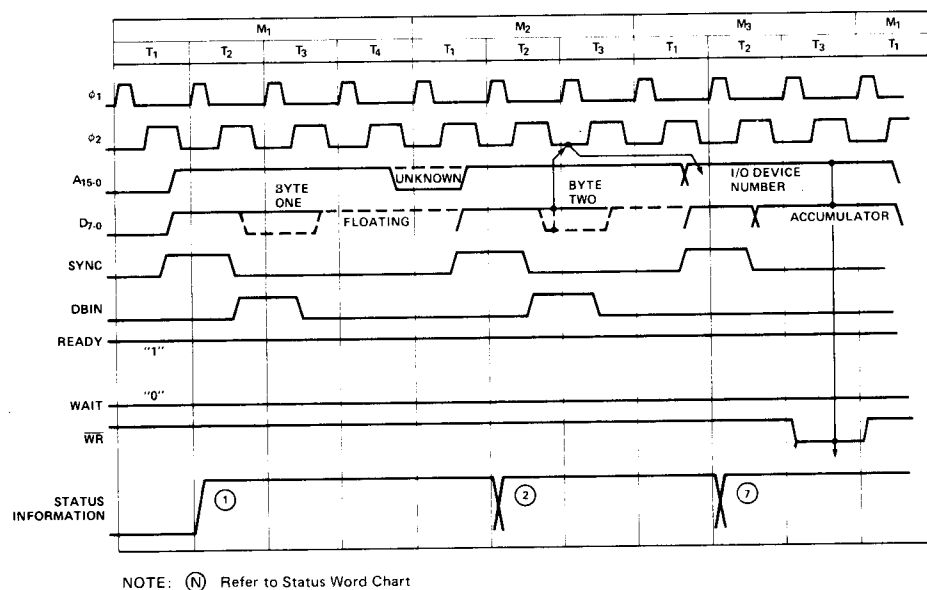


Figure 2-7. Output Instruction Cycle

“data output delay” interval (t_{DD}) following the ϕ_2 clock’s leading edge. Data on the bus remains stable throughout the remainder of the machine cycle, until replaced by updated status information in the subsequent T_1 state. Observe that a $READY$ signal is necessary for completion of an OUTPUT machine cycle. Unless such an indication is present, the processor enters the T_W state, following the T_2 state. Data on the output lines remains stable in the interim, and the processing cycle will not proceed until the $READY$ line again goes high.

The 8080 CPU generates a \overline{WR} output for the synchronization of external transfers, during those machine cycles in which the processor outputs data. These include MEMORY WRITE, STACK WRITE, and OUTPUT. The negative-going leading edge of \overline{WR} is referenced to the rising edge of the first ϕ_1 clock pulse following T_2 , and occurs within a brief delay (t_{DC}) of that event. \overline{WR} remains low until re-triggered by the leading edge of ϕ_1 during the state following T_3 . Note that any T_W states intervening between T_2 and T_3 of the output machine cycle will neces-

sarily extend \overline{WR} , in much the same way that $DBIN$ is affected during data input operations.

All processor machine cycles consist of at least three states: T_1 , T_2 , and T_3 as just described. If the processor has to wait for a response from the peripheral or memory with which it is communicating, then the machine cycle may also contain one or more T_W states. During the three basic states, data is transferred to or from the processor.

After the T_3 state, however, it becomes difficult to generalize. T_4 and T_5 states are available, if the execution of a particular instruction requires them. But not all machine cycles make use of these states. It depends upon the kind of instruction being executed, and on the particular machine cycle within the instruction cycle. The processor will terminate any machine cycle as soon as its processing activities are completed, rather than proceeding through the T_4 and T_5 states every time. Thus the 8080 may exit a machine cycle following the T_3 , the T_4 , or the T_5 state and proceed directly to the T_1 state of the next machine cycle.

| STATE | ASSOCIATED ACTIVITIES |
|---------------------------|--|
| T_1 | A memory address or I/O device number is placed on the Address Bus (A_{15-0}); status information is placed on Data Bus (D_{7-0}). |
| T_2 | The CPU samples the $READY$ and $HOLD$ inputs and checks for halt instruction. |
| T_W (optional) | Processor enters wait state if $READY$ is low or if $HALT$ instruction has been executed. |
| T_3 | An instruction byte (FETCH machine cycle), data byte (MEMORY READ, STACK READ) or interrupt instruction (INTERRUPT machine cycle) is input to the CPU from the Data Bus; or a data byte (MEMORY WRITE, STACK WRITE or OUTPUT machine cycle) is output onto the data bus. |
| T_4 T_5 (optional) | States T_4 and T_5 are available if the execution of a particular instruction requires them; if not, the CPU may skip one or both of them. T_4 and T_5 are only used for internal processor operations. |

Table 2-2. State Definitions

8080

INTERRUPT SEQUENCES

The 8080 has the built-in capacity to handle external interrupt requests. A peripheral device can initiate an interrupt simply by driving the processor's interrupt (INT) line high.


The interrupt (INT) input is asynchronous, and a request may therefore originate at any time during any instruction cycle. Internal logic re-clocks the external request, so that a proper correspondence with the driving clock is established. As Figure 2-8 shows, an interrupt request (INT) arriving during the time that the interrupt enable line (INTE) is high, acts in coincidence with the ϕ_2 clock to set the internal interrupt latch. This event takes place during the last state of the instruction cycle in which the request occurs, thus ensuring that any instruction in progress is completed before the interrupt can be processed.

The INTERRUPT machine cycle which follows the arrival of an enabled interrupt request resembles an ordinary FETCH machine cycle in most respects. The M_1 status bit is transmitted as usual during the SYNC interval. It is accompanied, however, by an INTA status bit (D₀) which acknowledges the external request. The contents of the program counter are latched onto the CPU's address lines during T₁, but the counter itself is not incremented during the INTERRUPT machine cycle, as it otherwise would be.

In this way, the pre-interrupt status of the program counter is preserved, so that data in the counter may be restored by the interrupted program after the interrupt request has been processed.


The interrupt cycle is otherwise indistinguishable from an ordinary FETCH machine cycle. The processor itself takes no further special action. It is the responsibility of the peripheral logic to see that an eight-bit interrupt instruction is "jammed" onto the processor's data bus during state T₃. In a typical system, this means that the data-in bus from memory must be temporarily disconnected from the processor's main data bus, so that the interrupting device can command the main bus without interference.

The 8080's instruction set provides a special one-byte call which facilitates the processing of interrupts (the ordinary program Call takes three bytes). This is the RESTART instruction (RST). A variable three-bit field embedded in the eight-bit field of the RST enables the interrupting device to direct a Call to one of eight fixed memory locations. The decimal addresses of these dedicated locations are: 0, 8, 16, 24, 32, 40, 48, and 56. Any of these addresses may be used to store the first instruction(s) of a routine designed to service the requirements of an interrupting device. Since the (RST) is a call, completion of the instruction also stores the old program counter contents on the STACK.

 

NOTE: (8) Refer to Status Word Chart

Figure 2-8. Interrupt Timing

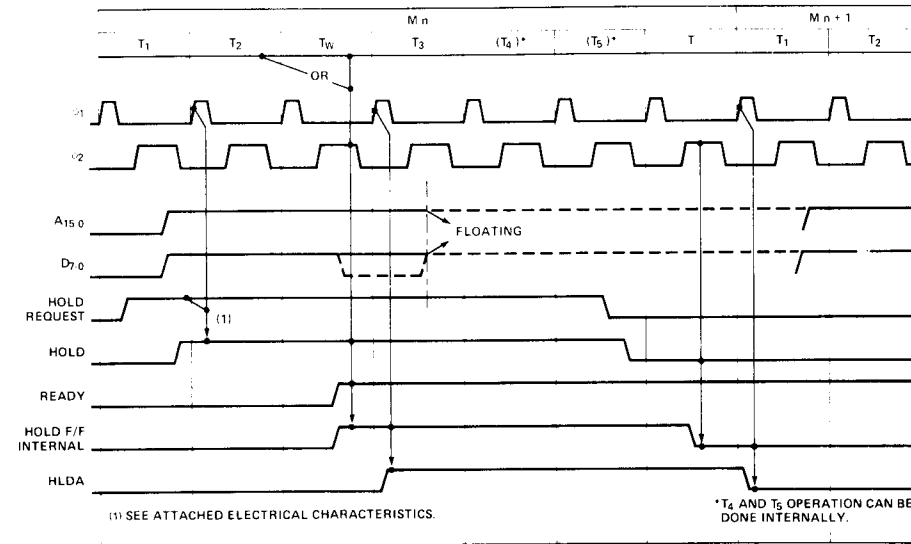

(1) SEE ATTACHED ELECTRICAL CHARACTERISTICS.

*T₄ AND T₅ OPERATION CAN BE DONE INTERNALLY.

Figure 2-9. HOLD Operation (Read Mode)

 


Figure 2-10. HOLD Operation (Write Mode)

8080

HOLD SEQUENCES

The 8080A CPU contains provisions for Direct Memory Access (DMA) operations. By applying a HOLD to the appropriate control pin on the processor, an external device can cause the CPU to suspend its normal operations and relinquish control of the address and data busses. The processor responds to a request of this kind by floating its address to other devices sharing the busses. At the same time, the processor acknowledges the HOLD by placing a high on its HLDA outpin pin. During an acknowledged HOLD, the address and data busses are under control of the peripheral which originated the request, enabling it to conduct memory transfers without processor intervention.

Like the interrupt, the HOLD input is synchronized internally. A HOLD signal must be stable prior to the "Hold set-up" interval (t_{HS}), that precedes the rising edge of ϕ_2 .

Figures 2-9 and 2-10 illustrate the timing involved in HOLD operations. Note the delay between the asynchronous HOLD REQUEST and the re-clocked HOLD. As shown in the diagram, a coincidence of the READY, the HOLD, and the ϕ_2 clocks sets the internal hold latch. Setting the latch enables the subsequent rising edge of the ϕ_1 clock pulse to trigger the HLDA output.

Acknowledgement of the HOLD REQUEST precedes slightly the actual floating of the processor's address and data lines. The processor acknowledges a HOLD at the beginning of T_3 , if a read or an input machine cycle is in progress (see Figure 2-9). Otherwise, acknowledgement is deferred until the beginning of the state following T_3 (see Figure 2-10). In both cases, however, the HLDA goes high within a specified delay (t_{DC}) of the rising edge of the selected ϕ_1 clock pulse. Address and data lines are floated within a brief delay after the rising edge of the next ϕ_2 clock pulse. This relationship is also shown in the diagrams.

To all outward appearances, the processor has suspended its operations once the address and data busses are floated. Internally, however, certain functions may continue. If a HOLD REQUEST is acknowledged at T_3 , and if the processor is in the middle of a machine cycle which requires four or more states to complete, the CPU proceeds through T_4 and T_5 before coming to a rest. Not until the end of the machine cycle is reached will processing activities cease. Internal processing is thus permitted to overlap the external DMA transfer, improving both the efficiency and the speed of the entire system.

The processor exits the holding state through a sequence similar to that by which it entered. A HOLD REQUEST is terminated asynchronously when the external device has completed its data transfer. The HLDA output

returns to a low level following the leading edge of the next ϕ_1 clock pulse. Normal processing resumes with the machine cycle following the last cycle that was executed.

HALT SEQUENCES

When a halt instruction (HLT) is executed, the CPU enters the halt state (T_{WH}) after state T_2 of the next machine cycle, as shown in Figure 2-11. There are only three ways in which the 8080 can exit the halt state:


- A high on the RESET line will always reset the 8080 to state T_1 ; RESET also clears the program counter.
- A HOLD input will cause the 8080 to enter the hold state, as previously described. When the HOLD line goes low, the 8080 re-enters the halt state on the rising edge of the next ϕ_1 clock pulse.
- An interrupt (i.e., INT goes high while INTE is enabled) will cause the 8080 to exit the Halt state and enter state T_1 on the rising edge of the next ϕ_1 clock pulse. NOTE: The interrupt enable (INTE) flag **must** be set when the halt state is entered; otherwise, the 8080 will only be able to exit via a RESET signal.

Figure 2-12 illustrates halt sequencing in flow chart form.

START-UP OF THE 8080 CPU

When power is applied initially to the 8080, the processor begins operating immediately. The contents of its program counter, stack pointer, and the other working registers are naturally subject to random factors and cannot be specified. For this reason, it will be necessary to begin the power-up sequence with RESET.

An external RESET signal of three clock period duration (minimum) restores the processor's internal program counter to zero. Program execution thus begins with memory location zero, following a RESET. Systems which require the processor to wait for an explicit start-up signal will store a halt instruction (EI, HLT) in the first two locations. A manual or an automatic INTERRUPT will be used for starting. In other systems, the processor may begin executing its stored program immediately. Note, however, that the RESET has no effect on status flags, or on any of the processor's working registers (accumulator, registers, or stack pointer). The contents of these registers remain indeterminate, until initialized explicitly by the program.

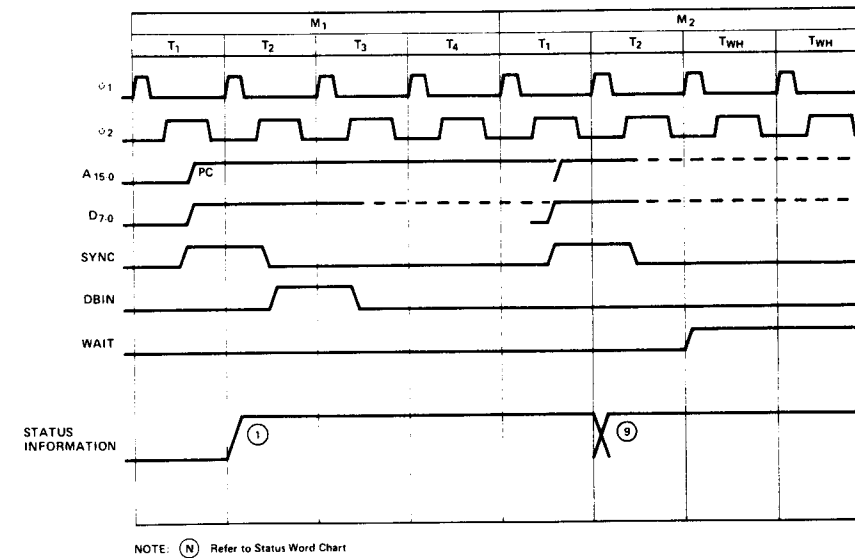

NOTE: (N) Refer to Status Word Chart

Figure 2-11. HALT Timing

 


Figure 2-12. HALT Sequence Flow Chart.

8080

NOTES:

1. The first memory cycle (M1) is always an instruction fetch; the first (or only) byte, containing the op code, is fetched during this cycle.
2. If the READY input from memory is not high during T2 of each memory cycle, the processor will enter a wait state (TW) until READY is sampled as high.
3. States T4 and T5 are present, as required, for operations which are completely internal to the CPU. The contents of the internal bus during T4 and T5 are available at the data bus; this is designed for testing purposes only. An "X" denotes that the state is present, but is only used for such internal operations as instruction decoding.
4. Only register pairs $rp = B$ (registers B and C) or $rp = D$ (registers D and E) may be specified.
5. These states are skipped.
6. Memory read sub-cycles; an instruction or data word will be read.
7. Memory write sub-cycle.
8. The READY signal is not required during the second and third sub-cycles (M2 and M3). The HOLD signal is accepted during M2 and M3. The SYNC signal is not generated during M2 and M3. During the execution of DAD, M2 and M3 are required for an internal register-pair add; memory is not referenced.
9. The results of these arithmetic, logical or rotate instructions are not moved into the accumulator (A) until state T2 of the next instruction cycle. That is, A is loaded while the next instruction is being fetched; this overlapping of operations allows for faster processing.
10. If the value of the least significant 4-bits of the accumulator is greater than 9 or if the auxiliary carry bit is set, 6 is added to the accumulator. If the value of the most significant 4-bits of the accumulator is now greater than 9, or if the carry bit is set, 6 is added to the most significant 4-bits of the accumulator.
11. This represents the first sub-cycle (the instruction fetch) of the next instruction cycle.

12. If the condition was met, the contents of the register pair WZ are output on the address lines (A₀₋₁₅) instead of the contents of the program counter (PC).
13. If the condition was not met, sub-cycles M4 and M5 are skipped; the processor instead proceeds immediately to the instruction fetch (M1) of the next instruction cycle.
14. If the condition was not met, sub-cycles M2 and M3 are skipped; the processor instead proceeds immediately to the instruction fetch (M1) of the next instruction cycle.
15. Stack read sub-cycle.
16. Stack write sub-cycle.
17. CONDITION CCC
 NZ — not zero (Z = 0) 000
 Z — zero (Z = 1) 001
 NC — no carry (CY = 0) 010
 C — carry (CY = 1) 011
 PO — parity odd (P = 0) 100
 PE — parity even (P = 1) 101
 P — plus (S = 0) 110
 M — minus (S = 1) 111

18. I/O sub-cycle: the I/O port's 8-bit select code is duplicated on address lines 0-7 (A₀₋₇) and 8-15 (A₈₋₁₅).
19. Output sub-cycle.
20. The processor will remain idle in the halt state until an interrupt, a reset or a hold is accepted. When a hold request is accepted, the CPU enters the hold mode; after the hold mode is terminated, the processor returns to the halt state. After a reset is accepted, the processor begins execution at memory location zero. After an interrupt is accepted, the processor executes the instruction forced onto the data bus (usually a restart instruction).

| SSS or DDD | Value | rp | Value |
|------------|-------|----|-------|
| A | 111 | B | 00 |
| B | 000 | D | 01 |
| C | 001 | H | 10 |
| D | 010 | SP | 11 |
| E | 011 | | |
| H | 100 | | |
| L | 101 | | |

 


Figure 2-13. Reset.

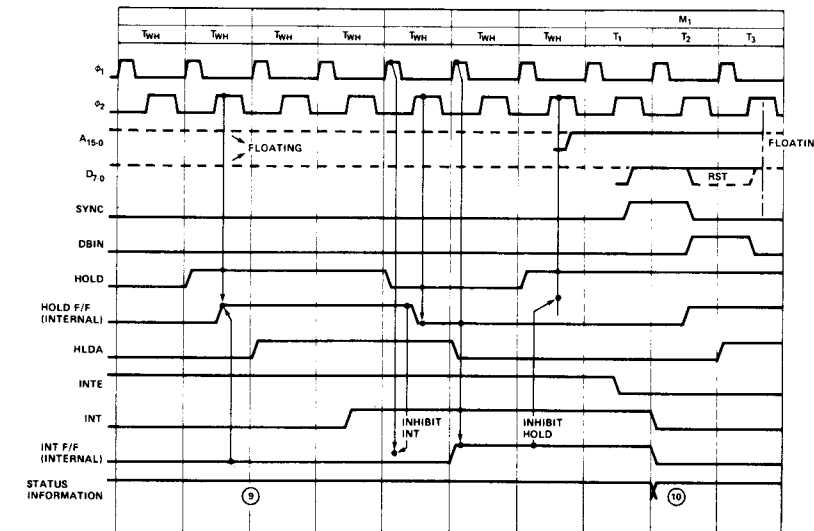



Figure 2-14. Relation between HOLD and INT in the HALT State.

8080

THE 8080 INSTRUCTION SET


The 8080 can directly address up to 65,536 bytes of memory, which may consist of both read-only memory (ROM) elements and random-access memory (RAM) elements (read/write memory).

 Data in the 8080 is stored in the form of 8-bit binary integers:



When a register or data word contains a binary number, it is necessary to establish the order in which the bits of the number are written. In the Intel 8080, BIT 0 is referred to as the **Least Significant Bit (LSB)**, and BIT 7 (of an 8 bit number) is referred to as the **Most Significant Bit (MSB)**.

 The 8080 program instructions may be one, two or three bytes in length. Multiple byte instructions must be stored in successive memory locations; the address of the first byte is always used as the address of the instructions. The exact instruction format will depend on the particular operation to be executed.



Addressing Modes:

Often the data that is to be operated on is stored in memory. When multi-byte numeric data is used, the data, like instructions, is stored in successive memory locations, with the least significant byte first, followed by increasingly significant bytes. The 8080 has four different modes for addressing data stored in memory or in registers:

- **Direct** - Bytes 2 and 3 of the instruction contain the exact memory address of the data item (the low-order bits of the address are in byte 2, the high-order bits in byte 3).
- **Register** - The instruction specifies the register or register-pair in which the data is located.
- **Register Indirect** - The instruction specifies a register-pair which contains the memory

address where the data is located (the high-order bits of the address are in the first register of the pair, the low-order bits in the second).

- **Immediate** - The instruction contains the data itself. This is either an 8-bit quantity or a 16-bit quantity (least significant byte first, most significant byte second).

Unless directed by an interrupt or branch instruction, the execution of instructions proceeds through consecutively increasing memory locations. A branch instruction can specify the address of the next instruction to be executed in one of two ways:

- **Direct** - The branch instruction contains the address of the next instruction to be executed. (Except for the 'RST' instruction, byte 2 contains the low-order address and byte 3 the high-order address.)
- **Register indirect** - The branch instruction indicates a register-pair which contains the address of the next instruction to be executed. (The high-order bits of the address are in the first register of the pair, the low-order bits in the second.)

The RST instruction is a special one-byte call instruction (usually used during interrupt sequences). RST includes a three-bit field; program control is transferred to the instruction whose address is eight times the contents of this three-bit field.

Condition Flags:

There are five condition flags associated with the execution of instructions on the 8080. They are Zero, Sign, Parity, Carry, and Auxiliary Carry, and are each represented by a 1-bit register in the CPU. A flag is "set" by forcing the bit to 1; "reset" by forcing the bit to 0.

Unless indicated otherwise, when an instruction affects a flag, it affects it in the following manner:

- Zero:** If the result of an instruction has the value 0, this flag is set; otherwise it is reset.
- Sign:** If the most significant bit of the result of the operation has the value 1, this flag is set; otherwise it is reset.
- Parity:** If the modulo 2 sum of the bits of the result of the operation is 0, (i.e., if the result has even parity), this flag is set; otherwise it is reset (i.e., if the result has odd parity).
- Carry:** If the instruction resulted in a carry (from addition), or a borrow (from subtraction or a comparison) out of the high-order bit, this flag is set; otherwise it is reset.

Auxiliary Carry: If the instruction caused a carry out of bit 3 and into bit 4 of the resulting value, the auxiliary carry is set; otherwise it is reset. This flag is affected by single precision additions, subtractions, increments, decrements, comparisons, and logical operations, but is principally used with additions and increments preceding a DAA (Decimal Adjust Accumulator) instruction.

- rh** The first (high-order) register of a designated register pair.
- rl** The second (low-order) register of a designated register pair.
- PC** 16-bit program counter register (PCH and PCL are used to refer to the high-order and low-order 8 bits respectively).
- SP** 16-bit stack pointer register (SPH and SPL are used to refer to the high-order and low-order 8 bits respectively).
- r_m** Bit m of the register r (bits are number 7 through 0 from left to right).

Z,S,P,CY,AC The condition flags:
Zero,
Sign,
Parity,
Carry,
and Auxiliary Carry, respectively.

- ()** The contents of the memory location or registers enclosed in the parentheses.
- ←** "Is transferred to"
- ∧** Logical AND
- ⊕** Exclusive OR
- ∨** Inclusive OR
- +** Addition
- Two's complement subtraction
- *** Multiplication
- ↔** "Is exchanged with"
- The one's complement (e.g., \bar{A})
- n** The restart number 0 through 7
- NNN** The binary representation 000 through 111 for restart number 0 through 7 respectively.

The following pages provide a detailed description of the instruction set of the 8080.

Symbols and Abbreviations:

The following symbols and abbreviations are used in the subsequent description of the 8080 instructions:

| SYMBOLS | MEANING |
|-------------|---|
| accumulator | Register A |
| addr | 8-bit address quantity |
| data | 8-bit data quantity |
| data 16 | 16-bit data quantity |
| byte 2 | The second byte of the instruction |
| byte 3 | The third byte of the instruction |
| port | 8-bit address of an I/O device |
| r,r1,r2 | One of the registers A,B,C,D,E,H,L |
| DDD,SSS | The bit pattern designating one of the registers A,B,C,D,E,H,L (DDD=destination, SSS=source): |

DDD or SSS REGISTER NAME

| | |
|-----|---|
| 111 | A |
| 000 | B |
| 001 | C |
| 010 | D |
| 011 | E |
| 100 | H |
| 101 | L |

- rp** One of the register pairs:
B represents the B,C pair with B as the high-order register and C as the low-order register;
D represents the D,E pair with D as the high-order register and E as the low-order register;
H represents the H,L pair with H as the high-order register and L as the low-order register;
SP represents the 16-bit stack pointer register.
- RP** The bit pattern designating one of the register pairs B,D,H,SP:

| RP | REGISTER PAIR |
|----|---------------|
| 00 | B-C |
| 01 | D-E |
| 10 | H-L |
| 11 | SP |

LDA addr (Load Accumulator direct)
(A) ← (byte 3)(byte 2)
The content of the memory location, whose address is specified in byte 2 and byte 3 of the instruction, is moved to register A.

| | | | | | | | | | |
|-----------------|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | |
| low-order addr | | | | | | | | 1 | 0 |
| high-order addr | | | | | | | | | |

Cycles: 4
States: 13
Addressing: direct
Flags: none

MVI r, data (Move immediate)
(r) ← (byte 2)
The content of byte 2 of the instruction is moved to register r.

| | | | | | | | | | |
|------|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | D | D | D | 1 | 1 | 1 | 0 |
| data | | | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: none

Data Transfer Group:
This group of instructions transfers data to and from registers and memory. Condition flags are not affected by any instruction in this group.

MOV r1, r2 (Move Register)
(r1) ← (r2)
The content of register r2 is moved to register r1.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 0 | 1 | D | D | D | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 5
Addressing: register
Flags: none

MOV r, M (Move from memory)
(r) ← ((H) (L))
The content of the memory location, whose address is in registers H and L, is moved to register r.

| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 0 | 1 | D | D | D | 1 | 1 | 1 | 0 |
|---|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: none

MOV M, r (Move to memory)
((H) (L)) ← (r)
The content of register r is moved to the memory location whose address is in registers H and L.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 0 | 1 | 1 | 1 | 0 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: none

SHLD addr (Store H and L direct)
(byte 3)(byte 2) ← (L)
(byte 3)(byte 2) + 1 ← (H)
The content of register L is moved to the memory location whose address is specified in byte 2 and byte 3. The content of register H is moved to the succeeding memory location.

| | | | | | | | | | |
|-----------------|---|---|---|---|---|---|---|--|--|
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | | |
| low-order addr | | | | | | | | | |
| high-order addr | | | | | | | | | |

Cycles: 5
States: 16
Addressing: direct
Flags: none

LDAX rp (Load accumulator indirect)
(A) ← ((rp))
The content of the memory location, whose address is in the register pair rp, is moved to register A. Note: only register pairs rp-B (registers B and C) or rp-D (registers D and E) may be specified.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 0 | 0 | R | P | 1 | 0 | 1 | 0 |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: none

STAX rp (Store accumulator indirect)
(rp) ← (A)
The content of register A is moved to the memory location whose address is in the register pair rp. Note: only register pairs rp-B (registers B and C) or rp-D (registers D and E) may be specified.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 0 | 0 | R | P | 0 | 0 | 1 | 0 |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: none

XCHG (Exchange H and L with D and E)
(H) ↔ (D)
(L) ↔ (E)
The contents of registers H and L are exchanged with the contents of registers D and E.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: none

STA addr (Store Accumulator direct)
(byte 3)(byte 2) ← (A)
The content of the accumulator is moved to the memory location whose address is specified in byte 2 and byte 3 of the instruction.

| | | | | | | | | | |
|-----------------|---|---|---|---|---|---|---|--|--|
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | | |
| low-order addr | | | | | | | | | |
| high-order addr | | | | | | | | | |

Cycles: 4
States: 13
Addressing: direct
Flags: none

LHLD addr (Load H and L direct)
(L) ← (byte 3)(byte 2)
(H) ← (byte 3)(byte 2) + 1
The content of the memory location, whose address is specified in byte 2 and byte 3 of the instruction, is moved to register L. The content of the memory location at the succeeding address is moved to register H.

| | | | | | | | | | |
|-----------------|---|---|---|---|---|---|---|--|--|
| 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | | |
| low-order addr | | | | | | | | | |
| high-order addr | | | | | | | | | |

Cycles: 5
States: 16
Addressing: direct
Flags: none

SUI data (Subtract memory)
(A) ← ((H) (L))
The content of the memory location whose address is contained in the H and L registers is subtracted from the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: Z,S,P,CY,AC

SUI data (Subtract immediate)
(A) ← (A) - (byte 2)
The content of the second byte of the instruction is subtracted from the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: Z,S,P,CY,AC

ADC r (Add Register with carry)
(A) ← (A) + (r) + (CY)
The content of register r and the content of the carry bit are added to the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

ACI data (Add immediate with carry)
(A) ← (A) + (byte 2) + (CY)
The content of the second byte of the instruction and the content of the CY flag are added to the contents of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: Z,S,P,CY,AC

ADDC r (Add Register with carry and Auxiliary Carry)
(A) ← (A) + (r) + (CY) + (AC)
The content of register r, the content of the carry bit, and the content of the Auxiliary Carry flag are added to the contents of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

ADC r (Add Register with carry)
(A) ← (A) + (r) + (CY)
The content of register r and the content of the carry bit are added to the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

ADDC r (Add Register with carry and Auxiliary Carry)
(A) ← (A) + (r) + (CY) + (AC)
The content of register r, the content of the carry bit, and the content of the Auxiliary Carry flag are added to the contents of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

Arithmetic Group:
This group of instructions performs arithmetic operations on data in registers and memory. Unless indicated otherwise, all instructions in this group affect the Zero, Sign, Parity, Carry, and Auxiliary Carry flag according to the standard rules. All subtraction operations are performed via two's complement arithmetic and set the carry flag to one to indicate a borrow and clear it to indicate no borrow.

ADD r (Add Register)
(A) ← (A) + (r)
The content of register r is added to the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 0 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

ADD M (Add memory)
(A) ← (A) + ((H) (L))
The content of the memory location whose address is contained in the H and L registers is added to the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: Z,S,P,CY,AC

ADI data (Add immediate)
(A) ← (A) + (byte 2)
The content of the second byte of the instruction is added to the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: Z,S,P,CY,AC

SUB r (Subtract Register)
(A) ← (A) - (r)
The content of register r is subtracted from the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 0 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

SUB M (Subtract memory)
(A) ← ((H) (L))
The content of the memory location whose address is contained in the H and L registers is subtracted from the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: Z,S,P,CY,AC

SUI data (Subtract immediate)
(A) ← (A) - (byte 2)
The content of the second byte of the instruction is subtracted from the content of the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: Z,S,P,CY,AC

SBB r (Subtract Register with borrow)
(A) ← (A) - (r) - (CY)
The content of register r and the content of the CY flag are both subtracted from the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | S | S | S |
|---|---|---|---|---|---|---|---|

Cycles: 1
States: 4
Addressing: register
Flags: Z,S,P,CY,AC

SBB M (Subtract memory with borrow)
(A) ← ((H) (L)) - (CY)
The content of the memory location whose address is contained in the H and L registers and the content of the CY flag are both subtracted from the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 |
|---|---|---|---|---|---|---|---|

Cycles: 2
States: 7
Addressing: reg, indirect
Flags: Z,S,P,CY,AC

SBI data (Subtract immediate with borrow)
(A) ← (A) - (byte 2) - (CY)
The contents of the second byte of the instruction and the contents of the CY flag are both subtracted from the accumulator. The result is placed in the accumulator.

| | | | | | | | |
|------|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| data | | | | | | | |

Cycles: 2
States: 7
Addressing: immediate
Flags: Z,S,P,CY,AC

INR r (Increment Register)
(r) ← (r) + 1
The content of register r is incremented by one. Note: All condition flags except CY are affected.

| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | D | D | D | 1 | 0 | 0 |
|---|---|---|---|---|---|---|---|---|

Cycles: 1
States: 5
Addressing: register
Flags: Z,S,P,AC

INR M (Increment memory)
((H) (L)) ← ((H) (L)) + 1
The content of the memory location whose address is contained in the H and L registers is incremented by one. Note: All condition flags except CY are affected.

| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
|---|---|---|---|---|---|---|---|---|

Cycles: 3
States: 10
Addressing: reg, indirect
Flags: Z,S,P,AC

DCR r (Decrement Register)
(r) ← (r) - 1
The content of register r is decremented by one. Note: All condition flags except CY are affected.

| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | D | D | D | 1 | 0 | 1 |
|---|---|---|---|---|---|---|---|---|


Cycles: 1
States: 5
Addressing: register
Flags: Z,S,P,AC

DCR M (Decrement memory)
((H) (L)) ← ((H) (L)) - 1
The content of the memory location whose address is contained in the H and L registers is decremented by one. Note: All condition flags except CY are affected.


| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | D | D | D | 1 | 0 | 1 |
|---|---|---|---|---|---|---|---|---|

Cycles: 1
States: 5
Addressing: reg, indirect
Flags: Z,S,P,AC

 
DCR M (Decrement memory)
 $(H) (L) \leftarrow (H) (L) - 1$
 The content of the memory location whose address is contained in the H and L registers is decremented by one. Note: All condition flags except CY are affected.



 
INX rp (Increment register pair)
 $(r) (r) \leftarrow (r) (r) + 1$
 The content of the register pair rp is incremented by one. Note: No condition flags are affected.



 
DCX rp (Decrement register pair)
 $(r) (r) \leftarrow (r) (r) - 1$
 The content of the register pair rp is decremented by one. Note: No condition flags are affected.



 DAD rp (Add register pair to H and L)
 $(A) \leftarrow (H) (L) + (r) (r)$
 The content of the memory location whose address is contained in the H and L registers is added to the content of the register pair H and L. The result is placed in the register pair H and L. Note: Only the CY flag is affected. It is set if there is a carry out of the double precision add; otherwise it is reset.



DAA (Decimal Adjust Accumulator)
 The eight-bit number in the accumulator is adjusted to form two four-bit Binary-Coded-Decimal digits by the following process:
 1. If the value of the least significant 4 bits of the accumulator is greater than 9 or if the AC flag is set, 6 is added to the accumulator.
 2. If the value of the most significant 4 bits of the accumulator is now greater than 9, or if the CY flag is set, 6 is added to the most significant 4 bits of the accumulator.

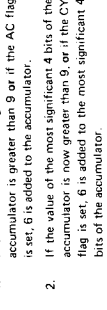


NOTE: All flags are affected.


Logical Group:
 This group of instructions performs logical (Boolean) operations on data in registers and memory and on condition flags according to the standard rules.

Unless indicated otherwise, all instructions in this group affect the Zero, Sign, Parity, Auxiliary Carry, and Carry flags according to the standard rules.

 
ANA r (AND Register)
 $(A) \leftarrow (A) \wedge (r)$
 The content of register r is logically ANDed with the content of the accumulator. The result is placed in the accumulator. The CY flag is cleared.



 
ANA M (AND memory)
 $(A) \leftarrow (A) \wedge (H) (L)$
 The contents of the memory location whose address is contained in the H and L registers is logically ANDed with the content of the accumulator. The result is placed in the accumulator. The CY flag is cleared.



 
ANI data (AND immediate)
 $(A) \leftarrow (A) \wedge \text{data}$
 The content of the second byte of the instruction is logically ANDed with the contents of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
XRA r (Exclusive OR Register)
 $(A) \leftarrow (A) \vee (r)$
 The content of register r is exclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
XRA M (Exclusive OR Memory)
 $(A) \leftarrow (A) \vee (H) (L)$
 The content of the memory location whose address is contained in the H and L registers is exclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
XRI data (Exclusive OR immediate)
 $(A) \leftarrow (A) \vee \text{data}$
 The content of the second byte of the instruction is exclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
ORA r (OR Register)
 $(A) \leftarrow (A) \vee (r)$
 The content of register r is inclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
ORA M (OR memory)
 $(A) \leftarrow (A) \vee (H) (L)$
 The content of the memory location whose address is contained in the H and L registers is inclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
ORI data (OR immediate)
 $(A) \leftarrow (A) \vee \text{data}$
 The content of the second byte of the instruction is inclusive-OR'd with the content of the accumulator. The result is placed in the accumulator. The CY and AC flags are cleared.



 
CMP r (Compare Register)
 $(A) - (r)$
 The content of register r is subtracted from the accumulator. The accumulator remains unchanged. The condition flags are set as a result of the subtraction. The Z flag is set to 1 if $(A) = (r)$. The CY flag is set to 1 if $(A) < (r)$.



 
CMP M (Compare memory)
 $(A) - (H) (L)$
 The content of the memory location whose address is contained in the H and L registers is subtracted from the accumulator. The accumulator remains unchanged. The condition flags are set as a result of the subtraction. The Z flag is set to 1 if $(A) = (H) (L)$. The CY flag is set to 1 if $(A) < (H) (L)$.



 
CPI data (Compare immediate)
 $(A) - \text{data}$
 The content of the second byte of the instruction is subtracted from the accumulator. The condition flags are set by the result of the subtraction. The Z flag is set to 1 if $(A) = \text{data}$. The CY flag is set to 1 if $(A) < \text{data}$.



 
RLC (Rotate left)
 $(A_{n+1}) \leftarrow (A_n) ; (A_0) \leftarrow (A_7)$
 $(CY) \leftarrow (A_7)$
 The content of the accumulator is rotated left one position. The low order bit and the CY flag are both set to the value shifted out of the high order bit position. Only the CY flag is affected.



 
RRC (Rotate right)
 $(A_n) \leftarrow (A_{n+1}) ; (A_7) \leftarrow (A_0)$
 $(CY) \leftarrow (A_0)$
 The content of the accumulator is rotated right one position. The high order bit and the CY flag are both set to the value shifted out of the low order bit position. Only the CY flag is affected.



 
RAL (Rotate left through carry)
 $(A_{n+1}) \leftarrow (A_n) ; (CY) \leftarrow (A_7)$
 $(A_0) \leftarrow (CY)$
 The content of the accumulator is rotated left one position through the CY flag. The low order bit is set equal to the CY flag and the CY flag is set to the value shifted out of the high order bit. Only the CY flag is affected.



 
RAR (Rotate right through carry)
 $(A_n) \leftarrow (A_{n+1}) ; (CY) \leftarrow (A_0)$
 $(A_7) \leftarrow (CY)$
 The content of the accumulator is rotated right one position through the CY flag. The high order bit is set to the CY flag and the CY flag is set to the value shifted out of the low order bit. Only the CY flag is affected.



 CMA (Complement accumulator)
 $(A) \leftarrow (A)$
 The contents of the accumulator are complemented (zero bits become 1, one bits become 0). No flag is affected.



 CMC (Complement carry)
 $(CY) \leftarrow (CY)$
 The CY flag is complemented. No other flags are affected.



STC (Set carry)
 $(CY) \leftarrow 1$
 The CY flag is set to 1. No other flags are affected.




Branch Group:
 This group of instructions alter normal sequential program flow.


Condition flags are not affected by any instruction in this group.
 The two types of branch instructions are unconditional and conditional. Unconditional transfers simply perform the specified operation on register PC (the program counter). Conditional transfers examine the status of one of the four processor flags to determine if the specified branch is to be executed. The conditions that may be specified are as follows:

| CONDITION | |
|-----------|-----------------------|
| NZ | - not zero (Z = 0) |
| Z | - zero (Z = 1) |
| NC | - no carry (CY = 0) |
| C | - carry (CY = 1) |
| PO | - parity odd (P = 0) |
| PE | - parity even (P = 1) |
| P | - plus (S = 0) |
| M | - minus (S = 1) |

 
JMP addr (Jump)
 $(PC) \leftarrow \text{addr}$
 Control is transferred to the instruction whose address is specified in byte 3 and byte 2 of the current instruction.



 Jcondition addr (Conditional jump)
 If (CCCC)
 $(PC) \leftarrow \text{addr}$
 If the specified condition is true, control is transferred to the instruction whose address is specified in bytes 3 and byte 2 of the current instruction; otherwise, control continues sequentially.




CALL addr (Call)
 $(SP) - 1 \leftarrow (PC)$
 $(SP) - 2 \leftarrow (PC)$
 $(PC) \leftarrow \text{addr}$ (byte 2)
 $(PC) \leftarrow \text{addr}$ (byte 3)
 The high-order eight bits of the next instruction address are moved to this memory location whose address is one less than the content of register SP. The low-order eight bits of the next instruction address are moved to the memory location whose address is two less than the content of register SP. The content of register SP is decremented by 2. Control is transferred to the instruction whose address is specified in byte 3 and byte 2 of the current instruction.

 

Stack, I/O, and Machine Control Group:

This group of instructions performs I/O, manipulates the Stack, and alters internal control flags. Unless otherwise specified, condition flags are not affected by any instructions in this group.

FLAG WORD

 

RST n (Restart)
 ((SP) - 1) ← (PCH)
 ((SP) - 2) ← (PCL)
 (PC) ← (SP) - 2
 (PC) ← 8 * (NNN)

The high-order eight bits of the next instruction address are moved to the memory location whose address is one less than the content of register SP. The low-order eight bits of the next instruction address are moved to the memory location whose address is two less than the content of register SP. The content of register SP is decremented by two. Control is transferred to the instruction whose address is eight times the content of NNN.




15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0
 0 0 0 0 0 0 0 0 0 0 0 0 N N N N 0 0 0 0

Program Counter After Restart


PCHL (Jump H and L indirect—move H and L to PC)
 (PCH) ← (H)
 (PCL) ← (L)

 The content of register H is moved to the high-order eight bits of register PC. The content of register L is moved to the low-order eight bits of register PC.




Condition addr (Condition call)
 If (CCC),
 (SP) - 1 ← (PCH)
 (SP) - 2 ← (PCL)
 (SP) ← (SP) - 2
 (PC) ← (byte 3) (byte 2)

 If the specified condition is true, the actions specified in the CALL instruction (see above) are performed; otherwise, control continues sequentially.




RET (Return)
 (PCL) ← ((SP));
 (PCH) ← ((SP) + 1);
 (SP) ← ((SP) + 2);

 The content of the memory location whose address is specified in register SP is moved to the low-order eight bits of register PC. The content of the memory location whose address is one more than the content of register SP is moved to the high-order eight bits of register PC. The content of register SP is incremented by 2.




Rcondition (Conditional return)
 If (CCC),
 (PCL) ← ((SP));
 (PCH) ← ((SP) + 1);
 (SP) ← ((SP) + 2);

 If the specified condition is true, the actions specified in the RET instruction (see above) are performed; otherwise, control continues sequentially.




PUSH rp (Push)
 ((SP) - 1) ← (rh)
 ((SP) - 2) ← (rl)
 (SP) ← (SP) - 2

 The content of the high-order register of register pair rp is moved to the memory location whose address is one less than the content of register SP. The content of the low-order register of register pair rp is moved to the memory location whose address is two less than the content of register SP. The content of register SP is decremented by 2. **Note: Register pair rp = SP may not be specified.**




POP PSW (Push processor status word)
 ((SP) - 1) ← (A)
 ((SP) - 2) ← (CY), ((SP) - 2) ← 1
 ((SP) - 2) ← (P), ((SP) - 2) ← 0
 ((SP) - 2) ← (AC), ((SP) - 2) ← 0
 ((SP) - 2) ← (Z), ((SP) - 2) ← 0
 ((SP) - 2) ← (S)

 The content of register A is moved to the memory location whose address is one less than register SP. The contents of the condition flags are assembled into a processor status word and the word is assembled to the memory location whose address is two less than the content of register SP. The content of register SP is decremented by two.




POP rp (Pop)
 (rh) ← ((SP) + 1)
 (rl) ← ((SP) + 2)
 (SP) ← (SP) + 2

 The content of the memory location whose address is specified by the content of register SP is moved to the low-order register of register pair rp. The content of the memory location whose address is one more than the content of register SP is moved to the high-order register of register pair rp. The content of register SP is incremented by 2. **Note: Register pair rp = SP may not be specified.**




POP PSW (Pop processor status word)
 (CY) ← ((SP) + 1)
 (P) ← ((SP) + 2)
 (AC) ← ((SP) + 4)
 (Z) ← ((SP) + 6)
 (S) ← ((SP) + 8)
 (A) ← ((SP) + 1)
 (SP) ← ((SP) + 2)

 The content of the memory location whose address is specified by the content of register SP is used to restore the condition flags. The content of the memory location whose address is one more than the content of register SP is moved to register A. The content of register SP is incremented by 2.




XTHL (Exchange stack top with H and L)
 (L) ↔ (SP);
 (H) ↔ ((SP) + 1)

 
The content of the L register is exchanged with the content of the memory location whose address is specified by the content of register SP. The content of the H register is exchanged with the content of the memory location whose address is one more than the content of register SP.



 SPHL (Move HL to SP)
 (SP) ← (H) (L)
 The contents of registers H and L (16 bits) are moved to register SP.



 
IN port (Input)
 (A) ← (data)
 The data placed on the eight bit, bi-directional data bus by the specified port is moved to register A.




OUT port (Output)
 (data) ← (A)
 The content of register A is placed on the eight bit bi-directional data bus for transmission to the specified port.



 
EI (Enable interrupts)
 The interrupt system is enabled following the execution of the next instruction.




 
DI (Disable interrupts)
 The interrupt system is disabled immediately following the execution of the DI instruction.



 HLT (Halt)
 The processor is stopped. The registers and flags are unaffected.



  NOP (No op)
 No operation is performed. The registers and flags are unaffected.



8080 Photomicrograph With Pin Designations

8080A FUNCTIONAL PIN DEFINITION

The following describes the function of all of the 8080A I/O pins. Several of the descriptions refer to internal timing periods.

A₁₅-A₀ (output three-state)

ADDRESS BUS; the address bus provides the address to memory (up to 64K 8-bit words) or denotes the I/O device number for up to 256 input and 256 output devices. A₀ is the least significant address bit.

D₇-D₀ (input/output three-state)

DATA BUS; the data bus provides bi-directional communication between the CPU, memory, and I/O devices for instructions and data transfers. Also, during the first clock cycle of each machine cycle, the 8080A outputs a status word on the data bus that describes the current machine cycle. D₀ is the least significant bit.

SYNC (output)

SYNCHRONIZING SIGNAL; the SYNC pin provides a signal to indicate the beginning of each machine cycle.

DBIN (output)

DATA BUS IN; the DBIN signal indicates to external circuits that the data bus is in the input mode. This signal should be used to enable the gating of data onto the 8080A data bus from memory or I/O.

READY (input)

READY; the READY signal indicates to the 8080A that valid memory or input data is available on the 8080A data bus. This signal is used to synchronize the CPU with slower memory or I/O devices. If after sending an address out the 8080A does not receive a READY input, the 8080A will enter a WAIT state for as long as the READY line is low. READY can also be used to single step the CPU.

WAIT (output)

WAIT; the WAIT signal acknowledges that the CPU is in a WAIT state.

WR (output)

WRITE; the WR signal is used for memory WRITE or I/O output control. The data on the data bus is stable while the WR signal is active low ($\overline{WR} = 0$).


HOLD (input)

HOLD; the HOLD signal requests the CPU to enter the HOLD state. The HOLD state allows an external device to gain control of the 8080A address and data bus as soon as the 8080A has completed its use of these buses for the current machine cycle. It is recognized under the following conditions:

- the CPU is in the HALT state.
- the CPU is in the T₂ or T_W state and the READY signal is active. As a result of entering the HOLD state the CPU ADDRESS BUS (A₁₅-A₀) and DATA BUS (D₇-D₀) will be in their high impedance state. The CPU acknowledges its state with the HOLD ACKNOWLEDGE (HLDA) pin.

HLDA (output)

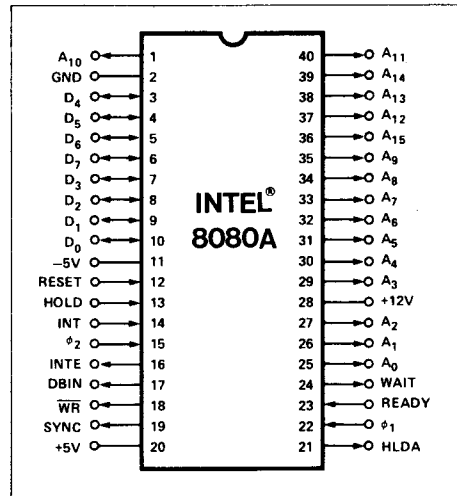HOLD ACKNOWLEDGE; the HLDA signal appears in response to the HOLD signal and indicates that the data and address bus



Pin Configuration

will go to the high impedance state. The HLDA signal begins at:

- T₃ for READ memory or input.
- The Clock Period following T₃ for WRITE memory or OUTPUT operation.

In either case, the HLDA signal appears after the rising edge of phi₁ and high impedance occurs after the rising edge of phi₂.

INTE (output)

INTERRUPT ENABLE; indicates the content of the internal interrupt enable flip/flop. This flip/flop may be set or reset by the Enable and Disable Interrupt instructions and inhibits interrupts from being accepted by the CPU when it is reset. It is automatically reset (disabling further interrupts) at time T₁ of the instruction fetch cycle (M1) when an interrupt is accepted and is also reset by the RESET signal.

INT (input)

INTERRUPT REQUEST; the CPU recognizes an interrupt request on this line at the end of the current instruction or while halted. If the CPU is in the HOLD state or if the Interrupt Enable flip/flop is reset it will not honor the request.

RESET (input) [1]

RESET; while the RESET signal is activated, the content of the program counter is cleared. After RESET, the program will start at location 0 in memory. The INTE and HLDA flip/flops are also reset. Note that the flags, accumulator, stack pointer, and registers are not cleared.

- V_{SS} Ground Reference.
- V_{DD} +12 ± 5% Volts.
- V_{CC} +5 ± 5% Volts.
- V_{BB} -5 ± 5% Volts (substrate bias).
- phi₁, phi₂ 2 externally supplied clock phases (non TTL compatible)

ABSOLUTE MAXIMUM RATINGS*

- Temperature Under Bias 0°C to +70°C
- Storage Temperature -65°C to +150°C
- All Input or Output Voltages
With Respect to V_{BB} -0.3V to +20V
- V_{CC}, V_{DD} and V_{SS} With Respect to V_{BB} -0.3V to +20V
- Power Dissipation 1.5W

*COMMENT: Stresses above those listed under "Absolute Maximum Ratings" may cause permanent damage to the device. This is a stress rating only and functional operation of the device at these or any other conditions above those indicated in the operational sections of this specification is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

D.C. CHARACTERISTICS

T_A = 0°C to 70°C, V_{DD} = +12V ± 5%, V_{CC} = +5V ± 5%, V_{BB} = -5V ± 5%, V_{SS} = 0V, Unless Otherwise Noted.

| Symbol | Parameter | Min. | Typ. | Max. | Unit | Test Condition |
|----------------------|--|--------------------|------|----------------------|----------|--|
| V _{ILC} | Clock Input Low Voltage | V _{SS} -1 | | V _{SS} +0.8 | V | I _{OL} = 1.9mA on all outputs, I _{OH} = -150µA. |
| V _{IHC} | Clock Input High Voltage | 9.0 | | V _{DD} +1 | V | |
| V _{IL} | Input Low Voltage | V _{SS} -1 | | V _{SS} +0.8 | V | |
| V _{IH} | Input High Voltage | 3.3 | | V _{CC} +1 | V | |
| V _{OL} | Output Low Voltage | | | 0.45 | V | Operation T _{CY} = .48 µsec |
| V _{OH} | Output High Voltage | 3.7 | | | V | |
| I _{DD} (AV) | Avg. Power Supply Current (V _{DD}) | | 40 | 70 | mA | |
| I _{CC} (AV) | Avg. Power Supply Current (V _{CC}) | | 60 | 80 | mA | V _{SS} ≤ V _{IN} ≤ V _{CC} |
| I _{BB} (AV) | Avg. Power Supply Current (V _{BB}) | | .01 | 1 | mA | |
| I _{IL} | Input Leakage | | | ±10 | µA | V _{SS} ≤ V _{CLOCK} ≤ V _{DD} |
| I _{CL} | Clock Leakage | | | ±10 | µA | V _{SS} ≤ V _{IN} ≤ V _{SS} + 0.8V |
| I _{DL} [2] | Data Bus Leakage in Input Mode | | | -100 -2.0 | µA mA | V _{SS} + 0.8V ≤ V _{IN} ≤ V _{CC} |
| I _{FL} | Address and Data Bus Leakage During HOLD | | | +10 -100 | µA | V _{ADDR/DATA} = V _{CC} V _{ADDR/DATA} = V _{SS} + 0.45V |

CAPACITANCE


T_A = 25°C V_{CC} = V_{DD} = V_{SS} = 0V, V_{BB} = -5V

| Symbol | Parameter | Typ. | Max. | Unit | Test Condition |
|------------------|--------------------|------|------|------|-----------------------------|
| C _φ | Clock Capacitance | 17 | 25 | pf | f _c = 1 MHz |
| C _{IN} | Input Capacitance | 6 | 10 | pf | Unmeasured Pins |
| C _{OUT} | Output Capacitance | 10 | 20 | pf | Returned to V _{SS} |


NOTES:

- The RESET signal must be active for a minimum of 3 clock cycles.
- When DBIN is high and V_{IN} > V_{IH} an internal active pull up will be switched onto the Data Bus.
- ΔI supply / ΔT_A = -0.45%/°C.

 TYPICAL SUPPLY CURRENT VS. TEMPERATURE, NORMALIZED. [3]



DATA BUS CHARACTERISTIC DURING DBIN

 

8080

INSTRUCTION SET

| Mnemonic | Description | Instruction Code ⁽¹⁾ | | | | | | | | Clock ⁽²⁾ Cycles |
|----------|------------------------------------|---------------------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|--------------------------------|
| | | D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ | |
| ACI | Add immediate to A with carry | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 7 |
| ADC M | Add memory to A with carry | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 7 |
| ADC r | Add register to A with carry | 1 | 0 | 0 | 0 | 1 | S | S | S | 4 |
| ADD M | Add memory to A | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 7 |
| ADD r | Add register to A | 1 | 0 | 0 | 0 | 0 | S | S | S | 4 |
| ADI | Add immediate to A | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 7 |
| ANA M | And memory with A | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 7 |
| ANA r | And register with A | 1 | 0 | 1 | 0 | 0 | S | S | S | 4 |
| ANI | And immediate with A | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 7 |
| CALL | Call unconditional | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 17 |
| CC | Call on carry | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 11/17 |
| CM | Call on minus | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 11/17 |
| CMC | Complement A | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 4 |
| CMC | Complement carry | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 4 |
| CMP M | Compare memory with A | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 7 |
| CMP r | Compare register with A | 1 | 0 | 1 | 1 | 1 | S | S | S | 4 |
| CNC | Call on no carry | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 11/17 |
| CNZ | Call on no zero | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 11/17 |
| CP | Call on positive | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 11/17 |
| CPE | Call on parity even | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 11/17 |
| CPI | Compare immediate with A | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 7 |
| CPO | Call on parity odd | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 11/17 |
| CZ | Call on zero | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 11/17 |
| DAA | Decimal adjust A | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 4 |
| DAD B | Add B & C to H & L | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 10 |
| DAD D | Add D & E to H & L | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 10 |
| DAD H | Add H & L to H & L | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 10 |
| DAD SP | Add stack pointer to H & L | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 10 |
| DCR M | Decrement memory | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 10 |
| DCR r | Decrement register | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 5 |
| DCX B | Decrement B & C | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 5 |
| DCX D | Decrement D & E | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 5 |
| DCX H | Decrement H & L | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 5 |
| DCX SP | Decrement stack pointer | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 5 |
| DI | Disable Interrupt | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 4 |
| EI | Enable Interrupts | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 4 |
| HLT | Halt | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 7 |
| IN | Input | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 10 |
| INR M | Increment memory | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 10 |
| INR r | Increment register | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 5 |
| INX B | Increment B & C registers | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 5 |
| INX D | Increment D & E registers | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 5 |
| INX H | Increment H & L registers | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 5 |
| INX SP | Increment stack pointer | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 5 |
| JC | Jump on carry | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 10 |
| JM | Jump on minus | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 10 |
| JMP | Jump unconditional | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 10 |
| JNC | Jump on no carry | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 10 |
| JNZ | Jump on no zero | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 10 |
| JP | Jump on positive | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 10 |
| JPE | Jump on parity even | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 10 |
| JPO | Jump on parity odd | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 10 |
| JZ | Jump on zero | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 10 |
| LDA | Load A direct | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 13 |
| LDAX B | Load A indirect | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 7 |
| LDAX D | Load A indirect | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 7 |
| LHLD | Load H & L direct | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 16 |
| LXI B | Load immediate register Pair B & C | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 10 |
| LXI D | Load immediate register Pair D & E | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 10 |
| LXI H | Load immediate register Pair H & L | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 10 |
| LXI SP | Load immediate stack pointer | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 10 |

Summary of Processor Instructions
By Alphabetical Order

| Mnemonic | Description | Instruction Code ⁽¹⁾ | | | | | | | | Clock ⁽²⁾ Cycles |
|----------------------|---------------------------------------|---------------------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|--------------------------------|
| | | D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ | |
| MVI M | Move immediate memory | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 10 |
| MVI r | Move immediate register | 0 | 0 | D | D | D | 1 | 1 | 0 | 7 |
| MOV M, r | Move register to memory | 0 | 1 | 1 | 1 | 0 | S | S | S | 7 |
| MOV r, M | Move memory to register | 0 | 1 | 0 | D | D | 1 | 1 | 0 | 7 |
| MOV r _{1,2} | Move register to register | 0 | 1 | 0 | D | D | S | S | S | 5 |
| NOP | No-operation | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 4 |
| ORA M | Or memory with A | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 7 |
| ORA r | Or register with A | 1 | 0 | 1 | 1 | 0 | S | S | S | 4 |
| ORI | Or immediate with A | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 7 |
| OUT | Output | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 10 |
| PCHL | H & L to program counter | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 5 |
| POP B | Pop register pair B & C off stack | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 10 |
| POP D | Pop register pair D & E off stack | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 10 |
| POP H | Pop register pair H & L off stack | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 10 |
| POP PSW | Pop A and Flags off stack | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 10 |
| PUSH B | Push register Pair B & C on stack | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 11 |
| PUSH D | Push register Pair D & E on stack | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 11 |
| PUSH H | Push register Pair H & L on stack | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 11 |
| PUSH PSW | Push A and Flags on stack | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 11 |
| RAL | Rotate A left through carry | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 4 |
| RAR | Rotate A right through carry | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 4 |
| RC | Return on carry | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 5/11 |
| RET | Return | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 10 |
| RLC | Rotate A left | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 4 |
| RM | Return on minus | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 5/11 |
| RNC | Return on no carry | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 5/11 |
| RNZ | Return on no zero | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 5/11 |
| RP | Return on positive | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 5/11 |
| RPE | Return on parity even | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 5/11 |
| RPO | Return on parity odd | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 5/11 |
| RRC | Rotate A right | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 4 |
| RST | Restart | 1 | 1 | A | A | A | 1 | 1 | 1 | 11 |
| RZ | Return on zero | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 5/11 |
| SBB M | Subtract memory from A with borrow | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 7 |
| SBB r | Subtract register from A with borrow | 1 | 0 | 0 | 1 | 1 | S | S | S | 4 |
| SBI | Subtract immediate from A with borrow | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 7 |
| SHLD | Store H & L direct | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 16 |
| SPHL | H & L to stack pointer | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 5 |
| STA | Store A direct | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 13 |
| STAX B | Store A indirect | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 7 |
| STAX D | Store A indirect | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 7 |
| STC | Set carry | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 4 |
| SUB M | Subtract memory from A | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 7 |
| SUB r | Subtract register from A | 1 | 0 | 0 | 1 | 0 | S | S | S | 4 |
| SUI | Subtract immediate from A | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 7 |
| XCHG | Exchange D & E, H & L Registers | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 4 |
| XRA M | Exclusive Or memory with A | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 7 |
| XRA r | Exclusive Or register with A | 1 | 0 | 1 | 0 | 1 | S | S | S | 4 |
| XRI | Exclusive Or immediate with A | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 7 |
| XTHL | Exchange top of stack, H & L | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 18 |

NOTES

NOTES: 1. DDD or SSS - 000 B - 001 C - 010 D - 011 E - 100 H - 101 L - 110 Memory - 111 A.
2. Two possible cycle times, (5/11) indicate instruction cycles dependent on condition flags.



microcomputer
design

NOTES

COMMENTS

We appreciate your comments on MICROCOMPUTER DESIGN:

Name _____

Title _____ Phone _____

Company/Institution _____

Address _____

City _____ State _____ ZIP _____

Please rush the following:

- A catalog on the modular micros from Martin Research, with prices.
- Another copy of this book, MICROCOMPUTER DESIGN. \$25.00 is enclosed.
- Brochure(s) on this book, including current prices: brochures.
- Quantity discount schedule for MICROCOMPUTER DESIGN.
- Educational discount schedule (for officials and representatives of educational institutions only).



microcomputer
design



microcomputer
design

COMMENTS.....Fill out.....fold in three.....seal.....and return!

modular micros!

We are proud to announce the *modular micros* from Martin Research. These versatile printed circuit modules can be configured to produce a variety of microcomputer systems, from the simple to the complex.

BEST VALUE !

Not just a collection of parts, with the wirewrapping left to you . . . but complete with commercial-grade printed circuit boards, made by top PC houses, with plated-through holes. Minimizes construction time, and greatly reduces troubleshooting.

MOST ADAPTABLE!

Our universal bus structure is compatible with all standard eight-bit microprocessors! This is a major advantage for the user who wishes to upgrade his system in the future. And, it is ideal for the OEM building prototypes with competing processors. Memory and accessory boards remain compatible when the CPU is changed.

MOST FLEXIBLE!

The system architecture, designed for optimum flexibility, allows any board to be inserted in any position on the bus. A flat cable and snap-on fifty-pin connectors make for easy expansion.

SUPERIOR SYSTEMS DESIGN!

Programs are entered on a calculator-style keyboard, and six bright LED digits display data and memory addresses. A Monitor program in a PROM makes program entry easy. This is a significant advance over console designs with cumbersome arrays of toggle switches and lamps.

FAST MEMORY AVAILABLE!

Our 4K static RAM board uses RAM chips fast enough--450 ns--to avoid making the CPU wait for memory access in most applications. Now in stock, this board is price-competitive with others' memory boards with far slower specifications. Warning: some manufacturers using slow RAM do not inform the buyer of this fact. The result is that the CPU must wait for memory, resulting in a computer much slower than the specs might imply.

BEST FOR YOUR APPLICATION!

With microcomputer systems starting at under \$400, the *modular micros* are ideal for:

- The computer enthusiast, in his home;
- The professional engineer or programmer, to keep up with the state of the art;
- The manufacturer, for prototyping microcomputer systems, or for incorporation in his product.

(OEMs: write for further information.)

modular micros


martin research



BUSINESS REPLY MAIL

First Class Mail Permit No. 663 • Northbrook, Illinois

 martin research
3336 Commercial Ave.
Northbrook, IL 60062



INSTRUCTION SET

| REGISTER INSTRUCTIONS | | | DESTINATION | | | | | | | | |
|--|-----------|-----|-------------|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | A | B | C | D | E | H | L | M | |
| EX.: LAM= LOAD ACCUMULATOR FROM MEMORY | | | | | | | | | | | |
| S O U R C E | A | 300 | 310 | 320 | 330 | 340 | 350 | 360 | 370 | | |
| | B | 301 | 311 | 321 | 331 | 341 | 351 | 361 | 371 | | |
| | C | 302 | 312 | 322 | 332 | 342 | 352 | 362 | 372 | | |
| | D | 303 | 313 | 323 | 333 | 343 | 353 | 363 | 373 | | |
| | E | 304 | 314 | 324 | 334 | 344 | 354 | 364 | 374 | | |
| | H | 305 | 315 | 325 | 335 | 345 | 355 | 365 | 375 | | |
| | L | 306 | 316 | 326 | 336 | 346 | 356 | 366 | 376 | | |
| M | 307 | 317 | 327 | 337 | 347 | 357 | 367 | — | | | |
| | MNE-MONIC | A | B | C | D | E | H | L | M | | |
| LOAD REGISTER IMMEDIATE | | | LrI | 006 | 016 | 026 | 036 | 046 | 056 | 066 | 076 |
| INCREMENT REGISTER | | | INr | — | 010 | 020 | 030 | 040 | 050 | 060 | — |
| DECREMENT REGISTER | | | DCr | — | 011 | 021 | 031 | 041 | 051 | 061 | — |

| ALU INSTRUCTIONS | MNE-MONIC | A | B | C | D | E | H | L | M | IMM. |
|---------------------------|-----------|------|-----|-----|-----|-----|-----|-----|-----|------|
| ADD r TO A → A | ADr | 200 | 201 | 202 | 203 | 204 | 205 | 206 | 207 | 004 |
| ADD r + C TO A → A | ACr | 210 | 211 | 212 | 213 | 214 | 215 | 216 | 217 | 014 |
| SUB. r FROM A → A | SUr | 220 | 221 | 222 | 223 | 224 | 225 | 226 | 227 | 024 |
| SUB. (r + C) FROM A → A | SBr | 230 | 231 | 232 | 233 | 234 | 235 | 236 | 237 | 034 |
| AND r WITH A → A | NDr | 240 | 241 | 242 | 243 | 244 | 245 | 246 | 247 | 044 |
| EXCL. OR r WITH A → A | XRr | 250 | 251 | 252 | 253 | 254 | 255 | 256 | 257 | 054 |
| OR r WITH A → A | ORr | 260 | 261 | 262 | 263 | 264 | 265 | 266 | 267 | 064 |
| COMPARE r WITH A | CPr | 270 | 271 | 272 | 273 | 274 | 275 | 276 | 277 | 074 |
| | | CODE | | | | | | | | |
| ROTATE A LEFT | RLC | 002 | | | | | | | | |
| ROTATE A RIGHT | RRC | 012 | | | | | | | | |
| ROTATE A LEFT THRU CARRY | RAL | 022 | | | | | | | | |
| ROTATE A RIGHT THRU CARRY | RAR | 032 | | | | | | | | |

| FLAGS AFFECTED | C | Z | S | P |
|---------------------|---|---|---|---|
| INCREMENT/DECREMENT | — | ✓ | ✓ | ✓ |
| ALU INSTRUCTIONS | ✓ | ✓ | ✓ | ✓ |
| ROTATE | ✓ | — | — | — |

| PC/STACK INSTRUCTIONS | | UNCONDITIONAL | | | | FALSE CONDITION | | | | TRUE CONDITION | | | |
|-----------------------|-----------|---------------|-----------|-------|------|-----------------|--------|-----------|-------|----------------|------|--------|--|
| OPERATION | MNE-MONIC | * | MNE-MONIC | CARRY | ZERO | SIGN | PARITY | MNE-MONIC | CARRY | ZERO | SIGN | PARITY | |
| JUMP | JMP | 1x4 | JFc | 100 | 110 | 120 | 130 | JTc | 140 | 150 | 160 | 170 | |
| CALL | CAL | 1x6 | CFc | 102 | 112 | 122 | 132 | CTc | 142 | 152 | 162 | 172 | |
| RETURN | RET | 0x7 | RFc | 103 | 113 | 123 | 133 | RTc | 143 | 153 | 163 | 173 | |
| | | MNEMONIC | CODE | | | | | | | | | | |
| RESTART | RST | OaO | Oa5 | | | | | | | | | | |

* X = DON'T CARE (0-7)

| I/O INSTR. | n | INP n | OUT 1n | OUT 2n | OUT 3n |
|------------|---|-------|--------|--------|--------|
| | 0 | 101 | 121 | 141 | 161 |
| | 1 | 103 | 123 | 143 | 163 |
| | 2 | 105 | 125 | 145 | 165 |
| | 3 | 107 | 127 | 147 | 167 |
| | 4 | 111 | 131 | 151 | 171 |
| | 5 | 113 | 133 | 153 | 173 |
| | 6 | 115 | 135 | 155 | 175 |
| | 7 | 117 | 137 | 157 | 177 |

| | |
|-------------|-----|
| UNDEFINED | 042 |
| INSTRUCTION | 052 |
| CODES | 062 |
| | 070 |
| | 071 |
| | 072 |

| | | |
|------|-----|-----|
| HALT | HLT | 000 |
| | HLT | 001 |
| | HLT | 377 |

INSTRUCTIONS

Summary of Processor Instructions in Alphabetical Order

| Mnemonic | Description | Octal Code | Mnemonic | Description | Octal Code |
|---------------------|-------------------------------|-----------------|-----------------|---|---------------|
| ACI <i>data</i> | Add immediate to A with carry | 3 1 6 | ORA <i>r</i> | OR register with A | 2 6 <i>r</i> |
| ADC <i>r</i> | Add register to A with carry | 2 1 <i>r</i> | ORI <i>data</i> | OR immediate with A | 3 6 6 |
| ADD <i>r</i> | Add register to A | 2 0 <i>r</i> | OUT <i>port</i> | Output | 3 2 3 |
| ADI <i>data</i> | Add immediate to A | 3 0 6 | PCHL | HL to program counter | 3 5 1 |
| ANA <i>r</i> | AND register with A | 2 4 <i>r</i> | POP <i>rp</i> | Pop register pair off stack (only B, D, H) | 3 <i>rp</i> 1 |
| ANI <i>data</i> | AND immediate with A | 3 4 6 | POP PSW | Pop A and flags off stack | 3 6 1 |
| CALL <i>addr</i> | Call unconditional | 3 1 5 | PUSH <i>rp</i> | Push register pair onto stack (only B, D, H) | 3 <i>rp</i> 5 |
| Cc <i>addr</i> | Call on condition | 3 <i>c</i> 4 | PUSH PSW | Push A and flags onto stack | 3 6 5 |
| CMA | Complement A | 0 5 7 | RAL | Rotate A left through carry | 0 2 7 |
| CMC | Complement carry | 0 7 7 | RAR | Rotate A right through carry | 0 3 7 |
| CMP <i>r</i> | Compare register with A | 2 7 <i>r</i> | Rc | Return on condition | 3 <i>c</i> 0 |
| CPI <i>data</i> | Compare immediate with A | 3 7 6 | RET | Return | 3 1 1 |
| DAA | Decimal adjust A | 0 4 7 | RLC | Rotate A left | 0 0 7 |
| DAD <i>rp</i> | Add register pair to HL | 0 <i>rp+1</i> 1 | RRC | Rotate A right | 0 1 7 |
| DCR <i>r</i> | Decrement register | 0 <i>r</i> 5 | RST <i>n</i> | Restart | 3 <i>n</i> 7 |
| DCX <i>rp</i> | Decrement register pair | 0 <i>rp+1</i> 3 | SBB <i>r</i> | Subtract reg. from A w/borrow | 2 3 <i>r</i> |
| DI | Disable interrupts | 3 6 3 | SBI <i>data</i> | Subtract imm. from A w/borrow | 3 3 6 |
| EI | Enable interrupts | 3 7 3 | SHLD | Store HL direct | 0 4 2 |
| HLT | Halt | 1 6 6 | SPHL | HL to stack pointer | 3 7 1 |
| IN <i>port</i> | Input | 3 3 3 | STA <i>addr</i> | Store A direct | 0 6 2 |
| INR <i>r</i> | Increment register | 0 <i>r</i> 4 | STAX <i>rp</i> | Store A indirect (only B, D) | 0 <i>rp</i> 2 |
| INX <i>rp</i> | Increment register pair | 0 <i>rp</i> 3 | STC | Set carry | 0 6 7 |
| JMP <i>addr</i> | Jump unconditional | 3 0 3 | SUB <i>r</i> | Subtract register from A | 2 2 <i>r</i> |
| Jc <i>addr</i> | Jump on condition | 3 <i>c</i> 2 | SUI <i>data</i> | Subtract immediate from A | 3 2 6 |
| LDA <i>addr</i> | Load A direct | 0 7 2 | XCHG | Exchange DE, HL register pairs | 3 5 3 |
| LDAX <i>rp</i> | Load A indirect (only B, D) | 0 <i>rp+1</i> 2 | XRA <i>r</i> | Exclusive OR register with A | 2 5 <i>r</i> |
| LHLD <i>addr</i> | Load HL direct | 0 5 2 | XRI <i>data</i> | Exclusive OR immediate with A | 3 5 6 |
| LXI <i>rp, data</i> | Load immediate register pair | 0 <i>rp</i> 1 | XTHL | Exchange top of stack with HL | 3 4 3 |
| MOV <i>d, s</i> | Move register to register | 1 <i>d s</i> | | | |
| MVI <i>r, data</i> | Move immediate register | 0 <i>r</i> 6 | | | |
| NOP | No operation | 0 0 0 | | | |

ABBREVIATIONS

| Abbrev. | Description | Bits |
|-------------|----------------|------|
| <i>addr</i> | Memory address | 16 |
| <i>c</i> | Condition | 3 |
| <i>d</i> | Destination | 3 |
| <i>data</i> | Data | 8/16 |
| <i>port</i> | I/O port | 8 |
| <i>r</i> | Register | 3 |
| <i>rp</i> | Register pair | 2 |
| <i>s</i> | Source | 3 |

INSTRUCTION CODE VALUES

| OCTAL CODE | REGISTER (<i>d, r, s</i>) | REGISTER PAIR (<i>rp</i>) (<i>rp+1</i>) | | CONDITION (<i>c</i>) | | |
|------------|-----------------------------|---|-------------|------------------------|-------------|--------|
| | | Abbrev. | Description | Flag | | |
| 0 | B | BC | -- | NZ | Not zero | Z = 0 |
| 1 | C | -- | BC | Z | Zero | Z = 1 |
| 2 | D | DE | -- | NC | No carry | CY = 0 |
| 3 | E | -- | DE | C | Carry | CY = 1 |
| 4 | H | HL | -- | PO | Parity odd | P = 0 |
| 5 | L | -- | HL | PE | Parity even | P = 1 |
| 6 | M | SP | -- | P | Plus | S = 0 |
| 7 | A | -- | SP | M | Minus | S = 1 |

8080 INSTRUCTIONS IN OCTAL FORMAT

The 8080 is an 8-bit microprocessor, and its instruction code tends to break down into a 2/3/3-bit grouping. This is why it was convenient in this chart to list 8080 instructions in octal format, where digits follow this same pattern.

Hexadecimal notation (4/4-bit grouping) is often used instead of octal, but since hex does not correspond directly to the way in which the 8080 is microcoded, hex instruction codes are not readily listed in condensed graphic form, and are more difficult for the programmer to learn.

REGISTER TRANSFERS

MOV B, H - MOVE TO THE B REG. THE CONTENTS OF THE H REGISTER.
 A-7 C-1 E-3 L-5
 B-0 D-2 H-4 M-6

| OPERATION | DESTINATION | | | | | | | | | | | | | | | |
|----------------|-------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|---|---|---|---|---|---|
| | A | B | C | D | E | H | L | M | A | B | C | D | E | H | L | M |
| S | 177 | 107 | 117 | 127 | 137 | 147 | 157 | 167 | | | | | | | | |
| O | 170 | 100 | 110 | 120 | 130 | 140 | 150 | 160 | | | | | | | | |
| U | 172 | 102 | 112 | 122 | 132 | 142 | 152 | 162 | | | | | | | | |
| R | 173 | 103 | 113 | 123 | 133 | 143 | 153 | 163 | | | | | | | | |
| C | 174 | 104 | 114 | 124 | 134 | 144 | 154 | 164 | | | | | | | | |
| E | 175 | 105 | 115 | 125 | 135 | 145 | 155 | 165 | | | | | | | | |
| M | 176 | 106 | 116 | 126 | 136 | 146 | 156 | 166 | | | | | | | | |
| MOVE IMMEDIATE | MVI | 7 | 076 | 006 | 016 | 026 | 036 | 046 | 056 | 066 | | | | | | |

DOUBLE-PRECISION TRANSFERS

| OPERATION | DESTINATION | | | | | | | | | | | | | | | |
|-----------|-------------|------|------|------|-----|------|------|------|------|----|--|--|--|--|--|--|
| | B, C | D, E | H, L | S, P | PC | B, C | D, E | H, L | S, P | PC | | | | | | |
| S | | | XCHG | | | | | | | | | | | | | |
| U | | XCHG | | | | | | | | | | | | | | |
| C | | | | | | | | | | | | | | | | |
| E | LXI | B | LXI | D | LXI | H | LXI | S | PHL | | | | | | | |
| | | | | | | | | | | | | | | | | |

INDIRECT TRANSFERS

| BYTES | INSTR. | REG. | DATA | MEMORY ADDR. BYT. |
|-------|-----------------------|--------------------|------|--------------------|
| 1 | MOV M, r SEE ABOVE | INDEX REG. r | ← | H, L |
| | MVI 098 M | 2ND BYTE OF INSTR. | ← | |
| | PUSH 305 B | B, C | ← | SP (Stack Pointer) |
| | POP 301 B | | ← | PUSH DOWN SP BY 2 |
| | PUSH 325 D | D, E | ← | |
| | POP 331 D | | ← | |
| | PUSH 345 H | H, L | ← | |
| | POP 341 H | | ← | |
| | PUSH PSW 365 | A, PSW | ← | |
| | POP PSW 361 | | ← | |
| | XTHL 343 | H, L | ↔ | SP |

DIRECT LOAD & STORE

| BYTES | INSTR. | REG. | DATA | MEMORY ADDR. BYT. |
|-------|----------|------|------|-------------------|
| 1 | STA 085 | A | → | 2nd |
| | LDA 072 | | ← | AND |
| | SHLD 042 | H, L | → | 3rd |
| | LHLD 052 | | ← | BYTES OF INSTR. |

INPUT/OUTPUT

| INPUT | OUTPUT |
|----------------------|---------|
| IN 333 | OUT 323 |
| 2ND BYTE - I/O ADDR. | |

Copyright © 1976
 MARTIN RESEARCH
 ALL RIGHTS RESERVED

| UNUSED |
|---------|
| 010 313 |
| 020 321 |
| 030 325 |
| 040 355 |
| 050 375 |
| 060 383 |
| 070 373 |

PROGRAM CONTROL

| OPERATION | UN. CONDI- TIONAL | DI- RECT | ZERO | | CARRY | | PARITY | | SIGN |
|-----------|-------------------|----------|-------|-------|-------|-------|--------|-------|------|
| | | | FALSE | TRUE | FALSE | TRUE | FALSE | TRUE | |
| JUMP | MR | PCHL | JZ | JNC | JC | JPO | JPE | SP | IM |
| CALL | CALL | RET | CZ | CNC | CC | CPO | CPE | CP | CM |
| RETURN | RET | — | RZ | RNC | RC | RPO | RPE | RP | RM |
| RESTART | RST 0 | RST 1 | RST 2 | RST 3 | RST 4 | RST 5 | RST 6 | RST 7 | |

BIT MANIPULATION

| OPERATION | INCR / DECR REGISTER | A | | | | | | | |
|-------------------------|----------------------|-----|-----|-----|-----|-----|-----|-----|-----|
| | | 074 | 004 | 014 | 024 | 034 | 044 | 054 | 064 |
| INCREMENT REGISTER PAIR | INR | 074 | 004 | 014 | 024 | 034 | 044 | 054 | 064 |
| DECREMENT REGISTER PAIR | DCR | 075 | 005 | 015 | 025 | 035 | 045 | 055 | 065 |

ALU INSTRUCTIONS

| OPERATION | A | | | | | | | | B | | | | | | | | C | | | | | | | | D | | | | | | | | E | | | | | | | | H | | | | | | | | L | | | | | | | | M | | | | | | | | | | | | | | | | | | | | | | |
|----------------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| | 007 | 017 | 027 | 037 | 047 | 057 | 067 | 077 | 003 | 013 | 023 | 033 | 043 | 053 | 063 | 073 | 007 | 017 | 027 | 037 | 047 | 057 | 067 | 077 | 003 | 013 | 023 | 033 | 043 | 053 | 063 | 073 | 007 | 017 | 027 | 037 | 047 | 057 | 067 | 077 | 003 | 013 | 023 | 033 | 043 | 053 | 063 | 073 | 007 | 017 | 027 | 037 | 047 | 057 | 067 | 077 | 003 | 013 | 023 | 033 | 043 | 053 | 063 | 073 | 007 | 017 | 027 | 037 | 047 | 057 | 067 | 077 | 003 | 013 | 023 | 033 | 043 | 053 | 063 |
| ADD r TO A → A | ADD | 207 | 217 | 227 | 237 | 247 | 257 | 267 | 277 | 203 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 207 | 217 | 227 | 237 | 247 | 257 | 267 | 277 | 203 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 207 | 217 | 227 | 237 | 247 | 257 | 267 | 277 | 203 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 207 | 217 | 227 | 237 | 247 | 257 | 267 | 277 | 203 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | | | | | | | | | | | | | | |
| ADD r + c TO A → A | ADC | 208 | 218 | 228 | 238 | 248 | 258 | 268 | 278 | 204 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 208 | 218 | 228 | 238 | 248 | 258 | 268 | 278 | 204 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 208 | 218 | 228 | 238 | 248 | 258 | 268 | 278 | 204 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 208 | 218 | 228 | 238 | 248 | 258 | 268 | 278 | 204 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | | | | | | | | | | | | | | |
| SUB r FROM A → A | SUB | 209 | 219 | 229 | 239 | 249 | 259 | 269 | 279 | 205 | 215 | 225 | 235 | 245 | 255 | 265 | 275 | 209 | 219 | 229 | 239 | 249 | 259 | 269 | 279 | 205 | 215 | 225 | 235 | 245 | 255 | 265 | 275 | 209 | 219 | 229 | 239 | 249 | 259 | 269 | 279 | 205 | 215 | 225 | 235 | 245 | 255 | 265 | 275 | 209 | 219 | 229 | 239 | 249 | 259 | 269 | 279 | 205 | 215 | 225 | 235 | 245 | 255 | 265 | 275 | | | | | | | | | | | | | | |
| SUB r + c FROM A → A | SBB | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 206 | 216 | 226 | 236 | 246 | 256 | 266 | 276 | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 206 | 216 | 226 | 236 | 246 | 256 | 266 | 276 | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 206 | 216 | 226 | 236 | 246 | 256 | 266 | 276 | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 206 | 216 | 226 | 236 | 246 | 256 | 266 | 276 | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 206 | 216 | 226 | 236 | 246 | 256 | 266 | 276 | | | |
| AND r WITH A → A | AND | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 207 | 217 | 227 | 237 | 247 | 257 | 267 | 277 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | 211 | 221 | 231 | 241 | 251 | 261 | 271 | | | | | | | |
| OR r WITH A → A | ORA | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 208 | 218 | 228 | 238 | 248 | 258 | 268 | 278 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | 212 | 222 | 232 | 242 | 252 | 262 | 272 | | | | | | | |
| OR r WITH A, WITH A | ORA | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 209 | 219 | 229 | 239 | 249 | 259 | 269 | 279 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | 213 | 223 | 233 | 243 | 253 | 263 | 273 | | | | | | | |
| COMPARE r WITH A | CMP | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 210 | 220 | 230 | 240 | 250 | 260 | 270 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | 214 | 224 | 234 | 244 | 254 | 264 | 274 | | | | | | | | |

FLAGS

| ALU INST. | NO. OF | ADJUST | ROTATE | INCR./DECR. | SET/COMP. | CARRY |
|-----------|--------|--------|--------|-------------|-----------|-------|
| ADD | 1 | NO | NO | NO | NO | NO |
| ADC | 1 | NO | NO | NO | NO | NO |
| SUB | 1 | NO | NO | NO | NO | NO |
| SBB | 1 | NO | NO | NO | NO | NO |
| AND | 1 | NO | NO | NO | NO | NO |
| ORA | 1 | NO | NO | NO | NO | NO |
| ORL | 1 | NO | NO | NO | NO | NO |
| CMP | 1 | NO | NO | NO | NO | NO |

MACHINE CONTROL

| NO. OPERATION | HALT | DISABLE INTERRUPT | ENABLE INTERRUPT |
|---------------|------|-------------------|------------------|
| NOP | 000 | | |
| HLT | 196 | | |
| DI | 363 | | |
| EI | 373 | | |