

T.			U _f V	I _f A	C _l V	U _a V	U _{g2} V	U _{g1} V	I _a mA	I _{g2} mA	S mA/V	R _i kΩ	R _t Ω	R _o kΩ	P _o W	U _{g1} ≈ h %		
EL 90 ¹⁾	Lor	1	6,3	0,45														
HL 90 ¹⁾	Lor	1	19	0,15														
5 AQ 5 ¹⁾	int	2	4,7	0,6														
5 CM 6	TS	6	4,7	0,6														
5 V 6-GT	int	3	4,7	0,45	A	26	—	—	25	0,25	1,75	57	10	0,02				
6 AQ 5 ¹⁾	int	2	6,3	0,45	A	100	—	—	10,5÷12,5	0,8÷1,7	2,6	85	530	7	0,5	3,8	10	
6 AY 5	amer	4	6,3	0,45	A	180	—	—	8,5	3÷4	3,7	58	270	5,5	2	8,5	8	
6 BW 6	int	5	6,3	0,45	A	200	—	—	12	2÷5,6	3,5	80	415	5	3	8,5	10	
6 CM 6	amer	6	6,3	0,45	A	250	—	—	12,5	4,5÷7	4,1	52	250	5	4,5	12,5	8	
6 II 1 II	CCCP	7	6,3	0,45	A	315	22,5	—	13	3÷35	2,2÷6	77	360	8,5	5,5	13	12	
6 T	Fiv	12	6,3	0,45	A	250	250	—	12,2	9,5	5÷13	60	120	10	9	18	2,5	
6 V 5-G	amer	11	6,3	0,45	A-PP	250	250	—	15	70÷79	3,75	60	390	10	10	30	5	
6 V 6	int	3	6,3	0,45	AB	250	250	—	19	70÷92	4÷13,5	70	—	8	14	38	3,5	
7 C 5	int	8	6,3	0,45	AB	285	285	—	19	—	5	1,9	(μ = 9,5)					
9 AQ 5 ¹⁾	Fiv	2	9,45	0,3	A	250	Fig. 1	—	12,5	49,5	—	5	150	4	1,7	19,2	0,4	
9 BW 6	int	5	9,5	0,3	A-PP	250	Fig. 1	—	13,8	92	—	5	250	4,5	3,1	27,5	0,5	
12 AB 5	amer	9	12,6	0,2	A-PP	285	Fig. 1	—	19,5	78	—	5	150	4,5	3,1	27,5	0,5	
12 AQ 5 ¹⁾	int	2	12,6	0,225	A	315	285	maximum	I _k = 60 mA; U _{f/k} = 90 V; R _{g1} = 0,5 MΩ; P _{g2} = 2 W; P _a = 12 W	—	—	—	—	—	—	—	—	—
12 CM 6	amer	6	12,6	0,225	A	12,6	12,6	—	22,5	—	23	2	—	6	1	—	—	
12 V 6-GT	int	3	12,6	0,225	A	12,6	12,6	—	22,5	—	32,5	3	3,4	200	6	1	—	
14 C 5	int	8	12,6	0,225	A	10	6,3	0,6	6,3	int	6 V 6	80	220	6	1	—	—	
5992 ²⁾	amer	4	6,3	0,6	A	130	130	—	180	180	—	—	—	—	—	—	—	
6287	amer	10	6,3	0,6	A	180	180	—	200	200	—	—	—	—	—	—	—	
6 AQ 5 L ¹⁾	SER	1	6,3	0,36	A	130	130	—	180	180	—	—	—	—	—	—	—	
18 AQ 5 ¹⁾	SER	—	18	0,125	A	200	200	—	—	—	—	—	—	—	—	—	—	

¹⁾ U_{a(max)} = U_{g2(max)} = 250 V
²⁾ vide * 4, a, b, c, d, e (U_f = 6,3 V + 5%)

³⁾ vide * 4, b, c = 10,000, d, e, f, g (U_f = 6,3 V (18 V) + 5%)

⁴⁾ vide * 4, a, b, c, f, g (U_f = 6,3 V ± 10%)

⁵⁾ U_f = 6,3 V ± 20%

⁶⁾ U_{a(max)} = 350 V; U_{g2(max)} = 315 V; P_a = 14 W; P_{g2} = 2,2 W; U_{f/k} = 200 V

⁷⁾ vide * 4, a, b, c, d, e

⁸⁾ vide * 4, a, b, c, d, e

Equivalents

BPM 04	SFR	= 6 AQ 5	6 AQ 5-W ¹⁾ int	= 6 AQ 5	6 II 6 C CCCP = 6 V 6-GT
CK 6005	Ray	= 6 AQ 5	6 L 31 ¹⁾ Tes	= EL 90	7 C 5-LT SyI = 7 C 5
HF 3/06	RFT	= 6 AY 6	6 V 5-GT zmer	= 6 V 5-G	7 C 5-TV SyI = 7 C 5
M 8245 ¹⁾	Mul	= 6 AQ 5	6 V 6 RFT	= 6 AY 5	amer = 6 V 6-GT
N 148	Erg	= 7 C 5	6 V 6-G int	= 6 V 6	60005 ¹⁾ amer = 6 AQ 5
N 727	Erg	= 6 AQ 5	6 V 6-GT int	= 6 V 6	Bri = 6 BW 6
OSW 3/06	RFT	= 6 AY 5	6 V 6-GTA int	= 6 V 6	60047 ¹⁾ amer = 6287
WT-2102	WT	= 6 V 6	6 V 6-GTY RCA	= 6 V 6	60947 ¹⁾ amer = 6 AQ 5
WT-T-123	WT	= 6 V 6	6 V 6-Y RCA	= 6 V 6	60951 ¹⁾ amer = 6 AQ 5
2 C 48	amer	= 7 C 5	6 V 6-Y RCA	= 6 V 6	66691 ¹⁾ amer = 6 AQ 5 L
2 C 50	amer	= 7 C 5	6 II 1 II-B ¹⁾ CCCP = 6 II 1 II	= 6 II 1 II	69281 ¹⁾ amer = 6 V 6-GT
6 AQ 5-A	RCA	= 6 AQ 5	6 II 1 II-E ¹⁾ CCCP = 6 II 1 II	= 6 II 1 II	GE = 6 V 6-GT

¹⁾ U_{a(max)} = U_{g2(max)} = 250 V
²⁾ vide * 4, a, b, c, d, e (U_f = 6,3 V + 5%)


³⁾ vide * 4, b, c = 10,000, d, e, f, g (U_f = 6,3 V (18 V) + 5%)

⁴⁾ vide * 4, a, b, c, f, g (U_f = 6,3 V ± 10%)

⁵⁾ U_f = 6,3 V ± 20%

⁶⁾ U_{a(max)} = 350 V; U_{g2(max)} = 315 V; P_a = 14 W; P_{g2} = 2,2 W; U_{f/k} = 200 V

⁷⁾ vide * 4, a, b, c, d, e

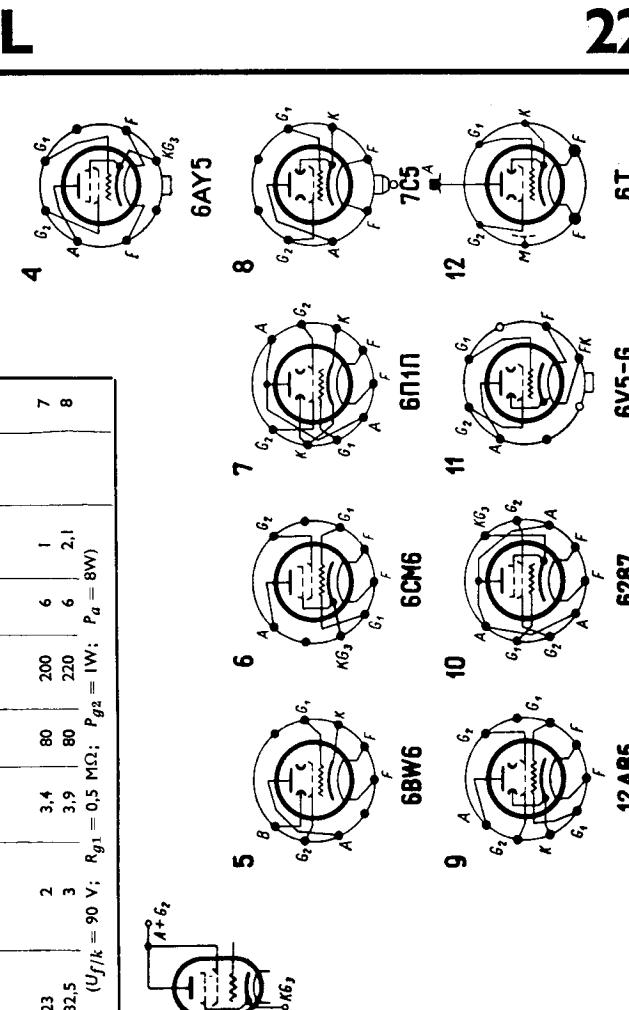

220**L****220**